

\$1.50


# *ham radio*

*magazine*


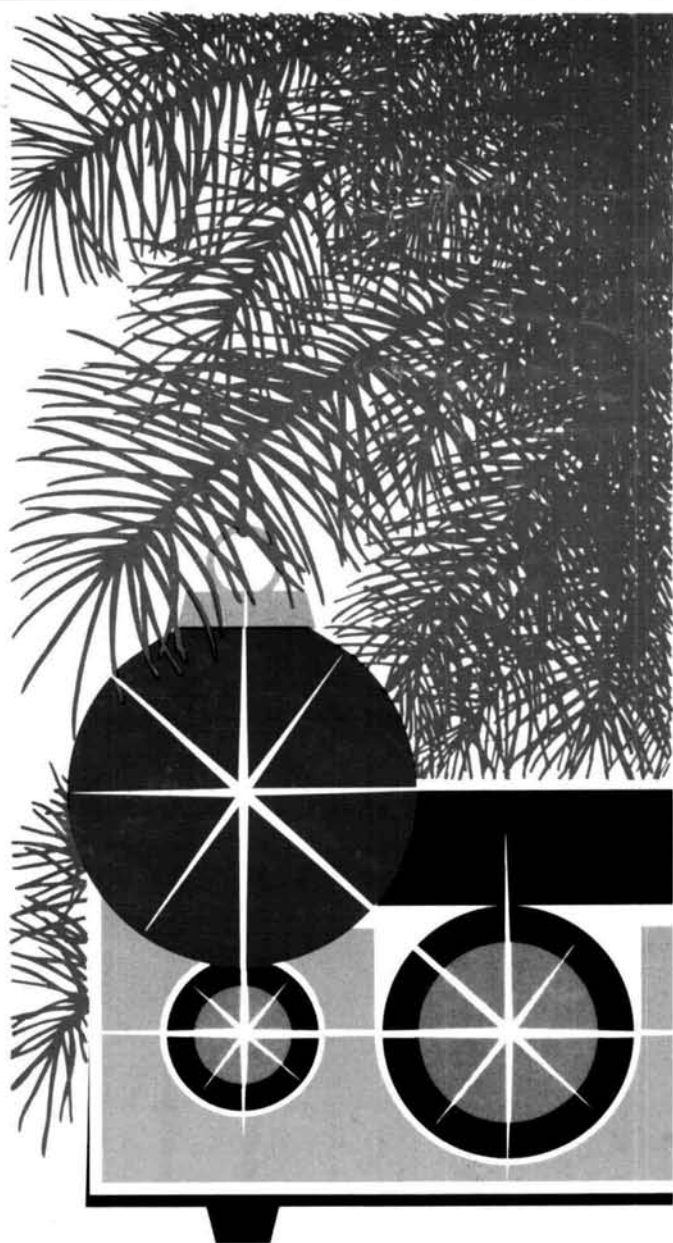
## DECEMBER 1977

- receiver problems and cures 10
- crystal filter converter 20
- rf wattmeter 38
- active bandpass filters 49
- phase-locked  
receiving converter 58
- 10-year cumulative index 130





## WE DON'T KNOW OF ANOTHER TRANSCEIVER OFFERING ALL THESE FEATURES AS STANDARD EQUIPMENT

- Hybrid digital frequency presentation . . . built-in
- AC and DC VDC power supplies . . . built-in
- CW filter . . . built-in
- High performance noise-blanker . . . built-in
- VOX and semi-break in CW keying . . . built-in
- Speaker . . . built-in
- Cooling fan . . . built-in
- Microphone . . . included

*When you buy the Tempo 2020 you don't have to spend a bundle on accessories . . . just hook up to a power source and an antenna and you're on the air. A truly fine transceiver at a modest price.*

The Tempo 2020 features a phase lock-loop (PLL) oscillator circuit that minimizes unwanted spurious responses. It is an advanced solid-state unit with only 3 tubes, including 2 rugged 6146-B final amplifier tubes. It covers all bands 80 through 10 meters, USB, LSB, CW and AM. Additional features worth noting is the 2020's crystal calibrator and WWV receiving capability, dual RIT control, fixed channel crystal control on two available positions, RF attenuator, adjustable ALC action, phone patch in and out jacks, separate PTT jack for foot switch, extraordinary receiver sensitivity (.3u S/N 10 db) and oscillator stability (100 Hz 30 min. after warm-up).


The **TEMPO 2020** ..... \$759.00  
**Model 8120 external speaker** ..... \$29.95  
**Model 8010 remote VFO** ..... \$139.00

*Send for descriptive information on the fine transceiver, or on the time proven Tempo ONE transceiver which continues to offer reliable, low cost performance. Both are available at select dealers throughout the U.S.*

# Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701  
 931 N. Euclid, Anaheim, Calif. 92801 714/772-9200  
 Butler, Missouri 64730 816/679-3127

# Get all this transceiver

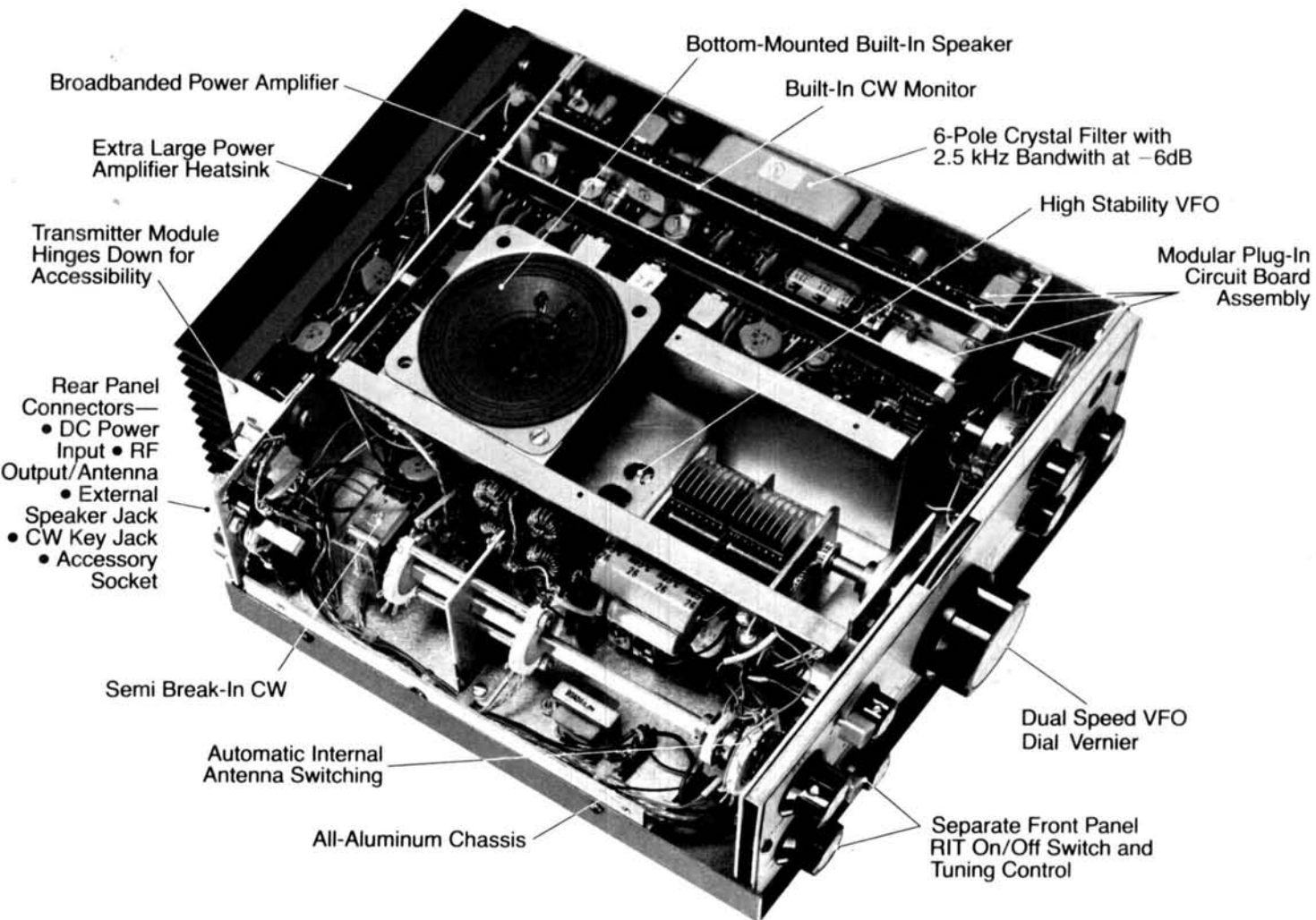

## for under \$500.

Available Options Include 100 kHz/10 kHz Dual Crystal Calibrator, Noise Blanker and Portable or Heavy Duty Power Supply

Microphone and mobile mount included.



ALDA 103 is completely manufactured in the U.S.A

# alda 103

totally solid state SSB Transceiver • 80 through 20 meters • 250 watts

ALDA Communications Inc., 214 Via El Centro, Oceanside, CA 92054 • (714) 433-6123

# Call toll-free 800-647-8660 for products by MFJ ENTERPRISES



**\$59<sup>95</sup>**

## MFJ-16010 ST Super Antenna Tuner

This NEW MFJ Super Antenna Tuner matches everything from 160 thru 10 Meters: dipoles, inverted vees, long wires, verticals, mobile whips, beams, balance lines, coax lines. Up to 200 watts RF OUTPUT. Built-in balun, too!

- Operate all bands with one antenna • Works with all solid state and tube rigs • Ultra compact: 5 x 2 x 6 inches • Uses toroid cores



**\$39<sup>95</sup>**

## MFJ-16010 Antenna Tuner

Now you can operate all bands — 160 thru 10 Meters — with a single random wire and run your full transmitter power output — up to 200 watts RF power OUTPUT.

- Small enough to carry in your hip pocket, 2-3/16 x 3-1/4 x 4 inches • Matches low and high impedance by interchanging input and output • SO-239 coaxial connectors • 12 position tapped inductor. Stacked toroid cores • At 1.8 MHz tuner matches 25 to 200 ohms.



**\$29<sup>95</sup>**

## CWF-2BX Super CW Filter

This MFJ Super CW Filter gives you 80 Hz bandwidth, and extremely steep skirts with no ringing for razor sharp selectivity that lets you pull signals out of heavy QRM. Plugs between receiver and phones or connect between audio stage for speaker operation.

- Selectable BW: 80, 110, 180 Hz • 60 dB down one octave from center frequency of 750 Hz for 80 Hz BW • Reduces noises 15 dB • 9 V battery • 2-3/16 x 3-1/4 x 4 inches • CWF-2PC, wired PC board, \$19.95.



**\$69<sup>95</sup>**

## MFJ-8043 IC Deluxe Electronic Keyer

This NEW MFJ Deluxe Keyer gives you more features per dollar than any other keyer available.

- Uses Curtis-8043 keyer chip • Sends iambic, automatic, semi-automatic, manual • Use squeeze, single lever, or straight key • Dot memory, self-completing dots and dashes, jam proof spacing, instant start • RF proof • Solid state keying  $\pm 300$  V max • Weight, tone, volume, speed controls • Uses 4 C-cells; external power jack • 6 x 6 x 2 inches • Sidetone and speaker • Optional squeeze key: \$29.95



**\$54<sup>95</sup>**

## CMOS-8043 Electronic Keyer

State of the art design uses CURTIS-8043 Keyer-on-a-chip.

- Built-in Key • Dot memory • Iambic operation with external squeeze key • 8 to 50 WPM • Sidetone and speaker • Speed, volume, tone, weight controls • Ultra reliable solid state keying  $\pm 300$  volts max • 4 position switch for TUNE, OFF, ON, SIDETONE OFF • Uses 4 penlight cells • 2-3/16 x 3-1/4 x 4 inches



**\$59<sup>95</sup>**

## LSP-520BX II Log Speech Processor

Up to 400% more RF power. Plugs between your microphone and transmitter.

- Gives your audio punch power to slice through QRM • 30 dB IC log amp and 3 active filters • RF protected • 9 V battery • Two Mic jacks: 1/4" phone jacks; uncommitted 4 pin jack • Output cable • 2-1/8 x 3-5/8 x 5-9/16 inches • LSP-520BX, in standard MFJ enclosure, electronically identical, \$49.95



**\$29<sup>95</sup>**

## SBF-2BX SSB Filter

Dramatically improves readability.

- Optimizes your audio to reduce sideband splatter, remove low and high pitched QRM, hiss, static crashes, background noise, 60 and 120 Hz hum • Reduces fatigue during contest, DX, and ragchewing • Plugs between phones and receiver or connect between audio stage for speaker operation • Selectable bandwidth IC active audio filter • Uses 9 volt battery • 2-3/16 x 3-1/4 x 4 inches



**\$29<sup>95</sup>**

## MFJ-200BX Frequency Standard

Provides strong, precise markers every 100, 50, or 25 KHz well into VHF region.

- Exclusive circuitry suppresses all unwanted markers • Markers are gated for positive identification. CMOS IC's with transistor output • No direct connection necessary • Uses 9 volt battery • Adjustable trimmer for zero beating to WWV • Switch selects 100, 50, 25 KHz or OFF • 2-3/16 x 3-1/4 x 4 inches



**\$49<sup>95</sup>**

## MFJ-1030BX Receiver Preselector

Clearly copy weak unreadable signals (increases signal 3 to 5 "S" units).

- More than 20 dB low noise gain • Separate input and output tuning controls give maximum gain and RF selectivity to significantly reject out-of-band signals and reduce image responses • Dual gate MOS FET for low noise, strong signal handling abilities • Completely stable • Optimized for 10 thru 30 MHz • 9 V battery • 2-1/8 x 3-5/8 x 5-9/16 inches



**\$29<sup>95</sup>**

## MFJ-40V QRP Transmitter

Work the world with 5 watts on 40 Meter CW.

- No tuning • Matches 50 ohm load • Clean output with low harmonic content • Power amplifier transistor protected against burnout • Switch selects 3 crystals or VFO input • 12 VDC • 2-3/16 x 3-1/4 x 4 inches

MFJ-40V, Companion VFO ..... \$29.95

MFJ-12DC, IC Regulated Power Supply, 1 amp, 12 VDC ..... \$29.95



**\$17<sup>95</sup>**

## CPO-555 Code Oscillator

For the Newcomer to learn the Morse code. For the Old Timer to polish his list.

For the Code Instructor to teach his classes.

- Send crisp clear code with plenty of volume for classroom use • Self contained speaker, volume, tone controls, aluminum cabinet • 9 V battery • Top quality U.S. construction • Uses 555 IC timer • 2-3/16 x 3-1/4 x 4 inches

TK-555, Optional Telegraph Key ..... \$1.95



**\$19<sup>95</sup>**

## C-500 Digital Alarm Clock

This digital alarm clock is also an ID Timer. Assembled, too!

- Gives ID buzz every 9 minutes automatically, or after tapping ID/doze button • Pressing ID/doze button displays seconds • Large 63 inch digits • Easily zeros to WWV • AM and PM LED indicators • Power out indicator • Fast set, slow set buttons • 110 VAC, 60 Hz • 3-1/8 x 3-3/4 x 3-3/8 inches • One year warranty by Fairchild

Order any product from MFJ and try it. If not delighted, return within 30 days for a prompt refund (less shipping).

Order today. Money back if not delighted. One year unconditional guarantee. Add \$2.00 shipping/handling.

Order By Mail or Call TOLL FREE 800-647-8660 and Charge It On



**MFJ ENTERPRISES**

P. O. BOX 494

MISSISSIPPI STATE, MISSISSIPPI 39762

In Europe contact: ING I. STERN, Lohkoppelstrasse 27, 2000 Hamburg 76, West Germany. Tel.: (040) 299-6110, Telex: 2161808 STEX D

# **ham radio**

**magazine**

**DECEMBER 1977**

**volume 10, number 12**

**T. H. Tenney, Jr., W1NLB**  
publisher

**James R. Fisk, W1HR**  
editor-in-chief

**editorial staff**

Charles J. Carroll, K1XX  
Alfred Wilson, W6NIF  
assistant editors

Patricia A. Hawes, WA1WPM  
Thomas F. McMullen, Jr., W1SL  
Joseph J. Schroeder, W9JUV  
associate editors

Wayne T. Pierce, K3SUK  
cover

**publishing staff**

Harold P. Kent, WA1WPP  
assistant publisher

Fred D. Moller, Jr., WA1USO  
advertising manager

James H. Gray, W1XU  
assistant advertising manager

Therese R. Bourgault  
circulation manager

**ham radio magazine**  
is published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**subscription rates**

U. S. and Canada: one year, \$12.00  
two years, \$22.00  
three years, \$30.00

Europe, Japan, Africa:  
(via Air Forwarding Service)  
one year, \$25.00  
two years, \$45.00

North America, South America, Australia  
and Asia (except Japan):  
(via Surface Mail)  
one year, \$18.00  
two years, \$34.00

**foreign subscription agents**

Foreign subscription agents are  
listed on page 113

Microfilm copies  
are available from  
University Microfilms, International  
Ann Arbor, Michigan 48106  
Order publication number 3076

Cassette tapes of selected articles  
from *ham radio* are available to the  
blind and physically handicapped  
from Recorded Periodicals  
919 Walnut Street, 8th Floor  
Philadelphia, Pennsylvania 19107

Copyright 1977 by  
Communications Technology, Inc  
Title registered at U. S. Patent Office

Second-class postage  
paid at Greenville, N. H. 03048  
and at additional mailing offices  
Publication number 23340

## **contents**

**10 problems and cures for  
present day receivers**

J. Robert Sherwood, WB0JGP  
George B. Heidelman, K8RRH

**20 i-f filter converter**

Howard J. Sartori, W5DA

**26 how to choose TTL sub-series**

Ian MacFarlane, WA1SNG

**30 500-watt power supply**

Chu Chung Lo, WA6PEC

**35 voice-operated gate**

Henry D. Olson, W6GXN

**38 low-power rf wattmeter**

James H. Bowen, WA4ZRP

**45 drift-correction circuit for  
free-running oscillators**

Klass Spaargaren, PA0KSB

**49 active bandpass filters**

Terry A. Conboy, WB6GRZ


**58 phase-locked receiving converter**

Keith H. Sueker, W3VF

**4 a second look**  
**150 advertisers index**  
**130 cumulative index**  
**113 flea market**  
**124 ham mart**

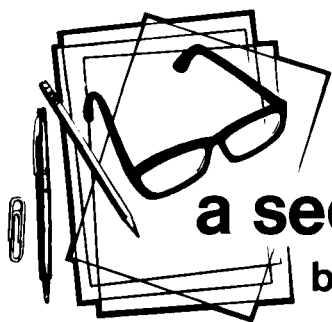**72 ham notebook**  
**84 new products**  
**6 presstop**  
**68 short circuits**





## a second look

by Jim Fisk

**During the holiday season** it's customary to take stock, to look back over the past year, and to make our resolutions for the next — resolutions, no doubt, which will be forgotten by the time the snow melts from the landscape and the trees begin to show their buds. The long winter nights are also a good time to plan that new antenna system or to dream about some new station equipment. With the snow swirling up to the window sills and the cold winds howling down from the north, perhaps it's a good idea to take some time to think about where amateur radio has been, and where it's going.

With the World Administrative Radio Conference (WARC) of 1979 now less than two years away, I can't help wondering what our amateur bands will look like in the 1980s. Will amateurs be given some of the additional high-frequency bands requested by the WARC planning committees, will the width of the amateur bands be pared down, or will we lose much or all of our high-frequency allocations? Nobody will know the answer to that until the final votes are tallied in 1979, but I suspect it will fall somewhere between the two extremes.

There are some who would have you believe there will be *no* high-frequency amateur bands after 1980, and very little vhf spectrum either, but I'm more optimistic than that. Optimism, unfortunately, leads to apathy and that, my friends, is our worst enemy. Perhaps it's best to prepare for the worst and approach WARC '79 with cautious optimism.

It must be remembered that the last international conference which had much effect on the high-frequency spectrum was held in 1947 when the United States and our Allies had considerable influence on the 50 member countries of the United Nations. Radio amateurs were highly regarded by our government for the part they played in war-time communications — not as amateurs, but because they provided a pool of trained technicians and communicators. To a lesser extent the same thing was true in Britain and the Soviet Union. Radio Amateurs were also the backbone of the communication networks set up by the resistance movement in Europe, and of the coast watchers in the South Pacific.

Governments which had severely curtailed amateur radio before the war now recognized its great potential as a national resource. Amateur radio was no longer considered a nuisance to be tolerated, but an activity which should be encouraged. Part of that encouragement was a new, exclusive 15-meter band. Old timers will hasten to point out that bits were shaved off the top ends of 10 and 20 meters, and 160 meters was dominated by Loran, but most amateurs agreed that 15 meters more than made up for the losses.

By the time the next ITU conference on high-frequency allocations was convened in 1959, the United States' sphere of influence had decreased and it looked like amateur radio was in serious trouble; the foreign broadcasters wanted big chunks of 40 and 80 as well as portions of 20 and it was uncertain if we could rally enough votes to save amateur radio. Fortunately some of the nations who weren't particularly friendly toward the United States but supported amateur radio came to the rescue, with the result that the amateur bands in the Western Hemisphere came through unscathed (amateurs in other parts of the world lost 50 kHz of shared space on 40 meters).

In general, the United States and other governments which were supportive of amateur radio in 1959 still are, but in the 20 years since that last conference the balance of power has changed; the emerging nations are now in the majority and they are not altogether in favor of amateur radio — a few ban it outright. Many of these nations have few amateurs, so to them the amateur bands represent wasted space — space they feel should be allocated to a radio service that better serves their national interest. These are the same countries which often oppose the policies of the rich western nations simply because it's in the vogue to do so.

Nevertheless, there's still hope, because many of the questions to be asked at WARC '79 will be answered on the basis of their scientific merits. There's bound to be a certain amount of political arm twisting, but if the delegates from the emerging nations can be made to see the value of an amateur radio service to the technological development of their nation, perhaps they can be persuaded to vote in favor of increased amateur spectrum.

**Jim Fisk, W1HR**  
editor-in-chief



# That's all, Folks!

All you need for All Mode Mobile, that is.

All Mode Mobile is now yours in a superior ICOM radio that is a generation ahead of all others. The new, fully synthesized **IC-245/SSB** puts you into FM, SSB and CW operation with a very compact dash-mounted transceiver like none you've ever seen.

- **Variable offset:** Any offset from 10 KHz through 4 MHz in multiples of 10 KHz can be programed with the LSI Synthesizer.
- **Remote programing:** The **IC-245/SSB** LSI chip provides for the input of programing digits from a remote key pad which can be combined with Touch Tone\* circuitry to provide simultaneous remote program and tone. Computer control from a PIA interface is also possible.

\* a registered trademark of AT&T.

- **FM stability on SSB and CW:** The **IC-245/SSB** synthesis of 100 Hz steps make mobile SSB as stable as FM. This extended range of operation is attracting many FM'ers who have been operating on the direct channels and have discovered SSB.

The **IC-245/SSB** is the very best and most versatile mobile radio made: that's all. For more information and your own hands-on demonstration see your ICOM dealer. When you mount your **IC-245/SSB** you'll have all you need for All Mode Mobile.

#### SPECIFICATIONS

FREQUENCY COVERAGE  
MODES  
SUPPLY VOLTAGE  
SIZE (mm)  
WEIGHT  
TRANSMITTER  
TX OUTPUT  
CARRIER SUPPRESSION

144.00 to 148.00MHz  
FM (F1)  
SSB (A3), CW (A1)  
DC 13.8V ± 15%  
30W × 150W × 230D  
2.7  
F3 10W  
1A2 10W (PER), A1 10W  
40 dB OR BETTER

SPURIOUS RADIATION  
MAXIMUM FREQUENCY  
DEVIATION  
MICROPHONE IMPEDANCE  
RECEIVER  
SENSITIVITY

40 dB BELOW CARRIER  
±5KHz  
600 OHMS  
1A2 0.5 MICROVOLT  
INPUT GIVES 10 dB S+N  
F3 0.5 MICROVOLT OR LESS  
FOR 20 dB CUE-TRNG  
S+N = 13 dB AT 1 MICROVOLT  
INPUT 30 dB

SQUELCH THRESHOLD  
SPURIOUS RESPONSE  
SYNTHESIZER  
FREQUENCY RANGE  
STEP SIZE  
STABILITY

9 dB OR LESS (F3)  
60 dB OR BETTER  
144 MHz to 148 MHz  
5 KHz for FM  
100 Hz or 5 KHz for SSB  
PER C in the RANGE OF -10°  
TO +60C ±0.000145%

\*VALID WITH SSB UNIT ONLY

VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

Distributed by:



## ICOM

ICOM WEST, INC.  
Suite 3  
13256 Northrup Way  
Bellevue, Wash. 98005  
(206) 747-9020

ICOM EAST, INC.  
Suite 307  
3331 Towerwood Drive  
Dallas, Texas 75234  
(214) 620-2780

ICOM CANADA  
7087 Victoria Drive  
Vancouver B.C. V5P 3Y9  
Canada  
(604) 321-1833



ARRL'S "CODE OF ETHICS" has been challenged in a formal written complaint filed with the Federal Trade Commission's Bureau of Competition.

Specific Complaints are that the Code will violate anti-trust laws by restraining trade, constitutes a "deceptive practice" as defined by the FTC, violates the First and Fourteenth Amendments to the Constitution, and that vendors who sign the ARRL pledge will become accessories after the fact in the above violations.

FCC'S DROPPING OF DOCKET 19759, the proposal that the 220-MHz Amateur band provide a home for a new CB service, doesn't mean that the band won't still become the new CB home. It does remove the immediate threat to the band, however, and many opinions have it that the longer the decision on where CB should go is delayed, the less likely 220 becomes as a choice.

In Announcing Its Termination of Docket 19759 the Commission pointed out that so many changes in related circumstances have occurred since several thousand comments were filed on it back in 1973, those comments were now obsolete. However, the question of a new CB band and where to put it is still very much alive, and 220 will undoubtedly be one of the options when the Commission considers the issue again in a future rulemaking.

A PETITION FOR RECONSIDERATION of the FCC's Report and Order on repeater deregulation (Docket 21033, Presstop, November), is being prepared by the ARRL. In it three issues will be emphasized: restoration of the WR-prefixed callsigns for repeaters, restoration of repeater licenses, and the need for formal consideration of the needs of the so-called "weak signal" vhf/uhf operations.

Plenty Of Support for the League position appears likely, as many repeater groups already oppose the dropping of repeater callsigns and licenses. In addition, reservations over the repeater sub-band expansion and even the proposed new bandplan for 144.5 - 144.5 MHz is starting to build among FM users as well as various SWOT and other VHF/UHF user groups.

AMATEUR LICENSING IRREGULARITIES will receive a full-fledged investigation run by an FCC Administrative Law Judge. The decision to go all-out on such a probe was reached at a closed meeting of the Commission, when information was presented that some Amateurs had apparently paid for the issuance or upgrading of their licenses or for special callsigns; that some of the same abuses may have occurred without payment; and that some Amateur callsigns have been issued inconsistent with normal FCC procedures.

ARTHUR C. CLARK, the noted science-fiction writer, was made an honorary AMSAT member in ceremonies attended by most of the AMSAT brass — Clark's honor came in recognition of his predictions of communications satellites and synchronous satellites in a 1945 Wireless World article.

1978 Orbital Prediction Booklets for OSCAR 7 only will be available shortly from Skip Reymann, W6PAJ, Box 374, San Dimas, California 91773. They're free to AMSAT Life members who request them; \$3 to AMSAT Annual members and \$5 to non-members — be sure to include AMSAT membership number and an self-addressed label with orders.

OSCAR 7's Mode Schedule will be changed effective January 1 to two days in Mode B for every day in Mode A, and the new schedule will be shown in W6PAJ's orbital calendar coming out in December. Ample Mode A operations will be provided by the Russian's "RS" spacecraft and AO-D, and OSCAR 7 is considerably more sensitive in Mode B than it is in Mode A.

A New Satellite Bandplan is also going into effect January 1 which will place CW only on the bottom third of the satellite downlink, mixed CW/SSB in the center third, and SSB only operation on the top third — the reverse of current practice.

OSCAR 6's Fifth Birthday was October 15, but revival efforts from VE3SAT failed to bring any response from it. RIP.


The Amateur Space Program made the Congressional Record in October when K7UGA lauded it during a Senate discussion of Sputnik's 20th anniversary.

THOSE PACIFIC AND CARIBBEAN prefix changes may not be as drastic as originally announced. FCC's news release announcing the change has now been "cancelled," and while it appears that prefix changes will still be made they'll be done in such a way that the resulting callsigns should identify the individual islands or island groups (Presstop, November).

FCC'S "GAG" ON DISCUSSIONS of current matters will remain in place as a result of the Supreme Court's decision not to review the Court of Appeals decision in the "Home Box Office" case (Presstop, June).

WESTINGHOUSE SCIENCE TALENT SEARCH is open to any high school student in the United States and Puerto Rico who'll graduate before October 1, 1978. Teachers who have an outstanding student who'd qualify for one of the many scholarships and awards must request entry materials from Science Service, 1719 N. Street, Washington, D.C. 20036 — entries are due by December 17, 1977.
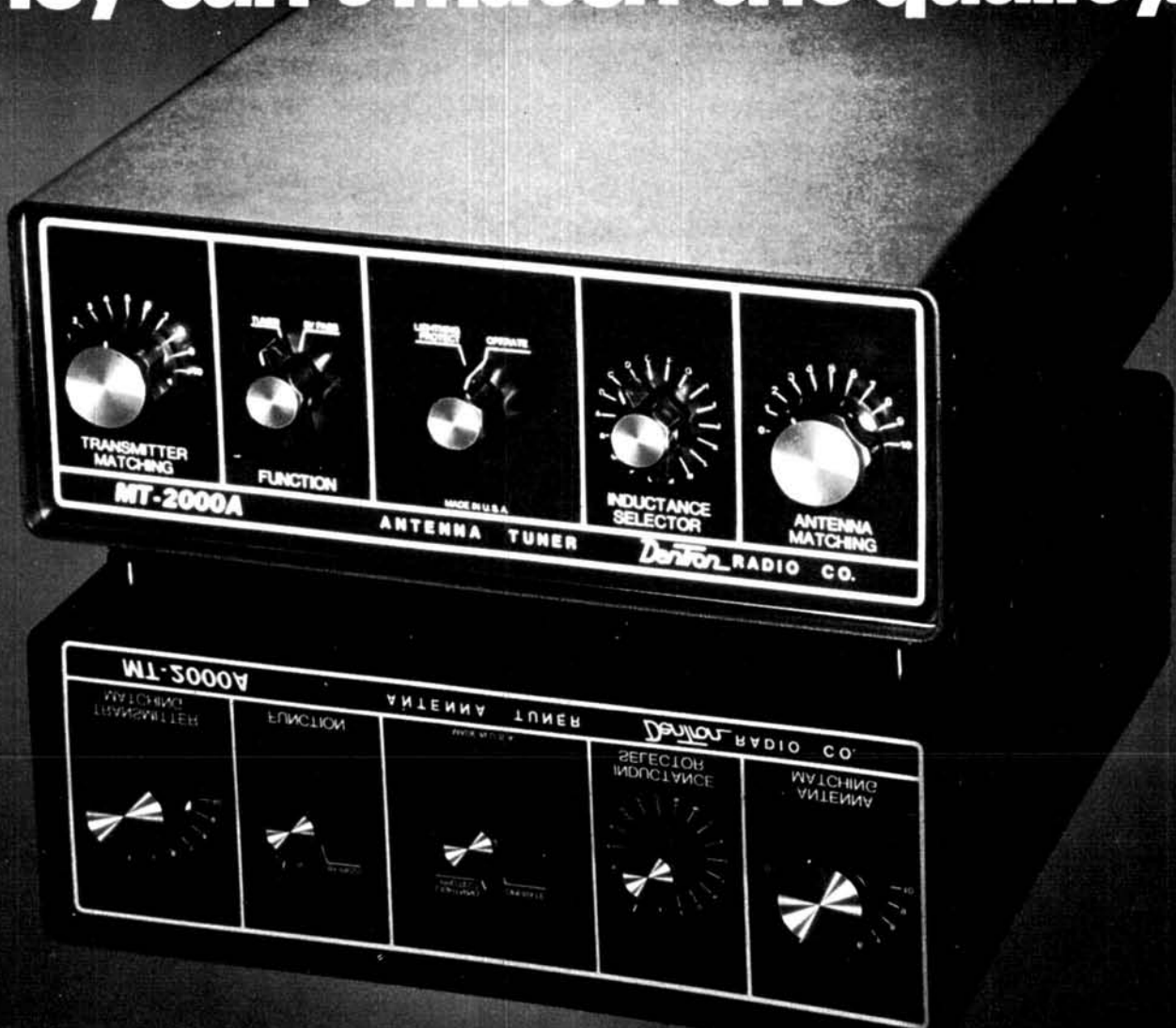
# If they copy the style, they can't match the quality.



# If they copy the quality, they can't meet the price.

The original DenTron Super Tuner. The original Super Super Tuner. The original MT-3000A. And now DenTron brings you the original MT-2000A, an economical, full-power tuner designed to handle virtually any type of antenna.

The sleek styling and low profile of the MT-2000A is beautiful, but be assured that is only a part of the excitement you'll derive from the MT-2000A. The MT-2000A is designed and engineered using heavy-duty all-metal cabinetry, and high quality American components throughout.

When you consider the MT-2000A's unique features: 5 1/2" H x 14" D x 14" W, front panel coax bypass switching, front panel lightning protection antenna grounding switch, 3KW PEP, and the ability to match

coax, random wire and balanced feedline, we're sure you'll decide to buy an American original and stay with DenTron.

**MT-2000A \$199.50** at your favorite dealer.

## DenTron






Radio Co., Inc.

2100 Enterprise Parkway  
Twinsburg, Ohio 44087

216 425-3173



# ATB-34

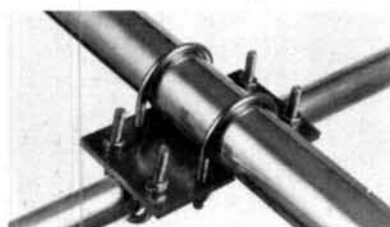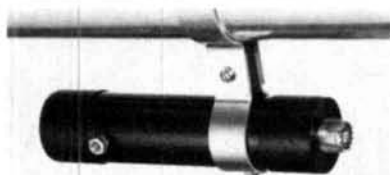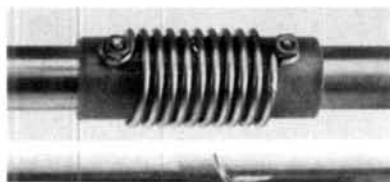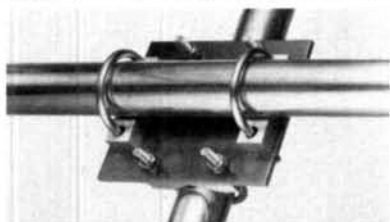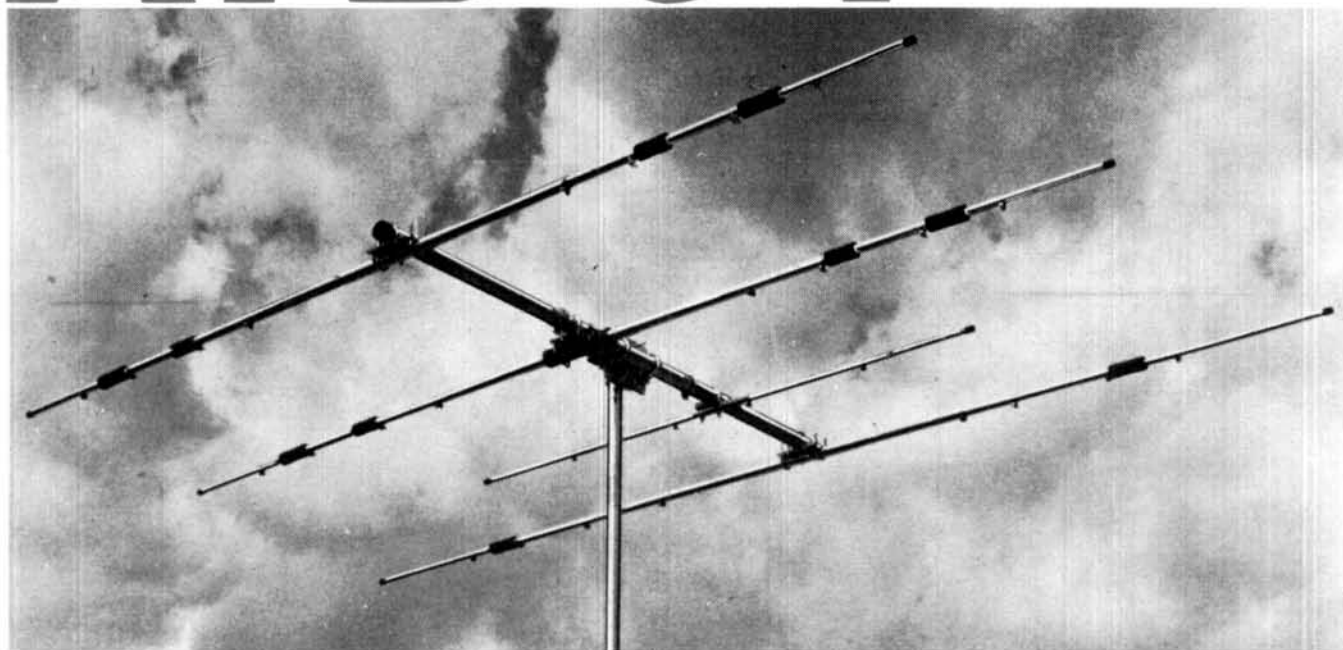

## 4 ELEMENT-3 BAND 10-15-20 METER BEAM

Cushcraft engineers have incorporated more than 30 years of design experience into the best 3 band HF beam available today. ATB-34 has superb performance with three active elements on each band, the convenience of easy assembly and modest dimensions. Value through heavy duty all aluminum construction and a price complete with 1-1 balun.

Enjoy a new world of DX communications with ATB-34!

### SPECIFICATIONS

FORWARD GAIN -	7.5 dBd	WIND SFC -	5.4 Sq.Ft.
F/B RATIO -	30 dB	WEIGHT -	42 Lbs.
VSWR -	1.5-1	WIND SURVIVAL -	90 MPH.
POWER HANDLING - 2000 WATTS PEP			
BOOM LENGTH/DIA. -	18' x 2 1/8"		
LONGEST ELEMENT -	32'8"		
TURNING RADIUS -	18'9"		

## \$239.95

COMPLETE

NO EXTRAS TO BUY

**UPS SHIPPABLE**

**IN STOCK WITH DISTRIBUTORS WORLDWIDE**




# cushcraft

CORPORATION

BOX 4680, MANCHESTER, N.H. 03108

# VHF DX

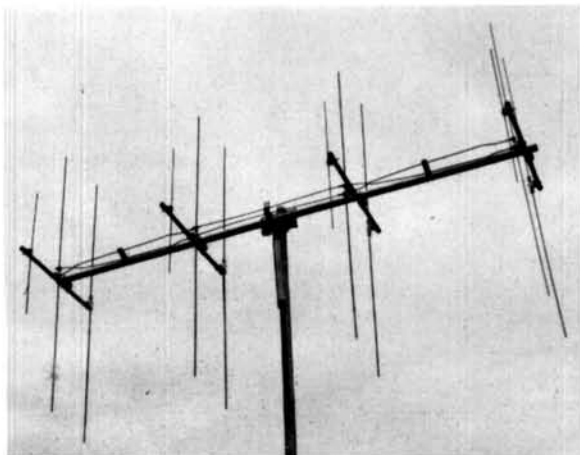


## FM —

Enjoy the thrill of dependable long distance contacts on simplex or thru remote repeaters. The 20 element co-linear DX-Array offers a precise pattern with large capture area. This vertically polarized, horizontally stacked array provides a narrow beamwidth for the discriminating FM user. Wide impedance and gain bandwidths make the DX-Array a natural choice for the serious FM'er. A vertical polarization bracket, model DX-VPB, is required (support boom and mast not supplied). Seek out new horizons with DX-Array!

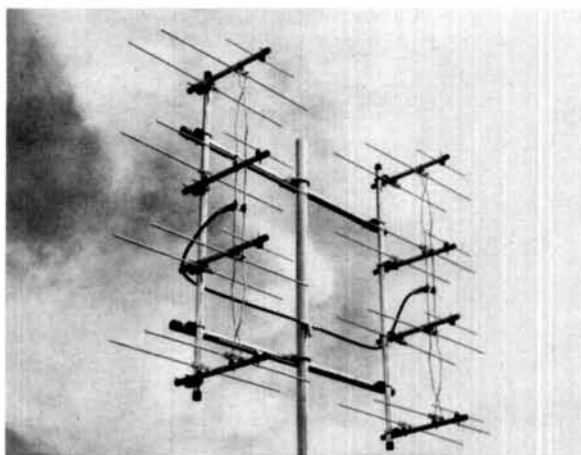
## SSB/CW —

Discover reliability in long-haul communications with VHF SSB and CW. The Cush Craft DX-Array also gives low angle, high gain performance for many exotic propagation modes — tropo, aurora, sporadic-E, and meteor scatter. Horizontally polarized DX-Arrays may be used singly or combined in pairs (twice Effective Radiated Power) or quads (4 x ERP). Each DXK stacking kit is complete with stacking frame and phasing harness (vertical mast not supplied). This year has seen some spectacular VHF band openings — Don't miss the next one!


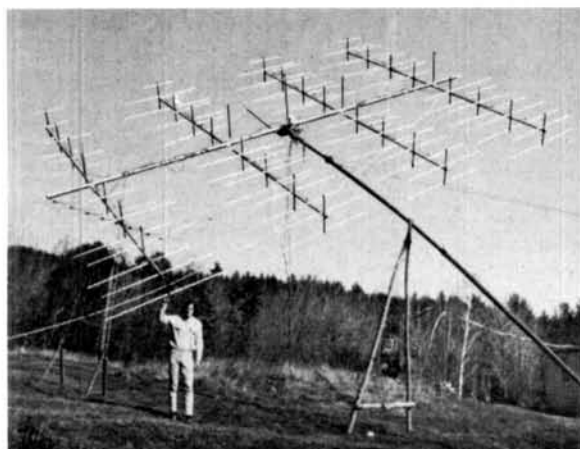
## EME —

Many VHF experimenters have found excitement in conquering the formidable Earth-Moon-Earth (EME) path. 2-meter moonbouncers have achieved outstanding success using eight stacked DX-Arrays. Impedance and gain characteristics of this antenna permit stacking without the critical detuning problems inherent in large arrays of Yagis. Enlarging system size will yield a more uniform gain increase with DX-Arrays than with many other large antennas. The physical configuration alleviates mounting and phasing/tuning problems. EME enthusiasts are setting new records — So can you!



Dave Olean, K1WHS, with his 160 Element DX-Array and Polar Mount EME System

**DX-ARRAY LEADS THE WAY!**

Description:	144 MHz.		220 MHz.		432 MHz.	
	Model:	Price:	Model:	Price:	Model:	Price:
20 Element DX-Array	DX-120	\$42.95	DX-220	\$37.95	DX-420	\$32.95
Frame & Harness (40 E.)	DXK-140	\$59.95	DXK-240	\$54.95	DXK-440	\$39.95
Frame & Harness (80 El.)	DXK-180	\$109.95	DXK-280	\$89.95	DXK-480	\$79.95
1-1 52-ohm Balun	DX-1BN	\$12.95	DX-2BN	\$12.95	DX-4BN	\$12.95
Vert. Pol. Bracket (20 El.)	DX-VPB	\$9.95	DX-VPB	\$9.95	DX-VPB	\$9.95

IN STOCK WITH  
DISTRIBUTORS WORLDWIDE



**cushcraft**  
THE ANTENNA COMPANY  
P.O. BOX 4680, MANCHESTER, N.H. 03108

# present-day receivers

## — some problems and cures

Some thoughts on  
and cures  
for problems  
encountered in  
modern amateur  
communications receivers

The modern-day communications receiver is going through a continuous evolution that has brought about significant improvement in certain operating features. Among these are greatly improved frequency stability and setability, better selectivity, a slow and consistent tuning rate from band to band, and a wide-range automatic gain control system that functions on CW and single sideband. At the same time, unfortunately, the design philosophies which have made the above advances possible have also reduced the typical receiver's ability to simultaneously handle weak desired and strong undesired signals. This absolute reduction in receiver dynamic range has occurred at the same time the number of high-power signals on the amateur bands has been increasing.

Insufficient dynamic range in a receiver can result in one or more stages being over-driven into nonlinearity by undesired strong signals. The result is internally-generated intermodulation distortion (IMD) products. These undesired products can occur in any mode of operation, but are easiest to identify on CW. Two CW signals which are overdriving a receiver will

generate IMD products, but only when both stations are transmitting simultaneously. In the extreme situation, not only may IMD occur, but one signal alone can block, deaden, or desensitize the receiver.

In a pileup or contest situation, many strong CW stations can cause serious receiver overload, intermodulating with each other, and resulting in multiple phantom signals; it will appear as if several operators are randomly tapping their keys, or that you are listening to the Novice band with a diode detector without a BFO.

Two or more ssb signals with the correct frequency relationship can also intermodulate with each other and result in IMD products on top of the station you are listening to. The interference, however, will be unintelligible. IMD can also occur from a single ssb station on an adjacent channel as the individual speech frequencies mix with their own harmonics. Generally speaking, transmitted IMD from an rf power amplifier will be worse than that internally generated in the receiver, with the result that the transmitted IMD may cover up a receiver's shortcomings. An operator may never be certain whether the unintelligible signals he hears are being generated within his receiver, or coming from the outside — there is enough rf interference to contend with without the receiver creating its own!

The improvements mentioned in the first paragraph have been generally obtained by using a double- or triple-conversion scheme, plus a non-bandswitched master oscillator (PTO or VFO). Depending on the design technique, the first i-f may have a bandwidth of as much as 500 kHz, as in the Heath SB-104, or as narrow as 6 kHz in the Drake R-4B. Assuming that most of a receiver's selectivity occurs at the second intermediate frequency, you might think that the wider the bandwidth of the first i-f, the greater the chance of picking up more strong signals which could overload the second mixer. Of greater importance than this bandwidth, however, is the *net gain* between the antenna and the mixer that drives the narrow crystal or mechanical filter.

The Collins R-390A, for example, has three mixers and two separate gain stages ahead of its mechanical

By J. Robert Sherwood, WB0JGP, and George B. Heidelman, K8RRH, Sherwood Engineering, Incorporated, 1268 South Ogden Street, Denver, Colorado 80210

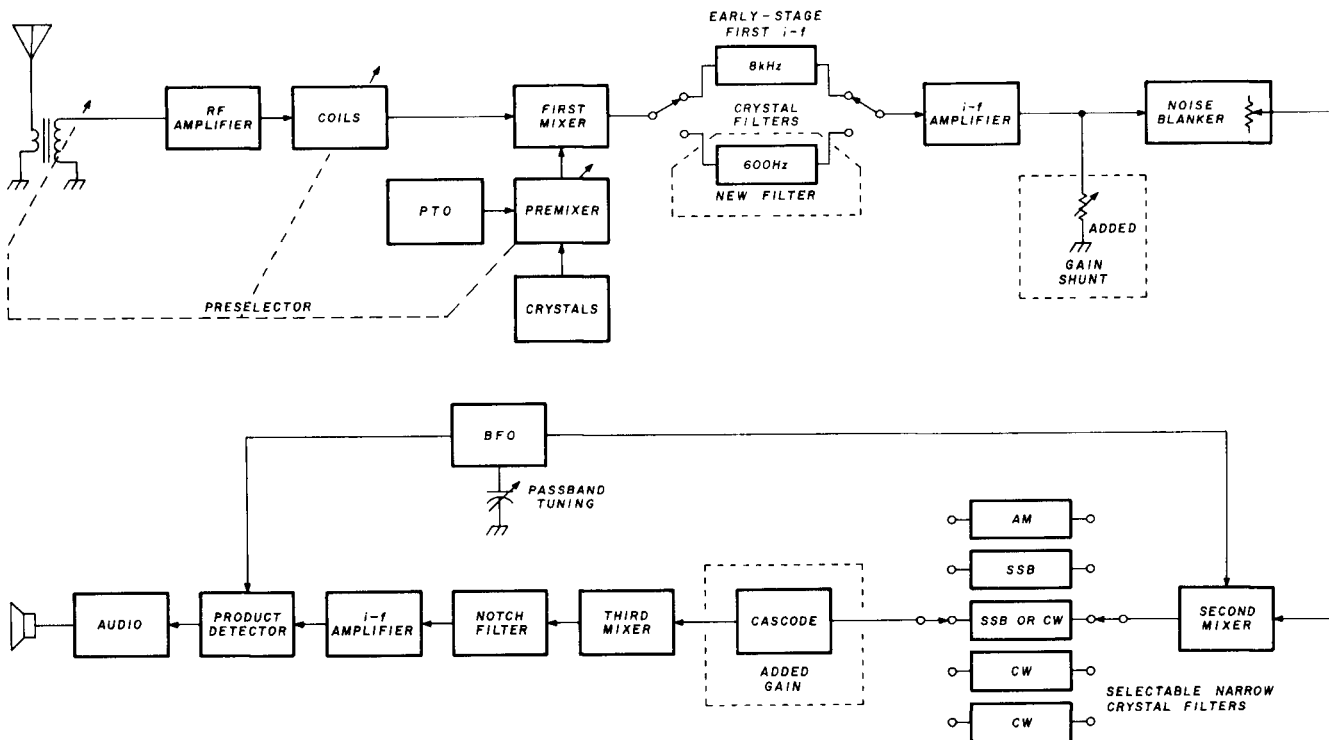


fig. 1. Block diagram of the Drake R4C receiver showing the gain redistribution. A shunt across the first i-f amplifier will reduce its gain the same amount as is added after the narrow i-f filters.

filters; it also has a set of elaborate, mechanically-tracked tuned circuits which have high  $Q$  and high insertion loss. Thus the net gain from the antenna to the major selectivity-determining elements is low enough to maintain good dynamic range.

Another receiver, the Heath SB-303, has a 500-

kHz wide first i-f *window*, but unlike the R-390A, it has little selectivity ahead of its narrow filters and too much gain. This results in higher susceptibility to overload from strong signals anywhere in the band, which then cause undesired IMD products to be generated within the receiver.

At the opposite end of the bandwidth scale is the Drake R-4C with its 8-kHz wide first i-f filter at 5645 kHz. This four-pole crystal filter does an excellent job of keeping most of the undesired signals in the band from passing on to a second high-gain mixer. However, any undesired strong signals that *do* pass through this 8-kHz *window* can proceed to the second mixer with disastrous results. The net gain from the antenna to the narrow second i-f crystal filter can be as high as 50 dB when a desired weak signal (S1) is being received; this puts an impossible demand on the i-f stages, since the 1-dB compression point of the second mixer output has occurred with any signal 30 dB over S9. An undesired signal, outside the narrow selectivity but inside the first i-f *window*, that is S9 + 40 dB (−33 dBm or 5 mV across the 50-ohm antenna input) for example, would have to be linearly amplified to a level of +17 dBm (1.58 volts across the 50-ohm narrow-filter input) and then be rejected by the filter. To supply this power level to the filter, the high-impedance plate of the second mixer would have to linearly swing more than 40 volts to yield a signal that is as great as 15

One topic that has received considerable attention by amateurs in recent years has been that of receiver performance and design. Many approaches have been covered, from the initial design of the "super receiver" to modification of existing equipment; but to the person with just a casual interest, the reasons behind some designs may not be readily apparent. In fact, the problems themselves may not be noticeable to the ordinary amateur. This article is another in a continuing series that shows you how to recognize the problems in typical modern receivers; in addition, it discusses modifications applied to one receiver and the motives behind these changes.

Of major importance is the reason for the modification. The intent of this article is *not* to prove that one particular receiver is superior to another for whimsical reasons, but to realistically and fairly compare different receivers by presenting test results on comparable circuits. On the basis of the test results, design changes were made in one receiver in an attempt to improve overall performance. You will notice while reading the article that the results are given in very specific terms; this will help you to better understand the basics of receiver performance standards. With this knowledge, you will be able to judge the merits of the different receivers on the market and choose one according to your own needs.

Editor

volts rms; even if this level could be produced in a low noise mixer, which is highly unlikely, the filter could be damaged.

What actually results when there are two undesired signals at  $S9 + 40$  dB with the correct frequency relationship, over loading the second mixer, is a spurious third-order IMD signal that is greater than  $S9$  in strength. This would certainly be strong enough to obliterate the desired weak signal!

One possible reason why such net-gain design errors are overlooked is our present method of testing receiver dynamic range. This subject has received considerable attention lately in *ham radio*<sup>1,2,3</sup> and *QST*.<sup>4</sup> An increasingly popular method of testing for dynamic range has been developed by Wes Hayward, W7ZOI, and is used by the ARRL.<sup>5</sup> Basically, it consists of applying two *well-isolated*, equal-strength signals, 20-kHz apart, to a receiver's input and then adjusting their level so that the undesired third-order IMD products generated within the receiver are just equal to the noise floor of the receiver. The difference in level between the noise floor and the test signals gives the receiver's dynamic range. The higher the receiver's dynamic range, the better it can handle both desired weak and undesired strong signals at the same time.

The choice of 20-kHz spacing for the two test signals is arbitrary and in many cases satisfactory. In a receiver which has all its significant selectivity far


Third-order IMD products, with 20-kHz spacing, will occur 20 kHz below the low frequency test signal and 20 kHz above the high frequency test signal. When the receiver is tuned to a third-order internally-generated spurious IMD signal, the test signals are 20 and 40 kHz up or down the band. The 25-kHz-wide crystal filter in the first i-f of the Signal-One transceiver, to name just one example, will greatly attenuate the test signals before they can reach the following stages. Thus, 20-kHz spacing will test only the front end and first mixer. What is needed is spacing narrow enough so that both test signals can pass through any selectivity prior to the narrow filter. We feel a spacing of 2 kHz will satisfy this requirement, and at the same time be wide enough so the narrow filter will adequately reject the test signals when the receiver is tuned to an IMD product.\*

The Drake R-4C, with its 8-kHz-wide first i-f filter, shows an inflated 20-kHz dynamic range of 83 dB. This reading has remained quite consistent over several receivers, including one we tested at the ARRL laboratory.<sup>†</sup> When the test signals are placed 2 kHz apart, however, so they *both* pass through the 8-kHz filter, the dynamic range drops to around 58 dB.
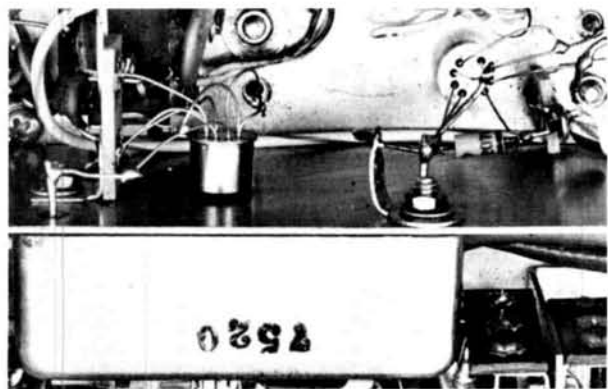
### improving receiver performance

There are three ways to improve a receiver's dynamic range. If the second mixer cannot handle the required level, one option is to replace it with a mixer that will do the job. Unfortunately, as WB4ZNV discovered,<sup>6</sup> the process of replacing an active mixer with the superior passive double-balanced mixer is a laborious task, even if it does improve the receiver's overload characteristics. Oscillator injection levels and impedances are usually not compatible with existing circuitry.

Another remedy is to redistribute the gain in the receiver, reducing it ahead of the overloaded stage and building it up again after the narrow filter. A third method is to insert more early-stage selectivity into the receiver so strong interfering signals are not as likely to get past the first mixer. We chose to inves-



Installation of the 600-Hertz first i-f filter. The filter is installed on a vertical shield near the original 8-kHz filter. The devices with 8 leads are TO-5 size relays that are used to select the appropriate filter.

down the i-f chain, this signal spacing is relatively unimportant. If the early-stage bandwidth is narrower than the test signal spacing, however, its selectivity will partially or completely reject one or both of the test signals, resulting in a highly inflated dynamic range reading. We feel these measurements should cover worst-case conditions since real-life interference on the amateur bands may be spaced less than 20 kHz.

\*When performing a 2-kHz IMD test, one very important factor must be taken into consideration: the noise sidebands of the signal generators. General test equipment, oscillators, or VFOs are more than adequate for testing, until a receiver's dynamic range nears 100 dB. At this point it will be impossible to accurately measure true receiver IMD products if the signal generators are producing excessive low-level spurs and noise. At this time there are only two or three generators that have the necessary sideband suppression; one manufactured by Hewlett-Packard and another by Rohde and Schwartz.

†The ARRL laboratory uses a pair of AN/URM-25 signal generators to perform IMD tests. A 2-kHz IMD test produced results within 2 dB of those obtained by the authors while using the high quality, low-noise sideband Rohde and Schwarz XUA signal generator.

tigate the latter two options, using our own R-4Cs.

The initial gain redistribution began with a 20-dB reduction of the signal level as seen by the second mixer. This gain loss was then restored after the narrow filters at the high-impedance grid of the third mixer. The original amplifier used a single jfet plus a step-up transformer to provide the necessary gain, but the circuit suffered from instability problems and noise. It was then decided to relocate the added gain outboard from the receiver and insert it at a convenient 50-ohm point, the output of the switchable second i-f crystal filters (see **fig. 1**).

A cascode jfet amplifier, with 50-ohm input and output impedances (**fig. 2**), was built and inserted into the i-f chain just prior to T-6. The coax cable that connects T-6 and the mode switch was lifted at the switch end; two lengths of miniature coax (RG-174/U) were then run out through a slot in the rear of the receiver. The first length is connected to the lugs on the mode-switch wafer, while the second is spliced into the cable that feeds the transformer.

This amplifier can possibly be located inside the receiver. Regardless of its location, it should be mounted in a metal box or other well-shielded enclosure. Two toroidal transformers provide the necessary impedance changes, their associated trimmer capacitors forming resonant circuits. While both trimmers can simply be peaked for maximum signal, the input may be fine-tuned for the best compromise signal-to-noise ratio among the switchable narrow filters. (The 2N5950 and 2N5953 jfets may be purchased from G. R. Whitehouse Company, Amherst, New Hampshire 03031).

We found the best way to attenuate the signal level into the second mixer was to swamp the output of the first i-f amplifier Q1 (V3/6BZ6 in early receivers). A miniature 5000-ohm multi-turn trimmer, from noise blanker socket pin 4 to ground, made a convenient way to adjust this level. Simply adjust the trimmer to drop the calibrator signal 20 dB on the S-meter; then adjust the gain pot on the cascode amplifier to restore the S-meter to its previous level. On certain receivers it may be necessary to peak T-6 to obtain 20 dB of gain from the cascode amplifier; always readjust both cascode trimmers after making a gain change.

If the noise blanker is installed in the receiver, significant IMD products can occur in its stages, too. Due to noise limitations, however, the blanker cannot be starved a full 20 dB. Instead, after replacing blanker resistor R1 with a 0.001  $\mu$ F disc capacitor, reduce the gain to the blanker about 12 dB, and then turn down the blanker output pot 8 dB to achieve the 20 dB reduction at the second mixer. Alternately, the gain of blanker transistor Q2 can be decreased by reducing its emitter resistor bypass capacitor, rather than readjusting the blanker output pot.

Take care not to use too much cascode amplifier or blanker gain; otherwise amplified 5645-kHz oscillator leakage can degrade system performance. With the antenna disconnected and the top and bottom covers of the receiver in place, make sure the S-meter does not kick upward more than one-quarter S-unit when the passband tuning is slowly turned through its range. In some receivers it may be necessary to jumper the cable-braid ground point of the Q4 oscillator board with a short clip lead to the shield tray on which the blanker board rests to reduce this oscillator leakage to an acceptable level. It might also be necessary to insulate the frame of the rear carrier-oscillator jack from the chassis ground.



The new product detector is installed next to the audio transformer and behind the variable capacitor used for passband tuning. The entire assembly is mounted on a 1-3/4 x 1-5/8 inch (4.5x4.1cm) board.

Also, if the cascode amplifier breaks into oscillation when the mode switch is between detent positions, reverse the leads of a high impedance winding of one of the toroids.

Proper operation of the gain redistribution circuits provided greatly reduced susceptibility to IMD overload problems on both CW and ssb, as was visibly demonstrated with strong nearby DX contest signals; yet the receiver was still able to meet its sensitivity specification. Agc attack distortion was also reduced somewhat. Dynamic range improved from 58 dB to around 70 dB, while using our 2-kHz spacing test method.

### i-f filters

As an additional CW remedy we chose to increase the selectivity (possibly on a switchable basis) following the output of the first mixer; the bandwidth is presently determined by an 8-kHz wide four-pole crystal filter. This bandwidth is needed on phone to pass an upper and/or lower sideband signal. A bandwidth of at least this magnitude is also required to pass undistorted noise pulses to the blanker. A noise blanker's usefulness, however, is marginal at best with one or more strong nearby signals, due to its agc greatly increasing the blanking threshold, or possible false triggering. Thus, the need for narrowing first i-f selectivity ahead of the noise blanker,

which reduces blanker effectiveness, occurs under conditions which are usually unfavorable to blanking in the first place.

Circumstances could occur where blanking would be necessary at all times, such as when you suffer from a continuous very high level of blankable noise. In these cases, the 8-kHz first i-f filter must remain ahead of the blanker. Then a properly-terminated narrow filter could be inserted just *after* the blanker, but before the second mixer. The signal path can be switched between the narrow filter and an attenuator equal to its loss. While the chance of second mixer overload is greatly reduced with this arrangement, there is no such narrow bandwidth IMD protection for the blanker; this limits the receiver's potential dynamic range considerably below what is otherwise obtainable. It is therefore mandatory to use the cascode gain redistribution system with this special, optional filter arrangement. With this arrangement close-in dynamic range will be in the high 70s.

We decided that the first i-f CW selectivity should be equal to the widest desirable under contest conditions. We then designed a new 600-Hz six-pole filter, keeping in mind package size limitations and insertion loss requirements. We've also developed a miniature relay system which allows instant interchange of our internally-mounted, CW-bandwidth, first i-f filter with the existing 8-kHz phone unit.

The project of minimizing overload in the R-4C was now complete and totally successful. When measured using our worst-case 2-kHz test method, the receiver's dynamic range jumped from an original unacceptable 58 dB to a final excellent 85 dB. This value ranks with the best of the commercially-available amateur gear on the market today, and

should be more than adequate for most practical situations. As a side note, a similar arrangement of first i-f filter switching can be used on ssb by inserting a set of 2.6 or 2.3-kHz phone filters in the first i-f for improved phone selectivity.

## simple receiver testing

While we made use of a considerable amount of test equipment during this project to measure dynamic range, you can make comparative tests using only a crystal calibrator and transmitter vfo, *loosely* coupled into the receiver. Comparative noise floor measurements, with no antenna connected, can be made by measuring the preselector noise peak (above later stage noise) with an ac voltmeter connected to the audio output line.

When making gain redistribution or selectivity changes, adjust the receiver to maintain its original net gain by measuring the calibrator level on some specific frequency. We use 7.2 MHz as our reference frequency. Here the calibrator level should read about 15 to 20 dB over S9 with nothing connected to the antenna input. (Don't readjust the S-meter sensitivity pot.) Two strong test signals, accurately set to a specific S-meter level, will produce a repeatable reference IMD that can also be measured on the S-meter. As improvements are made the IMD, read on the S-meter, will drop. We made our 2-kHz tests at S9 + 40 dB, and ended up reducing the IMD from greater than S9 to less than S3.

## filter rejection

The 600-Hz first i-f filter, in addition to greatly reducing the chance of overload, had the extra benefit of eliminating the annoying signal leakage around the narrow second i-f filters. This problem of not being able to realize the ultimate rejection capabilities of a well-designed filter is one that plagues all equipment that, to our knowledge, is presently on the market. It is really quite difficult to even design a test fixture to correctly measure the ultimate rejection of a filter. Obtaining adequate ultimate attenuation, which should be in excess of 100 dB for an eight-pole filter in a receiver or transceiver, requires tedious attention to detail. Current ground loops and stray capacitive coupling are the main problems that must be eliminated. We have had many frustrated amateurs ask us to provide a filter for their receiver or transceiver which would not leak like the factory installed units. Unfortunately, some of the limitations were in the receiver and not the filter. Although replacing or adding to an existing *late* narrow filter can often considerably improve skirt selectivity, the only way to eliminate the last traces of these leakage problems, in existing popular receivers, is to add a filter earlier in the set with a

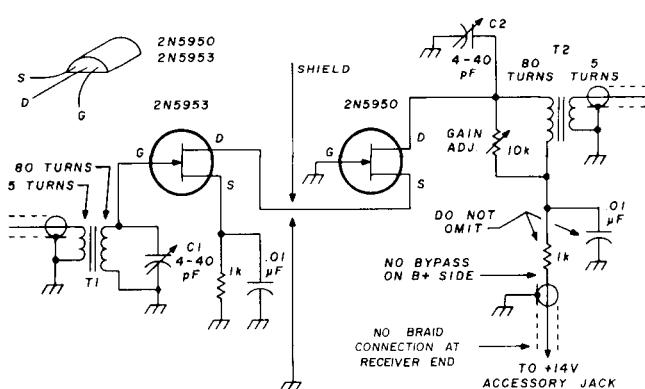


fig. 2. Schematic diagram of the cascode amplifier used for the gain redistribution. There is only one ground return on the circuit, through the input coax cable. The braid on the output coax cable goes to the primary of T6 which is not grounded at that point. T1 and T2 are wound on Micrometals T-50-2 toroidal cores. The high-impedance windings are 80 turns of no. 30 AWG (0.25mm) while the low-impedance windings are 5 turns of no. 24 AWG (0.5mm).

bandwidth closer to that of the main filter. The early filter should preferably be on a different frequency from the later one, such as in the R-4C or 2B.

We tested one all-solid-state American transceiver that had so much leakage around the CW filter that a 2-kHz dynamic range test could barely be made. The IMD was masked by the test signal leakage until special audio filtering was employed.

While discussing filters, we would like to emphasize the importance of a great variety of bandwidths being available to the operator. Most of the equipment on the market has just one standard phone bandwidth, with one CW filter available as an option, and when installed it must be used at all

with this trade-off, there is an additional insertion loss of 5 to 7 dB compared to the phone filter, and relatively poor skirt selectivity.

As a minimum, the receiver net gain should be designed around the lossiest filter, with the losses of the other filters increased to that constant level. Another school of thought suggests that the noise integrated by each of the filters should be the same, requiring increasing gain (or decreasing insertion loss) as narrower filters are selected. To our knowledge, no amateur equipment manufacturer is currently keeping the integrated noise constant, and only the R-4C provides for constant insertion loss with narrow bandwidth filters.

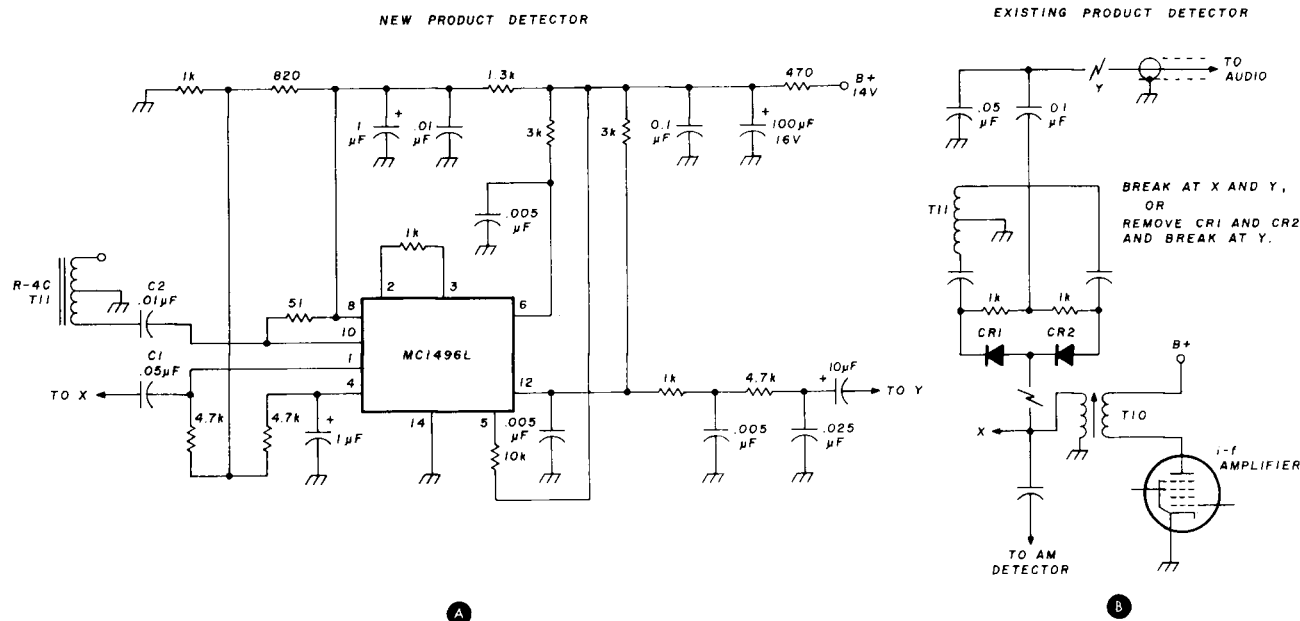


fig. 3. The MC1496L can be used as a product detector as shown in A. The IC plus associated components are mounted on a small circuit board which is installed next to the audio transformer in the receiver. C1 and C2 are critical values and should not be substituted. For smaller size, the 1- $\mu$ F capacitors may be tantalum. B shows the interconnections between the detector and the receiver.

times for that mode. Many of the imported rigs are examples of these limitations. The Yaesu FT-101B has only a six-pole 600-Hz filter, and the Kenwood TS-820 is limited to only a six-pole 500-Hz unit.

By today's standards a six-pole 500-Hz filter is quite broad and has a poor shape factor. One possible reason for offering only these filters is that the design of the equipment was based on the use of an ssb filter having an insertion loss of only 2 to 4 dB. Unless a manufacturer employs special technology in building, say, an eight-pole 350-Hz filter that is more advanced than required for a phone filter, the insertion loss will rise to an unacceptable 14 to 16 dB. It is quite undesirable to have the signal drop 12 dB when the CW filter is used; a compromise is made, and the six-pole filters mentioned above are offered. Even

We have noted with interest the comments from some of our Japanese and German filter customers about American rigs such as the R-4C and T-4XC. The cost of these units in their home countries, due to import duties, is 30 to 50 per cent higher than here in the United States, but the discriminating foreign amateur is willing to pay that premium partly because of the excellent filters which are available. Compared with the typical filter in the average set, the Drake eight-pole 250-Hz and the Sherwood eight-pole 125-Hz CW filters are valuable assets. Similarly, an optional 1500 to 1800-Hz ssb filter\* can make the dif-

\*Drake also offers the FL1500, a 1500-Hz filter. Though publicized as an RTTY filter, it provides exceptional performance, especially under difficult phone contest conditions.

Editor.



Cascode amplifier used for gain redistribution is installed in a small enclosure. The shield must be in place between the stages of the amplifier.

ference in being able to hold a contact under heavy interference and contest conditions.

It takes some practice to become proficient at using a narrow i-f filter, just as in learning to tune with the wide-skirted audio filters. But during crowded band conditions a 250-Hz filter can often be too broad! One CW operator used the 125-Hz filter in his R-4C almost exclusively during the hectic 160-meter contests.

The entire line of filters for the R-4C is excellent and can be adapted to any receiver or transceiver. A construction article in the 1977 ARRL *Handbook*<sup>7</sup> describes a method of adding bandpass tuning to a receiver lacking this feature. This circuit uses 455-kHz filters and is inserted in the receiver i-f chain by converting down to 455 kHz and back up again. This basic idea can be used with any pair of filter and receiver intermediate frequencies.

You could convert from 3395 kHz up to 5695 kHz and back down again, for example, or down from 9 and up again. As the difference between the two i-f frequencies becomes smaller, the difficulty of the conversion process increases. A Drake R-4B owner who wishes to add R-4C filters to his receiver has to cope with a conversion frequency difference of only 50 kHz. Howard Sartori, W5DA, has developed a circuit for use in his R-4B which can be adapted to any i-f by simply changing one crystal oscillator. It has been used on intermediate frequencies as low as 50 kHz and as high as 30 MHz with excellent results. His circuit is described on page 20 of this issue of *ham radio*. One precaution, when adapting the *Handbook* circuit or W5DA's i-f converter to a transceiver: make sure the transmitted signal does not have to pass through the added filters. Otherwise, with use of the two narrowest filters (the FL-250 and CF-125/8), the

transmitter carrier offset frequency adjustment would become quite critical, and keying on the transmitted signal could be too soft.

The Kenwood TS-820, which we have in the lab, has a noise floor and dynamic range in the ssb mode that is virtually identical to that of the Drake R-4C. Both units perform very well on phone; when you want to dig out a weak CW signal on a quiet band, however, the R-4C is significantly better. The R-4C's gain remains constant when a CW filter is switched in, but the TS-820's drops off 5 to 6 dB. Even if a weak received signal is above the noise floor, this gain reduction increases the agc threshold to the point where it may become necessary to manually ride the gain control. The Yaesu FT-101B we tested had a dynamic range, at any test signal spacing, as bad as the unmodified R-4C when measured with the *worst-case* 2-kHz test method. The bulk of the problems in the FT-101B were caused by a bipolar transistor in the noise blanker which was being over-driven.

A receiver's maximum net gain from the antenna to the detector can change significantly from band to band without having much effect on the measured sensitivity. Two sets with similar signal requirements for a given signal-to-noise ratio can have vastly different capabilities in handling weak, fluctuating signals, especially on the 10- and 15-meter bands. As the net gain falls off, more and more signals will fall below the agc threshold. The R-4C, for instance, holds a much more consistent net gain from 80 to 10 meters than the TR-4C. The TS-820 increases the net gain on 10 meters compared to 20 and 15 by changing a capacitive tap on the rf amplifier drain. Its gain, however, is too high on 160 meters, resulting in a higher susceptibility to overload by broadcast stations. When connected to a nearly self-resonant 160-meter vertical antenna at our lab in Denver, the TS-820 grossly overloads with the eighteen local broadcast stations, developing more than 1 volt across its antenna input. Without the 20-dB rf attenuator switched in, the 160-meter band is nothing but a solid mass of S9 + 30 dB IMD products.

The TS-820's front end is not selective enough to cope with this admittedly unusual receiving situation. On 1.8 MHz, the preselector attenuates signals that are 100 kHz off frequency by 18 dB. In comparison, the R-4C attenuates these same signals by 38 dB. On 3.6 MHz, the TS-820's front end is down 8 dB at 100 kHz off frequency, the TR-4C by 12 dB, and the R-4C by 24 dB. When tested on 10 meters, the 500-kHz attenuation is 8 dB on the TS-820, 8 dB on the TR-4C, and 15 dB on the R-4C.

One way to eliminate the need for a sharp preselector is to use an up-conversion scheme, with the first i-f above 40 MHz. The input may only need a

bandpass filter that rejects signals below 1.8 and above 30 MHz. Then image signals would fall above 80 MHz and be virtually eliminated by the bandpass filter. The first mixer must have a much greater signal-handling capability than in present receivers, however, because it would see all stations between 1.8 and 30 MHz. Two strong local signals, one on 14 and the other on 21 MHz, could produce a 7-MHz IMD product.

The R-4C and the TS-820 show a 20-kHz test-signal-spacing dynamic range in the ssb mode of about 80 dB when tested on 20 meters. At this frequency, the preselectors do not significantly enter into the dynamic range test, since they will not attenuate the test signals more than 1 dB. This is not the case on 160 meters, especially with the R-4C. Here, its high-Q front end attenuates the 20-kHz signals enough to raise the dynamic range by 12 dB. On the other hand, some receivers have too much gain on 80 and 160 meters which, even with sharp preselectors, could yield a dynamic range no better (or even worse) than on 20 meters.

While the 20-kHz dynamic range of the R-4C improves on the lower frequencies because of its preselector, the 2-kHz dynamic range measurement remains quite constant at just under 60 dB. Similarly, it is consistently above 83 dB with the 600-Hz first i-f filter that cures its *window* overload problem. The TS-820 does not have this *window* problem since it is a single-conversion design and has no overloadable stages between the wide noise blanker filter and its narrow filter. Any improvement in dynamic range with increasing frequency separation of the test signals can only be attributed to its preselector.

A detailed review of the TS-820 in *CQ-DL*,<sup>8</sup> far more comprehensive than anything published in this country, showed a 6-dB improvement in dynamic range as the test signal spacing was increased from 2 to 50 kHz. It is interesting to note that *CQ-DL* also feels that a close-in 2-kHz spacing is necessary for proper evaluation.\*

The Atlas 210X, without its noise blanker operational, has a better than average dynamic range of about 90 dB, which would be even better if its double-balanced mixer were properly terminated above the i-f frequency.<sup>2</sup> This could be accomplished with the use of a diplexer, as described by Wes Hayward,<sup>4</sup> or with a power jfet, as related by Ulrich Rohde.<sup>2,3</sup> There is one limitation in the 210X that cannot be easily remedied, however; its potential strong-signal handling capabilities cannot be fully realized due to its noisy conversion oscillator. Since this oscillator has noise sidebands that are only 65 dB down 10 kHz on each side of its center frequency, all


the signals passing through the mixer will take on similar noise sidebands. Consider a strong station near a desired signal that is weaker in amplitude. Reciprocal mixing of oscillator noise can cause noise sidebands to be transferred to the strong nearby station and cause interference to the desired signal. Thus, even if the i-f filter's ultimate rejection is actually realized in the receiver circuitry, which is doubtful in practice, this high level of rejection can be negated by wide-band mixer noise. So while it takes two strong signals to cause IMD which can interfere with weak signal reception, a noisy oscillator and one strong signal can cause the same unfortunate results.<sup>9</sup>

The noise blanker in the Atlas 210X also degrades its dynamic range, diminishing the advantage of the double-balanced passive mixer. The 210X transceivers we tested had a dynamic range of between 73 and 81 dB, depending on the band selected. When the blanker was turned on, these numbers dropped by 3 dB.

There is little reason for a noise blanker to include additional gain stages which can degrade receiver performance. The TS-820 has only a 4-diode balanced blanker gate in its i-f chain; therefore, it does not reduce the overload capability or significantly increase the noise floor. Alternately, a balanced mixer or push-pull i-f stage can be gated for noise blanking; this requires no additional gain stages in the signal path.
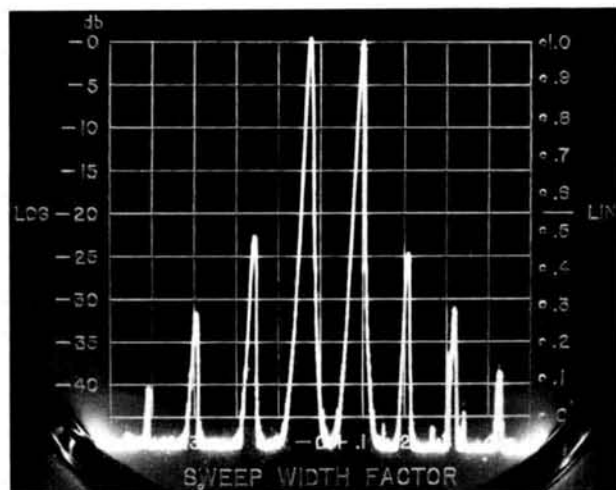
## product detectors

Another area that could use additional work is that of the product detector. As the name implies, its output should be the product of the two input signals. If



IMD generated at the output of the R-4C second mixer by two 5 mV signals at the antenna input. The signal spacing was 2 kHz. The receiver was tuned so that the narrow second i-f filter was positioned away from any test signals or IMD products. Therefore, with no signal reaching the AGC, the receiver gain is at maximum and the S meter reads S1.

\*A recent independent measurement by DJ2LR showed the intercept point of the TS820 to be -12 dBm.

BFO injection is removed, output should go to zero. If this is not the case, as in the Heath HW series, envelope detection is also occurring, which causes audio distortion. On the other hand, the 6GX6 product detector in the Drake R-4, TR-4, and TR-4C, and the 6BE6 in the Drake 2A and 2B, works very well.

Other extraneous outputs can occur even if the detector is acting solely as a product mixer. A detector should be a double-balanced, or other arrangement, which provides good isolation between input and output. The two-diode detector in the R-4B and R-4C is not a double-balanced design and allows the detected audio to leak back and envelope modulate the last i-f stage. This resultant signal is detected in the agc, which then tries to follow it at an audio rate, especially (but not only) when the faster time constants are in use. This audio output sounds slightly distorted, and is noticeable on ssb as well as CW. In addition, BFO injection is marginal, causing additional distortion on AGC attack.

We decided to replace the product detectors in our R-4C receivers, but wanted to use a device that was compatible with the existing drive and impedance levels. The MC1496L active double-balanced mixer looked like a good choice, and with minor circuit changes from the data sheet, was installed in the receiver. The modulation of the i-f by the detected audio was eliminated, resulting in cleaner sounding audio. AGC attack distortion was further reduced.

The MC1496's main drawback is its high number of associated components. Eleven 1/4-watt resistors, nine capacitors, and the IC had to be squeezed on a 1-3/4 by 1-5/8 inch (4.5x4.1cm) board which was nestled between the audio output transformer and the adjacent PC board (see **fig. 3**). All R-4C owners, whether they change product detectors or not, should add a 0.0015  $\mu$ F capacitor across R83 in the audio amplifier. This corrects a phase error in the feedback circuit, and eliminates an undesirable peak in the audio frequency response which accentuates harmonic distortion. The Kenwood TS-820 and the Atlas 210X both use a double-balanced diode product detector that works quite well, and needs considerably fewer parts, but they are low-impedance devices not easily adapted to some circuitry.

## conclusions

We have discussed several popular receivers and noted some of their strengths and weaknesses. Some problems can be corrected in the field, while others go beyond the scope of a weekend project. We've also investigated two ways to improve a receiver's susceptibility to overload, so that it can better handle today's high-level rf environment: redistributing the gain and increasing the early-stage

selectivity with an additional filter. The importance of having a wide choice of adequate narrow filter selectivity, without leakage, was also mentioned. While most of our circuit changes have been applied to one specific popular receiver, the Drake R-4C, the ideas can be extended to other sets. A method of checking a receiver's overload capabilities which requires no test equipment was also described. Thus receiver changes can be evaluated as to their effect on dynamic range.

The real key to how a receiver performs is its net gain distribution, particularly in relation to the location of selectivity determining elements. A receiver must have a great deal of gain from its antenna to the speaker to be able to receive weak signals. But if too much gain is placed ahead of a narrow filter, the receiver is bound to overload and generate interference of its own.

How a receiver will perform in real-life situations can be determined in the lab, but only if it is tested in a manner that approximates the real world. We feel that the present 20-kHz signal-spacing method can be quite misleading, and should be augmented with our 2-kHz test procedure. If the two readings are significantly different, then further investigation is warranted.

As we stated at the beginning of this article, receivers have improved in many ways, especially over the past 15 years; at the same time, dynamic range has diminished. Amateur radio operators should be demanding excellence in this critical parameter. Improvements in receiver versatility need not reduce system performance, as we have so often observed. Potential problems can be eliminated in new equipment by state-of-the-art design or by retrofitting existing receivers. All that will be lost is some internally-generated rf interference!

## references

1. James R. Fisk, W1HR, "Receiver Sensitivity, Noise Figure and Dynamic Range," *ham radio*, October, 1975, page 8.
2. Ulrich L. Rohde, DJ2LR, "High Dynamic Range Receiver Input Stages," *ham radio*, October, 1975, page 26.
3. Ulrich L. Rohde, DJ2LR, "High-Frequency Receiver Design," *ham radio*, October, 1976, page 10.
4. Doug DeMaw, W1FB, "His Eminence — the Receiver," *QST*, June, 1976, page 27.
5. Wes Hayward, W7ZOI, "Receiver Dynamic Range," *QST*, July, 1975, page 15.
6. Alex J. Burwasser, WB4ZNV, "Reducing Intermodulation Distortion in High-Frequency Receivers," *ham radio*, March, 1977, page 16.
7. Anthony Dorbuck, W1YNC, editor, *The Radio Amateur's Handbook*, American Radio Relay League, Newington, Connecticut, 1977, page 271.
8. Thomas Moiere, DL7AV, "Testbericht: Transceiver TS820," *CQ-DL*, (Germany) April, 1977, page 130.
9. Wes Hayward, W7ZOI, "A Competition-Grade CW Receiver," *QST*, March, 1974, page 19.

**ham radio**

TYPE	ALL SOLID STATE			HYBRID (VACUUM TUBE P.A.)			
MODEL	ATLAS 350-XL	TEN TEC	YAESU FT-301	DRAKE TR4-CW	HY-GAIN 3750	KENWOOD TS-820	TEMPO 2020
INPUT POWER	350 WATTS	200	200	300	200	200	180
BANDS	10-160M	10-80M 160M OPT	10-160M	10-80M	10-160M	10-160M	10-80M

TYPE	ALL SOLID STATE			HYBRID (VACUUM TUBE P.A.)			
MODEL	ATLAS 350-XL	TEN TEC	YAESU FT-301	DRAKE TR4-CW	HY-GAIN 3750	KENWOOD TS-820	TEMPO 2020
INPUT POWER	350 WATTS	200	200	300	200	200	180
BANDS	10-160M	10-80M 160M OPT	10-160M	10-80M	10-160M	10-160M	10-80M

Above is a chart comparing leading HF Transceivers that fall in approximately the same price range as the Atlas 350-XL. The Drake TR4-CW is least expensive, while the HY-Gain 3750 is the highest. Rated power input (SSB) and bands covered are listed in the chart, but below is a discussion on a number of other interesting comparisons which will help you choose the right transceiver for your station.

The first 3 transceivers listed above are all solid state. The real designs of the future! Having manufactured and sold over 12,000 of our little 210x/215x's, we can attest to the high performance and reliability of all solid state design. Tubes for the driver and P.A., with their tuning circuits and high voltage power supplies are rapidly becoming obsolete. As a result their resale value will be declining.

The higher power rating on the 350-XL provides you with a comfortable edge over the others. Running barefoot you can easily ride over the competition. If you're driving a linear you don't have to strain for every bit of drive from the transceiver. It can loaf along with ease. The 350 watt input rating is really very conservative. Typical input power runs upwards of 400 to 450 watts without flat-topping. Considerably more than the others.

Not only does the 350-XL cover the 10 through 160 meter bands (including all of 10 meters in four 500 kHz segments), but one of its exclusive features is that you can install up to 10 auxiliary 500 kHz ranges anywhere from 2 to 5 MHz, and from 6 to 23 MHz. This gives you great flexibility for MARS operation and possible future amateur bands. Crystals for Auxiliary Ranges are installed internally. In addition, the 350-XL provides reception of WWV at 5, 10, and 15 MHz, without having to add any auxiliary range crystals.



On the 350-XL, the optional Digital Dial can be installed, and you still retain the conventional analog dial, with the option of switching the digital dial off if you wish. With the Ten-Tec or Yaesu 301, you lose the analog dial if you purchase the digital dial model, making you totally dependent on the digital dial.

Only two rigs offer this feature; the Atlas 350-XL and the Ten-Tec 1. The others are all "semi-break-in". And the Atlas includes CW sidetone with pitch and volume adjustments.

This is another standard feature in the Atlas, optional on the Ten-Tec, Yaesu, and Kenwood. Ours is an I.F. filter with 500 Hz bandwidth, and shape factor of better than 3 to 1.

This 350-XL standard feature permits nulling out heterodynes and other interference. The Yaesu, Hy-Gain and Kenwood include a similar feature.

The standard Atlas ALC system provides up to 20 dB of R.F. compression which increases your talk power and at the same time reduces "flat-topping" and splatter. An optional speech processor to provide up to 20 dB additional A.F. compression will be

All of the rigs listed offer an optional second VFO for split frequency operation. But Atlas is the only one with an Auxiliary VFO that is not an add-on box. The Atlas Auxiliary VFO plugs right into a space provided in the upper right hand corner of the front panel. Although miniature in size it tunes the same 500 kHz as the primary VFO, and does it smoothly with coarse and fine controls that have 10:1 planetary drives. Green, yellow, and red LED's let you know which VFO you have set up for receiving and transmitting. Very neat, and all self-contained.

An option to the Model 305 Auxiliary VFO is the Model 311 crystal oscillator that provides up to 12 crystal controlled channels. It also plugs into the front panel just like the 305. Vernier controls provide fine tuning of the crystal frequency.

The Atlas, Ten-Tec, and Yaesu, being solid state, are unique in that they will operate mobile or portable directly from a 12-14 volt DC battery. Also, the solid state rigs are considerably smaller and lighter weight than the hybrid rigs. The Atlas is unique in having a very handy plug-in mobile bracket for the 350-XL that makes it a simple matter to plug-in and go mobile.

**FEATURES** include R.I.T., VOX, Crystal Calibration, ANL, and Noise Blanker.

Compare the Atlas 350-XL SSB-CW Transceiver with the others, and we think you'll agree the Atlas has everything you'll ever need in a transceiver. And it's made in America.

And let us not forget to mention Our Customer Service which is second to none. Just ask the ham who owns one.

**Model 305 Auxiliary VFO . . . . . \$155.**



# ATLAS

## RADIO INC.

(714) 433-9591

**\* MADE IN AMERICA \***

We're very proud that every Atlas transceiver is made right here in America, (as are the Ten-Tec and Drake). We think the American worker, and our employees in particular, are the most talented, industrious people in the world. The quality and versatility of our transceivers are proof of this.

And by using this American quality workmanship, advanced value engineering in design and manufacture, and rigid quality control, the Atlas transceiver is not only competitively priced with the imports, but is actually a better value!

***Merry Christmas and Holiday Greetings from all the gang at Atlas!***

# an up/down filter converter — matches any bandpass filter to any receiver i-f

Design and construction  
of an up/down converter  
that will interface  
any crystal filter  
with any receiver i-f.  
A design example  
shows how to add  
a 125-Hz filter  
to the Drake R-4B

**Ultimate receiver performance** is viewed by most amateurs as a moving target, with increasing cost just one factor that keeps the target out of reach. New inventions and techniques are constantly being announced by the fast-moving electronics industry; yesterday's dream of an ideal receiver becomes history long before the final receiver payment is due. Giant strides in IC technology have made receivers comfortable and easy to use through the addition of synthesizers, diode switches, and frequency counters. However, most *real* receiver performance improvements, in terms of signal-handling capability and selectivity, are still to be made. The name of the game is picking the weak signal out of the in-

terference caused by many nearby strong signals. Then receiver performance specifications such as third-order intercept point, dynamic range, receiver desensitization, and mixer overload suddenly come to mind.

One goal of modern high-frequency receiver design is to process the desired signal through the narrowest available filter, with the smallest number of active components. Maintaining a credible noise figure, however, tends to legislate against throwing out all of the active front-end components except the mixer.\* While giant strides have been made in semiconductor development, filter technology has been advancing rapidly, too.

This article will discuss the use of available crystal filters and will show you how to easily add high-performance filters to receivers without facing the frustrations of mixer design — frequency conversion, loss of sensitivity, and degradation of dynamic range.

## filter characteristics

A complete line of filters optimized at the same center frequency for CW, RTTY, ssb, and a-m, particularly the i-f in your receiver, is hard to find at a price you can afford, especially from a single manufacturer. Many receivers place the ultimate selectivity (that filter which passes the information bandwidth, such as a 2.4 kHz ssb filter) in the second i-f stage, or further down the active component chain than is desirable.

Frequently a receiver manufacturer does not offer filters which are optimized for RTTY or CW. If you find a filter with the desired response characteristics, chances are that it won't match the receiver i-f.

If you look to filter manufacturers who specialize in only crystal filters, you'll find that, within the past year or two, excellent crystal filters have become available that will optimize filtering for any mode of radio communications. The first stumbling block is the wide variety of filter center frequencies, typically

\*Recent developments in solid-state mixer design actually permit the omission of all active stages prior to the mixer. It is now possible to obtain a mixer noise figure of 10 dB or less on the high-frequency bands. This will be sufficient for all but the most demanding reception requirements, such as OSCAR 7, Mode A on 10 meters.

Editor

By Howard Sartori, W5DA, 721 James Drive,  
Richardson, Texas 75080

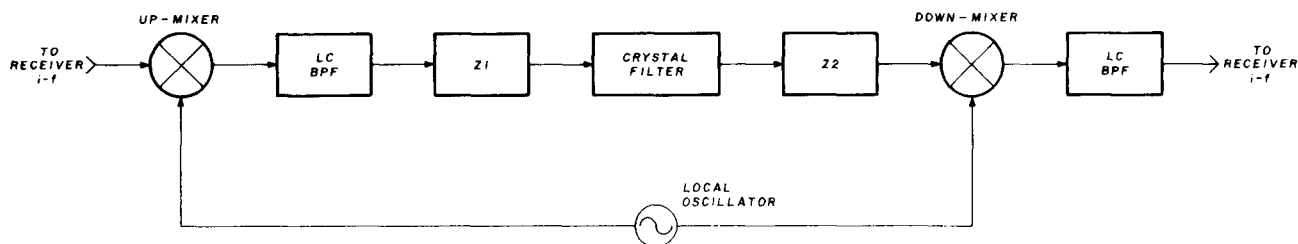


fig. 1. Block diagram of the up/down frequency converter for adding an additional filter to a receiver. Z1 and Z2 represent the impedance matching networks necessary to interface the mixers and filter.

in the range from 5 to 11 MHz. Rarely does one manufacturer produce a complete line of filters, optimized for the information bandwidth of each of the operating modes used by amateurs.

Cost has been a major factor in the past, but crystal filter production techniques have vastly improved and costs have turned downward. To put cost into perspective, and to consider the effects of inflation, excellent 8-pole crystal filters, with signal rejection floors below 100 dB, are now available for about the same price level as 4- and 6-pole crystal filters were about 5-10 years ago.

Describing a crystal filter by its shape factor, normally defined as the ratio of the 6-dB to 60-dB bandwidths, doesn't tell the whole story. This measure of squareness is typically 1.7 to 2.2 for a good quality ssb filter, the slope of the response curve in a simple filter is determined by the characteristics of the crystals. For a 2.4 kHz ssb filter with a shape factor of 1.75, for example, the attenuation/ $\Delta$  frequency of

the filter slope would be 54 dB/900 Hz. When narrower filters were designed, the bandwidth between corners was reduced but the slope remained essentially the same; a 500 Hz filter had a shape factor greater than 4.0. In fact, the bandwidth of the slope itself on one side of the ssb filter was wider than the 60 dB bandwidth of an optimized CW filter!

Eventually new fabrication techniques, such as mounting all crystals on the same header, permitted development of high-performance crystal filters. In some filters the entire passband may move as much as 2 Hz/ $^{\circ}$ F, but this is not objectionable when the entire filter shape moves. To further illustrate the tremendous achievements in crystal filter technology that have occurred during the past several years, consider the 125-Hz CW filter now on the market. At one time, not too many years ago, 125-Hz crystal filters were a novelty of the laboratory. Today CW filters with 125-Hz bandwidths and shape factors of 2.5 are available for approximately \$125.

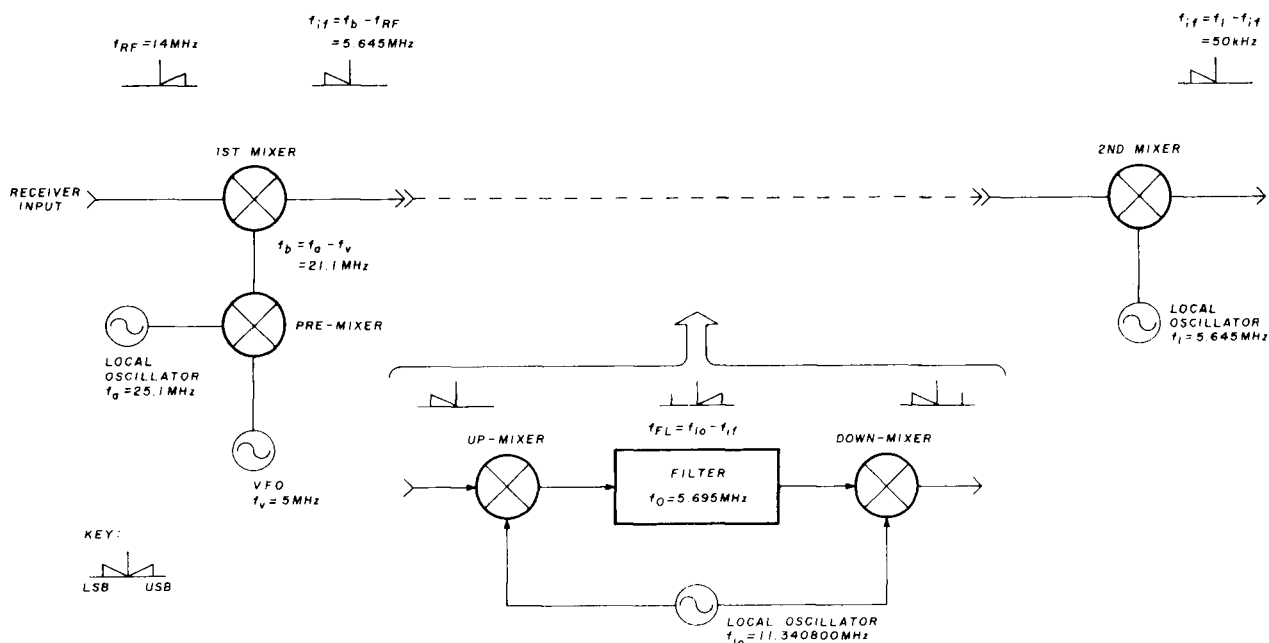


fig. 2. Block diagram of the Drake R-4B showing the receiver frequency conversion scheme. The conversion is necessary for the additional filter inserted between the first and second mixer. This diagram can be used to check for any sideband inversion.

By using the newer 8-pole crystal filters, receiver performance can be improved in the following ways:

1. Filters are optimized for the information bandwidth.
2. Signal-to-noise ratios are improved.
3. Filters placed as close to the front end as possible improve dynamic range.

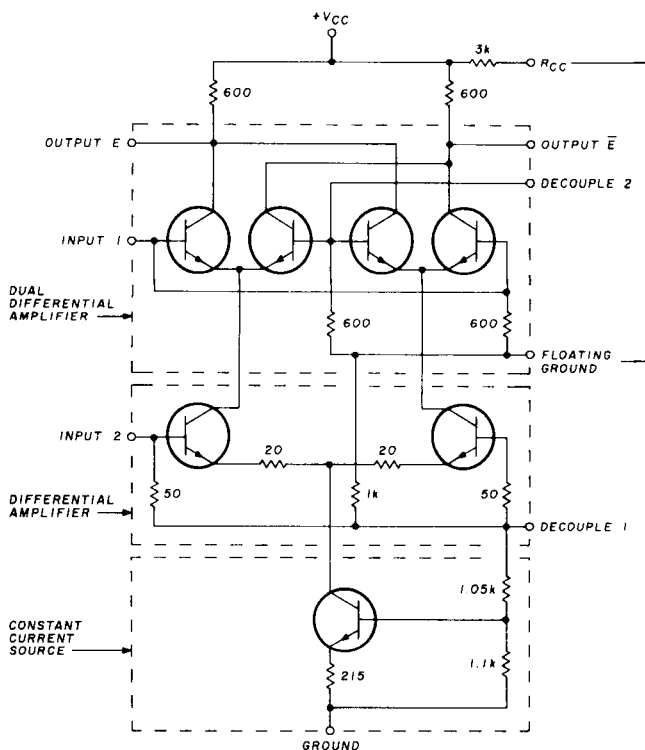


fig. 3. A representative schematic diagram of the Texas Instruments TL442 doubly balanced mixer IC. Input 1 has an input impedance of 600 ohms, while input 2 is 50 ohms. The output can be connected for 600 or 1200 ohms output impedance, depending whether the supply voltage is connected to  $+V_{CC}$  or OUTPUT E.

4. Cascading with an existing filter to achieve better filter skirt and out-of-band performance.

When you optimize filters, you not only reduce susceptibility to interference — you also reduce listener fatigue. Improved signal-to-noise ratios are particularly noticeable on the low bands for several reasons. First, if only an ssb filter is available for CW, when a 125-Hz bandwidth filter is switched into the circuit, the bandwidth improvement ratio will be  $10 \log 2400/125$  or 12.8 dB. Even if a 500-Hz CW filter were available, a 125-Hz filter would improve the signal-to-noise ratio by 6 dB. In addition, by the very nature of impulse and static noise, the filter will prevent overloading the following stages; this means that the signal-handling ability of the receiver has been improved.

Some receivers have a nominal 2- or 4-pole filter in

the first i-f, and the final selectivity in the second or last i-f stage. Obtaining all the needed selectivity at one i-f is difficult, however, because of signal radiation and leakage (even with the best shielding). By placing a high-performance crystal filter in the first i-f, overload of the second mixer can be greatly reduced. Further, spreading the selectivity over several stages is an excellent way to improve ultimate signal rejection.

Since the crystal filter you want to use will probably not agree with your receiver i-f, to say nothing of the input and output impedances, a convenient method is required to interface additional filters. Many receivers have a simple general purpose filter in the first i-f with an output impedance of 500 to 1000 ohms. This is an ideal place to add an outboard crystal filter.

Designing a conversion scheme can be a complicated process; consider all the variables. Fig. 1 shows a block diagram of the general approach for heterodyning the first i-f signal up or down to a high-performance crystal filter, and then heterodyning back to the receiver. The first mixer (up converter) can easily overload; the down-mixer is not nearly as susceptible to overload. In addition, the local oscillator can act as a source of spurious radiation for birdies in the amateur bands. Since only one local oscillator is generally used for the two mixers, it may serve as the leakage path for the signal around the filter. Or, the local oscillator signal could feed through the down-mixer into the next i-f stage. And consider the fact that since almost all commercial crystal filters are in the 5 to 11 MHz frequency range, the receiver i-f and the crystal filter frequency should be very close.

Having both the receiver i-f,  $f_{if}$ , and the filter,  $f_{FL}$ , at nearly the same frequency is probably the leading cause for abandoning the project. Mixers not only mix; they can amplify. Therefore, if  $f_{if}$  cannot be filtered out by the LC bandpass filter (BPF) at the output of the up-mixer, overload may eventually become a problem because both signals could be substantially amplified. To make matters worse, the conversion process usually results in some loss of desired signal; as much as 30 or 40 dB difference between the two mixer output signals,  $f_{if}$  and  $f_{FL}$ , is not uncommon. As a result, the filter signal rejection floor is greatly diminished. If the two frequencies are within several hundred kilohertz, the isolation of  $f_{FL}$  by the bandpass filter may be as big a task as manufacturing the high-performance crystal filter in the first place.

Finally, the filter must be very carefully matched to the up-mixer output and the down-mixer input. These matching networks are shown in fig. 1 as Z1 and Z2.

Selecting a frequency conversion scheme should be done with care. **Fig. 2** shows the first i-f signal, filter i-f, and local oscillator frequencies. It is well to consider the particular sideband, too, since sideband reversal may not be desirable. **Fig. 2A** shows the complete receiver conversion scheme, with the Drake R-4B used as an example. The sideband slope diagrams show the relative sideband with respect to the incoming rf signal.

**Fig. 2B** shows how the up/down filter converter is integrated into the receiver's first i-f. Using the filter's center frequency, the required local oscillator frequency can be determined from  $f_{LO} = f_{FL} \pm f_{if}$ . The Sherwood Engineering CF-125/8\* CW filter center frequency is 5695.0 kHz. Assuming an 800-Hz tone, the incoming frequency,  $f_{if}$ , would be  $5645.0 + 0.8 = 5645.8$  kHz; the local oscillator frequency would be  $5695.0 + 5645.8 = 11340.8$  kHz (or  $5695.0 - 5645.8 = 49.2$  kHz). The 11340.8 kHz frequency is, fortunately, not in any amateur band; but the 49.2-kHz local oscillator signal would fall within the passband of the receiver's second i-f! Therefore, 11340.8 kHz will be used as the local-oscillator frequency.

## solving the problems

The close proximity of the receiver's first i-f and the crystal filter frequencies was the toughest prob-

\*Sherwood Engineering, 1268 South Ogden Street, Denver, Colorado 80210.

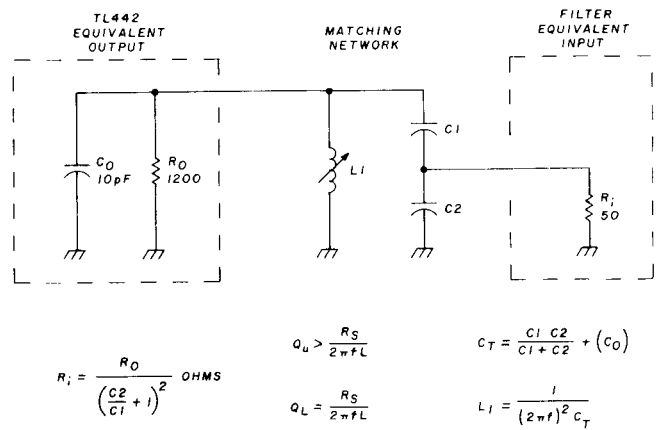


fig. 4. The capacitive tap-down network is used to match the up-mixer to the crystal filter. It can also be used to match a high-impedance first i-f stage to the 600-ohm input of the TL442 mixer IC.

lem to solve. Convenience and easy-to-do were words which guided this design project for more than six months. Building the LC filter at the output of the up-mixer, shown in **fig. 1**, however, was anything but easy. Combining it with the impedance matching network, Z1, was complicated and certainly not repeatable without diligent tuning. Doubly balanced mixers were considered, but many of them required large numbers of external components and even null adjustments.

Finally, a doubly balanced mixer IC was found that provides internal preset nulls in excess of 30 dB, for

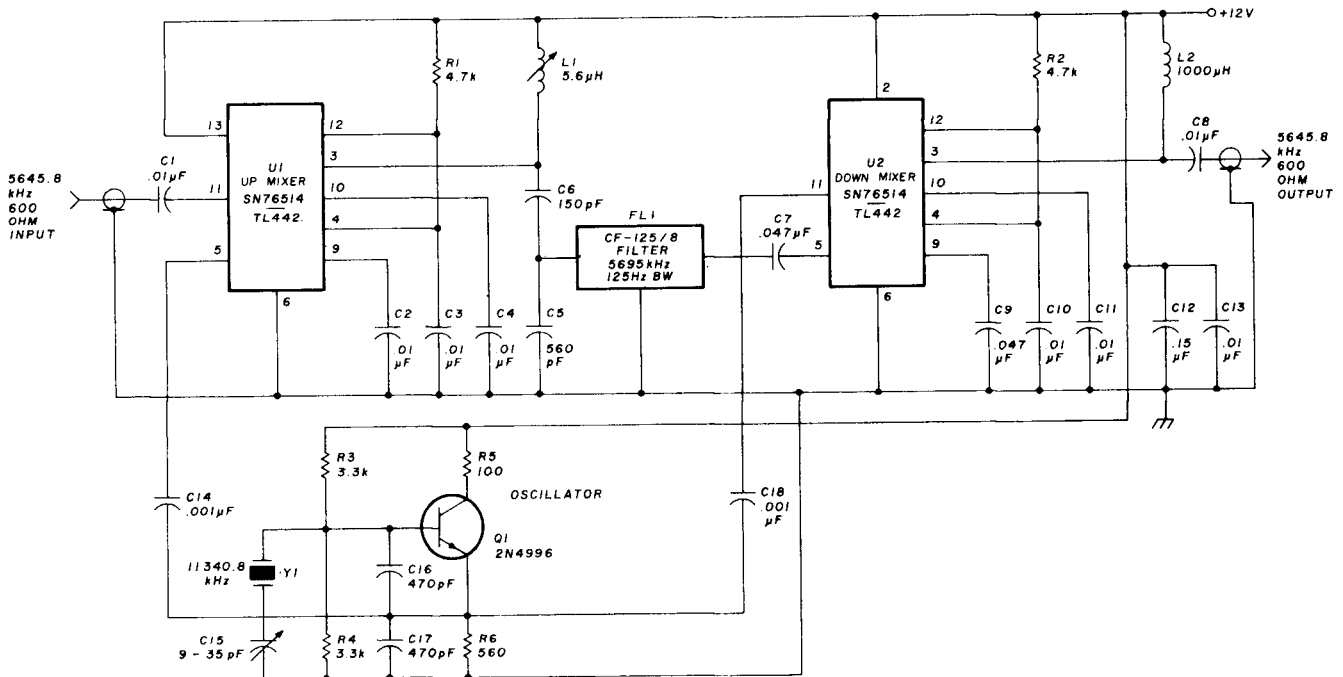


fig. 5. Schematic diagram of the up/down converter. All resistors are 1/4 watt, 10 per cent. The TL442 pin-out is shown for the dual in-line package. The active devices can be obtained from Texas Instruments Supply, 6000 Denton Drive, Dallas, Texas 75235.

both the input and the local oscillator signal. Fig. 3 shows a diagram of the Texas Instruments TL442 (old designation SN76514). This circuit was designed specifically for radio receiver applications. Its features include

1. Flat frequency response to 100 MHz; with tuning usable to 300 MHz,  $C_i = 3\text{--}5\text{ pF}$ ;  $C_o = 10\text{ pF}$
2. 50 and 600 ohms input impedances and 600/1200-output impedance
3. Factory-tuned null adjustments for both signal and local oscillator
4. Single- or double-ended voltage source
5. Differential amplifier with large signal-handling capability
6. Low-level local oscillator requirement
7. Noise figure of approximately 6 dB
8. Typical conversion gain of 14 dB

In the TL442 IC, uhf transistor chips are matched and the resistors are etch-trimmed in the manufacturing process to achieve balance. The IC actually consists of two cross-coupled differential amplifiers whose emitters are driven by a third differential amplifier. A constant-current source is connected to the third differential amplifier emitter. This device works best with 250 mV local-oscillator injection, and performs without significant overloading, up to about 300 mV of rf signal. Hence, the signal-handling characteristics of the TL442 are as good as or better than most vacuum-tube converters in current receiver designs.

An excellent description of the TL442 is also available from Texas Instruments.<sup>1</sup> Cost of the doubly balanced mixer is \$2.40, an excellent trade-off when you consider that no external components are required. With more than 30 dB separation between the desired  $f_{FL}$  signal and the nearby  $f_{if}$  signal, the re-

mainder of the high-performance crystal filter converter design is downhill.

Impedance matching, or the lack of it, is a big benefit of using the TL442. The fixed 600/1200-ohm output required no LC network, and only the most simple matching circuit to match the 50-ohm crystal filter. Going from the filter to the down-mixer does not require matching when using the 50-ohm input of the mixer! With isolation between the local oscillator and the output port of more than 30 dB, the local oscillator signal will have only minimal impact upon the receiver, and will provide more than 60-dB protection against signal leakage across the filter.

The gain/loss in the conversion process is also worth planning. The Sherwood CF-125/8 filter has a typical loss of 9 dB (maximum 11 dB). Another factor is the bandwidth reduction loss from 2.4 kHz to 125 Hz, which was shown to be about 13 dB. I like background noise to remain constant rather than to keep the signal strength constant when switching between the two filters; the noise floor is always a ready reference and a 13 dB drop in the noise floor is a noticeable deadening of the receiver! If the TL442 is connected for a 1200-ohm output impedance, about three S-units of excess gain can be provided to slightly more than account for loss of background noise due to bandwidth reduction.

Designing the matching network, from the TL442's 1200-ohm output impedance to the CF-125/8 crystal filter's 50-ohm input impedance, is based upon the capacitive tap-down network shown in fig. 4. The IC output impedance is 1200 ohms in parallel with 10 pF of source capacitance. L1 is used to resonate this 10 pF and the series connected tap-down capacitors, C1 and C2. Fig. 4 shows the relationships between the network components and the termination parameters. As discussed before, one of the advantages of the TL442 is that the crystal filter will directly match the 50-ohm input of the second TL442 mixer.

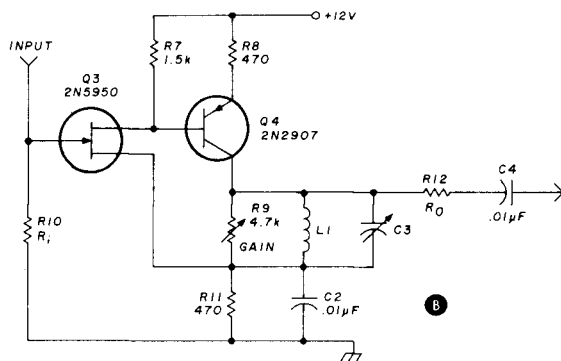
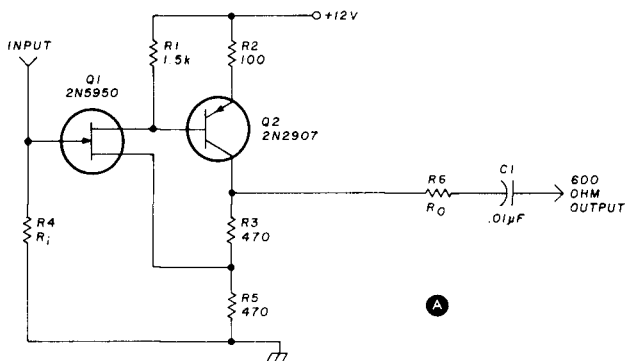


fig. 6. The 1:1 line isolation amplifier is shown in A, while the amplifier with the variable ratio is shown in B. This design is capable of handling large signals with low cross-modulation.

All that's needed to complete the converter are three semiconductor devices and one tuned circuit. **Fig. 5** shows the schematic. Both mixer ICs are configured in the same manner. Rf ground potentials are carefully bypassed with monolithic capacitors using short leads. The TL442 outputs are single ended, and the impedance is raised to about 1200 ohms by applying the supply voltage to pin 13. The constant-current source resistor network derives its voltage from the 3k resistor connected from pin 12 to pin 4; an additional 4.7k resistor is connected to pin 4 to increase gain. At the signal input, the 600-ohm input

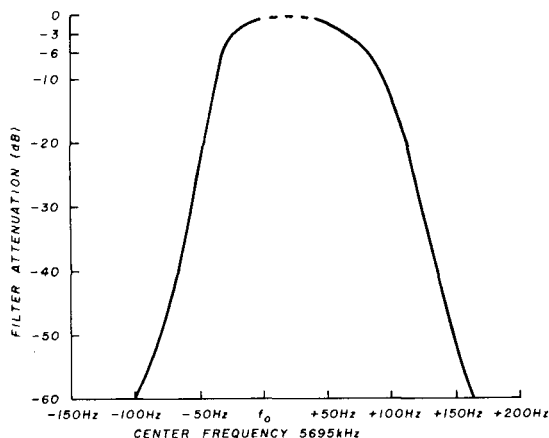


fig. 7. Frequency response of the Sherwood Engineering CF-125/8 crystal filter.

(pin 11) is used for the receiver first i-f signal because matching to 600 ohms is convenient.

The local oscillator was carefully designed to provide as much decoupling from the supply voltage as possible and also to provide a very low output impedance. A T-pad attenuator between the two mixers further decreases the possibility of signal leakage from the signal input through the input mixer, oscillator, and through the output mixer.

The capacitive tap-down network from the up-mixer, U1, to the crystal filter, FL1, is composed of L1, C6, and C5. Depending upon the  $Q$  of L1, and any other filter impedance, C5 and C6 can be adjusted to give the proper ratio for a good filter match. This occurs at or near maximum signal strength without objectionable ripple in the passband or out-of-band ripples.

Retune L1 each time C5 or C6 are changed; the adjustment is straightforward and noncritical. C15 provides a fine-tuning adjustment for the crystal.

## line amplifiers

When the output impedance of the receiver's first i-f is greater than one or two thousand ohms, a matching circuit will be required. Again, the

capacitance tap-down network will work well for ratios of 24:1 or more. Further, there is sufficient gain in the TL442 IC mixers to recover a few dB of circuit loss. When excessive loss is encountered, a line amplifier (**fig. 6**) will help recover gain, or match extremely high-impedance circuits to low-impedance circuits. This circuit features several S-units of gain while exhibiting very large signal-handling capabilities with low cross-modulation distortion. The output impedance is 1200 ohms, untuned, and should be easy to match to the second-mixer circuit in any receiver.

## construction

The whole system was built on a double-sided printed circuit board that fits over the pins on the CF-125/8 crystal filter. The filter is securely grounded to the back plane of the printed-circuit board to reduce signal leakage around the filter. A piece of double-stick *Scotch* mounting tape was used to attach the entire up/down crystal filter converter assembly to an unused panel inside the receiver. One word of caution: always place a metal shield between the input wafer and the output wafer of the crystal filter switch to minimize signal leakage.

## results

True single-signal reception with the CF-125/8 crystal filter in tandem with an ssb filter is most gratifying. **Fig. 7** shows the frequency response of the CF-125/8 crystal filter by itself. Other crystal filters give equally impressive results. My R4-B receiver is equipped with a 1:1 line amplifier which drives the Drake ssb filters from the 2-crystal filter in the first i-f stage. The output from the ssb filter drives the line driver (adjusted to make up the 6 dB filter loss) and then the second mixer. The up/down crystal filter converter is switched in between the ssb filter and the second line amplifier. The tandem combination of filters does not ring, and 40 word-per-minute CW copy is possible. The noise and static effects that were so bothersome when a 125-Hz audio filter (shape factor 3) was used are now annoyances of the past.

If you are lucky enough to find crystal filters that are on the same frequency as your receiver's first i-f, all that is needed is a line isolation amplifier to buffer the filter, a matching network, and a line amplifier to make up the gain of the return signal.

## reference

1. *Balanced Mixer Application Note*, Section 6.6 SN76514/TL442, Linear Circuits Application Department, Mail Station 964, Dallas, Texas 75222.

ham radio

# how to select TTL sub-series ICs for different digital designs

The popular TTL family  
of digital ICs  
is widely used  
in amateur applications,  
but low-power, high-speed,  
and Schottky TTL  
have been largely neglected —  
here's how to select  
the best TTL sub-series  
for your own designs

Through the years, as the 7400 series of ICs has become the mainstay of TTL logic designers, more and more devices have been added to the family. In the last few years, both Fairchild Semiconductor and Texas Instruments have increased their commitment to the market by introducing expanded lines of high speed, low power, and Schottky-clamped devices. At the same time, extensive use of foreign production facilities has allowed a 50 per cent drop in prices, which distributors are now beginning to pass along to the consumer. Where does that leave you when you decide to build that new keyer or frequency counter? Consider the popular 7400 quadruple 2-input NAND gate, for example. There are five versions: the 7400, 74H00, 74L00, 74LS00, and 74S00. Which version is best suited for your purposes? What advantages does one version have over another?

Actually, each 7400 sub-series (H, L, LS, and S) has clear cut strengths and weaknesses which make the choice a lot easier than it may appear. The two major differences between each sub-series are speed (maximum operating frequency) and power consumption. In general, to gain speed, power consumption must be increased. This speed-power trade-off would probably settle the matter because you would pick the lowest power version that meets the required speed and stop right there, but a third factor comes into play: cost. To either increase speed or decrease power, the cost at least doubles over that of the standard (and the least expensive) version. A good rule of thumb is to use these special devices *only* when the standard 7400-series chips can't do the job.

## performance comparison

Let's go back to the 7400 quad 2-input NAND gate and look at the differences between each version and set down some general characteristics for each sub-series.

The 7400 typically operates from dc to 35 MHz, as will the remainder of the 7400 series. This is a *typical* specification and does not hold true in devices of higher complexity such as the Texas Instruments SN74144, which contains a BCD counter, a four-bit latch, and a BCD to seven-segment decoder-driver. The SN74144 is intended to be a one-chip replacement for the popular SN7490A counter, SN7475 latch, and SN7447 decoder-driver combination. Because of the high component density in the SN74144 (an equivalent of 86 gates on one chip), however, the typical counting frequency only extends to 18 MHz. Some of the earlier devices were equally slow. There was a time, not too long ago, when it was sometimes necessary to go through a handful of 7490 counters before you could find one that would work to 30 MHz. Therefore, it's wise to buy only devices with current date codes, unless the application isn't critical. Problems shouldn't pop up with any major suppliers, like those who advertise in *ham radio*, because the turnover is too high for 1973 chips to be still floating around in the open market.

Digressing a moment, the date code is a three- or four-digit number standardized by the EIA (Electronic

**By Ian MacFarlane, WA1SNG, 102 Columbus Avenue, Greenfield, Massachusetts 01301**

Industries Association). It is stamped on every integrated circuit, usually, but not always, after inspection. Contrary to what you might think, you can get an untested IC with all the same markings as a first-rate unit. If the number has four digits, the first two represent the year of manufacture, such as 75, and the next two stand for the calendar week, such as 38, which would mean the thirty-eighth week of 1975 (the third week in September). If the number has three digits, the first is the year of manufacture (in the example above, the year would be cropped to 5), and the last two digits refer to the calendar week.

The typical low power 74L00 version will operate to 3 MHz, making it somewhat slower than the CMOS family. Every other sub-series is faster than the original type. Below is a list in terms of *typical* speed:

74L	3 MHz
74LS	45 MHz
74H	50 MHz
74S	125 MHz

These figures represent the highest typical clock rate for flip-flops. Once again, remember that each device must be considered on a one-by-one basis where speed is concerned, with the higher-density units having lower maximum frequencies than their less complicated brothers.

Power consumption is often compared using the power dissipation per gate for each series. This information is given in **table 1**, along with all other comparative figures, but in this case it is based on the average supply current, per gate, assuming a 50

the SN7490A, SN74L90 combination, and 13.15 for the SN7473, SN74L73 flip-flop pair. The average supply current values for the remainder of the devices are: 4.5 mA for the 74H00, 0.4 mA for the 74LS00, and 3.75 mA for the 74S00. Thus, if the 7400 is used to establish the standard unit of power consumption (2 mA = 1 unit), then the relative standings are 0.1, 0.2, 1.9, and 2.3 for the L, LS, S, and H sub-series, respectively.

## selecting a sub-series

There are three variables that must be considered when choosing the proper series: price, speed, and power. In general, the first and deciding requirement is that the chip will work up to the desired frequency. It is possible to approach the choice from a power consumption standpoint, but if power conservation is critical, it would be a good idea to see what can be done with a very low power series like the RCA CD4000 COS/MOS family. On a cost-effective basis the low-power 74L00 series is not as good as the COS/MOS family, which has a much lower power-cost product; COS/MOS will also work at higher frequencies (5 MHz for counters, 10 MHz for gates and flip-flops).

This brings us to the method for selecting the best sub-series once the speed requirements have been fulfilled: the *power-cost product*. Since both cost and power are to be minimized, it is easier to multiply the two figures together and deal with one variable instead of two. The lower the power-cost product, the more performance you get for your

**table 1. Comparison of the various TTL sub-series showing clock, rate, power dissipation, propagation delay, relative cost, and power-cost product**

series	maximum flip-flop clock rate	power dissipation per gate	gate propagation delay time	average cost increase over standard series	power-cost product
74L00	3 MHz	1 mW	33 ns	3.1	0.62
7400	35 MHz	10 mW	10 ns	1.0	2.00
74LS00	45 MHz	2 mW	9.5 ns	1.4	0.57
74H00	50 MHz	22 mW	6 ns	1.9	8.49
74S00	125 MHz	19 mW	3 ns	3.4	13.07

per cent duty cycle. The average supply current data is readily available for individual devices, whereas power dissipation is generalized for all gates in the series. The difference in consumption will hold true, when comparing more complicated devices, so long as it is treated as an approximate ratio. In other words, if the average supply current for one gate of a 7400 is 2 mA, and the average supply current, per gate, of a 74L00 is 0.2 mA, then it is fair to say that *any* standard 7400 series device will require approximately ten times the amount of power than an L-series unit does. In practice, the actual ratio may be more or less.

To take several cases, the power ratio is 7.25 for

money. In practice, the product is calculated by multiplying the average current per gate (in mA) for the series, by the average increase in price of the series over that of the standard 7400 series (given as a multiple, such as 3.1 times cost). Data is provided in **table 1**. This is a method for standardizing the selection process, or a mathematical replacement for common sense.

As an example of how to use the chart, suppose you are planning to build a 10-MHz frequency standard. The 10-MHz specification puts everything in the running except the L series. If cost effectiveness is the object, a look at the lowest power-cost product reveals that the LS series is your best bet. Sheer

low cost, providing that a husky power supply is available, would be provided by a switch to the standard series. Not all device selections are that simple.

Let's assume you are designing a frequency counter. The goal is to build a model capable of counting to the highest frequency and requiring the least possible power, and using only the TTL series (no CMOS or ECL integrated circuits); price is no object. In case the design goal will not be met by using only one 7400 sub-series, the lowest power version having the necessary speed will be selected. Excess speed margins, when not needed, will be sacrificed for power conservation. Starting with the 10 MHz oscillator, choose a 7400. The 74LS00 and other sub-series chips have a reputation for not performing well in oscillator service. A key to this problem is the different biasing requirements for each sub-series. It is impossible to just simply remove a 7400 from an oscillator circuit and plug in a 74LS00 without changing external resistor values. There are many proven oscillator circuits based on the 7400, but little published information about biasing for oscillator service, so sticking to the well trodden path will assure success.

The first divider must be able to toggle up to 10

build a higher current power supply than to purchase twenty-five special ICs at three times the cost of their standard TTL equivalents.

## TTL sub-series compatibility

One of the original design objectives for the different TTL sub-series was compatibility. All have the same maximum supply voltage rating of 7 volts, except for the L series, which is 8 volts. This gives plenty of leeway above the typical 5.0 V supply voltage, which is common to all sub-series. Operating temperature range extends from 0 to 70°C (32 to 158°F). The maximum input voltage for the L series is 7 volts, with 5.5 volts as the limit for all others. Because of these similarities, mixing devices from different sub-series will produce no problems so long as fan-out limits are observed.

Fan-out (the number of inputs a single output can drive) is figured only on the basis of outputs driving inputs from the same sub-series. The standard fan-out is 10 loads, except for the L and LS series, where it is 20. Mixing of devices is permitted as long as the output can source (provide) or sink (absorb) the *total* current to or from all inputs.

The high- and low-state input requirements are shown in **table 2** along with output sink capabilities.

**table 2.** Input and output data for the various TTL sub-series. Note that the L series had two different standard inputs; assume highest input current when calculating output requirements. Negative signs represent current flow out of terminal

series	input current (high state)	input current (low state)	maximum output sink current	maximum output source current
74L00	10/20 $\mu$ A	-0.18/ -0.8 mA	3.6 mA	-200 $\mu$ A
7400	40 $\mu$ A	-1.6 mA	16 mA	-400 $\mu$ A
74LS00	20 $\mu$ A	-0.4 mA	8 mA	-400 $\mu$ A
74H00	50 $\mu$ A	-2.0 mA	20 mA	-500 $\mu$ A
74S00	50 $\mu$ A	-2.0 mA	20 mA	-1000 $\mu$ A

MHz; a 74LS90 will require the lowest power. All remaining dividers operate at 1 MHz or below, making the 74L90 the best bet. The counter control circuitry, which generates the count enable, strobe, and reset pulses functions at a very low rate, since most counters can make no more than 10,000 counts per second, so L-series devices can be used. The gate must pass the highest counted frequency, as must the first decade counter, and this application calls for Schottky ICs such as a 74S00 for the gate, and a 74S196 for the first counter. The second decade counter must be LS to count up to 12.5 MHz, but the remaining counters may be L versions. Latches and decoder drivers can also be chosen from the L series.

It is important to note that no standard series TTL logic was used in this circuit. Only when performance can be sacrificed in favor of price is standard TTL a wise choice. Price is almost always important, which explains my rule of thumb which suggests that the standard series be used exclusively, except when it just won't do the job. It's less expensive to

From these figures it's easy to check to see whether a particular output can handle its loads. Just add up the low-state currents for all loads (inputs), and then check that the totals fall within the maximum sink limit for the output. The negative values of input current represent a flow out of the terminal, back into the output. If the output can sink the required current, it will always be able to source enough current for the loads.

## conclusion

While the use of standard and LS series TTL ICs has certainly caught on for amateur projects, the H, L, and S series have been largely neglected. As so often happens with new products, this is due more to insufficient information than it is to a lack of applications. It is hoped that this article has provided enough information to generate more interest in using the various TTL sub-series ICs in future designs.

**ham radio**

If you're ever

# DX-ing

on an island so small that  
the only things resembling coconuts  
are the traps on your beams—

## You'll be glad you're using a Drake C-Line...

R.L. Drake Company  
Miamisburg, Ohio

1977 DXpedition Group  
Palmyra / Kingman Reef

A DXpedition to Kingman Reef requires the operators to have an uncommon amount of faith in their equipment. For this reason we chose the Drake C-Line.

- Our two C-Lines were subjected to what we feel were some of the most adverse conditions possible:
1. Temperatures were 150° plus in the engine room of our chartered boat for 17 days.
  2. Generator voltage was low due to running 1kW amplifiers. (Typically 100 volts)
  3. AC-4 power supplies were sitting in water on several occasions due to severe rains.
  4. During one rain storm, water was actually coming out of the R-4C headphone jack.
  5. Numerous small lizards and spiders were crawling in and out of the C-Lines.

Despite all these adversities, the two Drake C-Lines were in operation for over 145 hours; the only "off time" was during the six hour trip from Palmyra Island to Kingman Reef. A total of over 16,000 contacts were made from KP6AL Palmyra and KP6BD Kingman Reef without a single transmitter or receiver failure.

I know that customer satisfaction has been the cornerstone of R.L. Drake Co. for 34 years. Let me say that as far as we are concerned, that cornerstone is firmly in place. Thank you for making a very reliable product.

*Barry J. Fairfax*

Barry J. Fairfax WB9KTA,  
operator: KP6AL Palmyra Island  
KP6BD Kingman Reef

Received 7/15/77 by:

**R. L. DRAKE COMPANY**



**DRAKE**

540 Richard St., Miamisburg, Ohio 45342 • Phone: (513) 866-2421 • Telex: 288-017

Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470



# 500-watt regulated power supply

Introducing  
Dragon One —  
a power source  
with built-in safety features  
for your  
high-power equipment

With solid-state devices making advances in the vhf and uhf spectrum, more powerful transmitters are made available to radio amateurs. Solid-state transmitters and linear amplifiers in the 150-200-watt range are not uncommon. Although most of the equipment is made to operate in automobiles using car batteries, many amateurs want to operate their higher-power solid-state devices in their homes. But here the power supplies become a problem, unless of course, you wish to purchase an auto battery and a battery charger as accessories for the modern equipment. Even then, the battery has a finite life, and the sulphuric acid in the battery is hazardous inside living quarters.

## the dragon one supply

This article describes a power supply system that delivers a whopping 500 watts of clean, regulated power. The regulation is better than 1 per cent from no load to full load, with a ripple voltage of less than 10 mV peak-to-peak. Safety features such as current limiting, overvoltage shutdown, and short-circuit protection are all built in. Optimum regulator efficiency is approximately 65 per cent at an output of 450 watts.

Fig. 1 shows the regulated-power supply schematic. Transformer T1 steps down the line voltage to 22 volts, which is rectified by full-wave bridge rectifier CR1. Filtering is by C1, which is a computer-grade electrolytic capacitor having a capacitance of 18,000  $\mu$ F. R1 discharges C1 after the power supply is turned off.

Regulation is provided by U1, the popular 723 regulator IC. The 12-15-volt voltage adjustment is by R4. C5 ensures oscillation-free operation of regulator

By C. C. Lo, WA6PEC, 5414 Barrett Avenue,  
El Cerrito, California 94530



723. U1 output drives Q2, an MJE3055, which in turn, drives Q3-Q6, 2N3055s. Current sensing is by R16, a special 15-milliohm resistor. The two output terminals are isolated from chassis ground. Grounding is achieved by connecting the positive or negative output terminal to the ground terminal with a jumper. A light-emitting diode indicates the presence of dc output voltage. R3, R4, and R5 make up the output voltage sensing divider; the voltage control signal is connected to U1 inverting input.

To protect the power supply from burning itself up in case of excessive load current, the short-circuit shutoff is done in conjunction with the current limiting provided by the regulator through R16. As load current exceeds 35 amps, the output voltage starts to drop. When the voltage drops below 8 volts, Q1 turns off and SCR1 turns on, pulling the regulator noninverting input close to ground potential, thus turning off the output power. This condition remains until the power supply is turned off and SCR1 unlatches.


Overvoltage shutdown is designed into the system to protect your expensive transceivers and linear amplifiers. If anything should happen to the regulator or any of the series transistors, chances are one of these devices will short out, putting the full voltage across C1 at the output. This could be disastrous to transceivers and amplifiers. Relay K1, together with CR2 and SCR2 ensure that this will not happen, even if all the pass transistors and regulator are shorted. As the voltage exceeds 16 volts, CR2 starts to conduct, supplying gate current to SCR2, which turns on and activates K1. In doing so, the main dc supply is cut off and will remain off for as long as the power is on and the defect has not been corrected. This special feature is valuable and its additional cost is well justified, although the overvoltage shutdown feature may never be needed in the lifetime of the power supply.

## construction

All components are packaged in a 7 x 8 x 10-inch (178x203x254mm) steel chassis box. Three heatsinks are used (photo).

All components shown inside the dotted line in the schematic diagram are mounted on the printed circuit board. Since this circuit is a high-current power source, no. 12 (2.1mm) wire should be used for all high-current paths. However, no. 16 (1.3mm) wire can be used for interconnections from the two relay contacts, which are wired in parallel to the individual transistor collector and from the individual emitter to point L or R16. R19 and C6 are mounted behind the output terminal block. Holes are punched on the top and bottom panels for ventilation purpose.

Output voltage can be adjusted between 12-15 volts dc. Load current is rated at 35 amps intermittent, and 22 amps continuous duty. For prolonged operation at high current and low output voltage (below 13 volts), a small external fan is recommended for cooling the heat sinks. However, the power supply can deliver 22 amps continuously without forced-air cooling if ambient temperature is below 77°F (25°C). The temperature of the pass bank tran-

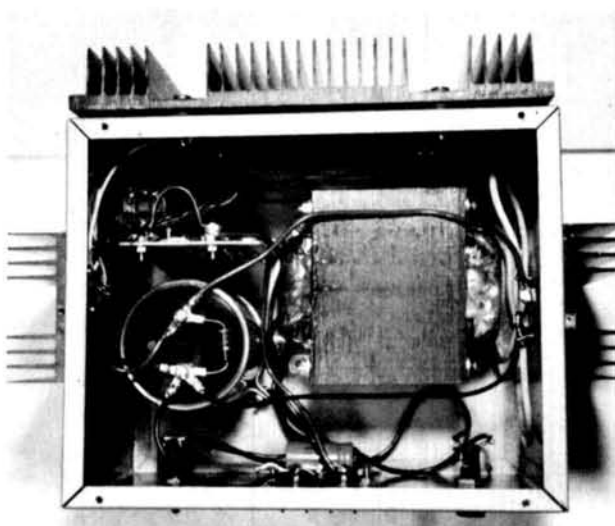

**Underchassis view of the power supply. Three heatsinks are used. The heatsink mounted on the rear of the chassis box is isolated from chassis ground. The four 2N3055s (Q3 - Q6) are mounted directly on the heatsink. The heatsink on the right-hand side is for bridge rectifier CR1; the other heatsink is for Q2. Heatsink compound was used for mounting Q2 - Q6.**

sistor under this condition stabilizes at around 221°F (105°C). With a 25-30 cfm (7 x 10<sup>5</sup> - 8 x 10<sup>5</sup> cm<sup>3</sup>/minute) fan blowing at the rectifier and the transistor heatsinks, the transistor heatsink temperature stabilizes at 122°F (50°C) with 30 amps continuous load current operation for one hour. Regulation is below 1 per cent from no load to full load (35 amps). The taps on transformer T1 are for optimum efficiency operation. It's obvious that if the line voltage is high, the unregulated dc voltage will also be high, making the voltage drop across the pass bank transistor high. That means higher power dissipation and lower system efficiency. Hence, if the input line voltage is connected to the proper tap, an optimum system efficiency is achieved.

## bibliography

1. *Voltage Regulator Handbook*, National Semiconductor, Santa Clara, California, May, 1975.
2. *Fairchild Voltage Regulator Application Handbook*, Fairchild Semiconductor, Mountain View, California, March, 1974.

**ham radio**

# HEATHKIT: The name in Amateur radio...and now computers!



## SB-104A Amateur Transceiver

The world-famous SB-104 with significant improvements. We've increased the sensitivity to 0.5  $\mu$ V on all bands and included a fully assembled and tested receiver front end circuit board for reduced assembly time. The optional 400 Hz filter is independently selectable for CW operation. We've maintained the features that made it famous too — totally broad-banded, all solid-state, digital frequency readout and more. Make the SB-104A the "heart" of your station. Only \$669.95



## HW-2036 2-Meter Mobile Transceiver

Our value-standard 2-meter rig offers true digital frequency synthesis in 5 kHz steps and a built-in tone encoder to access most repeaters! Also features built-in simplex, + and - 600 kHz offsets, and an aux. position that lets you add your own crystal for any other offset crystal you may want. The HW-2036 has 0.5  $\mu$ V receiver sensitivity and a transmitter that can operate into an infinite VSWR without damage! Come on up to 2-meters with one of the best mobile rigs you can get. Only \$269.95

## FREE! HEATHKIT CATALOG

Nearly 400 kits for you to build! Whatever your interest—hi-fi, television, automotive, marine, home appliances, test gear—it's all in our big new catalog.



Send Today! ▶

Prices are mail order net F.O.B. Benton Harbor, Michigan. Prices and specifications subject to change without notice.



## New The personal computer products you've been waiting for.

And the ones to which all others will be compared. Total computing systems for home, hobby, educational and business applications. Powerful, comprehensive software to get you up and running fast. Unequalled documentation and product support services coupled with low Heath prices make the difference.



LA36 DEC Writer II Keyboard Printer Terminal at Heath's SPECIAL LOW PRICE: \$1495 Assembled

## New Self-Instruction Course in Microprocessor Operation and Application

Another addition to Heath's famous Continuing Education Series. Learn microprocessor operation, interfacing and programming. Hardware and software experiments let you get hands-on experience using the ET-3400 Microprocessor Trainer.



HEATH Schlumberger	Heath Company, Dept. 122-360 Benton Harbor, Michigan 49022
Please send me my FREE Heathkit Catalog. I am not on your mailing list.	
Name _____	
Address _____	
City _____	State _____ Zip _____
AM-356	

# the latest gear for the VHF enthusiast




**Gamber-Johnson  
Deluxe slide mount  
\$17.88**

- Solid snap in design
- Attaches to radio mtg bkt (or directly to radio)
- Four molex pins for power and external speaker
- BNC RF slide connector
- pigtail UHF (SO-239) connections to radio and antenna
- designed for commercial use thru 1000 MHz

**Gamber-Johnson  
Console floor mount  
\$31.50**

- utilizes deluxe slide mount
- built in speaker
- mount attaches securely to floor

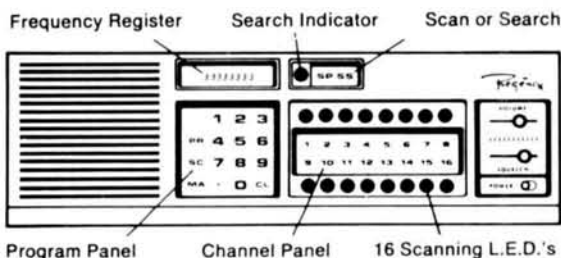**extra slide mount  
base \$8.40**  
stationary half of deluxe slidemount allows use of radio in second car or location



**Regency Digitally Programmable Scanner  
with Keyboard Entry  
special \$299**

Model ACT-T-16K

Frequency Range:  
Lo VHF .. 30- 50MHz  
Hi VHF .. 146-174 MHz  
UHF .. 440-512 MHz

Sensitivity:  
(20 DB quieting)  
Lo VHF ..... 0.5  $\mu$  V  
Hi VHF ..... 0.6  $\mu$  V  
UHF ..... 0.7  $\mu$  V

Selectivity  
 $\pm$  7 KHz (min.) @ 6 DB  
 $\pm$  15 KHz (max.) @ 60 DB  
Squelch: (threshold)  
Lo VHF ..... 0.4  $\mu$  V  
Hi VHF ..... 0.5  $\mu$  V  
UHF ..... 0.6  $\mu$  V

Search Scan Range:(max)  
Lo VHF 4000 channels  
Hi VHF 5600 channels  
UHF 5760 channels

## WESTCOM



**Westcom  
VHF Amplifiers**

Model	Band	Emission	P in	P out	Price
2M 3x30	144MHz	FM	1 - 4	30	72.95
2M 3x30L	144MHz	CW-FM-SSB/AM	1 - 4	30	82.95
2M 10x40	144MHz	FM	2 - 10	40	77.95
2M 15x80	144MHz	FM	5 - 15	80	129.95
2M 15x80L	144MHz	CW-FM-SSB/AM	5 - 15	80	139.95



## Ruggedized DC Power Supplies

Ideal for VHF Transceivers  
and Amplifiers

- 105-125 VAC, 50/60 Hz
- Fold back current limiting
- 13.8 VDC  $\pm$  .05V
- UL listed & computer grade components
- One year warranty
- 5 mV peak-peak max ripple

**Astron RS-6A \$49.95**

4.5 ADC Continuous  
6.0 ADC Intermittant  
Recommended for up to  
30 W amp's & xcvs

**Astron RS-20A \$89.95**

16 ADC Continuous  
20 ADC Intermittant  
Recommended for up to  
120 W amp's

**Astron RS-10A \$74.95**

8 ADC Continuous  
10 ADC Intermittant  
Recommended for up to  
70 W amp's

**Astron RS-35A \$129.95**

25 ADC Continuous  
35 ADC Intermittant  
Recommended for up to  
180 W amp's

## Larsen Electronics

### Larsen mobile antennas


$\frac{1}{8}$  wave, 3dB gain, 200 W rating

LM-150-K	2M roof mount	\$30.20
LM-150	w/magnetic mount	\$38.45
LM-150	w/trunk lid mount	\$37.90

for Motorola NMO type mount add \$5.25  
220 MHz and 450 MHz available at same price

Master Charge & B of A  
We ship prepaid in USA  
Calif. residents add 6% tax  
Check with order or COD

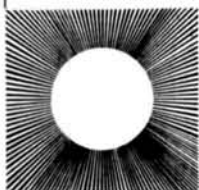10 day money back guarantee  
full satisfaction guaranteed  
Factory warranty on all items



# WESTCOM

COMMUNICATIONS DIVISION 1320 Grand Ave. San Marcos, CA. 92069 (714) 744-0728

# voice-operated gate to replace voice-operated relays for carbon microphones

Presenting a circuit  
using four ICs  
plus a couple  
of transistors and diodes  
to replace the old  
voice-operated relays  
in ssb transceivers

VOR is an acronym for what is often called the "voice-operated-relay" or "squawk-to-talk" circuit, as used in many modern ssb and fm transceivers. "Voice-operated-relay" was an adequate description when tubes and relay circuitry were used, but it's rather unusual to find such relays in today's all-solid-state designs. And so now we have the Voice Operated Gate, or VOG.

The VOG described here used four ICs plus a couple of transistors and diodes to accomplish pre-amplification, bandpass filtering, and audio gating. A logic output also comes out of the VOG (choice of 1 or 0 for *gate-on*), to serve as a turn-on signal for other sections of the system being voice controlled.

Incorporated in the VOG is a lowpass and highpass filter pair providing the equivalent of a 300-3000 Hz bandpass filter with 40 dB per decade rolloff at each edge. These filters are of the active type, built around operational amplifiers. Only the audio passing through the filters can actuate the gate (and thereby pass through the VOG); this helps to discriminate against ambient noise.

## VOG circuit

A diagram of the VOG is shown in **fig. 1**. The first section is a microphone preamp with an fet constant-current source for a carbon microphone. The carbon microphone is a variable resistance, so the injection of a constant-current into it causes the voltage across it to be representative of the variations in resistance of the microphone. The op amp that forms

By Hank Olson, W6GXN, P.O. Box 339, Menlo Park, California 94025

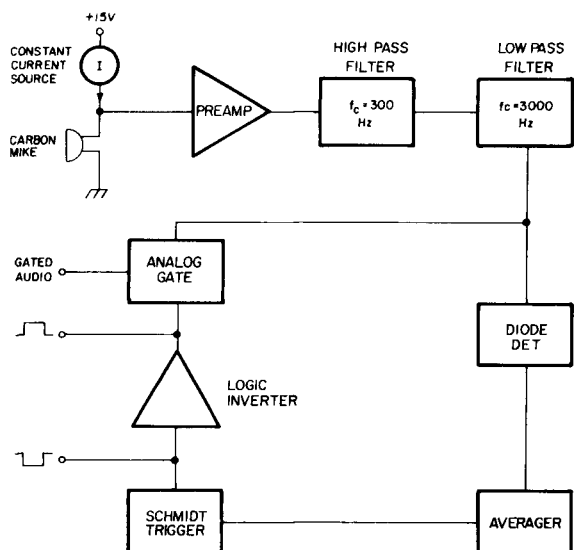


fig. 1. Voice-operated-gate (VOG) circuit block diagram. The circuit is a replacement for the old voice-operated relay systems prevalent in many modern ssb and fm transceivers.

the microphone preamp has a voltage gain of 100, which provides a voltage output of about 3 volts rms for usual carbon microphones during average close-talking use.

Following the microphone preamp is the highpass active filter followed by the lowpass active filter, each consisting of one section of the same quad op amp (U1) that's used as the preamp (see fig. 2). The last section of U1 is used as an *active* diode detector CR1, CR2, in which the op amp *linearizes* the detector. The diode detector is arranged to furnish the negative polarity of rectified audio.

The rectified audio from CR1, CR2 is then averaged by U2. Since the averager (U2) is also an inverter, the negative rectified audio is inverted and averaged to become a smoothed, long, positive pulse of the duration of the audio burst originally delivered by the microphone. This positive pulse is processed by U3, a Schmitt trigger, which sharpens the pulse leading and trailing edges and makes it

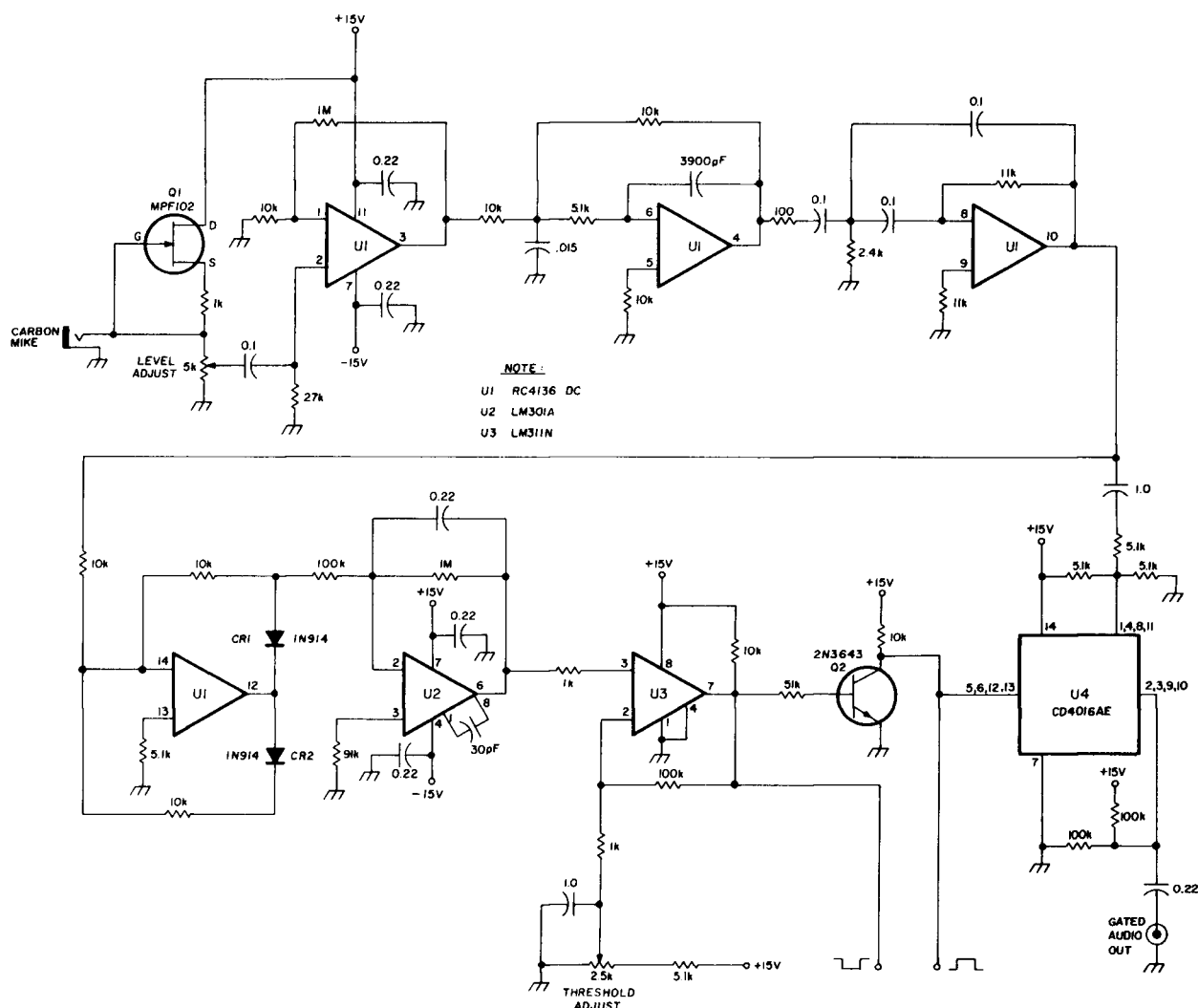


fig. 2. Schematic showing the carbon microphone preamp, bandpass filter, and voice-operated gate (VOG). Note that U1 is the equivalent of four  $\mu$ A741 op amps and could be replaced by four such ICs.

CMOS-logic compatible. The Schmitt trigger also inverts the pulse and adds an effect called hysteresis. That is, U3 output (pin 7) will go from 1 to 0 at an input level (set by the threshold-adjust pot) of say, 2 volts. U3 output will not return from 0 to 1 until the input voltage has dropped substantially below 2 volts. This hysteresis action prevents noise on the audio and minor voice level wavering from causing a chopping effect.

After the Schmitt trigger comes Q2, a simple transistor inverter, which inverts the audio-derived pulse to provide the proper polarity to turn on analog gate U4 when an audio signal is present. The inverter output and the Schmitt trigger output provide both 0 to 1 and 1 to 0 logic-level outputs, which can be used to actuate the turn-on function of the transmitter. Both polarities are handy, because this unit may be used with a number of transmitter designs.

The analog gate, U4, is a member of the RCA CD4000 CMOS logic family, which makes it much less expensive than some of the hybrid analog gates on the market. U4 consists of four analog gates. Since we need only one, all four sections have been wired in parallel. The CD4016 doesn't tolerate very large ac voltages without distortion, so the (filtered) audio input is attenuated at a ratio of 3:1 by a voltage divider at the analog input.

### adjustment and testing

Setup of the VOG is simple. Connect it to a carbon microphone and a  $\pm 15$ -volt supply. Connect a scope or ac VTVM to U1 pin 3 of U1. Talk into the microphone and adjust the LEVEL pot (fig. 2) until about 3 volts rms is seen, then adjust the THRESHOLD pot until about +2 volts is seen at its wiper arm. Connecting a scope or ac VTVM to the output should now show a pulse of audio when speaking into the microphone. A dc voltmeter at U3 pin 7 should jump from +15V for "no talking" to near zero for "talking". The same dc voltmeter at the Q2 collector should react in the opposite way: near zero for "no talking" and +15 volts for "talking."

### closing remarks

This VOG circuit was originally designed to replace one of the special-purpose ICs made by a large linear IC manufacturer. It surpasses the device it replaces in every way.

Note that U1 is the equivalent of four  $\mu A741$  op amps and could be replaced by four such ICs. Also, two  $\mu A747$ s (dual  $\mu A741$  op amps) or two MC1458s could also be used. U2 is best left as an LM301A, since the requirement here is for low input bias currents. When using other-than-called-for ICs, however, pin changes will have to be made.

ham radio

# the famous HAM KEYS

The keys that are easy  
to put your fingers on!




JUST DIAL  
**1-800-325-3636**  
TOLL FREE



#### Model HK-1

- Dual-lever squeeze paddle
- Use with HK-5 or any electronic keyer
- Heavy base with non-slip rubber feet
- Paddles reversible for wide- or close-finger spacing

**\$29<sup>95</sup>**

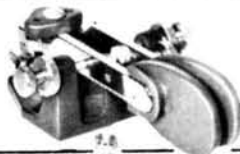

#### Model HK-2

- Same as HK-1, less base for incorporation in own keyer

**\$19<sup>95</sup>**



#### Model HK-3

- Deluxe straight key
- Heavy base, no need to attach to desk
- Velvet smooth action


**\$16<sup>95</sup>**

#### Model HK-3A

- Same as above, less base

**\$9.95**

Navy type knob, only \$2.75

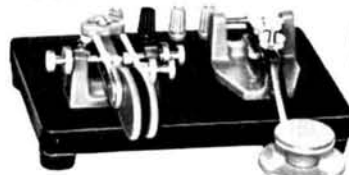

#### Model HK-4

- Combination of HK-1 and HK-3 on same base

**\$44<sup>95</sup>**

- Base only with rubber feet

**\$12.00**

Terminals, red or black, \$ .75 each



NEW AND IMPROVED

#### Model HK-5A Electronic Keyer

- New Cabinet Colored-Keyed to Match most modern radio equipment
- Iambic Circuit for squeeze keying
- Self-completing dots and dashes
- Dot memory
- Battery operated with provision for external power
- Built-in side-tone monitor
- Grid block or direct keying

**\$69<sup>95</sup>**

Same day shipment... PREPAID

We welcome the use of your



## HAM RADIO CENTER, INC.

8340-42 Olive Blvd. • P.O. Box 28271 • St. Louis, MO 63132

# accurate low power rf wattmeter

for high frequency  
and  
vhf measurements

How to build an  
accurate low-power wattmeter  
that measures  
up to 10 mW  
from 1 to 500 MHz —  
it uses small lamps  
as barretters

A pair of subminiature lamps used as an rf power detector make up the heart of a simple but accurate rf power meter, which can be calibrated directly from dc measurements. The instrument described in this article can be used to accurately measure rf power from 10 mW down to about 0.2  $\mu$ W, over a frequency range from 1 MHz to 500 MHz. Its high sensitivity makes it useful for a host of purposes including antenna gain measurements, local oscillator measurements, and vswr or filter response measurements in conjunction with low-power signal generators. Its maximum power capability can be extended to any level through the use of external calibrated attenuators or directional couplers. In

addition, homebrew attenuators and directional couplers can themselves be calibrated using the power meter.

The rf power detecting element in the wattmeter consists of a pair of incandescent lamps used as barretters. Barretters have been used for many years in commercial wattmeters and have been discussed in several previous articles.<sup>1,2</sup>

A barretter is a wire element whose resistance increases with temperature. Suppose a barretter is heated to a specific resistance (say 50 ohms) by a variable power source whose level is known. As long as the total power dissipated and the ambient temperature remain constant, the barretter resistance will remain at 50 ohms. Now suppose the barretter is also heated with power from a separate source (an rf generator in this case) whose level is unknown. The resistance of the barretter will increase. If the power supplied from the known source is then reduced until the barretter resistance returns to 50 ohms, the amount of power reduction from the known source will equal the power supplied by the unknown source. The unknown power level is thus measured by metering the decrease in the known power source.

The known power source can be adjusted automatically to maintain constant barretter resistance by using a bridge circuit in a closed loop with an amplifier. In many commercial microwave power meters the closed loop forms a self-balancing audio oscillator so that the known power source is an ac signal (in combination with some dc which is also applied). The oscillator technique has the advantage of eliminating dc offset drift errors in the balancing and metering circuits. In the power meter described here, however, the known power source is pure dc. The dc approach was chosen for ease of calibration and testing, for circuit simplicity, and to allow a wide rf frequency range. (The relatively large rf coupling capacitor required for low-frequency response would introduce excess phase shift and upset the balance


By James H. Bowen, WA4ZRP, 6500 Carefree Lane, Apartment B1-21, Roanoke, Virginia 24019

in an ac balanced bridge, depending on the low-frequency impedance of the rf source.)
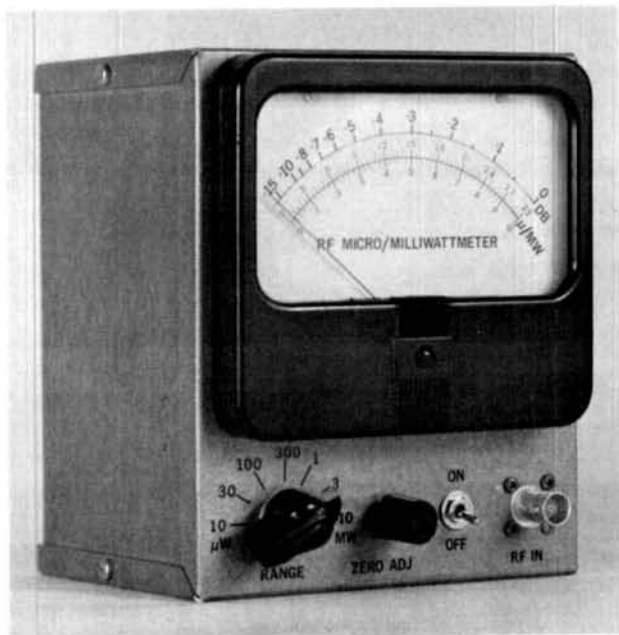
## circuit description

The circuit diagram of the rf wattmeter is shown in **fig. 1**. The design philosophy was to explore what useful sensitivity could be achieved in a simple circuit without the use of special low-drift components or special schemes for drift compensation. The experimenter who wishes to build his own version of the wattmeter is encouraged to try his hand at improvements.

The incandescent lamps, I1 and I2, used in the rf sensor are subminiature T-3/4 types obtained at a hamfest flea market. The lamps have wire leads and the glass envelopes are 0.187 inch (5mm) long by 0.094 inch (2.5mm) in diameter. Their dc characteristics indicate they are similar to Chicago Miniature types CM2, CM30, or CM3102. **Fig. 2** shows the measured current-voltage (I-V) characteristic of one of the lamps. Note the non-linear nature of the plotted data which indicates changing lamp resistance. This general characteristic is typical of all incandescent lamps with tungsten filaments. **Fig. 3** shows the same data plotted as dc resistance,  $V/I$ , versus power dissipated,  $VI$ . At rf frequencies, the resistance of the lamp during any rf cycle remains constant and equal to the dc resistance because one rf cycle is much shorter than the minimum thermal response time of the lamp filament (skin effect does not appear to seriously alter the resistance of the small diameter, high resistivity filament over the frequency range of interest).



The author's completed power meter.

In order to simultaneously feed dc and rf to the lamps over a wide bandwidth, the lamps are connected in series for dc and in parallel for rf. Chip capacitors C1 and C2 perform the functions of rf coupling and bypassing, respectively, with low impedance over a wide frequency range. If chip capacitors are not available, small ceramic disks with zero lead length may be used. For good uhf measurement accuracy, construction of the rf sensor must be based on good uhf construction practices, with emphasis on minimizing parasitic inductances by keeping all leads short. The rf paths through C1, either lamp, and C2 to ground must be as short as possible.

The rf sensor is built on a small piece of double-clad glass-epoxy printed-circuit board 1/16 inch (1.5mm) thick as shown in the photograph. Both sides of the board were soldered directly to the rear of a BNC connector, with the connector center pin soldered to a pad approximately 0.105 inch (2.5mm) wide. This pad forms a 50-ohm microstrip transmission line leading to chip capacitor C1. One lead of both I1 and I2 is soldered to a small pad connected to the other end of C1. A small hole is drilled through the board at the ground lead of I2 so this lead can be soldered to the ground plane on both sides of the board. The opposite lead of I1 is soldered to the pad in the upper right hand corner in the photo. A dc feed wire is also soldered to this pad and chip capacitor C2 is soldered from the point of attachment of I1 across a gap to the ground plane.

On the ground side of C2, another hole is drilled through the board and a wire is soldered through this hole to form a direct connection to the ground plane on the back of the board. The use of small filament lamps with low parasitic inductance, and this method of construction ensure good performance into the uhf portion of the spectrum. (**Warning:** chip capacitor ends must be soldered quickly with minimum heat; otherwise tin-lead solder will rapidly leach away the metallization from the ends of the capacitors.)

The layout of the remaining dc portion of the wattmeter circuit is not particularly critical and was built on a Vector DIP padboard mounted on the meter terminals. The unit is housed in a 4 x 5 x 6 inch (10.2 x 12.7 x 15.2cm) minibox.

The lamps are operated at sufficient dc current to bring their series resistance to 200 ohms. If the lamps are reasonably well matched, the resistance of each lamp will be about 100 ohms, making the parallel rf resistance equal to 50 ohms. If two lamps identical to the one plotted in **fig. 3** are used, each will dissipate about 7 mW at a resistance of 100 ohms, for a total dissipated power of 14 mW. Thus, 14mW is the maximum rf power which can be measured in a 50-

ohm system with two such lamps. A highest scale of 10 mW was therefore chosen for the wattmeter. Random drift establishes a practical limit of  $10\ \mu\text{W}$  for the most sensitive scale.

To maintain their series resistance at 200 ohms, the lamps are operated in a bridge circuit consisting of R1, R2, R3, and the rf sensor. For best accuracy, R1, R2, and R3 should all be selected to be as close as possible to 200 ohms with R1 and R2 selected for best match, and R3 selected closest to 200 ohms.

The voltage difference between the two legs of the bridge is sensed and amplified by U1, a  $\mu\text{A}741$  or similar type op-amp IC. The capacitors in the feedback loop of U1 form an integrator for very high dc gain and good stability. The output of U1 passes through diode CR1 to transistor Q1, the bridge current driver. Q1 is connected as an emitter follower, and supplies the necessary current to bring the bridge to a balanced condition. The 10k resistor across Q1 feeds a small residual positive bias to the bridge to ensure that the bridge will always come to balance with a positive potential, even though U1 may initially turn on with a negative output. Diode CR1 prevents emitter-base breakdown of Q1 if U1 turns on with a negative output.

Following turn-on, the output of U1 will quickly

become positive in response to the residual positive bias on the bridge. The voltage at the output of U1 will continue to increase until enough current flows through the rf sensor to bring its resistance to 200 ohms, at which point equilibrium is achieved. In practice, the bridge comes to balance within a second or two of turn-on, with some overshoot due to the thermal lag of the lamps.

The equilibrium voltage at the top of the bridge,  $V_B$ , (3.50 volts in the unit shown) is fed to the metering circuit made up of U2A, U2B, and associated components. Range switch S2A selects one of the calibration resistors, R4 through R10. A method for calculating the values of these resistors is covered in the calibration section.

Op-amp U2A compares the voltage selected by S2A to a reference voltage established at pin 3 of its input. Since the full-scale voltage change in  $V_B$  is only 1.1 mV for the  $10\ \mu\text{W}$  scale, the reference voltage supply must be extremely stable and minutely variable. To establish a stable reference voltage, fet Q2 is connected as a constant-current source feeding zener diode, CR2. Any fet having an  $I_{\text{DSS}}$  of 3 mA or more could be used for Q2. Alternatively, a 5-volt, three-terminal regulator IC could probably be used instead of Q2 and CR2.

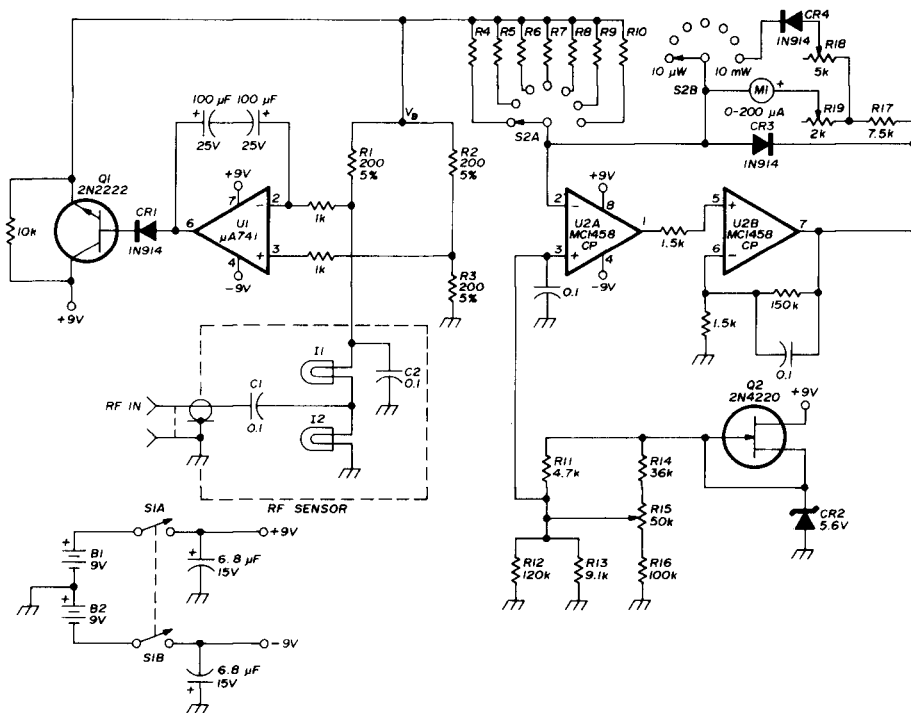



fig. 1. Schematic diagram of the rf wattmeter for 1 to 500 MHz. Fixed-value capacitors are disk ceramic except as noted; polarized capacitors are electrolytic or tantalum; resistors are  $\frac{1}{4}$  or  $\frac{1}{2}$  watt carbon composition types.

- C1, C2 0.1  $\mu\text{F}$  chip capacitor or miniature leadless ceramic discap  
 I1, I2 subminiature T-3/4 incandescent lamp (Chicago Miniature type CM2, CM30, or CM3102)  
 J1 BNC jack, flange mount  
 R15 miniature 50k 10-turn pot

- R18 5k trimmer  
 R19 2k trimmer  
 R4-R10 (see table 1 of text)  
 S1 dpst toggle switch  
 S2 2-pole, 7-position rotary wafer switch

Resistor network R11 through R16 divides the zener voltage down to the value required to match  $V_B$ . To get the required voltage resolution with a reasonable adjustment range, a miniature 10-turn pot was used at R15. If a 10-turn pot is not available, then both a coarse and a fine adjust pot must be used. Resistors R11 through R14 and R16 reduce the adjustment range of R15; this increases resolution. Resistors R11 through R13 are chosen to establish a reference voltage close to  $V_B$  with the wiper of R15 disconnected. Resistors R11 through R13 also serve to maintain a fairly low impedance for the reference voltage. Resistors R14 and R16 are selected to reduce the adjustment range of R15, and to establish a residual voltage close to  $V_B$  on the wiper of R15 when the wiper is set at mid-range.

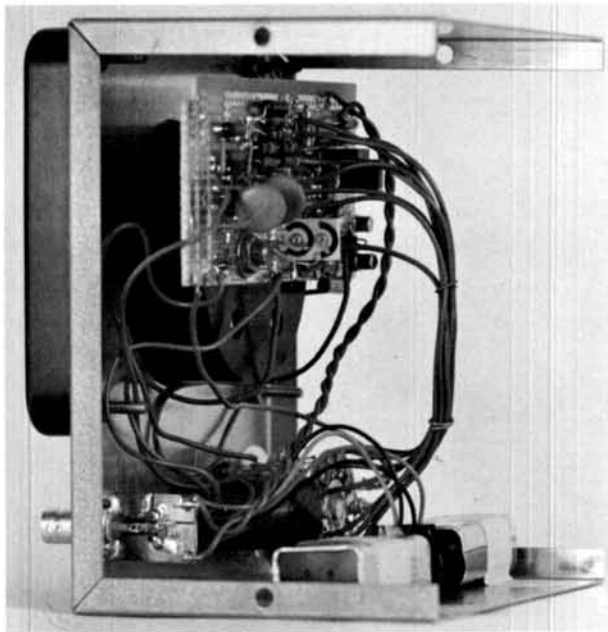Since the specified minimum open-loop gain of a single  $\mu A741$  op amp is marginally low for proper operation of the metering circuit, two op amps are con-



Interior of the rf power wattmeter. All active circuits are installed on the perf board mounted on the meter terminals. The two incandescent lamps are mounted on the small section of printed-circuit board soldered to the BNC jack (lower left).

nected in cascade. Op amp U2B supplies an additional gain of 100 to the open-loop gain of U2A. A dual op amp, the MC1458CP, was used for U2A and U2B, though two  $\mu A741$ s could have been used or a quad 741 could have been used for the entire unit.

The meter, M1, is connected in the feedback path of U2. Meter M1 is a 200  $\mu A$  meter removed from an old vacuum-tube voltmeter. The action of U2 is to supply enough current through the feedback path to maintain the voltage at pin 2 of U2A equal to the

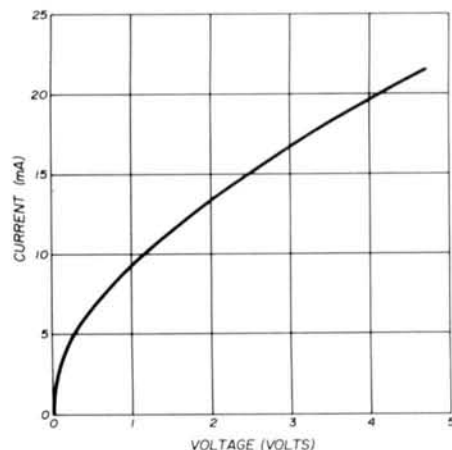


fig. 2. Current-voltage (I-V) characteristic of an incandescent lamp of the type used in the rf power meter.

reference voltage at pin 3. Since the current flowing in pin 2 of U2A is negligible, the current in the feedback circuit continues through the calibration resistor,  $R_{CAL}$ , selected by S2A. This current has no effect on  $V_B$  because it is automatically compensated for by U1. By Ohm's law, the feedback current is equal to  $\Delta V / R_{CAL}$ , where  $\Delta V$  is the difference between the reference voltage and  $V_B$ . On all scales except the 10 mW scale, all feedback current normally passes through meter M1. Diode CR3 conducts when the feedback current is negative, preventing M1 from pinning hard in the negative direction when the circuit is negatively unbalanced. Resistor R17 prevents M1 from being severely overloaded in the positive direction when the circuit is unbalanced positively. Resistor R17 is selected so that M1 reaches full scale somewhat before the output of U2B saturates in the positive direction. Resistor R18 and diode CR4 shunt some feedback current past M1 on the high end of the 10 mW scale to linearize the reading.

To allow portable operation, the unit is powered by two 9-volt batteries. Battery voltage sag following turn-on contributes some additional drift to the circuit. The miniature transistor radio batteries shown in the photograph sagged excessively and have been replaced by larger 9-volt batteries (Eveready 246). For enhanced stability, somewhat higher battery voltage could be used followed by electronic regulators to 9 or 12 volts. If it is desired to power the unit from the ac line, regulated dc supplies are a must.

The value of calibration resistance,  $R_{CAL}$ , for any scale is determined by calculating  $\Delta V$ , the change in  $V_B$  for a given applied rf power level. The total dc power dissipated in the bridge is given by  $V_B^2$  divided by 200 ohms, the series-parallel combination bridge resistance. Since each leg of the bridge has

equal resistance, the dc power dissipated in the rf sensor is 1/4 the total dc power dissipated in the bridge. The rf power applied to the sensor,  $P_{rf}$ , is equal to the difference in dc power dissipated in the sensor with no rf applied and the dc power dissipated in the sensor with rf applied, as expressed by

$$P_{rf} = \frac{1}{4} \frac{V_{BE}^2}{200} - \left( \frac{1}{4} \right) \frac{(V_{BE} - \Delta V)^2}{200} \quad (1)$$

where  $V_{BE}$  is the equilibrium voltage at the top of the bridge with no rf applied and  $\Delta V$  is the change in

table 1. Calculated values for calibration resistors for the rf power meter ( $V_{BE} = 3.5$  volts,  $I_{FS} = 200 \mu A$ ).

$P_{rf}$	$\Delta V$	$R_{CAL}$
10 $\mu W$	1.143 mV	R4 = 5.715 ohms
30 $\mu W$	3.430 mV	R5 = 17.15 ohms
100 $\mu W$	11.450 mV	R6 = 57.25 ohms
300 $\mu W$	34.460 mV	R7 = 172.30 ohms
1 mW	116.200 mV	R8 = 581.10 ohms
3 mW	361.500 mV	R9 = 1808.00 ohms
10 mW	1.438 V	7192 ohms (see text)

of  $R_{CAL}$  for proper full-scale reading is determined by dividing  $\Delta V$  by  $I_{FS}$ , the full-scale value of meter current. **Table 1** shows the calculated values for the meter shown. Similar calculations should be made when duplicating the wattmeter, using the measured values of  $V_{BE}$  and  $I_{FS}$ .

The equation for  $\Delta V$  is the equation of a parabola. Thus, the meter current varies parabolically instead of linearly with rf power. On the low-power scales, however, the voltage varies over such a small sector of the parabola that for all practical purposes it is linear. On the highest scale, the deviation from linear becomes significant, and is such that when the meter is calibrated for an accurate full-scale reading, the indicated power will be less than the actual applied power at levels below full scale. **Table 1** shows that a resistance value of 7192 ohms is needed for proper full-scale calibration of the meter on the 10 mW scale. For accurate calibration near the bottom of the 10 mW scale, a resistance 1000 times the value of the calibration resistor for the 10  $\mu W$  scale, or 5715 ohms, would be required. Therefore, without some form of compensation, readings made near the bottom of the 10 mW scale will be only 79 per cent of the actual value, or 1 dB low.

To avoid lettering a special nonlinear 10 mW scale on the meter face, I used a compensation network. A compromise value of the calibration resistor R10 was selected at about 6000 ohms to reduce the error at the low end of the 10 mW scale. On the same scale, switch S2B connects the series combination of CR4 and R18 across M1 and R19. Toward the high end of the 10 mW scale, CR4 begins to conduct, shunting the excess current past M1. Variable resistor R18 determines the amount of current shunted away from M1, and variable resistor R19 determines the point at which diode CR4 begins conducting.

Before adjusting R18 and R19, an accurate voltmeter is connected from the top of the bridge (at  $V_B$ ) to the reference voltage at pin 3 of U2A to read  $\Delta V$ . A value of  $\Delta V$  corresponding to a full-scale reading of 10 mW (1.438 volt in the meter shown) is artificially established by adjusting the reference voltage level. Then R18 is adjusted for a full-scale



Construction of the rf sensor showing the two incandescent lamps and chip capacitors C1, C2. Components are mounted on a small section of double-clad PC board which is soldered to the rear flange of the BNC connector.

bridge voltage following application of rf. Solving the above equation algebraically for  $\Delta V$  results in the following solution:

$$\Delta V = V_{BE} - \sqrt{V_{BE}^2 - 800P_{rf}} \quad (2)$$

A given desired full-scale rf power is used in **eq. 2** to determine a corresponding  $\Delta V$ . The required value

reading of the power meter. A  $\Delta V$  corresponding to a reading of 6 mW (0.7705 volt in the meter shown) is then set and R19 is adjusted for a reading of 6 mW.

Since these two adjustments interact, they should be repeated several times until the meter reads both 10 mW and 6 mW. Linearization is now complete and the meter should be found to be quite accurate at all power levels.

The adjustment of R19 has no effect on the calibration of the other scales, provided the output of U2B is not at saturation for full-scale deflection of

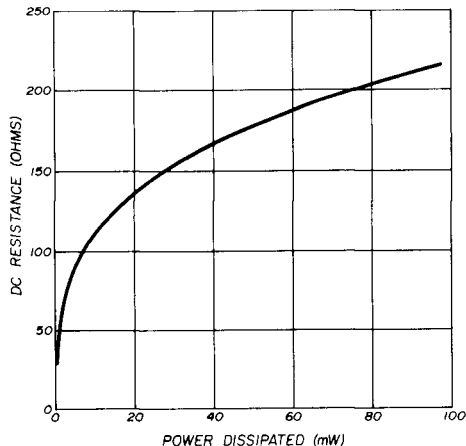


fig. 3. Plot of lamp resistance vs power dissipated in the lamp.

M1. Since the nonlinearity on the 3 mW scale is such that readings on the low end of this scale are only 5 per cent low ( $-0.23$  dB), no linearization was deemed necessary for this and lower scales.

For most accurate results, the values of  $R_{CAL}$  used for the lower scales should be as close to the calculated values as possible. Junk box resistors within a per cent or two of the desired values were selected using a digital ohmmeter. Where a proper value could not be found, a series or parallel combination was used.

The dB scale was added to the meter face so power could be read directly in dBm (dB with respect to a milliwatt) and so that losses and gains could be read out directly in dB. The scale position corresponding to each dB mark is given by

$$P = \frac{1}{\text{antilog}_{10}(0.1X)} \quad (3)$$

where  $P$  is the relative scale position (with 1 = full scale) and  $X$  is the number of dB below full scale.

### procedure for use

Following turn-on, the meter is allowed to stabilize and the desired scale is selected. In the meter shown,

stabilization is almost immediate on the higher power scales; several minutes are required on the  $10 \mu\text{W}$  scale before warm-up drift ceases. Once the meter has sufficiently stabilized, the zero adjust pot, R15, is adjusted for zero reading. The rf power is then applied and readings are made. Provided the lamps are not burned out, the meter will not be damaged by exceeding the maximum power for the scale selected. Since the lamps can safely dissipate 200 mW, a considerable margin of safety exists. Random drift is significant on the  $10 \mu\text{W}$  scale; thus the meter zero should be checked between readings for greatest accuracy when using that scale.

### measured performance

Following calibration as described, the rf wattmeter was connected through one foot (30cm) of RG-58/U coaxial cable to the calibrated output of a Wavetek 3001 rf generator. Over the frequency range from 1 to 500 MHz, the generator power setting agreed to within 0.3 dB of the wattmeter reading at full scale on all wattmeter scales. The good agreement cannot be taken as a claim for wattmeter accuracy, however, because the specified worst-case generator power error on the most accurate power range is only 1.25 dB.

At 432 MHz, the input swr of the wattmeter was measured at 1.6:1. When measuring power from a 50-ohm source at 432 MHz, the resulting reading is calculated to be 0.24 dB low, due to reflected power. If the impedance of the source is adjusted to conjugately match the load presented by the wattmeter and interconnecting low-loss cable, this source of error is eliminated. On lower frequencies, the swr and resulting mismatch loss are expected to be even less because the parasitic reactance of the lamps and fixtures will be lower.

The wattmeter sees nearly constant use in testing rf circuits and devices of all types. Used directly, or with attenuators, it measures gains and losses. Used with directional couplers, hybrids, or rf bridges, it measures reflected power, return loss, and standing wave ratio. Since the lamps are a high temperature 50-ohm load, the wattmeter is also used as a noise generator for receiver rf amplifier tuneup and testing. In the few months since its construction, the wattmeter has become a virtually indispensable addition to my test bench.


### references

1. Robert S. Stein, W6NBI, "How to Use the Lab-Type Rf Power Meter," *ham radio*, April, 1977, page 44.
2. Bruce Clark, K6JYO, "RF Power Detecting Devices," *ham radio*, June, 1970, page 28.

ham radio

# ALPHA...

## The Cool Kilowatt

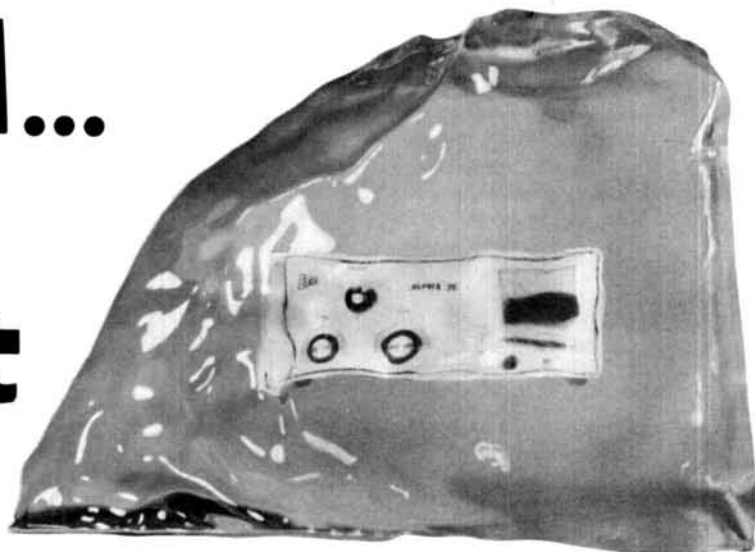

It's no trick to make a compact linear amplifier that'll put out a kilowatt or two . . . for a while.

What distinguishes **ALPHA** amplifiers from the rest is their ability to operate *indefinitely* at a full kilowatt average—2 KW PEP—and stay cool.


Every professional designer knows that heat is the arch-enemy of high power components. The keys to reliable amplifier performance are, therefore . . .

- Robust, conservatively-rated parts
- Efficient operational design
- Carefully engineered cooling

Short-cutting even one of these areas practically guarantees major failures!

Every **ALPHA** is engineered around ETO's exclusive and highly efficient 'ducted air' cooling system. Cool air is circulated around the power transformer and throughout the cabinet, then ducted through the tube cooling fins and directly out of the cabinet at the rear.

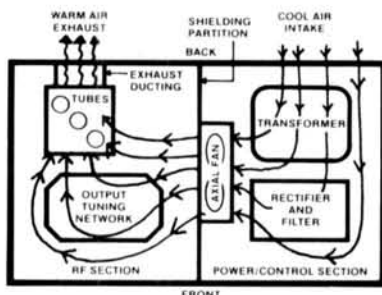**SIMPLIFIED DIAGRAM, ALPHA 374  
DUCTED-AIR COOLING SYSTEM  
(TOP VIEW)**



The standard **ALPHA 76** that ran key-down for 18 days at 1000 watts d-c input was finally shut down for inspection. It was in perfect shape, ready to go on indefinitely.

26,000 minutes key-down at full ratings! That typical **ALPHA** performance illustrates why every model—including the value-packed **ALPHA 76** and the No-Tune-Up **ALPHA 374**—can carry both a No-Time-Limit (NTL) full-power rating and an 18 month factory warranty!

(In shopping for a linear, it pays to investigate very carefully. Most manufacturers *do not* provide positive cooling for critical power supply or plate circuit components. Some widely-distributed models have their transformers located in virtual 'heat chambers'—with even natural air convection cut off—and blow heated air (from the tubes) over other circuitry before exhausting it forward!)

Buying or home-brewing, either way you may pick up useful do's and don'ts from ETO's guide, "Everything You Always Wanted To Know About (Comparing) Linears . . ."—It's yours free for the asking.

**ALPHA: Sure you can buy a cheaper linear . . . but is that *really* what you want?**



### ALPHA 374


- No Tune Up, 80-10 meters!
  - 2 KW PEP, 1 KW avg., NTL
  - RF output typically 1200+ watts PEP into 1.5:1 SWR
  - Harmonics -50db; IMD -30 db
  - 0.9 cu. ft.; 52 pounds
- 18 MONTH WARRANTY**



### ALPHA/VOMAX

New split band speech processor can boost your "talk power" 10db or more when conditions get rough. Very low distortion, easy to install and use with any rig.

**18 MONTH WARRANTY**

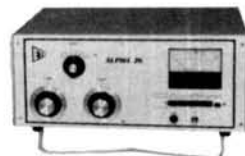

### ALPHA 76

- 2 KW PEP, 160-10 meters
  - 1000 watts average, NTL
  - Full pi-L; harmonics -52db
  - Nominal efficiency over 60%
  - Just 1 cu. ft.; 70 pounds. (Light-weight option, 50 lb.)
- 18 MONTH WARRANTY**

CALL OR WRITE YOUR DEALER—OR ETO DIRECT—FOR DETAILED LITERATURE AND FAST SERVICE ON THESE AND ALL **ALPHA** PRODUCTS

**ETO** Ehrhorn Technological Operations, Inc.

P.O. Box 708 · Cañon City, Colorado 81212 · (303) 275-1613

# drift-correction circuit

## for free-running oscillators

If you're bothered  
by warmup drift  
in your transceiver,  
here's a circuit  
that provides  
automatic compensation  
and uses  
readily available components

**The principle of drift** correction of an oscillator can be used in receivers or transmitters to compensate for warmup drift. The principle can also be used in new designs using simple free-running oscillators instead of the more complex types that use heterodyne mixing or phase-locked loops.

The idea is simple and straightforward. It can be best explained if you consider the operation of a frequency counter in which an oscillator frequency is measured. If the counter gate time is one second, and if sufficient displays are present, a 14-MHz signal could be displayed as 14.012.345 MHz. If, after the next measuring period, the least-significant digit changes from 5 to 7, for example, the oscillator frequency will have drifted 2 Hz high during that period. To counteract the drift, you could manually tune the oscillator back to its original frequency after each measurement. But there's a better way — read on.

In the system described here, oscillator drift is compensated automatically. Only the last digit of the counter display is inspected after a measurement period. It is checked if the number is above or below a fixed value (5 in the example above). For values of 6, 7, 8, or 9, a voltage on a varicap in the oscillator reduces the frequency; for values of 0, 1, 2, 3, and 4, the reverse action occurs.

From this simple example it can be seen that:

1. The oscillator frequency always varies at a slow rate around a fixed value.
2. Stable points occur within 10 Hz from each other over the vfo tuning range.
3. Drift and short-term stability of the oscillator must be within limits. In the example cited, the drift must not exceed a few Hertz per second, otherwise the circuit can't compensate for the drift.
4. The automatic correction should be *very light*. If, after one correction period, the frequency overshoots too much, the remedy is worse than without the system.

For proper operation the correction-circuit time constant must be rather long (but also short enough to counteract the "natural" drift). Because of the long time constant, tuning feels quite normal. After a manual frequency adjustment, the frequency will creep to its nearest "stable" point (actually an unstable point) and will remain there. Because these points are closely spaced you don't notice the operation of the system by listening to a CW or ssb signal.

Note that, for correct operation of the system, the time base frequency doesn't have to be exactly 1 Hz, but the time base must be very stable. Thus the time base must be derived from a crystal oscillator. Counting can be in binary instead of binary-coded decimal format.

### circuit description

The circuit is shown in **fig. 1**. Only one stage of a counter is required. A 74LS93 binary counter (U1) counts the oscillator frequency that is to be stabilized. This stage is preceded by a 2N709 transistor

**By Klaas Spaargaren, PAØKSB, Ruischenstein 29, Amstelveen, Holland**

(Q1) to obtain sufficient sensitivity. About 100 mV of input signal is required.

After each counting period, the value of the  $2^3$  output ( $Q_c$ , pin 8, of U1) is stored in a D-type flip-flop, U2, (half of a CD4013) at the rising edge of the time base signal. The flip-flop output drives an integrator (U3) up or down, which in turn drives a varicap in the oscillator to correct the frequency.

The time base frequency that actually determines system stability is derived by dividing the frequency of a crystal oscillator. A 1-MHz crystal oscillates with one input gate of a CD4060, (U4), which also contains 14 binary dividers. In combination with a CD4020, (U5), these two circuits divide the 1-MHz frequency by  $2^{18}$  to about 3.81 Hz, so the stabilization points are spaced at 3.81 times 8 Hz, or 30.5 Hz.

I found that FT241 crystals between 400 and 500 kHz oscillate very well in this circuit. The total dividing factor should be  $2^{17}$  in that case, which can be obtained by using output pin 2 of U4 instead of pin 3, as shown in fig. 1.

The counter counts almost continuously. Just after the transfer of the state of the  $Q_c$  output to the D-type flip-flop (U2), a short reset pulse is generated by the other half of the flip-flop (U6). To achieve this action, the clock input signal of U6 is delayed by R1C1. After the Q output is set, the flip-flop resets itself because the Q output is connected through R2C2 to its own reset input. The resulting positive-going pulse is about 0.5 microsecond duration (line 3, fig. 2). This pulse resets the 74LS93 counter to zero which starts counting again immediately thereafter.

Worth mentioning is the long time constant of the integrator, which is formed by R3 and C3 (fig. 1). Capacitor C3 must be a low-leakage type, not an

electrolytic. A polystyrene or polycarbonate type will do.

The switches labeled UP and DOWN (fig. 1) serve a dual purpose. First, after circuit switch-on, the integrator output can be brought into its range manually; but also, small frequency variations can be made by pushing the UP or DOWN button. So a push-button-controlled fine tuning is obtained, which is convenient if, for example, a CW signal slowly drifts out of a narrow CW-filter passband. (With this system installed you can be sure it's the other station that drifts.)

The CA3140, a very convenient operational amplifier, is used because of its high fet input impedance. The integrator output signal can be monitored on a meter to verify that it's still within its operating range. The action of the varicap in the oscillator must be such that a 10-volt output variation of the integrator shifts the frequency about 3 kHz.

## construction

The circuit was built onto a piece of Vero board and installed in my CW transceiver. A double-balanced diode mixer is used in my rig, so a high-level oscillator signal was available.

The UP and DOWN pushbuttons were mounted on the transceiver front panel. The control signal was monitored in a particular position of the transceiver meter switch.

Several prototype circuits were built using different construction methods, such as mounting all components on a copper-clad board with the ICs in sockets, but mounted upside down so that the socket pins could be wired directly. All these prototype circuits worked well, so the layout shown shouldn't be too critical. Just make sure that you avoid long wires between the ICs.

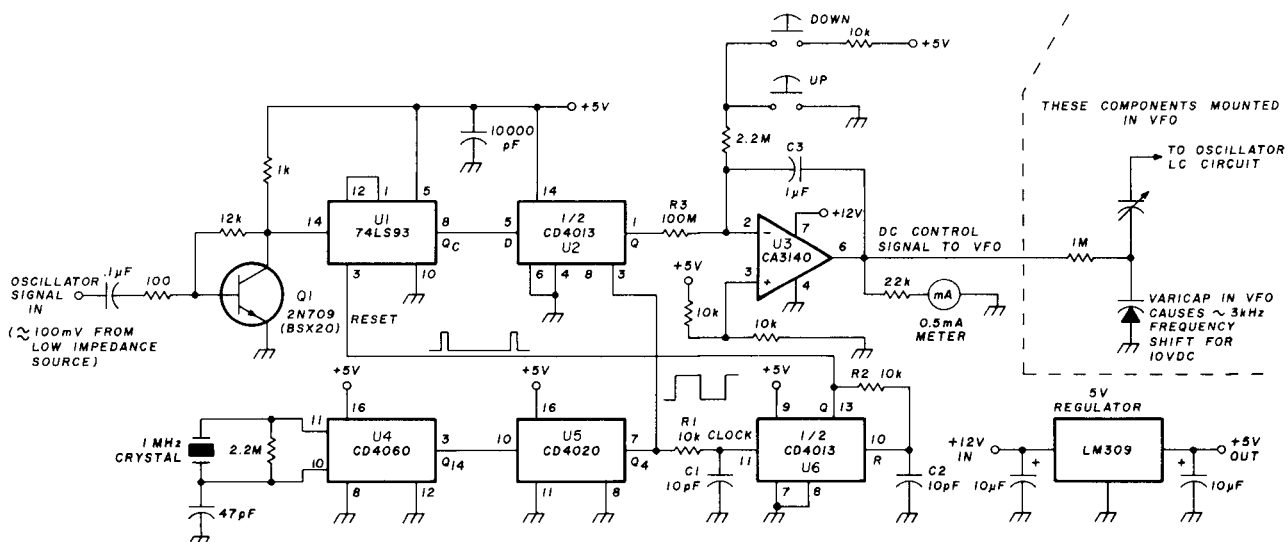


fig. 1. Circuit for vfo stabilization.

The circuit shown has been used for quite some time in my transceiver, which has a free-running oscillator on all bands. The highest frequency is 21 MHz, but the circuit has been used experimentally with oscillators operating to 40 MHz.

Within one minute after switch-on, the transceiver has crystal-quality stability on all bands. The 30-Hz frequency spacing between stabilization points is more than adequate for CW and ssb work. Also, during transmission, with about 200 watts to the anten-

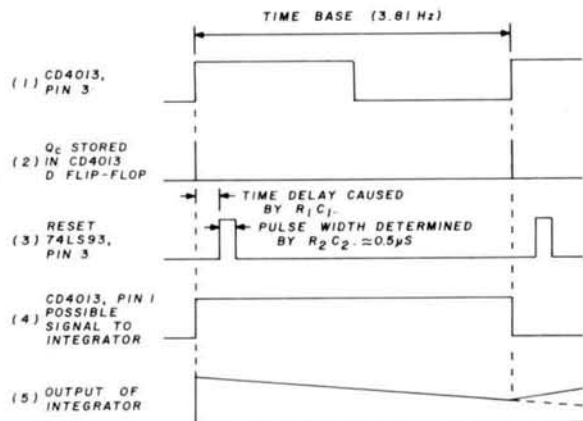


fig. 2. Timing sequence of signals in the circuit of fig. 1. The time base is 3.8 Hz.

na, a jump to another stabilization point has never occurred.

A kind of proportional control system was tried instead of the constant-speed system described above. In this system, the corrective action depended on the *offset* value. Although the control could be measured (to be more effective), I believe this idea is really not worth the more complex electronic circuitry. Reason: with both systems a vfo becomes virtually drift-free, and both systems are not noticed during operation.

## conclusion

The system described here doesn't turn a bad vfo into a good one but helps to make a good one even better. Especially where a low-noise oscillator is important, as for local oscillators in high dynamic-range front ends for receivers to obtain low reciprocal mixing, I believe this technique could be applied successfully at least for hf-band applications.

Synthesized oscillators appear to be noisier than good free-running types so if this system is used in combination with a digital frequency read out, on a well-designed, free-running oscillator, a much simpler system results than is possible with fully synthesized oscillators, giving at least the same or better results.

ham radio



**RF Power Meter** - identical to HP Model 430C - Read article April '77 HR Mag., Pg. 44 for use. Copies of article available on written request. Our **special purchase** is your gain at \$34.95 ea. Note: This is Gen'l Microwave, 451. Bolometer/thermistor mount available with purchase. \$45.00

## Audio Compressor AN/GSA-33

Five identical plug-in compressor amps with power supply in 19 inch rack, **all solid state**, 600Ω in & out, great for auto patch and phone patch. Weighs less than 30 lbs. Built like a battleship.

\$34.95

**HYBRIDS** - Two wire to four wire Telco with network build out capacitors, super for auto patch. \$5.95

## RECEIVERS



**ARR-41/R-648 Collins Airborne version of R-390.** Mechanical filters, Digital Tuning, 28 VDC. Easily converted to 115VAC, 190-500 kHz, 2-25 MHz. Modular construction. \$185.00 checked

**GPR-90RX** - 0.54 to 31.5 MHz, 110V, 60 Hz, info on request. \$375.00

**R-388/51J** - Collins 0.54 to 31 MHz \$375.00

**R-390A** - 0.54 to 31 MHz, overhauled complete \$595.00

**SPECIAL!** R-390 with CV591 SSB Converter and outboard audio amp. All in neat 19" rack. Special! \$500.00

**RACAL Model 6217A**, 980 kHz, 32 MHz, All Solid State, takes about 3 inches of rack space, digital tuning \$1600.00

**Stoddart UHF** tunable preamps, 375 MHz to 1 KMHz - It's really a converter, IF output 21.4 MHz. \$175.00

**LTV receivers:** G-111, 100-150 MHz \$150.00  
G-243, 400-1000 MHz \$225.00



**TMR-5** with front end plug-ins to cover 105-140 MHz and 200-260 MHz. \$250.00

**CEI type 415**, 60-250 MHz, all solid state, modular constr., xtal controlled, 4 channels. Incredible value. \$85.00

**SR-13A**, 2 to 30 MHz, good condition. \$285.00

## TEST EQUIPMENT

**Frequency Counter**, LTV Model G-195, all solid-state \$195.00

**Tektronics 545**, several to choose from, \$175 to \$375, depending upon condition; call or write.

**SA84-WA** Polarad 10 MHz to 63 GHz. \$475.00

**ANOTHER MICROWAVE GOODIE:** 2-8 GHz, contains high-pass filter and HP-423A XTAL detector. \$34.95

**HP608D**, 10-420 MHz. \$425.00

**Crystal Detectors**, HP-423A or equivalent. \$25.00

## TRANSMITTERS


**PAL-1K**, one kilowatt output linear amplifier, 2-32 MHz continuous, with all power supplies and manual; unit requires only 100-mW drive, uses 8295 final, vacuum-variable tuning, complete metering. A real buy . . . \$550.00

**GPT-750 Transmitter** mfd. by the Technical Material Corp., 2 to 32 MHz, CW/USB/LSB/ISB, one KW to the antenna, 24 hrs. a day if you're so inclined - with documentation, fair condition, built like a battleship. \$375.00



**T/T Decoder Board** - This board was removed from a language lab remote control system. You draw the schematic (because there wasn't one with the board). \$34.95

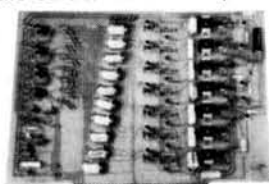**Standard T/T pad** mounted in a sturdy steel case incl. 2 volume pots & 1 push button labeled "Stereo" - Also has 2 phone jacks for headphones, microphone, etc. Will make a fine control head. \$24.95



**Line Filters** - 20 A or better at 115/230 VAC. Made by Filtron. \$8.95

**TRANSCIVER** - RF Commun. Inc. Model RF301, 2 to 15 MHz, 1 kHz steps, synthesized. Write for complete brochure. \$850.00

**Wanted:** Cables, Accessories, Test Set, etc. for RT400/ARC65, Especially Radio Set Control, C-451A/ARC-21.

**DISC-CAP**, 19075 BRAEMORE RD.

NORTHridge, CA. 91326

213-360-3387

Cal. Residents - add State Sales Tax. Unfortunately, Disc-Cap can only service U. S. customers.

# SPECSCAN-S Programmable Scanner

... The ONLY Digital Scanner made for the IC-22S. It adds a whole new dimension to 2M FM. If any other accessory can make your IC-22S as versatile as the SPECSCAN-S does, Buy It!

- Scans the entire 146-147 MHz Band in 15 kHz steps, automatically, or manually
- Automatically reads out your other 21 channels when they are used.
- Can be used as a remote programming unit with the radio hidden under the seat, etc.
- Exclusive VARI-SCAN™ control allows full control of scan rate in either direction!
- Full compatibility with the duplex mode.
- Uses state of the art CMOS logic.
- Low current drain. Less than 500 mA.
- RF immune. Unaffected by nearby equipment and in high RF areas.
- Large LED display lets you see every channel at a glance.
- Manual mode features lets you scan past any portion of the band and manually select a desired channel.
- Easy installation. Uses only one matrix position leaving the other 21 useable for manual programming.
- Plugs into 9 pin accessory socket.
- Adjustable scan delay feature.
- 90 day limited warranty.



ONLY **149<sup>95</sup>** Amateur Net  
Send S.A.S.E. for more SPECSCAN info.

Send S.A.S.E. for more  
SPECSCAN information



Our 1977 Convention Season is over, and we would like to thank the thousands who visited our booths.

We have some new display units at reduced prices. Most of these were opened and shown at a convention and put back in their boxes. All are new units and carry factory warranty.

	List	Display	ICOM	List	Display
ATLAS			IC-22S	\$299	\$249
Model 210X, less blander	\$679	\$579	IC-202	\$259	\$220
BRIMSTONE			IC-502	\$249	\$210
144, no warranty	\$650	\$349	IC-215	\$229	\$189
DENTRON			KLM		
160-10L/572B amplifier	\$574	\$499	Multi 2700	\$756	\$666
DRAKE			SWAN		
SSR-1 gen. cov. rcvr.	\$350	\$259	700CX	\$649	\$549
MN-4 Antenna tuner	\$120	\$105	TEN-TEC		
TR-4CW w/RIT xcvr	\$799	\$619	Triton IV	\$699	\$599

Terms of Sale: Cash, no trade. You may use your **MASTERCARD** or **VISA**. Many items are one-of-a-kind. We suggest your calling first to assure getting the unit you want.

See us at the **SAROC Convention**, Las Vegas, Nevada, **January 5-8, 1978.**

Thanks for your great response to our 1977 Buyers Guide. The **78 Buyers Guide** will be available soon. Watch our ads to get your **NEW BUYERS GUIDE**.



Midland  
13-510

- PLL Synthesized
- Switchable: 25W or 1W
- LED Frequency Indication
- 10kHz Steps Plus 5kHz Shift
- Compact: 2-5/8" x 6-3/4" x 9-5/8"

**\$359** Cash;  
No-Trade Special  
List Price \$399.00



Model 43  
\$120 + shipping



If you have been having difficulty locating the Wattmeter or element just right for you... You may have been looking in the wrong places. Our large inventory of most common elements lets you get what you want when you need it. Give us a call first for your **BIRD** needs.



## SPECTRONICS, INC.

1009 GARFIELD  
OAK PARK, IL. 60304  
312-848-6777  
TELEX 72:8310

## HOURS

### STORE HOURS:

Mon-Thurs 9:30-6:00, Fri. 9:30-8:00  
Sat. 9:30-3:00, Closed Sun. & Holidays.



# active bandpass filters —

## some staggering thoughts

Here's a rundown  
on stagger-tuned filters  
using op amps  
as active devices —  
great idea for many  
amateur applications

**Applications for active bandpass filters** in the audio-frequency range can be found in every part of amateur radio. Audio selectivity for CW, speech processing for ssb, tone-detector filters for RTTY, and control-tone separation for fm repeaters are only a few of the uses. In this article you'll learn an easy way to design and build stagger-tuned operational-amplifier active filters to fit your requirements. All you need is one of the readily available hand-held scientific calculators (or some other method for calculating square roots and logarithms).

Perhaps you've seen other types of active filters or filter designs using LC components. Why use stagger-tuned filters, and why use active filters? It's easy to build very narrowband audio filters by cascading, one after another, several identical simple filter sections. This may be adequate for some tasks but can often leave a lot to be desired in terms of transient response (*ringing*), peaked or *narrow-nosed* amplitude response, and poor skirt selectivity (*shape factor*). Conventional circuits using inductors can

give excellent performance if well designed, which is often done with complex computer-aided design programs. But inductors are often large and hard to tune. Many amateurs have been discouraged by the need to add or remove turns from the 88-mH toroidal inductors common in RTTY use.

### features

The filters described here offer many advantages. They give amplitude response with flat or slightly rippled characteristics in-band. Out of band, they have excellent skirt selectivity and a shape factor that improves directly as more filter sections are added. As a bonus, the transient response is usually much better than narrow-nosed filters. Best of all, each stage can be tuned separately with no measurable interaction or detuning of the other stages — this is a real plus for experimenters.

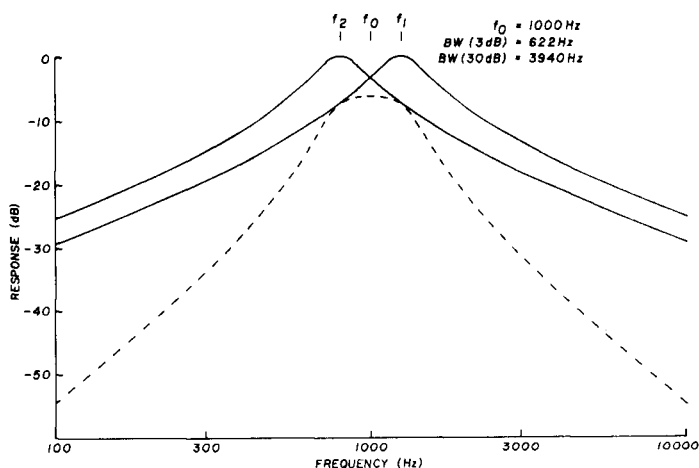


fig. 1. Typical stagger-tuned response. By choosing the correct peak frequency,  $f_n$ , and  $Q$  for each stage we get the response shown.


Now the bad news (which isn't really too hard to take). Stagger tuning requires that each stage provide enough gain so that the sum of the stage gains is *greater than that of the overall filter*. This is because of *staggering loss*, of which you'll see more shortly. With op amp ICs and their large open-loop (no feedback applied) gain, this parameter turns out to be of little concern. Another problem is that if one

By Terry A. Conboy, WB6GRZ, 1231 Crestview Drive, San Carlos, California 94070

of the stages is out of tune, the filter response can be poorer than in designs that purposely introduce interaction between filter sections, as in most LC designs or in *leapfrog* active filters, which are much more difficult to design.

## description

The stagger-tuned filter is made of two or more stages, each having a different peak frequency,  $f_n$ , with an associated  $Q$  (which *may* be the same as the  $Q$  of *one* of the other stages), and a certain amount of gain,  $G$ . The sum, in dB, of the gains versus frequency can be arranged to give a flat response over the band of interest. **Fig. 1** shows how this happens. In the area between the two peaks one response rises as the other falls. By choosing the right  $f_n$  and  $Q$  for each stage, we get the response shown. Note that, at the center frequency of the overall response  $f_0$  (where the stages have equal loss), the net loss is *twice* as much (in dB). This is the stagger loss,  $S$ , which must be made up by the sum of the individual stage gains to give unity gain overall. Compare **figs. 1** and **2**. **Fig. 2** shows a two-stage nonstaggered or "synchronously tuned" filter response with the same 3-dB bandwidth. Note the poorer skirts and the much rounder passband.

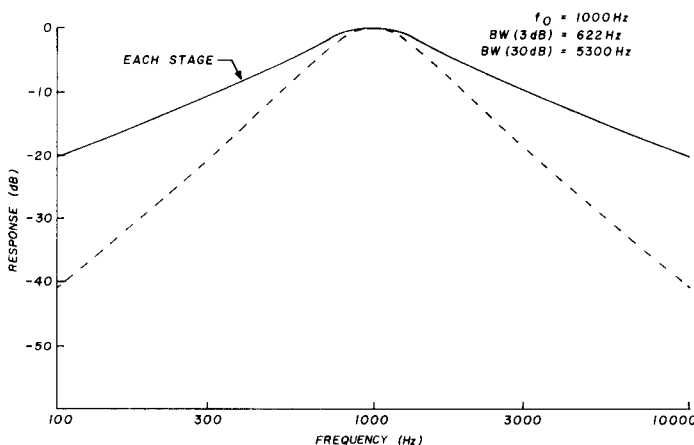


**fig. 2.** Response of a two-stage synchronously tuned filter (compare with the response in fig. 1).

In the stagger-tuned filter, the shape of each stage response is of the classic single-resonator shape (the same as that generated by a single parallel LC circuit with a shunt resistance to define the  $Q$ ). The amplitude response is defined mathematically (for those of you itching to use your HP-25) as follows:

$$\frac{V_{out}}{V_{in}} = -10 \log_{10} \left[ 1 + Q^2 \left( \frac{f}{f_n} - \frac{f_n}{f} \right)^2 \right] \quad (1)$$

Eq. 1 is of interest only and is not necessary for

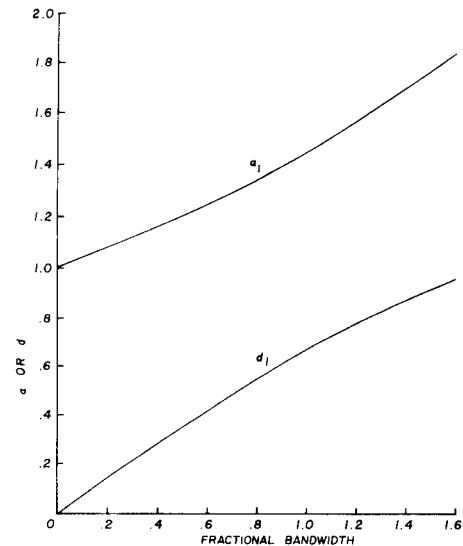

**fig. 3.** A two-stage Butterworth filter showing  $\alpha$  or  $d$  as functions of fractional bandwidth,  $\delta$ .

designing a filter. It can be used for analysis, however. You can find the response of each stage then add all responses together to find the overall filter response. One thing that's important to note is that the curve has *geometric symmetry*. All this means is that if the upper (x) dB-down point is two times the center frequency, then the lower (x) dB point will be at one-half  $f_n$ . This relationship is expressed by

$$f_n = \sqrt{f_L f_H} \quad (2)$$

where  $f_L$  is a frequency below  $f_n$  with the same attenuation as  $f_H$ , which is higher than  $f_n$ . Note that  $f_n$  is *not* the arithmetic average of  $f_L$  and  $f_H$ . The resultant overall filter response will exhibit the same type of symmetry as the stages of which it is composed. So eq. 2 holds for the complete filter, where  $n$  is zero.

**Design procedure.** In designing the filter, the first thing is to decide what type of filter is wanted. The Butterworth, or maximally flat filter, provides the flattest passband and a good skirt shape. The Chebychev or equal-ripple filter gives ripples in the passband (1 dB in the designs to follow), but in turn, it has very rapid cutoff of the band. Many other filter types are in use, but these two will serve you well.


Next you must determine how many stages you want. This requirement is determined by the required shape factor, with the other consideration being how much circuitry you want to build. High  $Q$ s and more precise tuning of the stages are also requirements of the higher-performance designs.

**Shape factor.** To refresh your memory, shape

**table 1. Shape factors for Butterworth and Chebychev filter designs.**

number of stages	butterworth		1-dB chebychev	
	3/30 dB	6/60 dB	3/30 dB	6/60 dB
1	31.60	577.00	31.60	577.0
2	5.62	24.00	4.70	20.8
3	3.16	8.33	2.30	6.6
4	2.37	4.90	1.75	3.5
5	1.99	3.57	1.60	2.5
6	1.78	2.89	1.30	2.0

factor (also called *selectivity ratio*) is the ratio of bandwidth at a higher attenuation to the bandwidth at a lower attenuation. Most common is the 6 - 60-dB

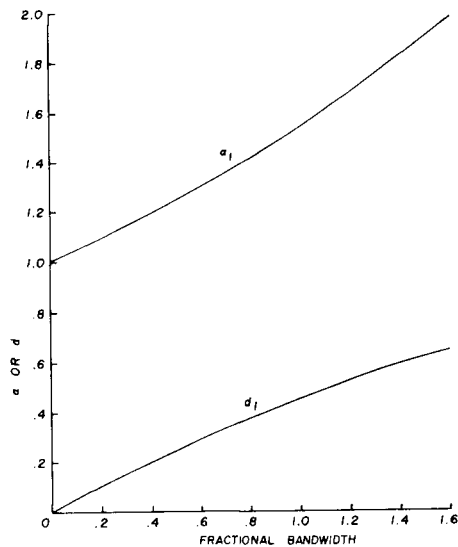

**fig. 4. Three-stage Butterworth filter showing  $\alpha$  or  $d$  versus fractional bandwidth,  $\delta$ .**

shape factor. **Table 1** shows this shape factor versus the number of stages for Butterworth and 1-dB-ripple Chebychev filters. Also given is the 3 - 30-dB shape factor.

After deciding the type and complexity of the filter, specify the lower 3-dB point,  $f_L(3 \text{ dB})$ , and the

**table 2. Approximations for fractional bandwidth,  $\delta$ , equal to or less than 0.3 for Butterworth and Chebychev active filters.**

Butterworth	
two-stage	
$\alpha_1 = 1 + 0.365\delta$	$d_1 = 0.707\delta$
three-stage	
$\alpha_1 = 1 + 0.450\delta$	$d_1 = 0.500\delta$
four-stage	
$\alpha_1 = 1 + 0.485\delta$	$d_1 = 0.380\delta$
$\alpha_3 = 1 + 0.195\delta$	$d_3 = 0.920\delta$
Chebychev (1-dB ripple)	
two-stage	
$\alpha_1 = 1 + 0.365\delta$	$d_1 = 0.433\delta$
three-stage	
$\alpha_1 = 1 + 0.450\delta$	$d_1 = 0.220\delta$

upper 3-dB point,  $f_H(3 \text{ dB})$ . Then use **eq. 2** to find  $f_0$ . Next find  $\delta$ , the fractional bandwidth.

$$\delta = \frac{(f_H - f_L)}{f_0} \quad (3)$$

This parameter,  $\delta$ , is the main design factor. It's used to find tuning data for each stage. Refer to **figs. 3, 4, or 5** for Butterworth filters of two, three, or four stages respectively. For a 1-dB Chebychev filter of

**table 3. Design equations for two-, three-, and four-stage filters. Parameter  $\alpha$  is the ratio of resonant to filter center frequency.**

for two-stage filters

$$\begin{aligned} f_1 &= (f_0)(\alpha_1) & f_2 &= f_0/\alpha_1 \\ Q_1 &= 1/d_1 & Q_2 &= 1/d_1 \\ G_1 &= G_2 = (S + G_0)/2 \end{aligned}$$

for three-stage filters


$$\begin{aligned} f_1 &= (f_0)(\alpha_1) & f_2 &= f_0 & f_3 &= f_0/\alpha_1 \\ Q_1 &= 1/d_1 & Q_2 &= 1/\delta & Q_3 &= 1/d_1 \\ G_1 &= G_2 = G_3 = (S + G_0)/3 \end{aligned}$$

for four-stage filters

$$\begin{aligned} f_1 &= (f_0)(\alpha_1) & f_2 &= (f_0)(\alpha_3) & f_3 &= f_0/\alpha_3 & f_4 &= f_0/\alpha_1 \\ Q_1 &= 1/d_1 & Q_2 &= 1/d_3 & Q_3 &= 1/d_3 & Q_4 &= 1/d_1 \\ G_1 &= G_2 = G_3 = G_4 = (S + G_0)/4 \end{aligned}$$

two or three stages, see **fig. 6 or 7** respectively. From the appropriate figure, obtain  $\alpha_1$  and  $d_1$  (and  $\alpha_3$  and  $d_3$  for a four stage Butterworth). If your filter has a  $\delta = 0.3$ , **table 2** offers approximations for  $\alpha$  and  $d$ , which usually give better accuracy than reading from the graph. Decide what overall gain,  $G_0$ , in dB you want from the filter, then use **table 3** to find the tuning frequency, the  $Q$ , and the gain for each stage.

It's a good idea to organize the stages as given, with the highest-frequency stage first. (This mini-

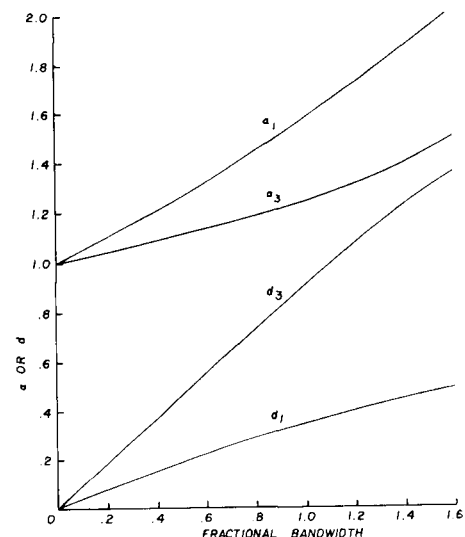

**fig. 5. Four-stage Butterworth, with  $\alpha$  or  $d$  as functions of fractional bandwidth,  $\delta$ .**

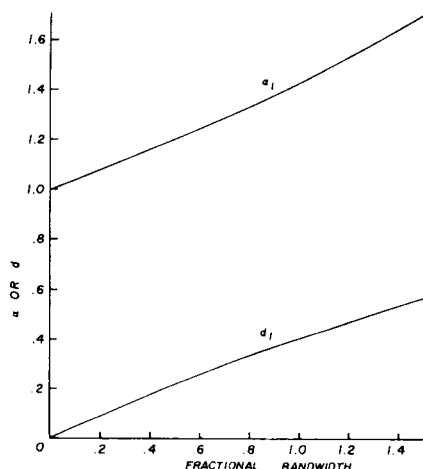


fig. 6. A Chebyshev two-stage filter (1-dB ripple) showing  $\alpha$  or  $d$  as functions of fractional bandwidth,  $\delta$ .

mizes harmonic distortion for the overall filter.) The higher-frequency stages have the lowest open-loop gain, which means that feedback will be less effective in reducing the distortion in these circuits than in the lower-frequency stages. Putting the low-frequency stages last gives maximum attenuation to any harmonics generated by the higher frequency stages.

**Multiple-feedback circuit.** Now that you know what the stages must do, the only thing remaining is to design circuits with the required  $f_n$ ,  $Q$ , and  $G$ . For stages with low  $Q$  (less than 10), the multiple feedback (MFB) circuit in fig. 9 performs well. Almost any op amp will work here, but depending on its bandwidth, limitations exist on maximum  $Q$  and maximum  $f_n$ .

The upper limit on  $Q$  for the MFB circuit is given by the smaller of

$$\begin{aligned} Q_{max} &\cong \sqrt{f_T/(5f_n)}, \\ Q_{max} &\cong 10 \end{aligned} \quad (4)$$

where  $f_T$  is the frequency at which the op-amp gain equals zero dB (unity gain). The frequency,  $f_n$ , should be limited to about 1 per cent of  $f_T$  (10 kHz for a 1-MHz  $f_T$  amplifier, such as the type 741).

These restrictions minimize the effects of amplifier gain on  $f_n$  and  $Q$ , which ensures accurate calculation of these parameters and freedom from drift because of amplifier gain changes with temperature.

The component values in the MFB circuit can be found easily. Choose convenient value of capacitor,  $C$ . The resistors are:

$$R3 = \frac{Q}{\pi f_n C} \quad (5)$$

$$R1 = \frac{R3}{2 \cdot 10^{G/20}} \quad (6)$$

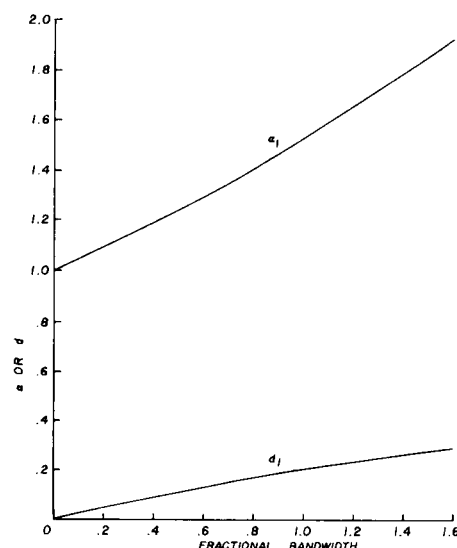


fig. 7. Chebyshev filter with three stages (1-dB ripple) showing  $\alpha$  or  $d$  versus fractional bandwidth,  $\delta$ .

$$R2 = \frac{1}{[(2\pi f_n C)^2 R3 - (1/R)]} \quad (7)$$

Note that  $[10^{(G/20)}$  equals  $\text{antilog}_{10}(G/20)$ ], where  $G$  is the gain, as described previously.

**State-variable design.** The limitations of the MFB circuit require that a higher-performance circuit be used in some cases. The state-variable circuit in fig. 10 can do some amazing things. It can provide very high  $Q$ s (over 100) and is hard to beat for stability and lack of sensitivity to passive component drift. However, it does take two more op amps and four more resistors than the MFB design.

There are several degrees of freedom in this design. Choose  $C$ ,  $R2$ , and  $R4$  for convenience.\* The remaining resistors are found from

$$R1 = R2 Q / (10^{G/20}) \quad (8)$$

$$R3 = \frac{1 - \frac{f_n}{f_T}}{2\pi f_n C} \quad (9)$$

$$R5 = \frac{R4}{\left[ \frac{2Q + (10^{G/20})}{1 + \frac{4Q + (10^{G/20})}{\frac{f_T}{f_n}}} \right] - 1} \quad (10)$$

\*A "convenient" capacitor is one as small as possible that doesn't require overly large resistors. Choosing resistors too much above 100k (for 741s or similar op amps) can lead to excessive dc offsets because of input-bias currents. Fet input op amps have extremely small bias currents and will tolerate resistors in the tens of megohms.

For the MFB circuit, capacitors with about 10 kilohms of reactance are in the ballpark. For instance, at 1500 Hz, a 0.01  $\mu\text{F}$  capacitor is suitable. In the state-variable circuit, capacitors of about 100k ohms of reactance can be used, such as 0.001  $\mu\text{F}$  at 1500 Hz. A reasonable value for  $R_2$  or  $R_4$  is between 10k - 100k.

Both circuits can be impedance-scaled if the calculations of component values reveal one or more values that are out of the desirable range. This means that all resistor values may be changed so long as all change by the *same ratio*, and the capacitors change by the *reciprocal* of that ratio. For example, if you find a 300k resistor where you'd like to have 100k, you can change it by making all the resistors one-third of their original value and by making the capacitors three times as large. In the state-variable circuit,  $R_4$  and  $R_5$  may be changed independently of the other resistors so long as the ratio  $R_4:R_5$  is constant.

## design example

The design procedure is used to create an input prefilter for an RTTY demodulator (TU). We'll

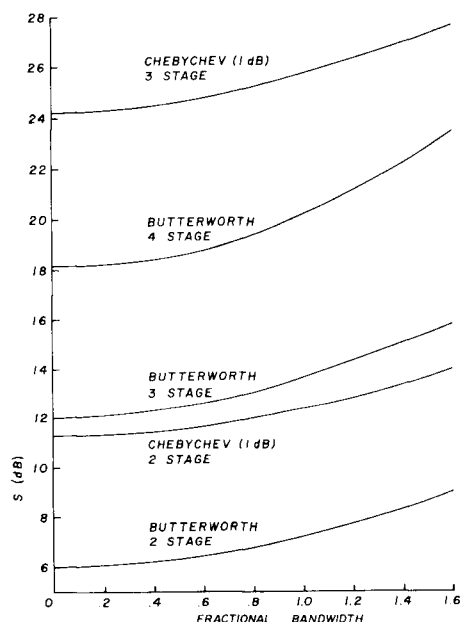


fig. 8. Loss due to staggering,  $S$ , as functions of fractional bandwidth,  $\delta$ , for various active filters.

choose an overall gain of 30 dB to provide adequate drive to the limiter from normal speaker signal levels. To give flat response in-band and reasonable delay distortion (associated with the transient response), we'll choose a Butterworth design. For good selectivity a four-stage configuration will be used. For 170-Hz shift and 45.45 Baud (standard 60 wpm), the

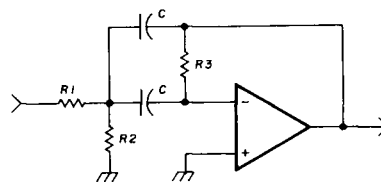


fig. 9. Schematic showing the MFB, or multiple-feedback circuit.

CCIR formula shows the bandwidth to be 246 Hz. To allow for tuning error and drift, a 300-Hz bandwidth at the 3-dB points will be used. The mark frequency is 2125 Hz; the space frequency is 2295 Hz. Thus the passband should be from  $f_L = 2060$  Hz to  $f_H = 2360$  Hz. Eq. 2 gives

$$f_o = \sqrt{(2060)(2360)} = 2205 \text{ Hz}$$

From eq. 3 we obtain the fractional bandwidth

$$\delta = \frac{(2360 - 2060)}{2205} = 0.1361$$

Since  $\delta$  is less than 0.3, use the approximations in table 2.

$$\begin{aligned} \alpha_1 &= 1 + (0.485)(0.1361) = 1.066 \\ d_1 &= (0.38)(0.1361) = 0.0517 \\ \alpha_3 &= 1 + (0.195)(0.1361) = 1.0265 \\ d_3 &= (0.92)(0.1361) = 0.1252 \end{aligned}$$

From fig. 8 the loss due to staggering,  $S$ , = 18.2 dB and from table 3 we have

$$\begin{aligned} f_1 &= (2205)(1.066) = 2351 \text{ Hz} & Q_1 &= 1/0.0517 = 19.3 \\ f_2 &= (2205)(1.0265) = 2263 \text{ Hz} & Q_2 &= 1/0.1252 = 8.0 \\ f_3 &= 2200/1.0265 = 2148 \text{ Hz} & Q_3 &= 1/0.1252 = 8.0 \\ f_4 &= 2205/1.066 = 2068 \text{ Hz} & Q_4 &= 1/0.0517 = 19.3 \end{aligned}$$

and  $G = (18.2 + 30)/4 = 12.05$  dB (per stage).

It's apparent that the state-variable circuit must be used for the first and fourth stages ( $Q > \text{than } 10$ ). At 2351 Hz a 741-type op amp is capable of

$$Q_{max} \approx \sqrt{\frac{10^6}{5(2351)}} = 9.2$$

Since the second and third stages have  $Q$ s less than this, the MFB circuit is usable.

Let the capacitors in the state-variable stages be 0.001  $\mu\text{F}$  and the capacitors in the MFB stages be 0.01  $\mu\text{F}$ . Let  $R_2$  and  $R_4$  be 100k in stages 1 and 4. From eqs. 8, 9, and 10 we obtain the values for the first state-variable stage:

$$R_1 = (100k)(19.3/10^{12.05/20}) = 482k$$

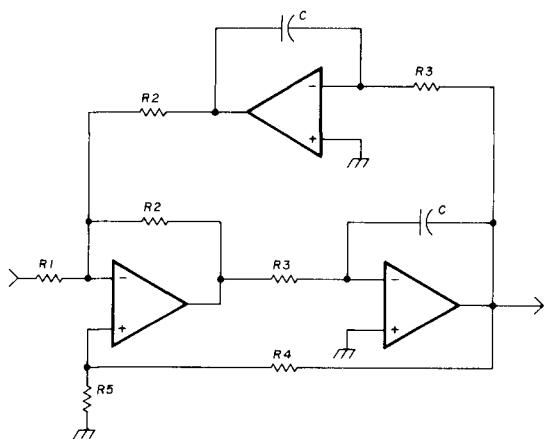


fig. 10. Schematic of the state-variable stage.

$$R3 = \frac{1 - \left[ \frac{2351}{10^6} \right]}{(2\pi)(2351)(10^{-9})} = 67.54k$$

$$R5 = \left[ \frac{\frac{10^5}{(2)(19.3 + 10^{12.05/20})}}{1 + \frac{(4)(19.3 + 10^{12.05/20})}{\frac{10^6}{2351}}} \right] - 1 = 2686 \text{ ohms}$$

Similarly, for stage four, we find

$$\begin{aligned} R1 &= 482k \text{ ohms} \\ R3 &= 76.8k \text{ ohms} \\ R5 &= 2626 \text{ ohms} \end{aligned}$$

Now for stage two, using eqs. 5, 6, and 7,

$$R3 = 8 / \pi(2263)(0.01 \times 10^{-6}) = 112.5k \text{ ohms}$$

$$R1 = 112.5k / (2)(10^{12.05/20}) = 14.05k \text{ ohms}$$

$$R2 = \frac{1}{[2\pi(2263)(0.01 \times 10^{-6})]^2 \left[ 112.5k - \left( \frac{1}{14.05k} \right) \right]} = 439.6 \text{ ohms}$$

And in the same fashion, for stage three, we have

$$\begin{aligned} R3 &= 118.6k \text{ ohms} \\ R1 &= 14.8k \text{ ohms} \\ R2 &= 462.9k \text{ ohms} \end{aligned}$$

## construction

The filter was constructed using two MC3303 quad op amps. Combinations of one per cent resistors were used to give the calculated values within 0.5 per cent or less, nominally. Polystyrene capacitors, 1 per cent tolerance, were used in all sections.

The measured response of the filter before tuning is shown in figs. 11 and 12. The calculated response which is given for comparison, was generated using eq. 1 for each stage and then adding the four responses.

Normally, filter sections will need trimming for frequency and/or  $Q$ . In many low  $Q$  filters ( $Q < 0.3$ ), 5-per cent tolerance resistors will give quite satisfactory results without trimming. The only penalty may be slight center frequency error and perhaps a small amount of skew in the passband frequency response.

For the narrowband filters, and especially those with three or four stages, an audio generator, ac voltmeter, and frequency counter will help in trimming each stage independently to the required parameters. In the state-variable circuit, adjust both  $R3$  values to set the center frequency, then use  $R5$  to fix the  $Q$ . Remember  $Q$  is the 3-dB bandwidth divided by  $f_n$ . For an MFB stage, adjust  $R3$  to give the desired 3-dB bandwidth. Then adjust  $R2$  to set  $f_n$ . Varying  $R2$  has virtually no effect on the bandwidth, which means the  $Q$  changes at the same rate as  $f_n$ . After tuning the RTTY demodulator input filter, the overall response was essentially indistinguishable from the calculated response.

## components

Generally, components should be the best you can get. Metal-film resistors and polystyrene or mylar capacitors are hard to beat, but may be *overkill*. Stay away from capacitors designed for bypass or coupling use; their tolerance is poor, as is their stability. Carbon resistors are usually adequate in all but the narrowest filters. For op amps, 741s are suitable (as are the 1458 dual versions and the quads like the

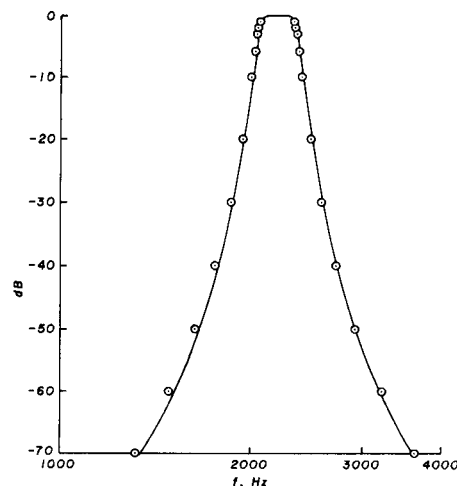


fig. 11. Response as a function of frequency for an RTTY input filter. Solid line: calculated; dots: measured data before tuning.

3303), when used within the limitations given above. The LM318 op amp gives much greater freedom from  $Q$  drift (in the state-variable circuit) and  $f_n$  drift (in the MFB circuit). Some of the new wideband fet-input op amps, such as the LF356, should be excellent performers. When external frequency compensation is required, use the values specified for unity gain amplifiers.

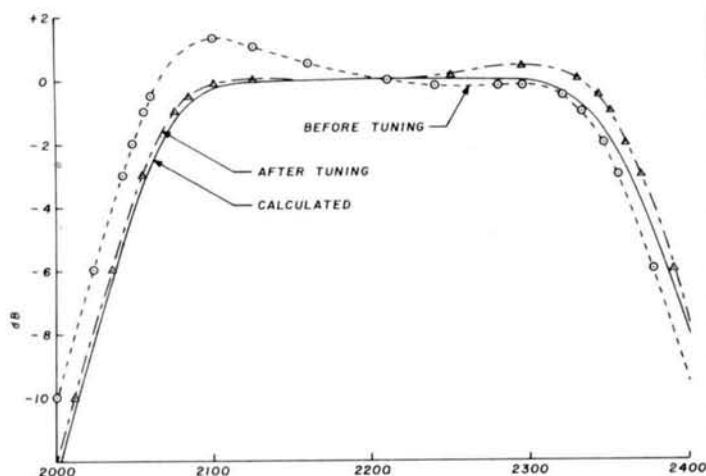


fig. 12. Passband response of an RTTY input filter.

When interfacing active filters, take care that the source impedance driving the filter is very low, i.e., less than 1 per cent of  $R_1$  in either circuit. Another op amp or a voltage follower provides an excellent driver. If the requirement for a low impedance can't be met, deduct the source resistance from the value of  $R_1$  in the first stage.

You've seen an easy-to-use method for designing stagger-tuned active filters to your own needs, and have learned to avoid some of the possible pitfalls. Now you can replace that filter you borrowed from someone else's circuit that never did work exactly the way you wanted.

### bibliography

1. G.E. Valley and H.T. Wallman, *Vacuum-Tube Amplifiers* (Stagger-tuned Butterworth filters), *MIT Radiation Laboratory Series*, 1948, pages 180-191.
2. J.M. Pettit and M.M. McWhorter, *Electronic Amplifier Circuits* (Butterworth and Chebyshev filters), McGraw-Hill, New York, 1961, pages 221-229.
3. *Reference Data for Radio Engineers*, ITT, 1975, (necessary bandwidth, page 1-23; filter shapes, page 8-5; MFB stage, page 10-12).
4. Lee Schaeffer, "Op Amp Active Filters — Simple to Design Once You Know the Game," *EDN*, April 20, 1976, pages 79-84 (state-variable filters).
5. Leonard H. Anderson, "Top-Coupled Bandpass Filter — a Chebyshev Design," *ham radio*, June, 1977, pages 37-40.

ham radio

# LUNAR



*Wishes Seasons Greetings  
to men of good will everywhere*

## NEW 2-Meter AMPLIFIER

PREAMPLIFIER  
the 2M10-80P

2-in-1

Single  
Package

### Features:

- Ten watts input — eighty watts output
- Harmonic reduction exceeds -60 dB to meet FCC R&O 20777 Specifications
- Variable T-R Delay for CW/SSB
- Functionally-Designed Extrusion Includes Mounting Lip
- Preamplifier Selectable Independently of Power Amplifier
- Automatic T-R Switching of Amp & Preamp
- Preamp gain: Nominally 11 dB  
Noise Figure: Nominally 2.5 dB  
(Including Relay Losses)
- Remote Control Head Available Separately)

### Introductory Price: . . .

. . . Lunar Model 2M10-80P . . . \$189.95

Please add \$3.00 shipping and handling.

## NEW Model DX-555P Counter-Generator with prescaler

Call us for immediate shipment and/or delivery date. Use your BankAmericard or Master Charge.



**NEW Counter-Generator**  
Two vital pieces of test equipment in one.

### Counter:

5 digit display, 7 digit readout capability. 10 Hz to over 30 MHz (250 MHz with prescaler). Input level 20m Vrms to 5 Vrms (Prescaler 200m Vrms to 2 Vrms). Base oscillator beats directly against WWV.

### Generator:

440 kHz to 30 MHz in 3 ranges  
Output displayed on counter and available at jack on rear panel 600 Hz modulation for AM receivers

### General:


110 VAC fused supply  
Size (in.) 2.3H x 6.3W x 8.5D  
Weight (lbs.) 4.4

MODEL DX-555P (to 250 MHz - incl. prescaler) \$239.95  
Please add \$3.00 shipping/handling. Model without prescaler also available.
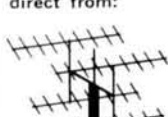
### The DX 'J' ANTENNA:

- Gold-alodined aluminum radiators
- Requires **no ground plane**
- VSWR typ. 1.3:1 (146-148 MHz)
- Handles 250 watts plus
- Weight: 8 oz.
- 144, 220, or 440 MHz Models, Your Choice
- Price \$29.95

California residents add 6%. Order today at your dealer or direct from:



# LUNAR

## electronics

SUITE 10  
2785 KURTZ ST.  
SAN DIEGO, CA 92110  
714-299-9740  
Louis N. Anciaux WB6NMT



On most 4, 5 and 6-element antennas, only 3 elements at any one time on any one band are working. The rest are goofing off.

So counting elements is no way to judge an antenna.

This 3-bander uses every one of its 4 elements all the time for maximum forward gain and maximum front-to-back ratio.

And that adds up to an antenna that works harder. With no idle elements to increase windage and bulk.


A good reason why the TB-4HA is known both for performance and toughness.

In fact, all of Swan's beam antennas share a reputation for working harder for every dollar you invest in them.

Swan beams are precision engineered for a full 2000-watt PEP rating and a VSWR of 1.5:1 or better at resonance. And besides optimum gain and front-to-back ratio, they're easy to install and tune.

Order a Swan beam today. Use your Swan credit card. Applications at your dealer or write to us. Who needs antennas that goof off?

**TB-4HA**

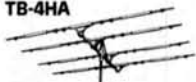


Heavy-duty, four-working-element antenna for 10, 15 and 20 meters. \$259.95

**TB-3HA**




Heavy-duty, three-working-element antenna for 10, 15 and 20 meters. \$199.95

**TB-2A**

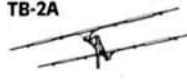

Light-weight, two-working-element antenna for 10, 15 and 20 meters. \$129.95

**MB-40H**

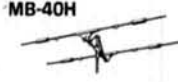

Heavy-duty, two-working-element antenna for 40 meters. \$199.95

**SWAN BEAM ANTENNA SPECIFICATIONS.** For 52-ohm coaxial feedlines.


ANTENNA MODEL NUMBER	BOOM LENGTH & DIAMETER	LOWEST ELEMENT	TUNING RADIUS	MAXIMUM WIND SURVIVAL	WIND LOAD @ 80 MPH	WIND SURFACE AREA	NET WEIGHT
TB-4HA	24' x 1.5"	28'-10"	18'-6"	100 mph	148 lbs.	6 sq.ft.	54 lbs.
TB-3HA	16' x 1.5"	28'-2"	16'	100 mph	110 lbs.	4 sq.ft.	44 lbs.
TB-2A	6.5' x 1.5"	27'-8"	14'-3"	80 mph	60 lbs.	1.8 sq.ft.	18 lbs.
MB-40H	15.75' x 1.5"	30'-4"	17'-6"	100 mph	80 lbs.	2.5 sq.ft.	40 lbs.

(Prices FOB Oceanside, CA)

Dealers throughout the world  
or order direct from

**SWAN<sup>®</sup>**  
**ELECTRONICS**  
A subsidiary of Cubic Corporation  
305 Airport Road, Oceanside, CA 92054  
(714) 757-7525
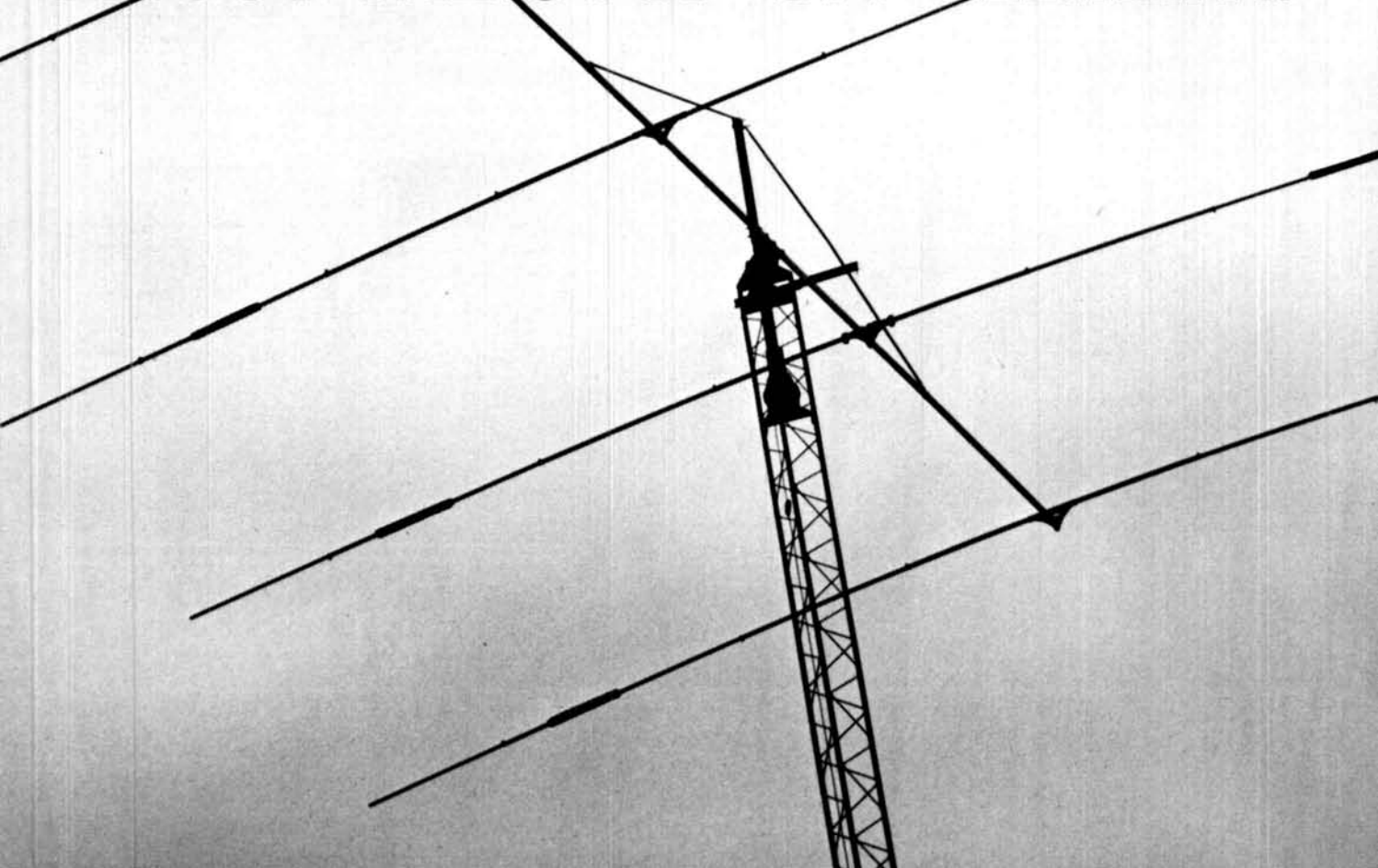
# SWAN TB-4HA. FINALLY, A BEAM ANTENNA THAT DOES SOMETHING ABOUT THE GOOF-OFF ELEMENT.



Our new 4010V expandable 4-band antenna is designed for the operator who wants to straddle continents at a down-to-earth price.

One reason the 4010V saves you money is because it's simpler. For example, it doesn't need a counterpoise. And it's easy to install.

The new 2000-watt PEP trap vertical comes in short lengths complete with mounting plate. So with easy set-up and no ground radials to contend with, you can't beat it for getting on the air fast when you're in the great outdoors.

And it's also ideal for mobile homes and apartments.

Then when you feel like exploring 75 meters, expand your 4010V to five bands with the Swan 75 AK kit and you're into a whole new world.

75 AK 75-meter kit

#### 1040V Vertical Antenna.

But if you're interested in a more permanent installation with one of the most effective verticals made, check out our 1040V.

The rugged 4-band 1040V trap vertical for 40 through 10 meters is well-known for completeness.

When you open your 1040V box what you see is what you need.

Like copper wire to make two counterpoise radial wires for each band, egg insulators and a base mounting plate.

And when you're ready for 75 meters you can expand to five bands with the Swan 75 MK kit. Which is noted for the same attention to completeness as the 1040V.

Buy a Swan 4010V or 1040V expand-a-band-later vertical today.

75 MK 75-meter kit

Use your Swan credit card and pay later, too. Applications at your dealer or write to us.

4010V 4-band trap vertical antenna.	\$ 74.95
75 AK 75-meter kit.	\$ 39.95
1040V 4-band trap vertical antenna.	\$122.95
75 MK 75-meter kit.	\$ 39.95

(Prices FOB Oceanside, CA)  
Dealers throughout the world  
or order direct from

 **SWAN**  
ELECTRONICS®  
A subsidiary of Cubic Corporation  
305 Airport Road, Oceanside, CA 92054  
(714) 757-7525

## NEW 4010V VERTICAL ANTENNA.

IT LOOKS AS GOOD TO  
YOUR POCKETBOOK AS  
IT DOES TO YOUR  
TRANSCEIVER.

1040V Vertical

4010V Vertical

# crystal-controlled phase-locked receiving converter

Circuit details and  
construction information  
for a converter  
that receives signals  
between 0-28 MHz  
when used with  
a receiver that tunes  
from 28 to 29 MHz

**Over the years** many amateurs have traded their old, general-coverage receivers for shiny new "ham-band-only" models. We've gained in stability, sensitivity, selectivity, dial accuracy, and many other attributes; but we've lost on frequency coverage. Except for a few narrow windows to the outside world, we can listen only to each other. Those with interests outside the amateur bands have had to use a second receiver (frequently an old general-coverage job) and put up with drift, bulk, and lack of accurate calibration. The *XPL Converter*, described here, is designed to work with a modern receiver to give the best of both worlds — extremely broad frequency coverage together with crystal stability and calibration accuracy. The converter receives all frequencies between 0 and 28 MHz when used with a receiver tuning 28 to 29 MHz. Construction is simple, straightforward, and inexpensive thanks to integrated circuits.

## description

The *XPL Converter* consists of a wide-range tuned input circuit, 60 kHz to 28 MHz; a local oscillator with injection frequency switch-selectable in 1-MHz steps from 29 to 56 MHz; and a mixer circuit with output 28 to 29 MHz feeding the receiver as a tunable

i-f amplifier. A block diagram is shown in **fig. 1**. Local oscillator output is taken from a vfo (vco), which is phase locked to a 100-kHz reference oscillator through a counter chain preset by thumbwheel switches for band selection. The various sections are described in more detail later.

An example may help clarify the frequency conversion technique employed in the *XPL*. If the vco is set at, say, 38 MHz, the tunable i-f range of 28 to 29 MHz will allow reception of signals from  $38-29 = 9$  MHz to  $38-28 = 10$  MHz. A 9330-kHz signal in this range would be received at  $38-9.33 = 28.67$  MHz. The receiver tunes *backwards*, in that the low-frequency end of each range will be received at 29 MHz and the high end at 28 MHz. This turns out to be only a minor operating annoyance, however. Low-side injection could be used for forward tuning but only at the sacrifice of tuning range at the upper end.

The vco is phase locked to the reference crystal, so the local oscillator is of crystal quality as far as accuracy and stability are concerned. Any input frequency can be precisely located and will be stable within the accuracy and stability of the receiver on the 10-meter range. For most modern receivers, this means 1-2 kHz accuracy and a few hundred hertz drift on warmup. What a difference from the old general-coverage boat anchors!

## input circuitry

Input-circuit details are shown in **fig. 2**. A single-tuned circuit provides input selectivity for the *XPL*. Six switch positions cover 60-150 kHz, 150-450 kHz, 450-1400 kHz, 1.4-4.5 MHz, 4.5-10 MHz, and 10-30 MHz. The four high-frequency ranges use a commercially available coil set having high-impedance balanced antenna windings. On the two low-frequency ranges pi-section single-ended input circuits are used with rf chokes for the inductors. Tuning is by a miniature broadcast superhet variable capacitor having a total capacitance of about 560 pF with the two sections in parallel.

Two input traps are used: a balanced lowpass filter to eliminate TV/fm pickup and a series-resonant

**By Keith H. Sueker, W3VF**, 110 Garlow Drive,  
Pittsburgh, Pennsylvania 15235

There's no need to conform to the input circuit shown. In fact, the antenna tuning section from a scrapped general-coverage receiver could be used to

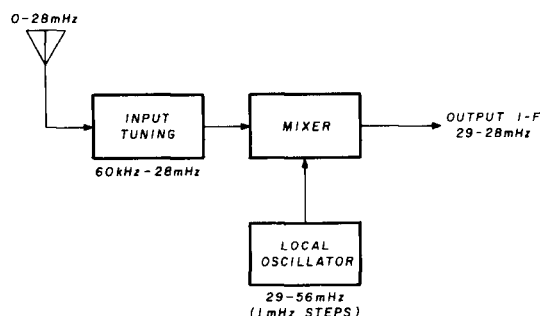


fig. 1. Block diagram of the *XPL* converter.

handle the high-frequency end of the range. The low end can be extended with larger inductors, but the tuning range for each band will be quite limited because of distributed capacitance in the coils. Two additional coils, however, will allow tuning to about 15 kHz.

The heart of *XPL* is the local oscillator. This circuit consists of a voltage-controlled oscillator (vco), programmable divider chain, crystal-reference oscillator, and phase comparator. A block diagram is shown in **fig. 3**.

Phase-locked-loop operation has been well described in the literature, but a quick review may be worthwhile. A phase-locked loop is a feedback control system that measures the phase difference between two frequency sources and generates an error voltage that changes the frequency of one frequency source until the two sources are in phase synchronism. For continuing phase errors, the phase detector will function on frequency difference and steer the system into phase lock.

Two basic systems can be used to generate a selectable series of integrally related frequencies. If the phase comparator is sensitive to reference-oscillator harmonics, the controlled oscillator can be directly locked to a selected harmonic by first tuning it manually to a nearby frequency, then allowing the phase detector to lock up. This is the system used in several commercial receivers. The only objection from a construction point of view is that it requires a manually variable oscillator with dial calibration sufficient to resolve adjacent harmonics. A lock indication is also useful in identifying the proper harmonic.


A more direct way of generating the integrally

related frequencies is to divide the controlled-oscillator frequency by programmable digital dividers before phase comparison to the reference frequency. If the oscillator frequency is divided by, say, 24 before the comparison is made, the effect is to lock the oscillator to the 24th harmonic of the reference frequency. In *XPL*, a fixed divide-by-ten and two programmable divide-by-*n* counters are used to enable lock from the 290th harmonic to the 560th harmonic of the 100-kHz reference frequency in steps of 1 MHz.

### oscillator and phase comparator

**Fig. 4** is the schematic for the reference oscillator and phase comparator. A 7400 quad NAND gate is used with a 100-kHz crystal to generate the reference frequency. There's no special merit to this scheme other than simplicity, and any convenient oscillator circuit could be used so long as it provides TTL output levels. In the circuit shown, the 0.0047  $\mu\text{F}$  capacitor at the input to the last gate was necessary to eliminate a double-pulsed output to the phase comparator.

A Motorola MC4044P phase-lock chip was chosen because it offers TTL logic, a nonharmonic-sensitive

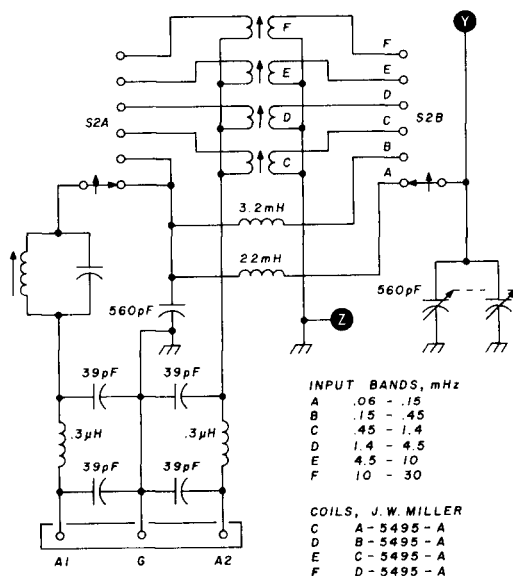

**fig. 2. Input-circuit schematic.**

comparator, and some internal auxiliary transistors. Also, its use in synthesizers has been described in recent articles.

Output from the MC4044P is buffered by an external 2N5457 fet follower and the internal emitter followers. The comparator has unity gain from the phase detector to the output. An active filter is backed up by two poles of rolloff for loop stability and high 100-kHz ripple attenuation. The reference

oscillator and phase comparator are supplied from an on-board regulator that provides both isolation and filtering.

### voltage-controlled oscillator

The voltage-controlled oscillator in the *XPL* (fig. 5) uses a Motorola MC1648L ECL chip designed for this service. Spectral purity requirements preclude a voltage-controlled multivibrator, so this chip was used with an external high-Q toroidal inductor and a Motorola MV1401 variable-capacitance diode or varicap. Since ECL has a very low logic swing, an

however, the swing is wrong. The sum of one diode drop and a base-emitter drop from the 5-volt-supply rail places the 2N4403 base voltage in the ECL logic voltage range. The 2N4403 collector voltage swings from 0.5V to about 3.5V to drive the counter. A 22-ohm base-emitter resistor aids junction recovery and cleans up the output waveform.

The entire vco section is quite susceptible to hum and modulation disturbances. For this reason, a separate voltage regulator is again used. The vco should be located well away from transformer fields or ac power wiring.

### programmable counters and translators

This circuit is shown in fig. 6. Before getting into counter details, a related matter must be considered. The count set into the preset counters must always be 29 (MHz) higher than the bottom end of the input tuning range, so that the switches can read input range directly. This requirement leads to the necessity of translating switch settings to the counters. Table 1 summarizes the required relationships. If decimal switches are used, the offset of minus 1 in the units digit can be provided by simply rewiring into the decimal-to-BCD diode matrix, as shown in fig. 6. Note, for example, that a switch indication of 4 is translated to BCD  $1 + 2 = 3$ , which is 4 minus the required one unit. The 390-ohm resistors establish a TTL logic zero for open-switch positions.

The tens digit is somewhat more messy. Switch indications must be translated up by 3 *except* when the units position is zero, which requires an up-translation of only 2. Thus, 00 goes to 29, 01 goes to 30, 10 goes to 39, 11 goes to 40, and so on. Since a zero-units digit is translated to a 9 in the output, the presence of this 9 can be used to change the tens digit to an output lower by one integer.

Two sections of a 7400 quad NAND are used to accomplish this magic. A decimal-to-BCD diode matrix with an offset of +3 is used in conjunction with a second matrix with offset of +2. The proper matrix

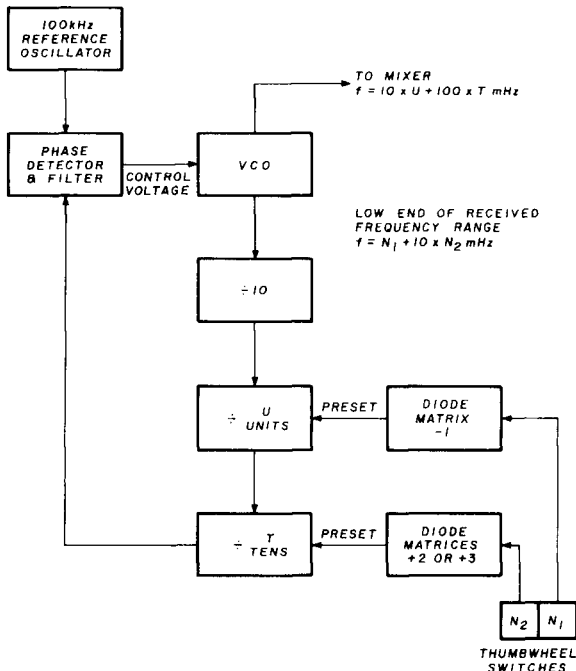


fig. 3. Local-oscillator block diagram.


output translator, 2N4403, is used to regenerate the TTL signal level. At this point you might ask whether the ECL chip is worth the effort. The answer is a qualified "Yes," since it functions from a two-terminal tank circuit and eliminates the need for fussing with feedback in a transistor oscillator.

The MV1401 varicap is rather expensive (in the \$9.00 range), but it has a guaranteed 3:1 tuning range and high *Q*. This application requires only a 2:1 range, but allowances for temperature variation component tolerances, and other considerations make it necessary to have some overrange. Less-expensive limited-range diodes could be used, but they would require changing fixed capacitors to cover the tuning range for the vco. The inductor is a T-25 mix 6 toroid with four turns of no. 22-28 AWG (0.6-0.3mm) enameled wire.

An output to the mixer is taken directly from the 50 ohm vco output at pin 3. For the TTL counters,

table 1. Relationship between switch settings and counters.

input range	switch readings		counter presets	
	ten	units	ten	units
0-1	0	0	2	9
1-2	0	1	3	0
2-3	0	2	3	1
9-10	0	9	3	8
10-11	1	0	3	9
11-12	1	1	4	0
12-13	1	2	4	1
19-20	1	9	4	8
20-21	2	0	4	9
21-22	2	1	5	0
27-28	2	7	5	6

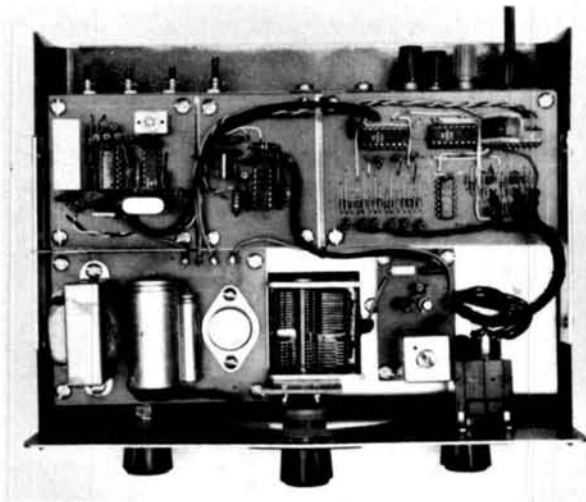

Looking down on the XPL converter. Components and wiring are shown on top of the chassis.

is chosen by clamping diodes from the two 7400 outputs. If a units 9 is present, the 9 bus is high and the 9 bus is low. Under this condition, the +3 matrix diodes are clamped low, and the +2 matrix diodes are released. For units digits other than 9, the situation is reversed.

Those familiar with counter techniques may immediately conclude that this is the long way around the barn, and so it is. A simpler solution to the translation would be to use a precounter set to 29 to delay activation of the programmable counters until the first 29 counts have passed. However, this requires two more counter chips, involves a clock gate, and is more difficult to troubleshoot if problems develop. The approach shown was devised with the less-experienced builder in mind, since troubleshooting of the diode matrices can be done with a vtvm.

Returning now to the counters, a high-speed 74196/8290 is used as a divide-by-10 prescaler to get the signal into TTL frequency range. This unit has a typical toggle frequency of 75 MHz and handles the 56-MHz maximum input with little effort. The programmable counters, 74192s, are preset by their respective diode matrices. Both are operated in the countdown mode and are cascaded and loaded through the borrow outputs.

Counter operation is as follows: The  $C_0$  output of the 74196/8290, pin 2, goes high once every ten input pulses from the vco. Each output pulse causes the units 74192 to count down by one count. When the count reaches zero, the borrow output goes low between pulses and causes the tens 74192 to count down by one count. It, too, generates a borrow pulse after reaching zero, and it is this pulse that's used to reset the system. The borrow pulse from the tens counter is used to load the preset number into each counter.

As an example of operation, suppose the thumb-wheel switches are set to 08 (8-9 MHz range). The units counter will be preset to a count of 7 (8-1) and the tens counter to 3 (0+3). Following a reset pulse, the units counter will count down one count every ten vco cycles and first generate a borrow pulse after 70 vco cycles.

After this first 70 cycles from the reset pulse, the counter will again generate a borrow pulse every 100 vco cycles. Each of these borrow pulses causes the tens counter to count down by one count from its preset of 3 and to generate its own borrow pulse after 70 + 100 + 100 + 100 vco cycles. The tens counter borrow and reset pulse thus occurs 370 vco cycles after the first reset and then immediately resets the counters again.

The tens counter borrow output frequency is equal

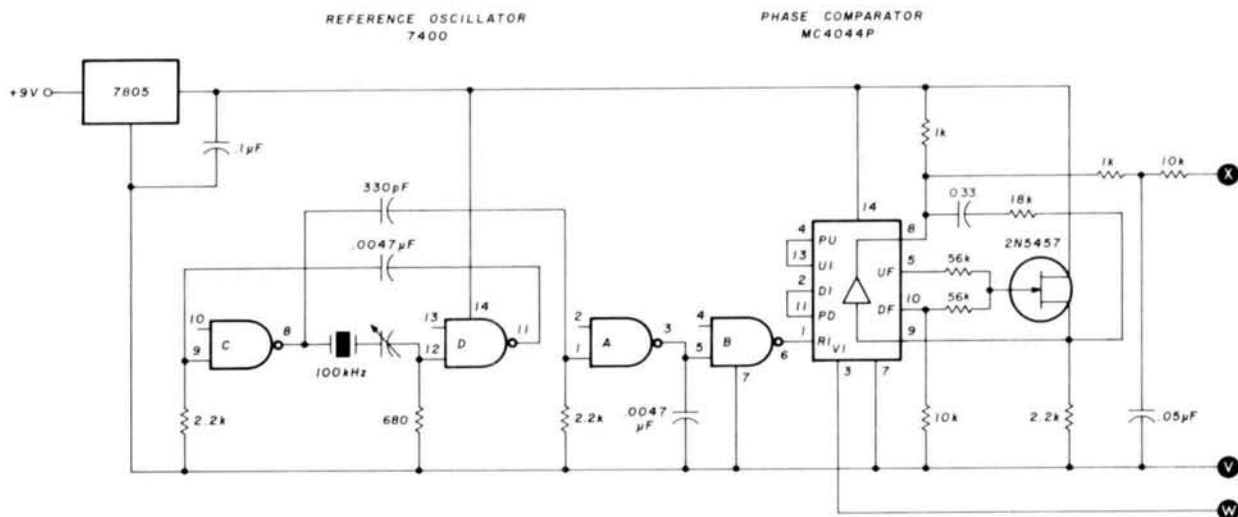


fig. 4. Reference oscillator and phase-comparator schematic.

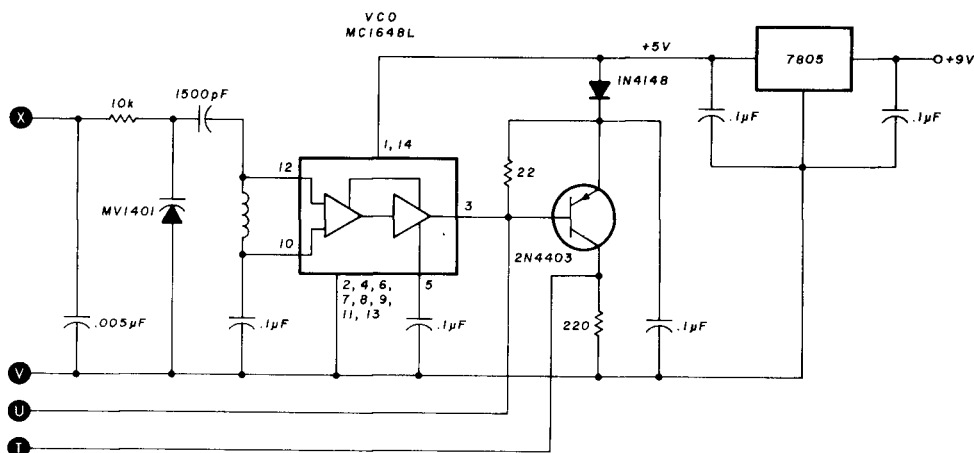


fig. 5. Voltage-controlled oscillator schematic.

to the vco frequency divided by  $(10 \times U + 100 \times T)$ , where U and T are the units and tens presets respectively (7 and 3 in our example).

The tens-counter borrow output is also used to feed the phase comparator so that the vco frequency is locked to  $10 \times 7 + 100 \times 3 = 370$  times the reference frequency of 100 kHz. The vco is thus locked at 37 MHz, which is the required local-oscillator injection frequency for receiving 8 MHz with a 29-MHz i-f.

Resistor values shown for the diode matrices are fairly critical. Germanium diodes would provide more margin, but the circuit works well as shown. If the same nominal values are used, no problems should be experienced. Power for the counters and transistors is provided by still another 5-volt regulator. This system draws several hundred milliamperes and may need a regulator heat sink.

## mixer

A dual-gate, diode-protected mosfet is used for the mixer (fig. 7). The 40673 has good intermodulation characteristics and is simple to use. Output from the drain is taken through an output transformer, broadly resonant at 28.5 MHz, which provides a low impedance output to the receiver. This stage is powered directly from the 9-volt power supply, since decoupling is not a problem. An output switch pole allows the receiver input to be connected to the converter or to a high-frequency antenna. A second pole is used to ground the high-frequency antenna to minimize pickup when the *XPL Converter* is in use.

## power supply

All operating power for the *XPL* is derived from a 12-volt transformer and bridge rectifier at about 10 volts (fig. 8). A 2N3055 is used as an active filter to reduce ripple. This transistor is much larger than required, but it's cheap, readily available, and needs no

heatsink. If the 9-volt rail is not reasonably clean, the received signal may be hum modulated. Ac input is switched by a third pole of the IN-OUT switch, and a pair of  $0.02 \mu\text{F}$  capacitors are used for line bypassing. Note that these capacitors should have 600-volt ratings.

## construction

Each circuit section was built on a separate printed-circuit board for easy testing and debugging. There's no real need to do this, however, and a single PC board might be easier to handle mechanically. The layout shown is also more compact than necessary. The entire unit could be built on perf board if generous ground conductors are used.

Coax cable should not be used for interconnecting circuits except for the vco output to the mixer, mixer output to the receiver, and input from the hf antenna. Other leads should be run in twisted pairs of no. 22-26 (0.6-0.4mm) hookup wire to minimize shunt capacitive loading on the TTL gates and to reduce inductive pickup in the phase-comparator circuitry. Coax cable should not be used in the input circuit, since the high capacitance of this cable could appreciably decrease the tuning range.

The 28.5-MHz output coil was a junk-box relic of unknown parentage. Any coil with a turns ratio of about 5:1 with a slug capable of resonating at 28.5 MHz will do. An inductance of about  $3 \mu\text{H}$  is required.

Most of the parts for the *XPL* are available from surplus houses or other *ham radio* and *QST* advertisers. The MC4044P, MC1648L, and MV1401, however, will probably have to be ordered from a franchised Motorola distributor. Total cost is about \$20 for these items.

The individual regulators were Motorola types, but various National LM-series are equally satisfactory and widely available. The 2N4403 transistor can be

replaced with almost any high-frequency pnp transistor. Similarly, the 2N5457 can be replaced by other N-channel jfet devices, such as the MPF102 series.

All signal diodes should be 1N4148/1N914 or similar silicon computer diodes. As mentioned earlier, germanium diodes can be used in the diode matrices if desired. Power diodes are low voltage, plastic-lead-mounted types.

Capacitors can be ceramic units except for the antenna input capacitor (560 pF) and the vco 1500-pF capacitors which should be of low-loss polystyrene or mica construction.

The entire counter and phase-lock system could be designed around CMOS circuitry except for the vco and the prescaler. CMOS chips are not widely available in surplus outlets but are rather inexpensive when purchased new. Power supply current could be considerably reduced by shifting to CMOS, and the diode translators could be run at a much higher impedance level.

## adjustments and troubleshooting

The power supply forms a logical first item if the XPL is built in steps. Output voltage must be at least

### TRANSLATORS

### DIVIDERS

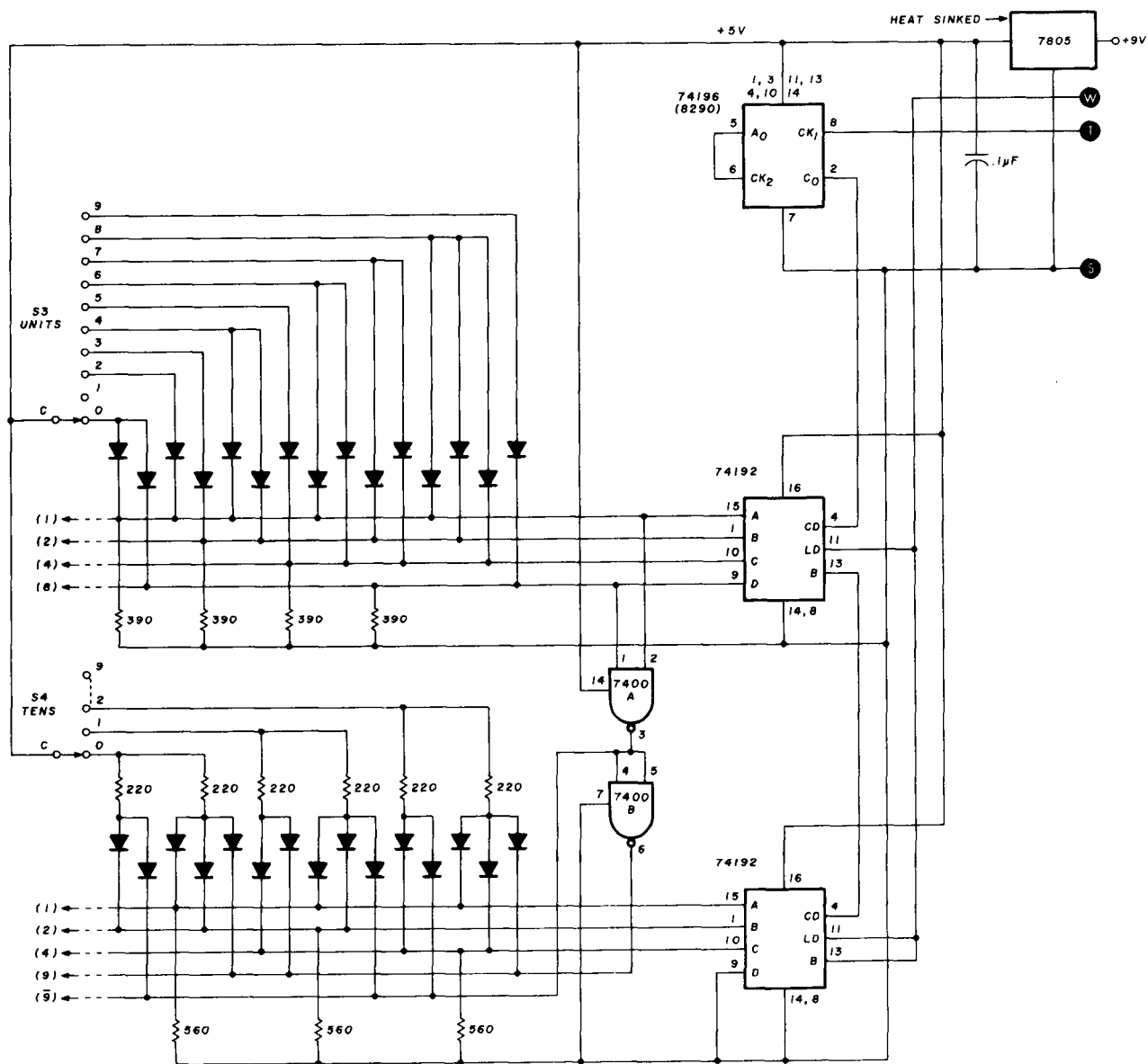


fig. 6. Schematic of the XPL programmable counters and translators.

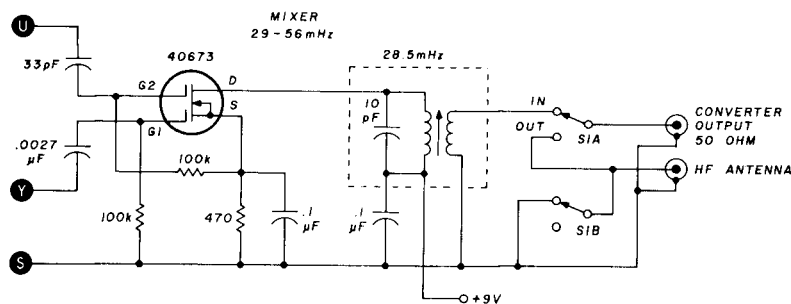


fig. 7. Mixer schematic.

7 volts to allow the individual regulators their required 2-volt input margin over 5-volt regulated output voltage. Frequency calibration of the reference oscillator can be done by zero beating with WWV or with WCFL, Chicago, on 1000 kHz. The vco should be checked for range by coupling a grid-dip oscillator to the toroidal coil. An input of 0.5 to 3.5-volts positive, derived from a separate source, should drive the vco from 25 to 60 MHz or so. If the frequency range is off, toroid turns may be trimmed or the 1500-pF capacitor value changed to suit. Input-coil slugs should be adjusted to allow coverage of all input frequencies with a bit of overlap.

Operation of the translators can be checked with a vtvm. Logic zero must be 0.8 volt or less, and logic 1 must be 2.4 volts or more — standard TTL levels. Preset counter operation can be checked with a triggered oscilloscope and a low capacitance (10X) probe. The 74196 output pulses will be visible on most inexpensive scopes.

## operation

For best results, a good antenna system should be used with the *XPL*. One of the best is an 80-meter inverted V or dipole with open-wire feeders. Except for those few frequencies at which the antenna happens to be an odd number of quarter wavelengths long, its impedance will be quite high. Thus, the high capacitance of a grounded coax antenna feeder would result in serious signal attenuation. A simple long-wire antenna can be used if the end is brought directly to the *XPL* input terminals. If a separate

antenna system isn't available, any ungrounded antenna feeder system can be used by connecting either lead to the **A1** antenna terminal. Terminal **A2** should be grounded for single ended inputs.

The input circuit should be calibrated at least roughly so you can be sure the desired signal is being peaked. The input circuit provides the only rejection for 10-meter signals present on the antenna. Above about 15 MHz, this rejection may be inadequate to prevent strong 10-meter signals from coming directly through the mixer to the i-f. A resonant trap or a loosely coupled input circuit can be added if this problem proves troublesome. A balanced mixer would reduce the feedthrough, but the added complication seemed unnecessary. I suggest this as an alternative approach for those interested in experimentation.

## final remarks

The *XPL Converter* has been fun to use. Broadcast stations pop up exactly where they are supposed to be. The *Selected Cities Weather Summary*, broadcast from Miami on RTTY has been interesting to print and peruse. WWV is available on all frequencies for calibration or a check on propagation conditions.

Aviation weather and general information is broadcast on the local low-frequency range station. Every international shortwave band can be received. International air-route traffic control from Miami and New York can also be monitored. And, near the top end, you can even listen to CB operations.

## bibliography

1. R. W. Wilmark, W1MCR, and W. R. Wade, K1IJZ, "Synthesized Two-Meter FM Transceiver," *ham radio*, January, 1976, page 10.
2. K. W. Robbins, W1KNI, "Six Meter Frequency Synthesizer," *ham radio*, March, 1974, page 26.
3. P. J. Bertini, K1ZJH, and R. Van Hooft, WB2MBI, "A Practical Approach to Two Meter Frequency Synthesis," Part 1, *QST*, June, 1973, page 31; Part 2, *QST*, July, 1973, page 34.
4. *Motorola Application Notes AN-535, AN-533, and AN-564*, Motorola, Inc., Technical Information Center, P. O. Box 20912, Phoenix, Arizona 85036.

ham radio

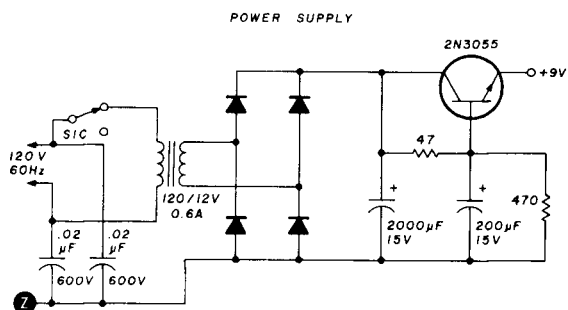


fig. 8. Power-supply schematic.

# This one's for you.

Because you asked for it . . . we built it. The all-new JR. MONITOR™ Antenna Tuner.


Call it what you will — antenna tuner, matchbox, or matching network, the JR. MONITOR™ has it all wrapped up in one neat 5¼"Wx2¾"Hx6"D all metal cabinet.

Here are the features you said you wanted:

Continuous tuning from 1.8-30 MHz. 300 watt power capability. Forward reading relative output power meter — simply tune JR. MONITOR™ controls for maximum RF output on the meter. Built-in balun. Mobile mounting bracket. Ceramic rotary 12-position switch. Capacitor spacing 1000 volts. Tapped toroid inductor. Antenna inputs: coax unbalanced SO 239, random wire, balanced feed line 75-660 ohm. Weight: 2½ pounds.

With so many special features — think of the unlimited possibilities you'll have for experimenting with dozens of antennas! For instance, the DenTron All Band Doublet fed with balanced feed line hooked to the JR. MONITOR™ covers 1.8-30 MHz in one antenna. . . or try this mobile suggestion: 108" mobile whip fed with coax to the JR. MONITOR™ located under the dash will give you 10-40 meter mobile coverage and no coils to change!

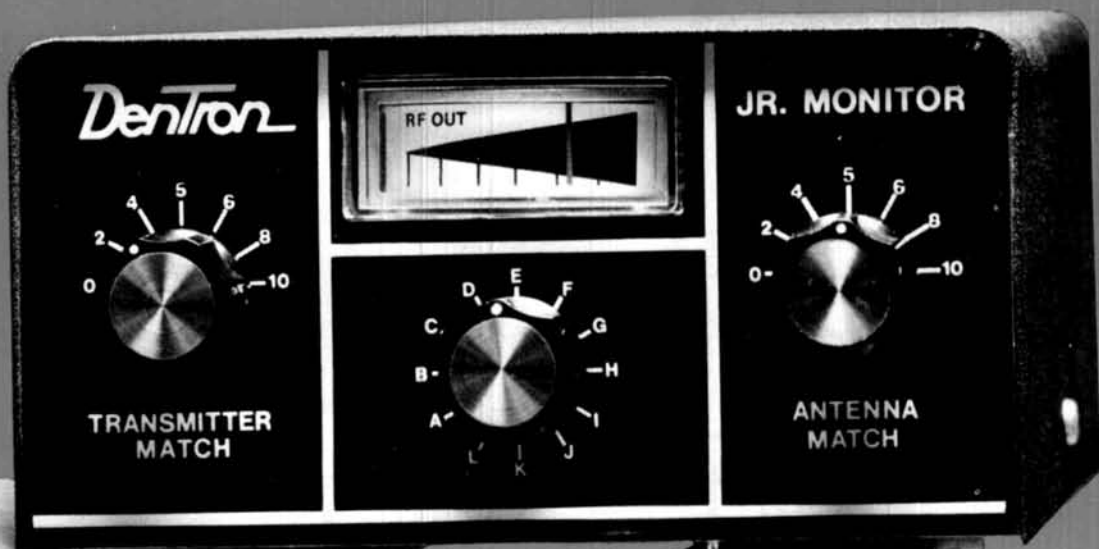It's easy to understand the excitement the JR. MONITOR™ has created. Wherever you are — home, boat, car, plane, or campsite you'll always be in contact. It's a fun little tuner that easily fits in a briefcase or coat pocket — but why would anyone want to smuggle it into their radio room?



JR. MONITOR™ \$79.50  
ALL BAND DOUBLET \$24.50

**DenTron**  
Radio Co., Inc.


2100 Enterprise Pkwy.,  
Twinsburg, Ohio 44087

(216) 425-3173


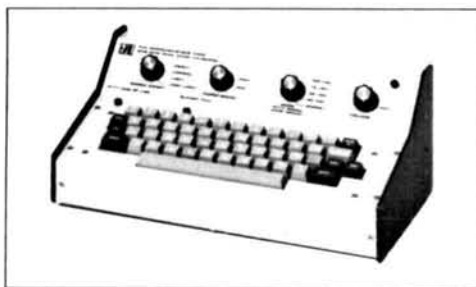
# RTTY Can Be Easy!

Have You Wondered . . .  
What Owning a RTTY Station Would be Like?  
Have You Thought . . .  
About Finding Out but Didn't Know Who to Ask?



## ASK THE GUYS AT HAL!

Our sales and service staff will be happy to assist you in your choice of RTTY equipment, answer questions about RTTY, and provide assistance if problems do arise. In addition, all HAL amateur RTTY equipment manuals can be purchased for \$10.00 each for an advance look (applicable to future purchase of that unit).

Answers to common RTTY questions are featured in the center fold of our new amateur radio catalog. Such questions as "What do I need?," "How do I hook it up?," and "What frequencies do I use?" are discussed. Technical points concerning RTTY pulses, FSK and AFSK, and high-tones vs low-tones are covered.

Write today for HAL'S new catalog and RTTY guide and discover how much fun RTTY can be.




**HAL COMMUNICATIONS CORP.**  
Box 365  
Urbana, Illinois 61801  
217-367-7373

For our European customers  
see HAL equipment at:

Richter & Co., Hannover  
I.E.C. Interco, Bissone  
Primetek Systems, Handen, Sweden  
Radio Shack of London

# A Component System for RTTY

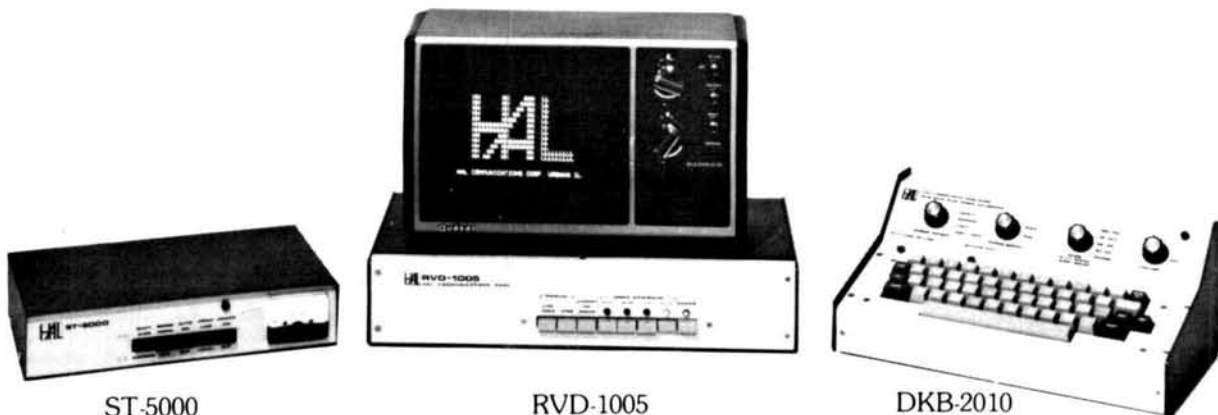

ST-5000

RVD-1005

DKB-2010

Active amateur, short wave listener, beginner, or old-timer—you'll enjoy RTTY with the HAL component system. Shown above are our ST-5000 Demodulator, RVD-1005 Visual Display Unit, and DKB-2010 Dual-mode Keyboard. The RVD-1005 is a time-proven display generator that converts BAUDOT coded RTTY pulses into a video display. It receives the 4 standard RTTY speeds (60, 66, 75, and 100 words per minute) and generates a 25 line, 40 characters per line display. The low-bandwidth video output can drive either a TV monitor or a modified TV Set (power transformer and video connection required). The DKB-2010 will transmit these same four RTTY speeds as well as MORSE code at 8 to 60 wpm. The DKB also features N-key rollover, adjustable CW weight, HERE IS message, and internal CW side-tone oscillator. The 3-key standard buffer can be extended to 128 keys with the EMO-128 buffer option. The ST-5000 is the newest of HAL's line of RTTY equipment, offering 2-shift operation with high-performance active filter circuitry. It also has built-in AFSK oscillator and loop supply and can be factory tuned for either the "High" or "Low" frequency tone pairs. Autostart and printer control circuitry make the ST-5000 ideal for both electronic and mechanical RTTY terminals. For a high-performance and cost-effective RTTY station, the RVD-1005/DKB-2010/ST-5000 combination is hard to beat!

## ST-5000

- 170 and 850 Hz Shift
- Low or High Tones
- Integral Tone Keyer
- Active Filters
- Autostart
- Meter Tuning Indicator
- Internal Loop Supply
- Attractive, Small Cabinet
- High-gain, Wide-bandwidth Limiter
- For either HF or VHF operation
- 120/240V, 50/60 Hz Power

ST-5000 ..... \$275.00  
(Specify High or Low Tones)

## RVD-1005

- 4 RTTY Speeds  
(60, 66, 75, 100 wpm)
- Crystal Controlled
- Baudot RTTY Code
- Unshift-on-Space  
(Switch Selectable)
- Loop or RS-232 Input
- 40 Character Lines  
25 Line Display
- Table or Rack Cabinet
- Use with modified TV Set
- 120/240V, 50/60 Hz Power

RVD-1005 ..... \$395.00  
(Specify Table or Rack Cabinet)

RVD-2110 Quasar TV ..... \$150.00  
(Shown above)

## DKB-2010

- Baudot RTTY & Morse Codes
- 4 RTTY Speeds (60, 66, 75, 100 wpm)
- Crystal Controlled
- 8 to 60 wpm Morse Code
- Programmable HERE IS message
- N-Key Rollover
- 3-Key Buffer Standard  
(128 Key with 128 EMO option)
- Quick Brown Fox test message
- Automatic FIGS/LTRS for RTTY
- Internal CW Sidetone Oscillator
- 120/240V, 50/60 Hz Power

DKB-2010 ..... \$395.00  
(Specify HERE IS message)

EMO-128 Buffer Option .... \$ 85.00

Write for our new catalog and RTTY guide.



**HAL COMMUNICATIONS CORP.**  
Box 365  
Urbana, Illinois 61801  
217-367-7373

For our European customers  
see HAL equipment at:  
Richter & Co., Hannover  
I.E.C. Interelco, Bissone  
Primetek Systems, Handen, Sweden  
Radio Shack of London


## short circuit

### RTTY time/date printout

An important point was missed in **table 1** of the RTTY printout article which appeared in June, 1976, *ham radio*. Pin 4 of U15 should not be grounded but should have the appropriate BCD information for the tens of minutes digit.

As shown, the ten, minutes digit will only display up to 39 minutes instead of 59 minutes. In **fig. 4A**, pins 6 and 7 of the 7490s must be grounded; otherwise the circuit will only print the 19th as the date.

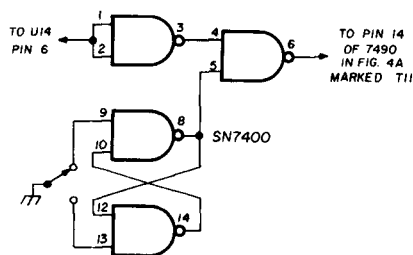Advancing the date by moving the clock is a very tedious process. Over-shooting will mean doing the entire thirty days over again. The diagram below shows a circuit that will permit



you to advance the date by one day with the flip of the switch. When the date resets at the end of the month, flipping the switch will advance the clock to 01, much easier than advancing the digital clock a complete 24-hour period. Note that this advance circuit is designed to work with a low input so the date advance must be done before 2000 hours.

### pi network design and analysis

**Eq. 8** in the pi network design article, September, 1977, *ham radio*, should not have the radical sign on the right hand side of the expression; it should read

$$R1 \text{ (at minimum point of } X_{C1} \text{ curve)} = R_{1B} = \frac{2X_L^2}{R_2} \quad (8)$$

Also, **eq. 12** should read as follows:

$$X_L = (R1 + R2) \frac{Q_o^2 + \sqrt{Q_o^2 - (Q_o^2 + 4) \left( \frac{R2 - R1}{R1 + R2} \right)^2}}{Q_o^2 + 4} \quad (12)$$

### direct output synthesizer for two meters

In **fig. 4** of the direct output synthesizer in August, 1977, *ham radio*, the lines connected to pins 10 and 8 of U3C have been transposed. For correct operation, pin 10 is connected to the pin 9s of the 74161s, and pin 8 of U3C is connected to pin 1 of U2B. On U1, pin 2 is the input from U3D and pin 1 should be connected to the junction of the 100 and 360 ohm resistors. U1 may exhibit some temperature and voltage sensitivity at times causing the divide-by-21 function to become a divide-by-22. This problem can be cured by either of two methods: putting a 330 pF capacitor from pin 2 of U1 to ground or replacing U3 with a 74L00 instead of the 7400. U8 is a 7483, not a 7473. In **fig. 6**, the 0.1  $\mu$ F capacitor connected to pin 2 of U18 should be a 0.01  $\mu$ F disc capacitor. Also, the 40k-ohm resistor on the output of U18B should be 10k.

### serial converter for 8-level teleprinters

The serial converter in August, 1977, *ham radio*, uses a 74121 for U16, not a 7474.


### audio frequency speech processing

The circuit board layout for the audio speech processor in August, 1977, *ham radio* was missing several connections. The diagram above shows the correct circuit board layout. The output is taken from the center of R13 and not as shown in **fig. 5** in the article. The numbering for the pins of the ICs in the schematic diagram should be changed to correspond with the 8-pin mini DIPs used on the finished board.

fig. 3	change to
5	3
4	2
6	4
10	6
11	7
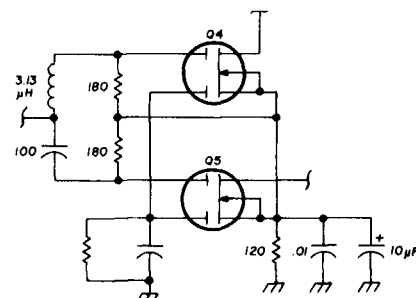
### phasing-type single-signal detector

In **fig. 2**, page 72 of October, 1976, *ham radio*, the two 180-ohm resistors should be connected between gate 2 and the source of the dual-gate mosfet as shown below. Also, gate number 1 is not connected to the source.



## spectrum analyzer

There are several errors in the spectrum analyzer construction article which appeared in the June, 1977, issue. The 75.1 ohm resistor in the rf attenuator should be 71.5 ohms; the six 69.1 ohm resistors should be 61.9 ohms (fig. 10). The i-f attenuator should have three, *not two*, 20 dB sections (like the rf attenuator).

The mixer diodes used by the author are Hewlett-Packard part number 5082-2900; most any hot-carrier diodes should work if they are all the same type.

The crystal in the second local oscillator is 150 MHz  $\pm$  2 MHz; the crystal in the third local oscillator is 39.3  $\pm$  1 MHz. The 10k resistor associated with CR401 should go to switch S601A, the 250 kHz position; the same for the 10k resistor associated with the second crystal filter, Y401 (fig. 11). The 2.4k resistor in series with CR402 should go to switch S601A, the 10 kHz position. The coil located near CR403, and the switch contacts near R402, are parts of the same relay.

Large size Xerox copies of the top and bottom chassis photographs are available from *ham radio*, and will be sent to interested readers upon receipt of a self-addressed, stamped envelope.

## reducing IMD in high-frequency receivers

The 3-dB pad between the local oscillator input and the balanced mixer, in fig. 6 on page 30 of the March, 1977, issue of *ham radio*, should have the values transposed (the series resistor should be 18 ohms, the shunt resistor 300 ohms.)

## bandspreading techniques for resonant circuits

In eq. 19 on page 49 of the February, 1977, issue of *ham radio*, the term  $C_r$  should not be included under the radical sign. The equation should read:

$$C_p = \frac{\sqrt{C_q + C_r^2}}{2V} - C_r$$



**Regency**  
the first name in solid state®

## INTRODUCES THE VERSATILE NEW



# HR-312

### More Channels...at the flip of a switch

Unlock the unique mode switch and 12 channels become 144

### More Sensitivity, Less Interference.

.25  $\mu$ V Sensitivity plus 75 db adjacent channel selectivity and 70 db image rejection

### More Power Out

35 watts nominal with a minimum of 30 watts across the band

... for a lot less

**\$269<sup>00</sup>**

Amateur Net



**REGENCY ELECTRONICS, INC.** 7707 Records Street  
Indianapolis, Indiana 46226

## THE FM LEADER


2 METER

220 MHz


6 METER

440 MHz

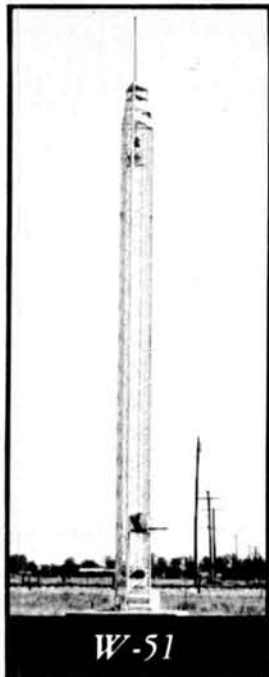
**NOW.**  
*Top-of-the-Line*  
**Tri-Ex Towers**  
*for HAM operators*  
*at basic prices!*




**W-51**

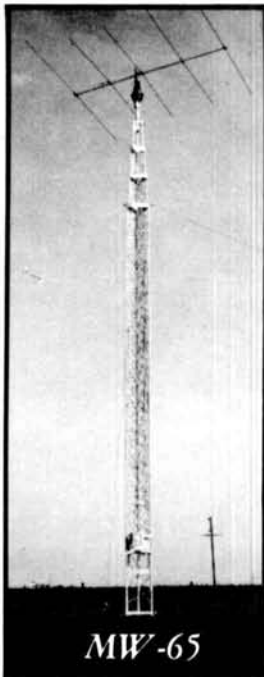


**MW-65**

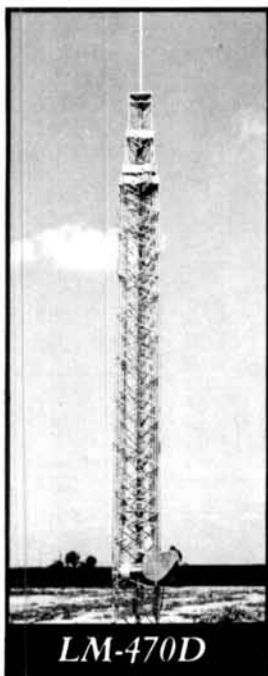

**LM-470D**

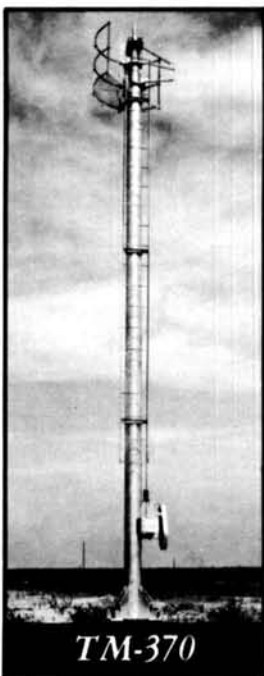

**TM-370**

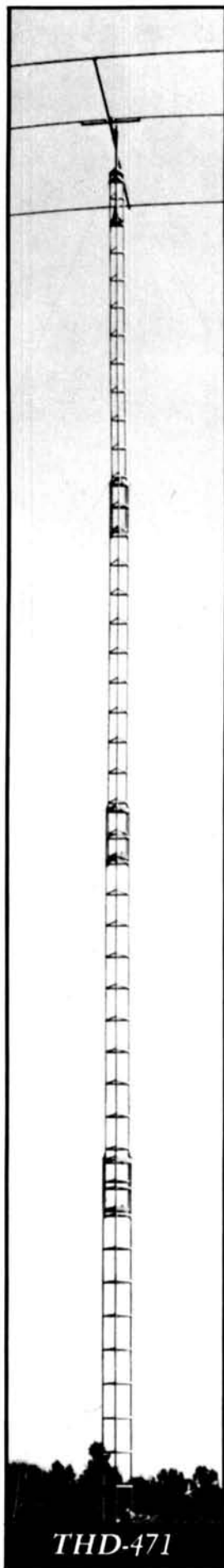

**THD-471**

Now you can afford the best! Free-standing or guyed, Tri-Ex Towers stress quality. All towers are hot dipped galvanized *after* fabrication for longer life. Each series is specifically engineered to HAM operator requirements.

### *W Series*

An aerodynamic tower designed to hold 9 square feet in a 50 mph wind. Six models at different heights.

### *MW Series*

Self-supporting when attached at first section — will hold normal Tri-Band beam. Six models.

### *LM Series*

A 'W' brace motorized tower. Holds large antenna loads up to 70 feet high. Super buy.

### *TM Series*

Features tubular construction for really big antenna loads. Up to 100 feet. Free-standing, with motors to raise and lower.

### *THD Series*

Very popular. Low Cost. Holds Tri-Band antennas. Eight models — all support 7 square feet of antenna at full height in 70 mph winds. Guyed.

Start with Top-of-the-Line Tri-Ex Towers. At basic prices. Write today, for your best buy.


  
**Tri-Ex<sup>®</sup>**  
**TOWER**  
**CORPORATION**

7182 Rasmussen Ave.  
 Visalia, Calif. 93277

# WHERE RELIABILITY & ACCURACY COUNT

## INTERNATIONAL CRYSTALS 70 KHz to 160 MHz

### HOLDER TYPES

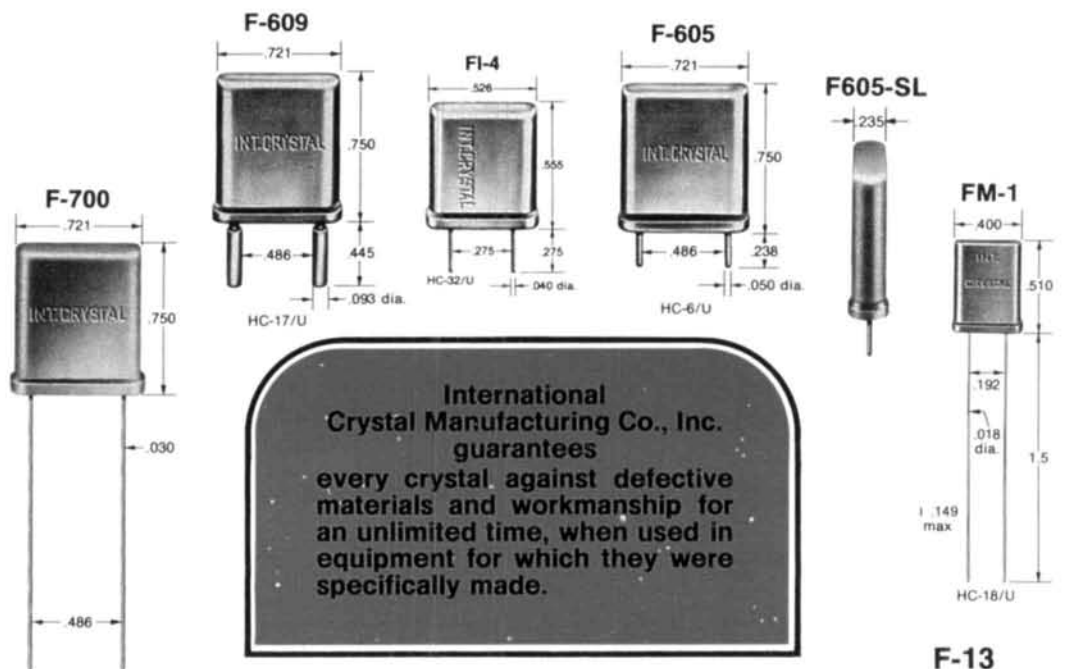

### CRYSTAL TYPES


- (GP) for "General Purpose" applications
- (CS) for "Commercial" equipment
- (HA) for "High Accuracy" close temperature tolerance requirements


International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders.

WRITE FOR INFORMATION



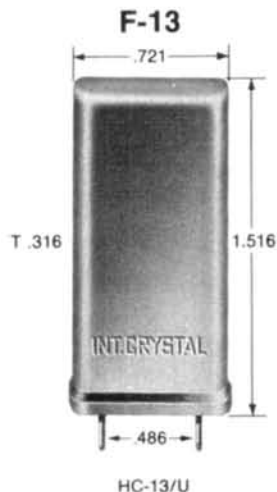**INTERNATIONAL CRYSTAL MFG. CO., INC.**  
10 North Lee, Oklahoma City, Oklahoma 73102  
405/236-3741



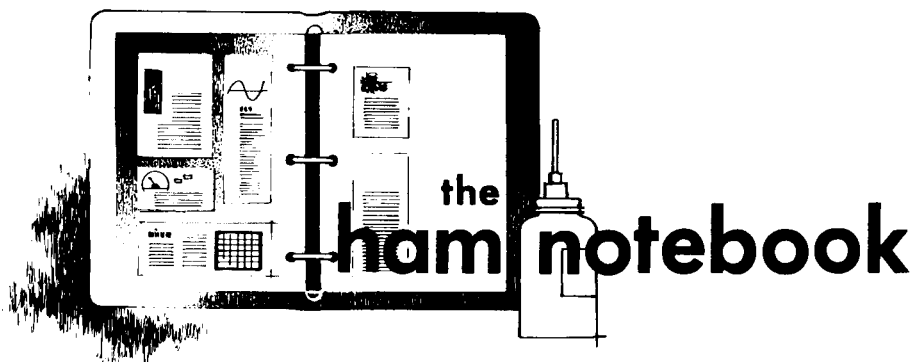

## simple formula for microstrip impedance

In many amateur vhf and uhf applications strip transmission lines etched on printed-circuit board are used for impedance matching and as components in tuned resonant circuits. Although several methods are available for calculating the characteristic impedance of microstrip transmission line, the formula derived by Sobol<sup>1</sup> is the most popular. It has been widely publicized in Motorola Semiconductor's application notes and appeared recently in *QST*<sup>2</sup>. Sobol's equation:

$$Z_o = \frac{120\pi h}{\sqrt{\epsilon_r} w (1 + 1.735\epsilon_r^{-0.0724} w/h^{-0.836})}$$

where  $w$  is strip width,  $h$  is the dielectric thickness, and  $\epsilon_r$  is the relative dielectric constant of the substrate.

Sobol's equation gives  $Z_o$  as a function of microstrip geometry, but in practical applications you usually need to know what size microstrip is required for a given impedance. Since the equation can't be solved directly for  $w/h$ , an interactive trial-and-error solution is necessary. This can be done rather quickly with a high-speed computer, but an iterative solution with a programmable calculator such as the HP-25 may require a minute or more — an iterative solu-

tion with a non-programmable calculator is impractical.

Some time ago N6TX (ex WA6UAM) sent me an iterative HP-25 program for Sobol's microstrip

then be refined with the HP-25 program. My first step was to rewrite Sobol's equation as

$$Z_o = \frac{120\pi}{\sqrt{\epsilon_r} \frac{w}{h}} \left[ \frac{1}{1 + 1.735 \epsilon_r^{-0.0724} w/h^{-0.836}} \right]$$

By inspection, to a first approximation  $Z_o$  is equal to the first term on the right-hand side of the equal sign; the term inside the parenthesis is a modification term which is a function of both  $\epsilon_r$  and  $w/h$ . Designating the

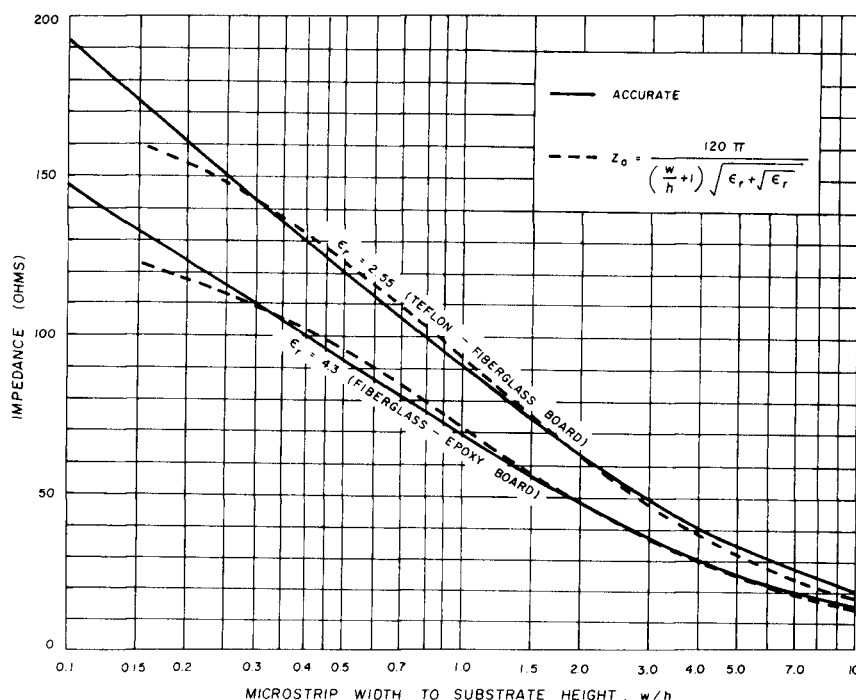


fig. 1. Microstrip impedance calculated with simple formulas developed by W1HR (dashed lines), as compared to actual impedance (solid line). For  $\epsilon_r > 4$ , accuracy is very good for  $w/h > 0.2$ .

equation which provided acceptable accuracy for most design work. This program begins at  $w/h = 1$  and iterates out to the required value. Therefore, for low and high values of  $Z_o$  a solution requires considerable calculation time. To reduce calculation time I decided to see if I could develop a simple equation for an approximate value of  $w/h$  which could

quantity  $(1.735\epsilon_r^{-0.0724} w/h^{-0.836})$  as  $K$ , eq. 1 was rewritten as

$$\frac{120\pi}{Z_o \sqrt{\epsilon_r}} = \frac{w}{h} (1 + K) = \frac{w}{h} + K \cdot \frac{w}{h}$$

All that remained was to find a value for  $K \cdot w/h$  which satisfied varying values of  $\epsilon_r$  and  $w/h$ . After calculating several tables of values, it was ap-

1. H. Sobol, "Extending IC Technology to Microwave Equipment," *Electronics*, March 20, 1967, page 112.  
2. R. Olsen, N6NR, "Designing Solid-State RF Power Circuits," *QST*, September, 1977, page 15.

parent that  $K \cdot w/h = 1$  would give the desired results. Substituting and rearranging terms yielded the expression

$$\frac{w}{h} \approx \frac{120\pi}{Z_o \sqrt{\epsilon_r}} - 1 \quad (3)$$

When this equation was plotted on graph paper and compared to a graph of Sobol's equation, the similarity was much closer than I expected — the curve had essentially the correct shape, but all values were slightly larger than those given by Sobol's formula. This was the desired result; rewriting the HP-25 program around eq. 3 considerably reduced calculation time.

Later it occurred to me that it might be possible to further factor eq. 3 to obtain a more accurate formula for microstrip impedance. After calculating numerous tables of  $Z_o$  vs  $w/h$  and  $\epsilon_r$ , and inspecting the values, I found that the impedance of microstrip etched on a substrate with  $\epsilon_r > 4.0$  could be approximated within a few per cent by the following equations:

$$\frac{w}{h} \approx \frac{120\pi}{Z_o \sqrt{\epsilon_r + \sqrt{\epsilon_r}}} - 1 \quad (4)$$

$$Z_o \approx \frac{120\pi}{\left(\frac{w}{h} + 1\right) \sqrt{\epsilon_r + \sqrt{\epsilon_r}}} \quad (5)$$

For microstrip etched on glass-epoxy circuit board ( $\epsilon_r = 4.8$ ), these equations can be reduced to

$$\frac{w}{h} \approx \frac{142.6}{Z_o} - 1 \quad Z_o \approx \frac{142.6}{\frac{w}{h} + 1}$$

For Teflon-fiberglass circuit board ( $\epsilon_r = 2.55$ ) the simplified expressions are

$$\frac{w}{h} \approx \frac{185.1}{Z_o} - 1 \quad Z_o \approx \frac{185.1}{\frac{w}{h} + 1}$$

The dielectric constant of Teflon-fiberglass is below the value recommended for these equations, but accuracy is still acceptable for many applications.

These formulas can be solved quickly by hand (or with a simple four-function calculator), and should be a big help to amateurs who want to design their own microstrip circuits. They can also be used to determine the approximate impedance of circuit traces for digital logic boards (for best results the  $V_{cc}$  and ground lines for TTL should have low impedance).

The accuracy of these simplified equations is surprisingly good. As shown in fig. 1, for  $w/h > 0.2$ , the simplified formulas are within a few per cent of the impedance calculated with more accurate equations; this covers the microstrip impedance range most commonly used in radio communications work. With fiberglass-epoxy board the formulas are within about 1 ohm of the exact expression for all values of  $Z_o$  below 60 ohms. The values for Teflon-fiberglass board are somewhat less accurate, but are still acceptable for most amateur work.

James R. Fisk, W1HR

## improved (vfo) stability for the Atlas 180

Early versions of the Atlas 180 transceiver have exhibited poor vfo stability with a varying dc supply voltage. In some cases, the vfo will actually be frequency modulated at

dc input voltages below 13 volts. Atlas owners can check for this condition by listening to a signal or the calibrator beat note and adjusting the dc supply from about 11.5 volts to 14.5 volts. A 500-milliampere supply is more than ample to operate the receiver. The test can also be made in the car by first setting up the beat note with the engine off and then starting the engine. After a few moments the battery system will come up to full-charge voltage of 14.5 volts. Any change in pitch during this time indicates poor vfo power supply regulation. The units in which this is most likely to occur are those which use a 10-volt regulator circuit consisting of a transistor with a 10-volt Zener on the base.

The solution to the problem is to remove the 27-ohm decoupling resistor (R401 in my Atlas 180) on the vfo board (PC-400), and replace it with a 78L08ACP low-power 8-volt regulator. The wire that previously connected to the 10-volt bus is then reconnected to the 13-volt bus. After making this change, retuning is unnecessary for dc inputs of 11.5 volts to 14.5 volts, and there are no reports of frequency modulation when operating mobile without the engine running. There is no other noticeable change in the operation of the vfo due to the 8-volt rather than 10-volt supply.

Dave Sargent, K6KLO

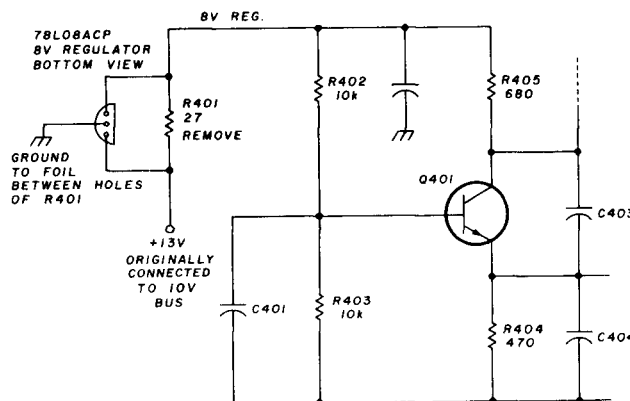


fig. 1. Modification to the Atlas 180 vfo power supply to prevent any frequency modulation due to voltage changes. The 78L08ACP voltage regulator is used to prevent voltage changes. It is fed from the normal 12.6-volt dc supply.

# KENWOOD

...pacesetter in amateur radio

## TS-520S

AND DG-5 DIGITAL FREQUENCY DISPLAY



The TS-520S combines all of the fine, field-proven characteristics of the original TS-520 together with many of the ideas and suggestions for improvement from amateurs worldwide.

### FULL COVERAGE TRANSCEIVER

The TS-520S provides full coverage on all amateur bands from 1.8 to 29.7 MHz. Kenwood gives you 160 meter capability, WWV on 15.000 MHz., and an auxiliary band position for maximum flexibility. And with the addition of the TV-506 transverter, your TS-520S can cover 160 meters to 6 meters on SSB and CW.

### DIGITAL DISPLAY DG-5 (option)

The Kenwood DG-5 provides easy, accurate readout of your operating frequency while transmitting and receiving.

### OUTSTANDING RECEIVER SENSITIVITY AND MINIMUM CROSS MODULATION

The TS-520S incorporates a 3SK35 dual gate MOSFET for outstanding cross modulation and spurious response characteristics. The 3SK35 has a low noise figure (3.5 dB typ.) and high gain (18 dB typ.) for excellent sensitivity.

### NEW IMPROVED SPEECH PROCESSOR

An audio compression amplifier gives you extra punch in the pile

ups and when the going gets rough.

### VERNIER TUNING FOR FINAL PLATE CONTROL

A vernier tuning mechanism allows easy and accurate adjustment of the plate control during tune-up.

### FINAL AMPLIFIER

The TS-520S is completely solid state except for the driver (12B-Y7A) and the final tubes. Rather than substitute TV sweep tubes as final amplifier tubes in a state of the art amateur transceiver,

Kenwood has employed two husky S-2001A (equivalent to 6146B) tubes. These rugged, time-proven tubes are known for their long life and superb linearity.

#### HIGHLY EFFECTIVE NOISE BLANKER

An effective noise blanking circuit developed by Kenwood that virtually eliminates ignition noise is built into the TS-520S.

#### RF ATTENUATOR

The TS-520S has a built-in 20 dB attenuator that can be activated by a push button switch conveniently located on the front panel.

#### PROVISION FOR EXTERNAL RECEIVER

A special jack on the rear panel of the TS-520S provides receiver signals to an external receiver for increased station versatility. A switch on the rear panel determines the signal path... the receiver in the TS-820 or any external receiver.

The VFO-520 remote VFO matches the styling of the TS-520S and provides maximum operating flexibility on the band selected on your TS-520S.

The TS-520S is completely self-contained with a rugged AC power supply built-in. The addition of the DS-1A DC-DC converter (optional) allows for mobile operation of the TS-520S.

The TS-520S has 2 convenient RCA phono jacks on the rear panel for PHONE PATCH IN and PHONE PATCH OUT.

The CW-520-500 Hz filter can be easily installed and will provide improved operation on CW.

The AGC circuit has 3 positions (OFF, FAST, SLOW) to enable the TS-520S to be operated in the optimum condition at all times whether operating CW or SSB.

The TS-520S retains all of the features of the original TS-520 that made it tops in its class: RIT control • 8-pole crystal filter • Built-in 25 KHz calibrator • Front panel carrier level control • Semi-break-in CW with sidetone • VOX/PTT/MOX • TUNE position for low power tune up • Built-in speaker • Built-in Cooling Fan • Provisions for 4 fixed frequency channels • Heater switch.


## TS-520 Specifications

Amateur Bands: 160-10 meters plus WWV (receive only)  
Modes: USB, LSB, CW  
Antenna Impedance: 50-75 Ohms  
Frequency Stability: Within  $\pm 1$  kHz during one hour after one minute of warm-up, and within 100 Hz during any 30 minute period thereafter  
Tubes & Semiconductors:  
Tubes ..... 3 (S2001A x 2, 12BY7A)  
Transistors ..... 52  
FETs ..... 19  
Diodes ..... 101  
Power Requirements: 120/220 V AC, 50/60 Hz, 13.8 V DC (with optional DS-1A)  
Power Consumption: Transmit: 280 Watts Receive: 26 Watts (with heater off)  
Dimension: 333(13 1/4) W x 153 (6-0) H x 335(13-13/16) D mm(inch)  
Weight: 16.0 kg(35.2 lbs)  
**TRANSMITTER**  
RF Input Power: SSB: 200 Watts PEP CW: 160 Watts DC  
Carrier Suppression: Better than -40 dB  
Sideband Suppression: Better than -50 dB  
Spurious Radiation: Better than -40 dB  
Microphone Impedance: 50k Ohms  
AF Response: 400 to 2,600 Hz  
**RECEIVER**  
Sensitivity: 0.25  $\mu$ V for 10 dB (S+N)/N  
Selectivity: SSB: 2.4 kHz/-6 dB, 4.4 kHz/-60 dB  
Selectivity: CW: 0.5 kHz/-6 dB, 1.5 kHz/-60 dB (with optional CW-520 filter)  
Image Ratio: Better than 50 dB  
IF Rejection: Better than 50 dB  
AF Output Power: 1.0 Watt (8 Ohm load, with less than 10% distortion)  
AF Output Impedance: 4 to 16 Ohms

### DG-5
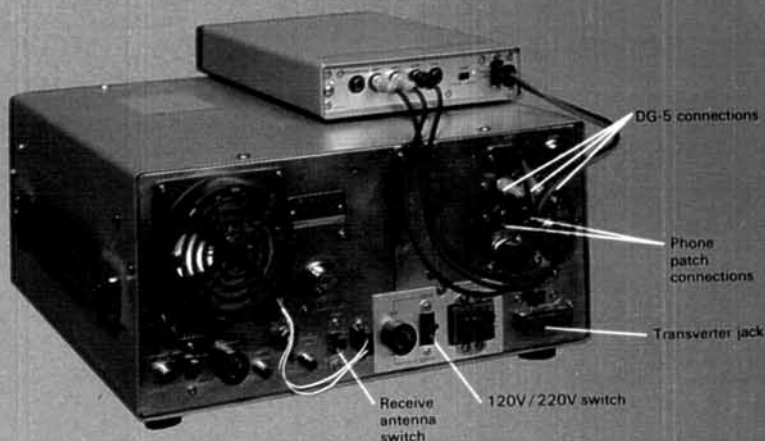
#### SPECIFICATIONS

Measuring Range: 100 Hz to 40 MHz  
Input Impedance: 5 k Ohms  
Gate Time: 0.1 Sec.  
Input Sensitivity: 100 Hz to 40 MHz... 200 mV rms or over, 10 kHz to 10 MHz... 50 mV or over  
Measuring Accuracy: Internal time base accuracy  $\pm 0.1$  count  
Time Base: 10 MHz  
Operating Temperature: -10° to 50° C/14° to 122° F  
Power Requirement: Supplied from TS-520S or 12 to 16 VDC (nominal 13.8 VDC)  
Dimensions: 167(6-9/16) W x 43(1-11/16) H x 268(10-9/16) D mm(inch)  
Weight: 1.3 kg(2.9 lbs)



## DG-5

The luxury of digital readout is available on the TS-520S by connecting the DG-5 readout (option). More than just the average readout circuit, this counter mixes the digital, VFO, and heterodyne frequencies to give you your exact frequency. This handsomely styled accessory can be set almost anywhere in your shack for easy to read operation... or set it on the dashboard during mobile operation for safety and convenience. Six bold digits display your operating frequency while you transmit and receive. Complete with DH (display hold) switch for frequency memory and 2 position intensity selector. The DG-5 can also be used as a normal frequency counter up to 40 MHz at the touch of a switch. (Input cable provided.)  
NOTE: TS-520 owners can use the DG-5 with a DK-520 adapter kit.

# KENWOOD

...pacesetter in amateur radio



# TS-820S

## WITH DIGITAL FREQUENCY DISPLAY

We told you that the TS-820 would be best. In little more than a year our promise has become a fact. Now, in response to hundreds of requests from amateurs, Kenwood offers the TS-820S\*... the same superb transceiver, but with the digital readout factory installed. As an owner of this beautiful rig, you will have at your fingertips the combination of controls and features that even under the toughest operating conditions make the TS-820S the Pacesetter that it is.

Following are a few of the TS-820S' many exciting features.

**PLL** • The TS-820S employs the latest phase lock loop circuitry. The single conversion receiver section performance offers superb protection against unwanted cross-modulation. And now PLL allows the frequency to remain the same when switching sidebands (USB, LSB, CW) and eliminates having to recalibrate each time.

**DIGITAL READOUT** • The digital counter display is employed as an integral part of the VFO readout system. Counter mixes the carrier VFO, and first heterodyne frequencies to give *exact* frequency. Figures the frequency down to 10 Hz and digital display

reads out to 100 Hz. Both receive and transmit frequencies are displayed in easy to read, Kenwood Blue digits.

**SPEECH PROCESSOR** • An RF circuit provides quick time constant compression using a true RF compressor as opposed to an AF clipper. Amount of compression is adjustable to the desired level by a convenient front panel control.

**IF SHIFT** • The IF SHIFT control varies the IF passband without changing the receive frequency. Enables the operator to eliminate unwanted signals by moving them out of the passband of the receiver. This feature alone makes the TS-820S a pacesetter.

\*The TS-820 and DG-1 are still available separately.

# TS-600



Experience the excitement of 6 meters. The TS-600 all mode transceiver lets you experience the fun of 6 meter band openings. This 10 watt, solid state rig covers 50.0-54.0 MHz. The VFO tunes the band in 1 MHz segments. It also

has provisions for fixed frequency operation on NETS or to listen for beacons. State of the art features such as an effective noise blanker and the RIT (Receiver Incremental Tuning) circuit make the TS-600 another Kenwood "Pacesetter".



## TV-506

An easy way to get on the 6 meter band with your TS-520/520S, TS-820/820S and most other transceivers. Simply plug it in and you're on... full band coverage with 10 watts output on SSB and CW.



# TR-8300

Experience the luxury of 450 MHz at an economical price. The TR-8300 offers high quality and superb performance as a result of many years of improving VHF/UHF design techniques. The trans-


ceiver is capable of F<sub>3</sub> emission on 23 crystal-controlled channels (3 supplied). The transmitter output is 10 watts. The TR-8300 incorporates a 5 section helical resonator and a

two-pole crystal filter in the IF section of the receiver for improved intermodulation characteristics. Receiver sensitivity, spurious response, and temperature characteristics are excellent.

**KENWOOD**  
...pacesetter in amateur radio

# TS-700S

WITH DIGITAL FREQUENCY DISPLAY

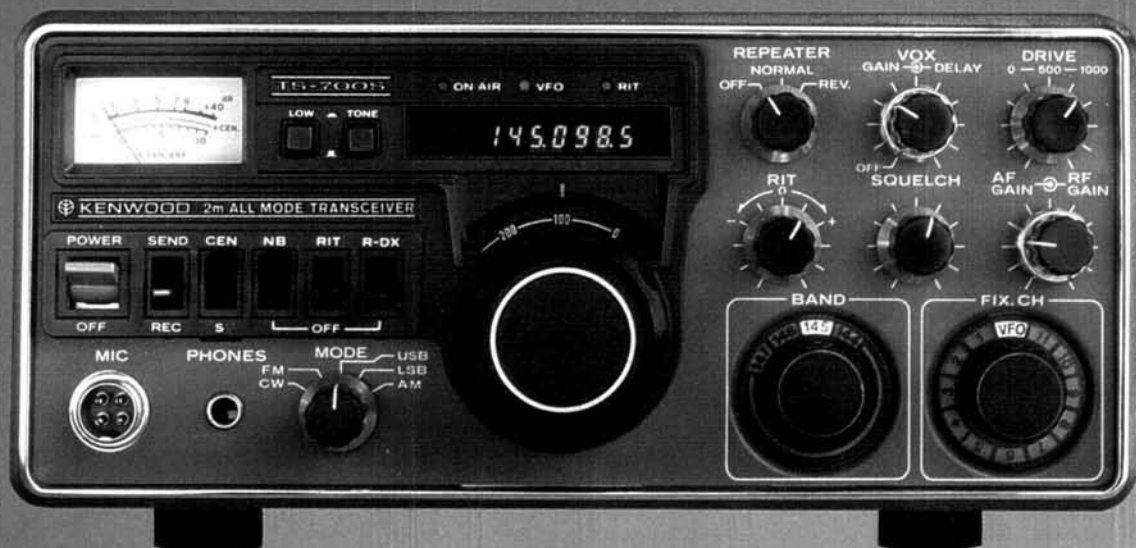

Check out the new "built-ins": digital readout, receiver pre-amp, VOX, semi-break in, and CW sidetone! Of course, it's still all mode, 144-148 MHz and VFO controlled.

Features: Digital readout with "Kenwood Blue" digits • High gain receiver pre-amp • 1 watt lower power switch • Built in VOX • Semi-break in on CW • CW sidetone • Operates all modes: SSB (upper & lower), FM, AM and CW • Completely solid state circuitry provides stable, long lasting, trouble-free operation • AC and DC capability (operate from your car, boat, or as a base station through its built-in power supply) • 4 MHz band coverage (144 to 148 MHz) • Automatically switches transmit frequency 600 KHz for repeater operation. Simply dial in your receive frequency and the radio does the rest... simplex, repeater, reverse • Or accomplish the same by plugging a single crystal into one of the 11 crystal positions for your favorite channel • Transmit/Receive capability on 44 channels with 11 crystals.



## VFO-700S

Handsomely styled and a perfect companion to the TS-700S. This unit provides you with the extra versatility and the luxury of having a second VFO in your shack. Great for split frequency operation and for tuning off frequency to check the band. The function switch

on the VFO-700S selects the VFO in use and the appropriate frequency is displayed on the digital readout in the TS-700S. In addition a momentary contact "frequency check" switch allows you to spot check the frequency of the VFO not in use.



# TR-7400A

Features Kenwood's unique Continuous Tone Coded Squelch system, 4 MHz band coverage, 25 watt output and fully synthesized 800 channel operation. This compact package gives you the kind of performance specifications you've always wanted in a 2-meter amateur rig.

Outstanding sensitivity, large-sized helical resonators with High Q to minimize undesirable out-of-band interference, and give a 2-pole 10.7 MHz monolithic crystal filter combine to give your TR-7400A outstanding receiver performance. Intermodulation characteristics (Better than 66dB), spurious (Better than -60dB), image rejection (Better than -70dB), and a versatile squelch system make the TR-7400A tops in its class.

Shown with the PS-8 power supply

(Active filters and Tone Burst Modules optional)



# TR-7500

This 100 channel PLL synthesized 146-148 MHz transceiver comes with 88 pre-programmed channels for use on all standard repeater frequencies (as per ARRL Band Plan) and most simplex channels. For added flexibility, there are 6 diode-programmable switch positions. The 15 KHz shift function makes these 6 positions into 12 channels. 10 watt output,  $\pm 600$  KHz offset and LED digital frequency display are just a few of the many fine features of the TR-7500. The PS-6 is the handsomely styled, matching power supply for the TR-7500. Its 3.5 amp current capacity and built-in speaker make it the perfect companion for home use of the TR-7500.



# TR-2200A

The high performance portable 2-meter FM transceiver. 146-148 MHz, 12 channels (6 supplied), 2 watts or 400 mW RF output. Everything you need is included: Ni-Cad battery pack, charger, carrying case and microphone.

# KENWOOD

...pacesetter in amateur radio

Kenwood developed the T-599D transmitter and R-599D receiver for the most discriminating amateur.

The R-599D is the most complete receiver ever offered. It is entirely solid-state, superbly reliable and compact. It covers the full amateur band, 10 through 160 meters, CW, LSB, USB, AM and FM.

The T-599D is solid-state with the exception of only three tubes, has built-in power supply and full metering. It operates CW, LSB, USB and AM and, of course, is a perfect match to the R-599D receiver.

If you have never considered the advantages of operating a receiver/transmitter combination... maybe you should.

Because of the larger number of controls and dual VFOs the combination offers flexibility impossible to duplicate with a transceiver.

Compare the specs of the R-599D and the T-599D with any other brand. Remember, the R-599D is all solid state (and includes four filters). Your choice will obviously be the Kenwood.



## R-599D

## T-599D

## R-300

Dependable operation, superior specifications and excellent features make the R-300 an unexcelled value for the shortwave listener. It offers full band coverage with a frequency range of 170 KHz to 30.0 MHz • Receives AM, SSB and CW • Features large, easy to read drum dials with fast smooth dial action • Band spread is calibrated for the 10 foreign broadcast bands, easily tuned with the use of a built-in 500 KHz calibrator • Automatic noise limiter • 3-way power supply system (AC/Batteries/External DC) take it anywhere • Automatically switches to battery power in the event of AC power failure.





*Fine equipment that belongs in every  
well equipped station*

#### HF LINES

##### 820 Series

- TS-820S... TS-820 with Digital  
Installed
- TS-820... 10-160 M Deluxe  
Transceiver
- DG-1... Digital Frequency Display  
for TS-820
- VFO-820... Deluxe Remote VFO for  
TS-820/820S
- CW-820... 500 Hz CW Filter for  
TS-820/820S
- DS-1A... DC-DC Converter for  
520/820 Series

##### 520 Series

- TS-520S... 160-10 M Transceiver
- DG-5... Digital Frequency Display  
for TS-520 Series
- VFO-520... Remote VFO for TS-520  
and TS-520S
- SP-520... External Speaker for  
520/820 Series
- CW-520... 500 Hz CW Filter for  
TS-520/520S
- DK-520... Digital Adaptor Kit for  
TS-520

##### 599D Series

- R-599D... 160-10 M Solid State  
Receiver
- T-599D... 80-10 M Matching  
Transmitter
- S-599... External Speaker for 599D  
Series

- CC-29A... 2 Meter Converter for  
R-599D

- CC-69... 6 Meter Converter for  
R-599D

- FM-599A... FM Filter for R-599D

#### SHORT WAVE LISTENING

- R-300 General Coverage SWL Receiver

#### VHF LINES

- TS-600... 6 M All Mode Transceiver
- TS-700S... 2 M All Mode Digital  
Transceiver
- VFO-700S... Remote VFO for TS-700S
- SP-70... Matching Speaker for  
TS-600/700 Series
- TR-2200A... 2 M Portable FM  
Transceiver
- TR-7400A... 2 M Synthesized Deluxe  
FM Transceiver

- TR-7500... 100 Channel Synthesized  
2 M FM Transceiver

- TR-8300... 70 CM FM Transceiver  
(450 MHz)

- TV-506... 6 M Transverter for  
520/820/599 Series


#### POPULAR STATION ACCESSORIES

- HS-4... Headphone Set
- MB-1A... Mounting Bracket for  
TR-2200A
- MC-50... Desk Microphone
- PS-5... Power Supply for TR-8300
- PS-6... Power Supply for TR-7500
- PS-8... Power Supply for TR-7400A
- VOX-3... VOX for TS-600/700A

Trio-Kenwood stocks a complete line of  
replacement parts, accessories, and manuals  
for all Kenwood models.

#### MORE ACCESSORIES:

Description	Model #	For use with
Rubber Helical Antenna	RA-1	TR-2200A
Telescoping Whip Antenna	T90-0082-05	TR-2200A
Ni-Cad Battery Pack (set)	PB-15	TR-2200A
4 Pin Mic. Connector	E07-0403-05	All Models
Active Filter Elements	See Service Manual	TR-7400A
Tone Burst Modules	See Service Manual	TS-700A; TR-7400A
AC Cables	Specify Model	All Models
DC Cables	Specify Model	All Models

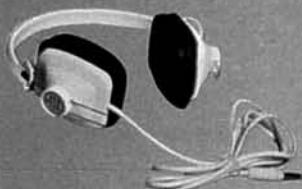

The Kenwood HS-4 headphone set adds  
versatility to any Kenwood station. For  
extended periods of wear, the HS-4 is com-  
fortably padded and is completely adjustable. The  
frequency response of the HS-4 is tailored  
specifically for amateur communication use.  
(300 to 3000 Hz, 8 ohms).



The MC-50 dynamic microphone has been  
designed expressly for amateur radio operation  
as a splendid addition to any Kenwood shack.  
Complete with PTT and LOCK switches, and a  
microphone plug for instant hook-up to any  
Kenwood rig. Easily converted to high or low  
impedance. (600 or 50k ohm)

TRIO-KENWOOD COMMUNICATIONS INC.  
1111 WEST WALNUT/COMPTON, CA 90220

**KENWOOD**  
...pioneer in amateur radio



# QSA 599

Amateur Radio Center  
11 S. Morris, Mesa, AZ 85202

(602)833-8051



## 1.1 GHz Portable Counter

PROFESSIONAL QUALITY BUT AFFORDABLE!

### Specifications

No Pre-Scaler Needed  
Calibrated to .0002%  
Rechargeable Ni-Cd Pack Built In  
Weight: 2 lb. 1 oz. Size: 4"x4.15"x7"  
Front Panel FAA Approved Lettering  
Guaranteed One Year Parts and Labor  
Price: \$599.95 postpaid

## EIMAC Tubes

New with Guarantee

3-400Z	\$67.00	4CX250B	\$43.00
3-500Z	\$67.00	4-400A	\$74.00
3-1000Z	\$165.00	4-1000A	\$221.00
7289	\$56.50	8874	\$116.00
8873	\$116.00	8877	\$260.00

## HY-GAIN

TH6DXX	\$249.95	5 element, 2m	\$16.95
TH3MK3	\$199.95	14 element, 2m	\$27.95
Hy Tower	\$279.95	14RMQ	\$28.95
18AVT/WB	\$97.00	14AVQ/WB	\$67.00

## WILSON

1402SM	2.5W Handheld, 2m	\$212.00
1405SM	1W/5W Handheld, 2m	\$279.00
4502SM	1W/1.8W Handheld, 70cm	\$349.00
WR-500	Rotor	\$149.95
SY-1	Deluxe Triband Beam	\$259.95

## USED EQUIPMENT

AM-479/GR serial number 1, 5KW Amplifier;  
with MD-135/GR & 4 new 4-1000A's \$3400.00\*  
Ballantine 300HS/2 VTVM calibrated \$75.00\*  
Ballantine 300HS/2 VTVM uncalibrated \$35.00\*  
Kay Mega-Sweep Model 111A \$175.00\*  
Antenna Tuner TN-339/GR \$85.00\*  
Transmitter T-368A/URT \$185.00\*  
WU Desk-Fax \$20.00\*  
Model 15 Printer (Teletype) \$45.00\*  
MORE! Write for free list.

\* Allow for shipping charges.

## PARTS

## PARTS

## PARTS

Air Variable Capacitors ■ Vacuum Variable  
Capacitors ■ Roller Inductors ■ New Tubes  
Used Tubes ■ Transformers ■ Miniductors  
Chokes ■ Ceramic Standoffs ■ RF Switches

MORE! Write for free list or quotes.

## MAKE CW MORE ENJOYABLE



## MVD-1000 MORSE VIDEO DISPLAY

- Enjoy Morse Code copy on your TV screen
- Displays letters, numbers, and punctuation
- 16 lines of 32 characters per page
- 2 page display with Recall feature
- Automatic scrolling
- Automatic or Manual speed control
- Copy Morse Code from 6-60 WPM
- Easily connects between receiver and TV set

ONLY \$350



## MK-1 REPROGRAMMABLE MEMORY KEYS

- Stores up to 100 characters
- Iambic keying, dot, dash memories
- Dual keyed outputs
- Operates on 120 VAC or 12 VDC

ONLY \$169.95

## CMOS KEYS, ASSEMBLED PCB ONLY \$24.95


## MORSE KEYBOARD COMING SOON

Wisconsin residents add 4% sales tax

**DGM ELECTRONICS**

787 BRIAR LANE, BELOIT, WISCONSIN 53511

## K-ENTERPRISES

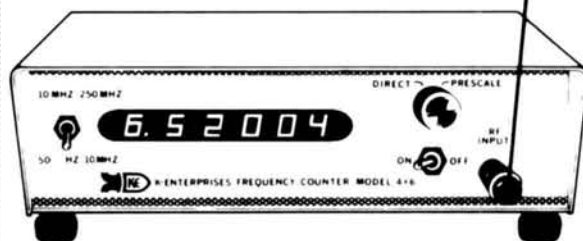

## MODEL 4X6C

50 HZ—250 MHZ ..... \$270.00

## 300 and 500 MHZ PRESCALERS

## FREQUENCY STANDARDS

## MARKER and PEAKING GENERATORS

## POWER SUPPLIES AMPLIFIERS

## WRITE FOR FREE CATALOG



Phone:  
918-676-3752



## K-ENTERPRISES

Box 410 (N.W. of town)

FAIRLAND, OK 74343

# Great gift ideas from Ham Radio's Bookstore



## ☐ 1978 ARRL RADIO AMATEUR'S HANDBOOK

World's best selling technical reference; a standard for every Radio Amateur's bookshelf. Revised and updated with state of the art technology. Guaranteed to please every ham. Softbound.

(AR-HB) \$8.50

## ☐ AMATEUR SINGLE SIDEBAND

Originally published by Collins Radio Company, reissued by tremendous popular demand. The bible of SSB; a complete intro to SSB and its equipment. Softbound.

(HR-SSB) \$4.95

## ☐ RADIO HANDBOOK 20th Edition

Famous communications handbook for engineers and Amateurs alike. How to design and build radio communications equipment and accessories.

**Holiday Special Save \$2.00**  
(24032) Only \$17.50

## ☐ 1978 US RADIO AMATEUR CALLBOOK

Brand new format! Calls in new bold-face, large, easy to read type. Over 350,000 entries vs. 303,000 last year. Thousands of new hams and new 1 X 2 calls. Same price as before.

(CB-US) Only \$14.95

(Please include \$1.50 shipping and handling)

## ☐ Two Volume 5th Edition RADIO COMMUNICATIONS HANDBOOK

Completely revised edition from the RSGB. One of the most thorough and handsome books in Amateur Radio. The perfect gift.

(RS-RCH12) Only \$29.95

## ☐ 3rd Edition ELECTRONIC COMMUNICATION

The most fantastic Amateur and commercial license study guide we know of! Comprehensive, includes questions and answers.

(MH-57138) Only \$18.95

## ☐ TUNE IN THE WORLD WITH HAM RADIO

Tells you what Amateur Radio is, how to pass the Novice exam and set-up your first station. Includes booklet, code cassette and map.

(AR-HR) \$7.00

## ☐ OSCAR-AMATEUR RADIO SATELLITES

The comprehensive book on Amateur satellites. Learn the principles, then examine OSCAR from concept to actual use. Softbound.

(RS-O) \$8.50

## ☐ Ham Radio HORIZONS Magazine

☐ One Year...\$10.00 (12 issues) ☐ Three Years...\$24.00 (36 issues)

## ☐ HAM RADIO Magazine

☐ 1 yr....\$12.00 (12 issues) ☐ 2 yrs....\$22.00 (24 issues) ☐ 3 yrs....\$30.00 (36 issues)



\*Please enclose names and addresses on all gift subscriptions.

## ☐ THE FRENCH ATLANTIC AFFAIR

International suspense and romance in a dynamic novel where Amateur Radio is the hero. A real spellbinder!

(A-FAA) \$10.95

(Much sex and violence; for mature readers only)

## ☐ 80 METER DXing

A must for every DX'er. A foremost authority has compiled many of his secrets into this book. Meet this exciting challenge and get the most from your station.

(HR-80M) \$4.50

Yes! Please enter my order as checked on the boxes by each book on this page.

Number of books checked \_\_\_\_\_ Total amount \$ \_\_\_\_\_

☐ Check or money order enclosed

☐ Charge my Mastercharge

☐ Charge my VISA (BAC)

Acct. No. \_\_\_\_\_ Exp. \_\_\_\_\_ Interbank No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Send to: **HAM RADIO'S BOOKSTORE**  
GREENVILLE, NH 03048

or call **TOLL FREE 800-258-5353**



For literature on any of the new products, use our **Check-Off** service on page 150.

## crystal filters


Sherwood Engineering has announced two new additions to their crystal filter line. As complements to the CF-600/6, the new CF-2.6K/8 or CF-2.3K/8 crystal filter sets will replace the normal 8-kHz wide first i-f filter in the Drake R-4C. Each set has two filters, USB and LSB, that must be switched for the correct sideband. The individual filters are 8-pole crystal-ladder filters.

The CF-2.6K/8 is a set of ssb-bandwidth filters that are approximately 200 Hz wider than the normal second i-f phone filter. This allows a limited amount of passband tuning, while still reducing the second i-f bandwidth from 32 kHz, at -60 dB, to approximately 4 kHz. The other phone filter pair is the CF-2.3K/8, which is slightly narrower (100 Hz nominally) than the second i-f filter. Having the new filter sharper than the normal filter produces the equivalent of a 2 to 2.1 kHz filter, with 16 poles distributed over two frequencies. The passband tuning is then used to align the center frequencies, of the two filters, for proper cascading. This narrow combination offers the ultimate in phone selectivity. The bandwidth using the CF-2.6K/8, with the normal phone filter, is 2.3 kHz, at -6 dB, and 3.1 kHz at -60 dB; the bandwidth for the CF-2.3K/8 is 2.1 kHz and 2.9 kHz, at the 6 and 60 dB points. The additional advantages gained by dis-

tributing selectivity over two i-f frequencies are: virtual elimination of the chance of overloading the second mixer, and elimination of off-frequency signals that leak around the normal second i-f filter.

In addition to offering the basic filters, Sherwood Engineering also sells switching kits for the first i-f filters. The simplest arrangement is for the operator who wants to switch only between the two ssb bandwidth filters (CF-2.3K/8 or CF-2.6K/8). Custom-designed kits are also available to permit switching of all first i-f filters, 8 kHz, 2.6/2.3 kHz, or 600 Hz. Prices for the new filters are \$120. The basic switching kit is \$29.00 with the cost increasing approximately \$25.00 per additional filter switched. Exact price quotes are given based on an individual's needs. For more information, contact Sherwood Engineering, Incorporated, 1268 South Ogden Street, Denver, Colorado 80210.

## two-meter preamplifier

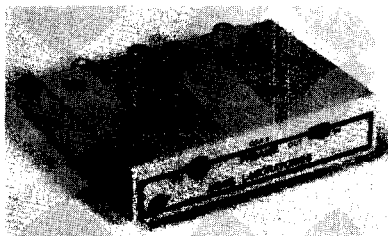

A new two-meter preamp has been introduced by Janel Labs. This preamp is specially designed to improve the sensitivity of transceivers and includes bypass circuitry for carrying transmit power through the unit. The preamp has a low noise figure, which gives excellent sensitivity for weak signals. An adjustable delay circuit (similar to that used in VOX circuits) allows for its use on all modes — f-m, ssb, am and CW.


The gain of the QSA 5 has been optimized for transceivers. It has a 15-dB gain level, which is sufficient to improve the sensitivity as much as practical but low enough to avoid creating overload problems.

A front-panel switch on the QSA 5

disables the preamp from the antenna line. This switch allows you to reduce gain on local signals and also allows experimentation on weak signals. A LED pilot light indicates when the preamp is in the line. This same LED also indicates when transmit power is being sensed.

The QSA 5 preamp is available from Janel Laboratories, 3312 S.E. Van Buren Blvd., Corvallis, Oregon 97330. The QSA 5 is available from stock at \$39.95 plus postage. A full one-year warranty is provided. Specifications are available upon request.
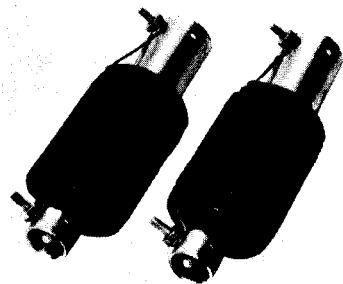
## multiband antenna coils (40 through 10 meters)



Microwave Filter Company announces a set of antenna coils that will convert an amateur antenna from a single-frequency band of limited operation to operation on all amateur hf bands (40-10 meters).


Known as Reyco antenna coils, they are designed to shorten the overall physical length of an original single-frequency-band antenna. Model numbers are KW-40, 20, 15, and 10. Used in pairs, the model KW-40 coils will give flexibility of operation on all five hf amateur bands. Ideal performance is obtained by using all four coil pairs (KW-40 through KW-10).

In today's crowded apartment and suburban communities, the shortened antenna using Reyco multiband coils provides flexibility in minimum space. For additional information, write Microwave Filter Company, 6743 Kinne Street, East Syracuse, New York 13057.

# All in the family.

## Feather Touch Keyer


\$69.95

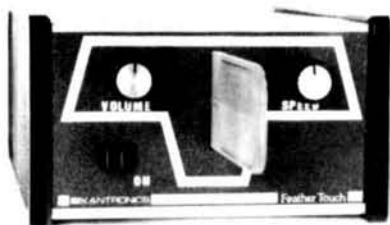

No moving parts! The **Kantronics Feather Touch Keyer** responds to the lightest touch. No more slapping or sloshing! No moving parts also means the end of adjusting and readjusting before each QSO.

The **Feather Touch** sends self completing dots and dashes, adjustable from 7½ WPM, and gives you a great fist on the air. Attractive design and compact size make the **Feather Touch** a professional addition to the sharpest ham station. Design features keep the keyer from creeping away as you send.

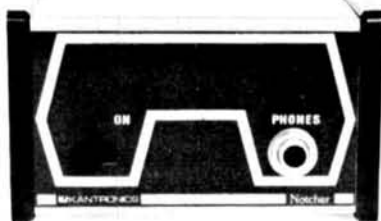This **battery powered** unit is great for portable use or home operation with the aid of any DC power supply from 5-15 volts. Pick up a motionless keyer today!



## Notcher CW Filter \$34.95


Make your CW receiver selectivity razor sharp with the **Kantronics Notcher Audio CW Filter**. This filter makes sense out of the biggest pileups! The **Notcher** funnels down to 150 Hz @ -3dB to separate signals that appeared to be on top of each other before.

Your **Notcher** will operate portable with a 9 volt internal battery, or from your 5-15 volt DC power supply.

**Designed to look sharp too**, the **Notcher** is one in a growing family of **Kantronics** quality products. Our quality is more than skin deep. One look inside will tell you the **Notcher** is built to perform!

## The Standard Frequency Calibrator

\$39.95

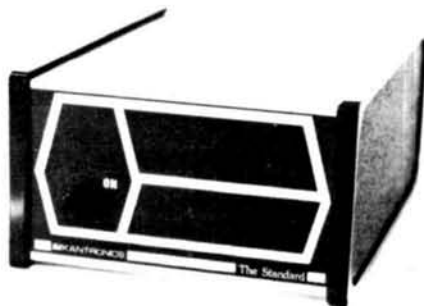

**Kantronics** frequency calibrator is **The Standard**. Advanced CMOS circuitry checks your frequency with crystal controlled accuracy. Zero beat your transceiver to **The Standard** at 50 KHz intervals.

No direct connections are needed, the unit transmits to your receiver. Internal jumpers adjust **The Standard** for a choice of 25 KHz, 50 KHz or 100 KHz intervals.

**Powered by battery for portable operation**, or 5-15 volt DC power supply. **The Standard** is a handsome station accessory that looks sharp, inside and out.

Be confident of your frequency.

## Magnetic Mount



The **Kantronics Mobile 2 Antenna** offers a reasonable alternative to the high priced VHF antenna! The **Mobile 2** is a high-quality, quarter-wavelength antenna that is quickly installed.

Choose between **magnetic or trunk mounting** bases. Both include 18 feet of RG-58/U coax cable and standard PL-259 connector. Specify 147 MHz or 220 MHz whip and coil assembly.

**All these features . . . for a low, low price!**



## Trunk Mount

The **Kantronics Code Speed-Building Kit** offers perfect **computer generated** code. Code is sent to exact Morse specifications as used by the FCC. Choose 5, 7½, 10, 13, 16 or 20 words per minute tapes. Oscillator and brass key included.



## KANTRONICS The Lightweight Champs.

1202 East 23rd Street Lawrence, Kansas 66044

Name			
Address			
City	State	Zip	
Card No.	Expires		
<input type="checkbox"/> Code Kit with _____ WPM tape - \$19.95 <input type="checkbox"/> Notcher - \$34.95 <input type="checkbox"/> Feather Touch - \$69.95 <input type="checkbox"/> Mobile 2 Trunk - \$6.95 <input type="checkbox"/> The Standard - \$39.95 <input type="checkbox"/> Mobile 2 Magnetic - \$14.95 <input type="checkbox"/> Whip and Coil - \$4.95      147      220			
KS & MO add 3% sales tax			
Master Charge, Visa, check or money orders only!			

(913) 842-7745



# The New Sigma XR3000D Linear Amplifier Compare!




HOLIDAY SALE

**\$699**

2 Day Air Shipment  
Anywhere in U.S.

Airport to Airport \$35

Alaska and Hawaii Slightly Higher

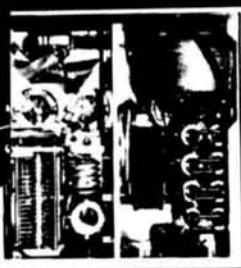

## Features:

Custom computer grade commercial components, capacitors, and tube sockets manufactured especially for high power use—heavy duty 10Kw silver plated ceramic band switches • Silver plated copper tubing tank coil • Huge 4" easy to read meters—measure plate current, high voltage, grid current, and relative RF output • Continuous duty power supply built in • State of the art zener diode standby and operating bias provides reduced idling current and greater output efficiency • Built in hum free DC heavy duty antenna change-over relays • AC input 110V or 220V AC, 50-60Hz • Tuned input circuits • ALC-rear panel connections for ALC output to exciter and for relay control • Double internal shielding of all RF enclosures • Heavy duty chassis and cabinet construction and much, much more.

- Full band coverage 160-10 meters including mars.
- 2000 watts P.E.P. SSB input. 1000 watts input continuous duty, CW, RTTY & SSTV.
- Two Eimac 3-500Z conservatively rated finals.
- All major HV and other circuit components mounted on single G-10 glass plug in board. Have a service problem? (Very unlikely) Just unplug board and send to us.
- Heavy duty commercial grade quality and construction second to no other unit at any price!
- Weight: 90 lbs. Size: 9 1/2" (h) x 16" (w) x 15 3/4" (d).

## HOLIDAY INTRODUCTORY SPECIAL!

### New! Sigma Model AF250L Deviation/Modulation Meter

Fully Certifiable for Commercial Use

#### Features:

Extremely stable local oscillator for easy measurement of HF, VHF, and UHF bands employing negative feedback to insure extremely high stability • Easy to read, accurate linear scale • Direct off the air signal measurement capability.

HOLIDAY SALE

**\$169**



#### Specifications:

Frequency: 1.8MHz-520MHz/3 range select (A, B, C, EXT). A range: 26.5 MHz-40MHz, B range: 48MHz-60MHz, C range: 140MHz-156MHz, EXT. range: 1.8MHz-520MHz (Need Signal Generator) • Generous overranges • Input level: (1) Through type input level: 1W-200W (RF Input Terminal) (2) Direct input level: More than 80db/50ohm impedance • Amplitude modulation degree: 0-100% • Frequency deviation: 0-20KHz • Accuracy: +/- 3% of full scale • Intermediate frequency: 10.7MHz • Local input frequency (EXT Range) • Measuring frequency +/- 10.7MHz • RF Attenuator: 0-60db variable • Audio signal oscillator: (1) Audio Frequency—1,000Hz (1 KHz), (2) Output level—More than 1V RMS • Power Source: AC117V • Dimensions: H-5 1/2" (140mm), W-10 1/4" (260mm), D-7 1/4" (184mm) • Weight: 7 lbs.

## SIGMA RF-2000 SWR & POWER METER



**\$29**

Introductory Price



Cal PWR Scales 200W-2000W Freq Range 3.5-150 MHz. Please do not confuse the RF2000 with similar appearing lower priced units. RF2000 is an individually calibrated professional quality instrument. Unequaled at many times the price. Size 7" (w) x 2 1/3" (d).

## SPECIAL SCANNER SALE

FOR KENWOOD TR-7400A



14 Channel Programmable  
reg \$109 — **\$65**



FMSC-1 reg \$169 — **\$99**  
7400 Scanner II Reg \$189-\$119

FMSC-1 Scanner for KDK FM 144 and 7400 Scanner II for Trio-Kenwood TR-7400A. • Full scan 146 and 147 MHz consecutively or 1 MHz, or any MHz range • Scan rate: 1 MHz/2 seconds (adjustable) • Controls: Scan/Hold, Latch/Delay, 600 KHz offset (off, up, down), program 1 MHz • Simple installation.



## SPECIAL SALE FM 144 Accessories

FMT-1 Touch Tone Pad	\$59
FMT-2 Touch Tone Pad with 10 Number Programmable Memory	\$99
FMTD-1 Private Call Decoder for use with and Programmed by Any Touch Tone Pad	\$75
SC-12A Audible Tone Encoder Decoder	\$65
FMSC-1 Scanner-Random Any Range, Any Split	\$99
MARS-CAP Option Kit - Any Frequency.	\$12
FMOF-1 Offset Option Kit - 2 Extra Positions, Crystals Required	\$10

FMOF-2 1 MHz Offset Option Kit (No Crystals to Buy)	\$10
FMT-1 Sub Audible Tone (100 Hz-Adjustable 67-203 Hz)	\$15
Owners Manual (Extra)	\$5
FM 2015R Accessories:	
FMPS-4R Regulated AC PS	\$49
FMSC-1 Microphone with Built-in Touch Tone Pad	\$49
MARS-CAP* Option Kit - Any Frequency, Any Split	\$6
FMT-1 1/2 Wave Portable Antenna for Hotel, Motel or Apartment	\$7.95
Extra DC Cord & Plug	\$3.50
Service Manual	\$2.00
Mounting Bracket (Extra)	\$6.00

## Standard New 2 Meter FM Transceivers Model SRC 146A Special Sale

SRC 146A	\$314
4 Xtlals 34/94 and 94/94	NC
USA 2 Deluxe Base Charger	\$47
PT3644 Leather Case	\$12
AT 19 Rubber Ant and Whip	\$10
N1-cads	\$30



NEW!!! Touch Tone pad completely wired and ready to plug in—\$69.00

Reg. \$413  
Our Price **\$289**

## NEW! 6 METER FM50-10SXRII



51.00-53.995 MHz. 600 channels  
Holiday Sale—Price **\$339**

NEW CDE HAM III ROTATORS—  
Reg. \$159.95—\$125



Atlas 210X-215X and 350-XL  
Please write for special bonus and package offers.

# AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176

COURTEOUS PERSONAL SERVICE—SAME DAY SHIPMENT • Prices subject to change without notice.

Telephone: (305) 233-3631 • Telex 51-5628 • Store Hours: 10-5 Mon.-Fri.



# NEW! THE FUTURE NOW! FM2015R



Does Your Unit Cover The New  
Sub-band 144.5 - 145.5 MHz?  
The FM2015R Does, PLUS MARS-CAP!

All Solid State-CMOS PLL digital synthesized - No Crystals to Buy! 5KHz steps - 144 - 149 MHz-LED digital readout PLUS MARS-CAP.\*

● 5 MHz Band Coverage - 1000 Channels (instead of the usual 2MHz to 4MHz-400 to 800 Channels) ● 4 CHANNEL RAM IC MEMORY WITH SCANNING ● MULTIPLE FREQUENCY OFFSETS ● ELECTRONIC AUTO TUNING - TRANSMIT AND RECEIVE ● INTERNAL MULTIPURPOSE TONE OSCILLATOR ● RIT ● DISCRIMINATOR METER - 15 Watts Output - Unequaled Receiver Sensitivity and Selectivity - 15 POLE FILTER, MONOLITHIC CRYSTAL FILTER AND AUTOMATIC TUNED RECEIVER FRONT END, COMPARE! ● Superb Engineering and Superior Commercial Avionics Grade Quality and Construction Second to None at ANY PRICE.

INTRODUCTORY  
PRICE

**\$399<sup>00</sup>**

Regulated AC/PS  
Model FMPS-4R... \$49.00



FMMC-1 Micro-  
phone with Built-in  
Touch Tone Pad.

- LED indicator
- Adj. level and tone balance
- only 3-3/4" x 2"

**\$49<sup>00</sup>**

- **FREQUENCY RANGE:** Receive and Transmit: 144.00 to 148.995 MHz, 5KHz steps (1000 channels) INCLUDING NEW BAND 144.5-145.5MHz + MARS-CAP.\*
- **LED DIGITAL READOUT.**
- **4 CHANNEL RAM SCANNER WITH IC MEMORY:** Program any 4 frequencies and reprogram at any time using the front panel controls-scan all or part of the memory-search for occupied (closed) channel or vacant (open) channels. Internal Ni-Cad included to retain memory (no diode matrix to wire or change).
- **MULTIPLE FREQUENCY OFFSETS:** Three positions A,B,C, provided for installation of optional crystals: EXAMPLE - 1 MHz offset. Duplex Frequency Offset Built in - 600 KHz PLUS or MINUS 5 KHz steps, plus simplex, any frequency.
- **INTERNAL MULTIPURPOSE TONE OSCILLATOR BUILT IN:** 1750Hz tone burst for "whistle on operation" and sub-audible tone operation possible by simply adding a capacitor across the terminals provided. Internal 2 position switch for automatic and manual operation, tone burst or sub audible tone PL - adjustable 60-203Hz (100 Hz provided).
- **AIRCRAFT TYPE FREQUENCY SELECTOR:** Large and small coaxially mounted knobs select 100KHz and 10KHz steps respectively. Switches click-stopped with a home position facilitate frequency changing without need to view LED's while driving and provides the sightless amateur with full Braille dial as standard equipment.
- **FULL AUTOMATIC TUNING OF RECEIVER FRONT END AND TRANSMITTER CIRCUITS:** DC output of PLL fed to varactor diodes in all front end RF tuned circuits provides full sensitivity and optimum intermodulation rejection over the entire band. APC(AUTO POWER CONTROL) - Keeps RF output constant from band edge to band edge. NO OTHER AMATEUR UNIT AT ANY PRICE has these

features which are found in only the most sophisticated and expensive aircraft and commercial transceivers.

- **TRUE FM:** Not phase modulation - for superb emphasized hi-fi audio quality second to none.
- **RIT CONTROL:** Used to improve clarity when contacting stations with off frequency carrier.
- **MONITOR LAMPS:** 2 LED's on front panel indicate (1) incoming signal-channel busy, and (2) Transmit.
- **FULLY REGULATED INTEGRAL POWER SUPPLY:** Operating voltage for all 9v circuits independently regulated. Massive Commercial Hash Filter.
- **MODULAR COMMERCIAL GRADE CONSTRUCTION:** 6 Unitized modules eliminate stray coupling and facilitate ease of maintenance.
- **ACCESSORY SOCKET:** Fully wired for touch tone, phone patch, and other accessories. Internal switch connects receiver output to internal speaker when connector is not in use.
- **MULTI-PURPOSE METER:** Triple Function Meter Provides Discriminator Meter, "S" Reading on receive and Power Out on Transmit.
- **RECEIVE:** Better than .25uv sensitivity, 15 POLE FILTER as well as monolithic crystal filter and AUTOMATIC TUNED LC circuits provide superior skirt selectivity - COMPARE!
- **HIGH/LOW POWER OUTPUT:** 15 watts and 1 watt, switch selected. Low power may be adjusted anywhere between 1 and 15 watts. Fully protected-short or open SWR.
- **OTHER FEATURES:** Dynamic Microphone, Built In Speaker, mobile mount, external 5 pin accessory jack, speaker jack, and much, much more. Size 2 1/2 x 7 x 7 1/2. All cords, plugs, fuses, microphone hanger, etc. included. Weight 5 lbs.

Manufactured by one of the world's most distinguished Avionics manufacturers, Kyokuto Denshi Kaisha, Ltd.  
First in the world with an all solid state 2 meter FM transceiver.



## AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176 DEALER INQUIRIES INVITED.  
Telephone (305) 233-3631 • Telex: 51-5628  
U.S. DISTRIBUTOR PLEASE ORDER FROM YOUR LOCAL  
DEALER OR DIRECT IF UNAVAILABLE.

Regional Sales & Service Centers:  
Northeast: Buzzards Bay Electronics  
Buzzards Bay, Mass.  
(617) 759-3376  
East: Sanford Communications, Inc.  
Colonie, N.J.  
(201) 674-3003  
Midwest: Universal Service  
Columbus, Ohio  
(614) 221-2336

Plug it in like a key and send perfectly timed Morse code as easily as typing a letter. Sidetone and buffer register make it simple to send at the speed you select.

## KEYBOARD TO MORSE CODE

# ATRONICS

BOX 2946, LAGUNA HILLS, CA 92653

(714) 830-6428

Available directly from the factory for only \$225 plus postage & handling. MasterCard or BankAmericard accepted. Call or write to order or request complete specifications and options.

## QUALITY KENWOOD TRANSCEIVERS ... from KLAUS RADIO

The TS-820 is the rig that is the talk of the Ham Bands. Too many built-in features to list here. What a rig and only \$830.00 ppd. in U.S.A. Many accessories are also available to increase your operating pleasure and station versatility.



TS-820S  
160-10M TRANSCEIVER

Super 2-meter operating capability is yours with this ultimate design. Operates all modes: SSB (upper & lower), FM, AM and CW. 4 MHz coverage (144 to 148 MHz). The combination of this unit's many exciting features with the quality & reliability that is inherent in Kenwood equipment is yours for only \$599.00 ppd. in U.S.A.



TS-700A  
2M TRANSCEIVER

Guess which transceiver has made the Kenwood name near and dear to Amateur operators, probably more than any other piece of equipment? That's right, the TS-520. Reliability is the name of this rig in capital letters. 80 thru 10 meters with many, many built-in features for only \$629.00 ppd. in U.S.A.



TS-520S  
80-10M TRANSCEIVER

This brand new mobile transceiver (TR-7400A) with the astonishing price tag is causing quite a commotion. Two meters with 25W or 10W output (selectable), digital read-out, 144 through 148 MHz and 800 channels are some of the features that make this such a great buy at \$399.00 ppd. in U.S.A.



TR-7400A  
2M MOBILE TRANSCEIVER


Send SASE NOW for detailed info on these systems as well as on many other fine lines. Or, better still, visit our store Monday thru Friday from 8:00 a.m. thru 5:00 p.m. The Amateurs at Klaus Radio are here to assist you in the selection of the optimum unit to fulfill your needs.

# KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria, IL 61614  
Jim Plack W9NWE — Phone 309-691-4840

## SUB-AUDIBLE GENERATOR for FM

THE CUBE

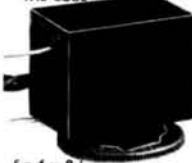

5 x 6 x 8 in.

- Inexpensive multi tone encoder
- Compatible with PL-CG-QC
- Low distortion sinewave
- Input 8-18 VDC unregulated
- Rugged, plastic encased with leads
- Adjustable frequency (98-250 Hz), Lower available
- Excellent stability

Price \$19.95

Freq. set at factory \$5.00 extra

Calif. res. add 6%

Send for more info

lyle  
Products

Dept. hr P.O. Box 2083 Santa Clara, CA. 95051

## ROTOR PROTECTION WITH AUTOBRÄK DELAY



Have you had rotator damage? Removed the rotator? Been off the air? Waited for parts? No more! AUTOBRÄK is a complete conversion kit, including punched and finished cabinet for all HAM-M series 1 through 5 rotator control units.


AUTOBRÄK reduces the inherent problem of damaged rotator components due to instant brake engagement. AUTOBRÄK allows the antenna array to come to a coasting stop before brake engagement, thereby reducing stress on rotator components.

Other features include Zener regulated meter circuitry, adjustable brake delay, and handsome up-to-date styling compatible to most Ham gear. Cabinet measures 6"X7½"X7¼"

Price \$39.95. Shipping and handling \$1.75 in U.S. Illinois residents add 5% sales tax.

Kampp Electronics Inc.  
Box 43, Wheaton, IL 60187  
312-665-3556

# SST T-1 RANDOM WIRE ANTENNA TUNER

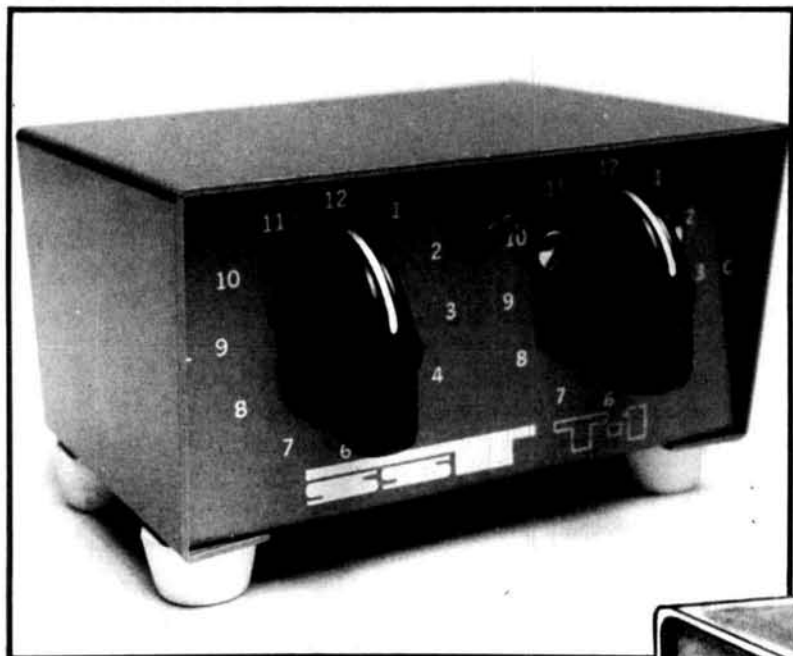

All band operation (160-10 meters) with any random length of wire. 200 watt **output** power capability—will work with virtually any transceiver. Ideal for portable or home operation. Great for apartments and hotel rooms—simply run a wire inside, out a window, or anyplace available. Toroid inductor for small size: 4-1/4" X 2-3/8" X 3." Built-in neon tune-up indicator. SO-239 connector. Attractive bronze finished enclosure.

only **\$29.95**


## sst t-2 ULTRA TUNER

Tunes out SWR on any coax fed antenna as well as random wires. Works great on all bands (160-10 meters) with any transceiver running up to 200 watts power output.

Increases usable bandwidth of any antenna. Tunes out SWR on mobile whips from inside your car.

Uses toroid inductor and specially made capacitors for small size: 5 1/4" x 2 1/4" x 2 1/2." Rugged, yet compact. Attractive bronze finished enclosure. SO-239 coax connectors are used for transmitter input and coax fed antennas. Convenient binding posts are provided for random wire and ground connections.

only **\$49.95**

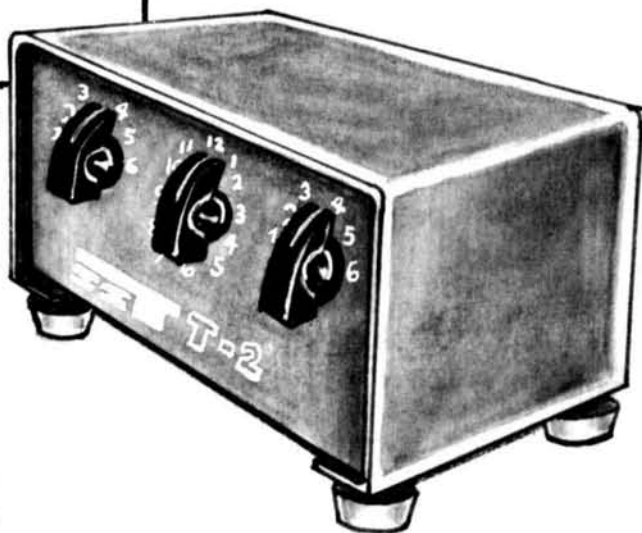

## sst t-3 IMPEDANCE TRANSFORMER

Matches 52 ohm coax to the lower impedance of a mobile whip or vertical. 12 position switch with taps spread between 3 and 52 ohms. Broadband from 1-30 MHz. Will work with virtually any transceiver—300 watt output power capability. SO-239 connectors. Toroid inductor for small size: 2-3/4" X 2" X 2-1/4." Attractive bronze finish.

only **\$19.95**

## GUARANTEE

All SST products are guaranteed for 1 year. In addition, they may be returned within 10 days for a full refund (less shipping) if you

you are not satisfied for any reason. Please add \$2 for shipping and handling. Calif. residents, please add sales tax. COD orders OK by phone.



**ELECTRONICS**

P.O. BOX 1 LAWDALE, CALIF.  
90260 (213) 376-5887

# PARTS PANIC!!

Having parts problems such as Minimum Orders, Unanswered Letters, Uninterested Suppliers, Too Much Time at Flea Markets?

Let G. R. Whitehouse & Co., the New Parts Specialists solve your problems.

## NOW IN STOCK

Transmitting Variables — Roller Inductors — Counter Dials  
Air Wound Coils — Couplings — Knobs — Receiving Variables  
Toroids — R.F. Chokes — Coil Forms and more

From


Millen - E. F. Johnson - Barker & Williamson - JW Miller - Hammarlund

Send First Class Stamp for Flyer

## G. R. WHITEHOUSE & CO.

10 NEWBURY DRIVE, AMHERST, N. H. 03031

"The Parts Finders"

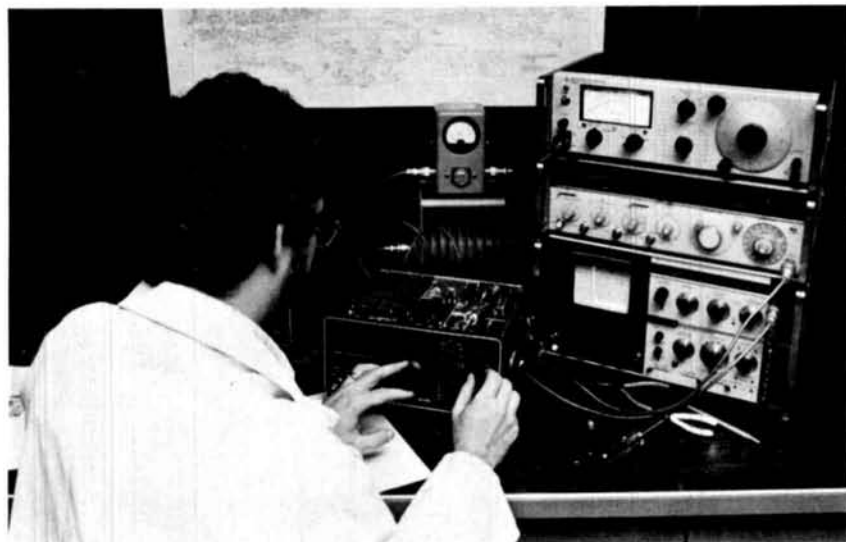


## Clegg won't sell you a radio in a factory sealed carton!

When you purchase your YAESU, WILSON, KLM, DENTRON, HY-GAIN, ATLAS or other selected product from Clegg, please don't expect to receive it in a factory sealed carton. When we deliver any of these fine pieces of equipment to you, we want to be certain it meets or exceeds all the manufacturers specs. First of all, we want to warrant that it does; secondly—you're entitled to that extra assurance! We thoroughly test each unit before we ship it. And we furnish you with test data:

If getting a super discount on your new radio is important to you—or if you insist on a factory sealed carton, we suggest you shop elsewhere. But—if you want the positive assurance that you are receiving the value and performance you're entitled to—then we are the guys to talk to.

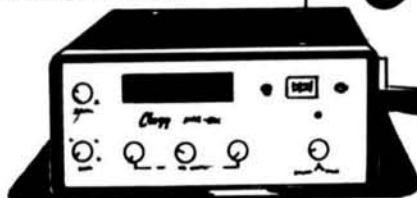For complete details and prices on any Clegg-approved product, telephone Toll Free 1-(800)-233-0250 (In Pennsylvania call Collect (717)-299-7221). Or drop a card to Clegg Communications Corp., 1911 Old Homestead Lane, Greenfield Industrial Park East, Lancaster, PA 17601.



## PARAFRAME

# PARABOLIC ANTENNA

## FRAMEWORKS

FOR...

- ☐ EME ☐ TV DXing
- ☐ Radio Astronomy
- ☐ Experimenting
- ☐ Student projects

Apertures available —

12', 16', 20' TBA: 24'

With PARAFRAME you can build a complete 20' parabolic antenna for \$1300. With interchangeable feeds you can have several antennas for the price of one.

## JAMES K. VINES

611 Farmview Rd.

Park Forest South, IL

60466

(312) 534-0889

after 7 PM CDT

## TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied — equipment being returned must be shipped prepaid. Include check or money order with order. Prices listed are FOB Monroe.

BOONTON 190A Q mtr 30-200MHz	\$425
FLUKE 803B Diff ac-dc vtm	295
GR916A RF Imp bridge 420kHz-60MHz	325
GR1001A LF sig gen 5kHz-50mHz	385
HP120B 450kHz gen pur scope	215
HP160B (USM105) 15mHz scope with reg horiz, dual trace vert plugs	375
HP166B (Mil) Delay sweep for above	130
HP170A (USM140) 30mHz scope with reg horiz, dual trace vert plugs	475
HP175A 50mHz scope with reg horiz, dual trace vert plugs	565
HP185A Sampling scope to 1 GHz	
186B xstr rise time plug	585
HP202B LF Osc 5Hz-50kHz 10v out	75
HP205AG Lab audio gen .02-20kHz	195
HP212A Pulse gen .06-5kHz PRR	65
HP524D Freq counter basic range 10Hz-10mHz extends w plug ins	195
HP540B Trans osc to 12.4GHz for use w HP524 type counters	145
HP616 Sig gen 1.8-4GHz FM CW	365
HP686 Sweep gen 8.2-12.4GHz sweep range 4.4mHz-4.4GHz	495
HP803A VHF Ant bridge 50-500mHz	135
HP2801A Prec dig thermometer 80 to 250 deg Cels with 1 osc. less sensors	1295
Tek181 Time mark scope calib	55
Tek190 Sig gen (const ampl) 50mHz	125
Tek 545 (mil vers by Hickok/Lavoie) 33MHz gen pur scope less plugin	495
Tek565 Dual beam 10mHz scope less plug ins (3 series)	625
Tek585 80MHz gen pur scope less plugin	645

For complete list of all test equipment send stamped, self-addressed envelope

## GRAY Electronics


P.O. Box 941, Monroe, Mich. 48161

Specializing in used test equipment.
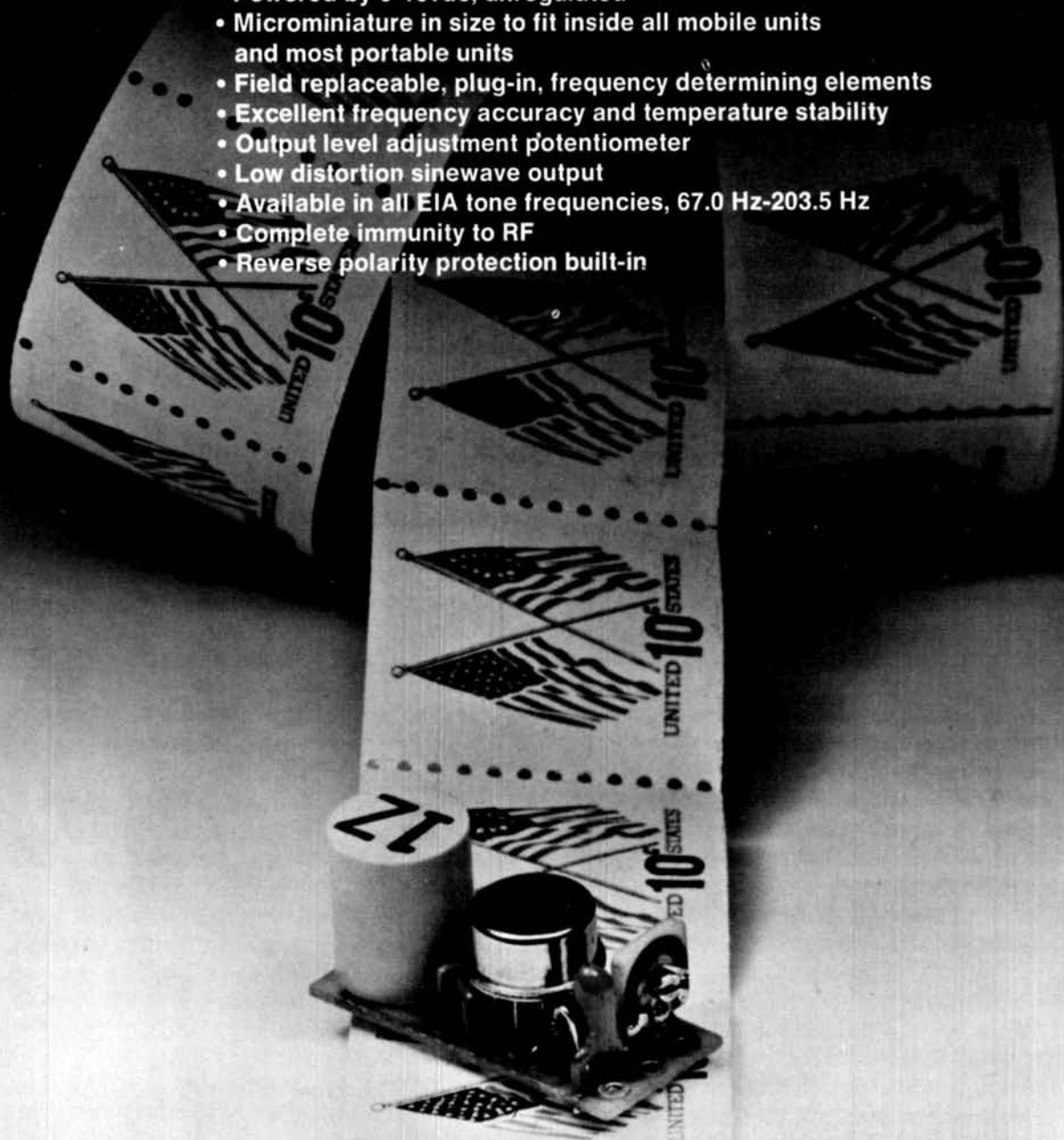
# ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16vdc, unregulated
- Microminiature in size to fit inside all mobile units and most portable units
- Field replaceable, plug-in, frequency determining elements
- Excellent frequency accuracy and temperature stability
- Output level adjustment potentiometer
- Low distortion sinewave output
- Available in all EIA tone frequencies, 67.0 Hz-203.5 Hz
- Complete immunity to RF
- Reverse polarity protection built-in



**\$29.95 each**

Wired and tested, complete with K-1 element

**communications specialists**

P. O. BOX 153  
BREA, CALIFORNIA 92621  
(714) 998-3021



K-1 FIELD REPLACEABLE,  
PLUG-IN, FREQUENCY  
DETERMINING ELEMENTS

**\$3.00 each**

## OLD TESTAMENT

**H**erefore the Lord himself shall give you a sign; Behold, a virgin shall conceive, and bear a son, and shall call his name Immanuel (which means God with us)."

Isaiah 7:14 740-687 BC

**B**ut thou Bethlehem, though thou be little among the thousands of Judah, from you shall come forth one who is to be ruler in Israel, whose origin is from old, from ancient days.

Micah 5:2 740 BC

## NEW TESTAMENT

"... the angel Gabriel was sent from God to a city of Galilee, to a virgin betrothed to Joseph, of the house of David; and the virgin's name was Mary... The angel said to her "Do not be afraid Mary, for you have found favor with God. And behold, you will conceive in your womb and bear a son, and you shall call his name Jesus."

Luke 1:27-31 70-90 AD

**K**ing Herod was troubled and inquired where the Christ was to be born. They told him in Bethlehem of Judea; for so it is written by the prophet (Micah).

Matthew 2:4-5 60-70 AD

Historical evidence clearly points to Jesus as the man God, who fulfills the literal prophecies of Isaiah and Micah within 800 years. The same God who chose the Virgin Mary to bear Jesus and who chose Bethlehem for the birthplace reveals himself in holy scripture today. We thank him for the birth of Christ this Christmas,

**Dentron**  
Radio Co., Inc.

2100 Enterprise Parkway  
Twinsburg, Ohio 44087  
(216) 425-3173

**ICOM**




**IC-22S**  
146 MHz FM 10 W  
TRANSCIVER



**IC-211**  
144 to 148 MHz  
SSB/FM/CW  
10 W TRANSCIVER

IMMEDIATE DELIVERY  
SHIPPING PREPAID IN USA

**MASTERS COMMUNICATIONS**  
"SINCE 1932"  
7025 N. 57th DR.  
GLENDALE, AZ 85301

PHONE  
602-939-8356

BankAmericard  
Master Charge

**TROUBLE FREE TOUCH-TONE ENCODER**



NEW  
PP-1K = \$55.00, PP-2K = \$58.00, PP-1A = \$64.00, PP-1M = \$55.00, PP-2M = \$58.00, M series-Mobile  
PP-1K = \$66.00, PP-2K = \$69.00, K-series = Self-Contained Delay Relay

NEW  
PP-1  
PP-2

See You at SAROC

Available at: Ham Radio Center (800) 325-3636  
Denver, CO, CW Electronics (303) 893-5525  
Medford, MA, Tufts (617) 394-8280  
Los Angeles, Henry Radio (213) 272-0861  
New York City, Harrison (800) 645-9187

**Pipo Communications**  
P.O. Box 3435 DEPT. B  
Hollywood, California 91608  
213/852-1515

**NEW FROM GLB**

A complete line of **QUALITY 50** thru 450 MHz **TRANSMITTER AND RECEIVER KITS**. Only two boards for a complete receiver. 4 pole crystal filter is standard. Use with our **CHANNELIZER** or your crystals. Priced from \$69.95. Matching transmitter strips. Easy construction, clean spectrum, **TWO WATTS** output, unsurpassed audio quality and built in **TONE PAD INTERFACE**. Priced from \$29.95.

**SYNTHESIZER KITS** from 50 to 450 MHz. Prices start at \$119.95.

Now available in **KIT FORM** — GLB Model 200 **MINI-SIZER**.

Fits any HT. Only 3.5 mA current drain. Kit price \$159.95 Wired and tested. \$239.95

Send for **FREE 16 page catalog**. We welcome Mastercharge or VISA

**GLB ELECTRONICS**  
1952 Clinton St., Buffalo, N. Y. 14206

# The Touch.

It's the best value available in scanners.



## Searching Receiver

Touch SP, then enter the starting frequency of your choice. The Touch will search up through the action radio channels in the search band until it hears an active call. You'll probably discover "live" frequencies you never before knew existed.

## Priority Receiver

Touch 2., then sit back. Any call coming in over the frequency you choose for channel one will automatically override calls on other channels. You'll never miss a call on your favorite frequency.

## Search or Scan

Touch SS to Search the unknown. Touch SC to scan the known. You can either search through all bands for unknown frequencies, or listen to the stored frequencies you've selected for the sixteen scanning channels. There's so much versatility, and it's all at the tip of your finger.

## Scanning Receiver

Touch PR, then enter the frequency you want as you watch it appear on the L.E.D. display. Next, touch the channel number you wish to use. Then touch SC, the scanning lights will begin the search for action.

Model ACT-T-16K

Selectivity

Frequency Range:

Lo VHF ... 30-50 MHz  
Hi VHF ... 146-174MHz  
UHF ... 440-512MHz

$\pm 7$  KHz (min.) @ 6 DB  
 $\pm 15$  KHz (max.) @ 60 DB

Squelch: (threshold)

Lo VHF ..... 0.4  $\mu$  V  
Hi VHF ..... 0.5  $\mu$  V  
UHF ..... 0.6  $\mu$  V

Sensitivity

(20 DB quieting)

Lo VHF ..... 0.5  $\mu$  V  
Hi VHF ..... 0.6  $\mu$  V  
UHF ..... 0.7  $\mu$  V

Search Scan Range: (max)


Lo VHF 4000 channels  
Hi VHF 5600 channels  
UHF 5760 channels

## REGENCY DIGITALLY PROGRAMMABLE SCANNER WITH KEYBOARD SPECIAL \$299

Master Charge & B of A  
We ship prepaid in USA  
Calif. residents add 6% tax  
Check with order or COD

10 day money back guarantee  
full satisfaction guaranteed  
Factory warranty on all items

IN STOCK FOR IMMEDIATE DELIVERY

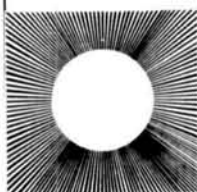

# WESTCOM

COMMUNICATIONS DIVISION 1320 Grand Ave. San Marcos, CA. 92069 (714) 744-0728

1-800-432-1234

1-800-233-0250

1-800-527-4634

1-800-645-9187

1-800-233-0250

1-800-432-1234

# Don't play the numbers!

## Just call us... Toll Free!

# 1-800-325-3636

**FOR NEW OR USED AMATEUR RADIO GEAR**... we're specialists and carry in stock most of the famous-brand lines. Or, we will talk trade.

**FOR FAST, DOOR-STEP DELIVERY**... give us a call. You'll be amazed: for we guarantee we'll ship your equipment the same day. Plus, most shipments are PRE-PAID.

**TO SAVE MONEY**... join thousands of our satisfied customers who buy from us as easily as from their local supplier. So, remember your call is Toll Free.



We welcome your Master Charge or VISA/BankAmericard.



## HAM RADIO CENTER, INC.

8340-42 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132

### YOU'VE SEEN THE MAGAZINE ARTICLES

Here's what you can expect from the **DX ENGINEERING** RF Speech Processor

- 6 db INCREASE IN AVERAGE POWER
- MAINTAINS VOICE QUALITY
- IMPROVES INTELLIGIBILITY
- NO CABLES OR BENCH SPACE REQUIRED
- EXCELLENT FOR PHONE PATCH
- NO ADDITIONAL ADJUSTMENTS — MIKE GAIN ADJUSTS CLIPPING LEVEL
- UNIQUE PLUG-IN UNIT — NO MODIFICATIONS REQUIRED



This is RF Envelope Clipping—the feature being used in new transmitter designs for amateur and military use.


Models Now Available  
Collins 32S, KWM-2 ..... \$ 98.50 ea.  
Drake TR-3, TR-4, TR-6, TR-4C,  
T-4, T-4X, T-4XB, T-4XC \$128.50 ea.  
Postpaid—Calif. Residents  
add 6% Tax

Watch for other models later!

**DX Engineering**

1050 East Walnut, Pasadena, Calif. 91106
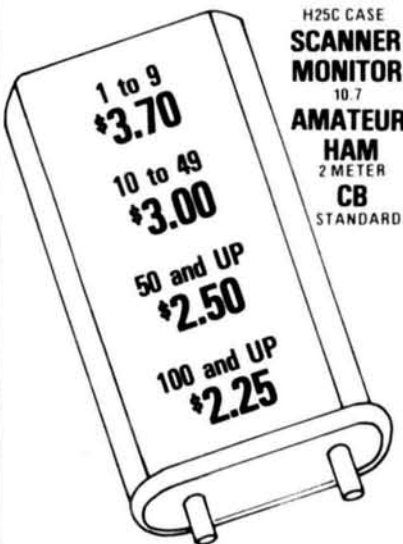
### 10's OF THOUSANDS OF CRYSTALS IN STOCK!



H25C CASE  
**SCANNER MONITOR**  
10.7  
**AMATEUR HAM**  
2 METER  
**CB**  
STANDARD

Immediate delivery on most frequencies!  
OTHERS ARE SPECIAL ORDER

**CRYSTAL BANKING SERVICE**  
P.O. BOX 683  
LYNNFIELD, MASSACHUSETTS  
01940



**Radio Amateurs Reference Library of Maps and Atlas**

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country... DX zones, time zones, cities, cross referenced tables **\$1.25**

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities: Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. **\$1.25**

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus useful information on each of the 50 United States and other Countries **\$1.25**

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. Size 8 3/4" x 12" **\$2.50**

Complete reference library of maps — set of 4 as listed above **\$3.75**

See your favorite dealer or order direct.

Mail orders please include \$1.25 per order for shipping and handling.

RADIO AMATEUR

**callbook INC.**

WRITE FOR FREE BROCHURE!



Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# Wilson's

# SYSTEM ONE

## TRIBANDER ANTENNA IS HERE...

### SYSTEM ONE

FOR 20, 15 and 10 METERS

Monoband performance  
with 4 elements on 20 meters  
on a 26' boom.

THE SY 1000 TRIBANDER  
ANTENNA IS SHOWN HERE  
WITH THE WR 500 ROTOR  
AND SST-64 CRANK-UP  
TOWER @ 50 FT.  
(Guy System not shown)

The new standard of performance for Tribanders is the Wilson System One!!! A DX'er's delight operating 20 meters on a full 26' boom with 4 elements, 4 operational elements on 20-15-10, plus separate reflector element on 10 meters for correct monoband spacing. Featured are the large diameter High-Q Traps, Beta matching system, heavy duty Taper Swaged Elements, rugged Boom to Element mounting . . . and value priced at \$259.95. Additional features: • 10 dB Gain • 20-25 dB Front-to-Back Ratio • SWR less than 1.5 to 1 on all bands.

#### MODEL SY-1 SPECIFICATIONS:

Matching Method: Beta  
Band MHz: 14-21-28  
Maximum Power Input: Legal Limit  
Gain: 10 dB  
VSWR (at Resonance): 1.5 to 1  
Impedance: 50 ohms

F/B Ratio: 20-25 dB  
Boom Length: 26'  
(2" O.D.)  
No. of Elements: 5  
Longest Element: 26' 7"  
Turning Radius: 18' 6"


Mast Diameter: 2" O.D.  
Boom Diameter: 2" O.D.  
Surface Area: 7.3 sq. ft.  
Windload Area: 146 lbs.  
Shipping Weight: 50 lbs.




WILSON'S  
WR500  
ROTOR



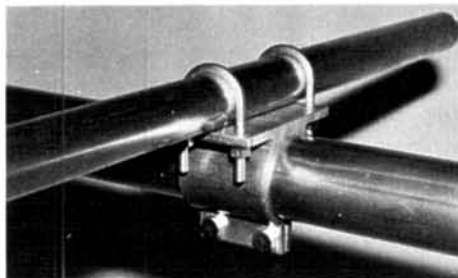
ADVANCED DESIGN LARGE DIAMETER  
HIGH-Q TRAPS FOR MINIMUM LOSS AND  
MAXIMUM POWER CAPACITY



HEAVY DUTY BOOM  
TO ELEMENT EXTRUSION

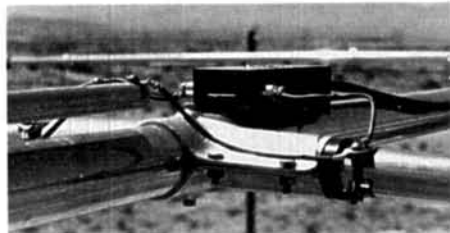

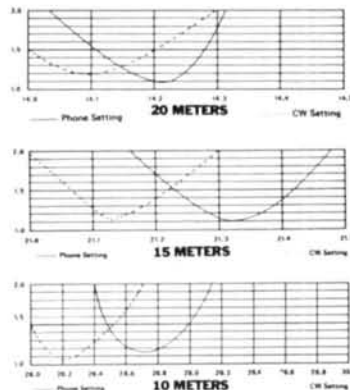INSULATED DRIVEN ELEMENT WITH  
PRECISION BETA MATCH AND HEAVY  
DUTY ELEMENT MOUNTS



**AMATEUR PRODUCTS DEALERSHIPS  
FOR MANY AREAS ARE AVAILABLE!!!**  
If you are interested in the profits you can  
make as a Wilson Dealer, contact us.

For complete specifications on the above products or a copy of our new Amateur Products Buyers Guide, write:  
Consumer Products Division



## Wilson Electronics Corp.

P.O. BOX 19000 • LAS VEGAS • NEVADA • 89119 • (702) 739-1931 • TELEX 684-522

State  
of the art



by  
**K.V.G.**

## CRYSTAL FILTERS and DISCRIMINATORS

### 9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$31.95
XF9-B	2.4 kHz	SSB RX/TX	\$45.45
XF9-C	3.75 kHz	AM	\$48.95
XF9-D	5.0 kHz	AM	\$48.95
XF9-E	12.0 kHz	NBFM	\$48.95
XF9-M	0.5 kHz	CW (4 pole)	\$34.25
XF9-NB	0.5 kHz	CW (8 pole)	\$63.95

### 9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$4.00
XF901	8998.5 kHz	USB	\$4.00
XF902	9001.5 kHz	LSB	\$4.00
XF903	8999.0 kHz	BFO	\$4.00
F-05	Hc25/u	Socket Chassis	.50
F-06	Hc25/u	Socket P.C. Board	.50

Export  
Inquiries  
Invited

Shipping  
\$1.25  
per filter

## LINEAR AMPLIFIERS

COMPATIBLE WITH OUR LOW  
POWER TRANSVERTERS.

10W DRIVE, 50Ω IN/OUT

EDL432, 50W (ILLUS.) \$129.95



EDL432P, INCL. POWER SUPPLY/CABINET \$299.95

EDL144, 100W 2M, IN CABINET, WITH 115V POWER SUPPLY \$299.95


UPS Shipping at Cost

## 432 MHz SSB TRANSVERTERS

Use your HF Transceiver on the 432 MHz band with the addition of the MM432 linear Transverter. The MM432 operates on all modes; SSB, CW, AM, FM. It contains BOTH the linear transmit up-converter and the receive down-converter. An internal PIN diode T/R connects to your Transceiver T/R line. The MM432 is FT101 and similar HF rig compatible. Add the 70/MBM48 MULTIBEAM and operate direct into OSCAR 7 mode B. Write for application note.

### Specifications:

Output Power	10 W PEP
Drive, 10 meters	1/2 W max
Receiver N.F.	3.0 dB typ
Receiver gain	30 dB typ
Prime Power	12 V D.C.
Shipping:	\$3.50

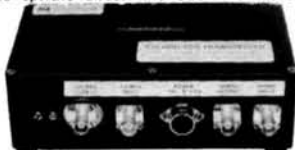

MM432-28 MK4	\$229.95	MM432-144	\$199.95
MM432-50	\$249.95	FM440-146	\$154.95
MM432-ATV	\$259.95	QM432-144	\$154.95
MM432-144	\$319.95		

## VARACTOR TRIPLERS

The low cost, easy way to operate on the 432 MHz and 1296 MHz bands. For OSCAR 7, mode B, drive the MMv432 family varactor tripler with your 2 meter transmitter. The wideband varactor triplers cover the full 2M/432 band without retuning.

NO power supply required for varactor triplers; efficiency approximately 50%. Three models available at 432, two at 1296.

Model	Max Drive	
MMv432	30 W	\$65.95
MMv432M	50 W	79.95
MMv432H	70 W	125.50
MMv1296	20 W	77.50
MMv1296H	35 W	99.95
Shipping		\$2.50



Send 26¢ (2 stamps) for full line catalogue of KVG crystal products and all your VHF & UHF equipment requirements.

Pre-Selector Filters	Amplifiers	SSB Transverters
Varactor Triplers	Crystal Filters	FM Transverters
Decade Pre-Scalers	Frequency Meters	VHF Converters
Antennas	Oscillator Crystals	UHF Converters

**si**

Spectrum  
International, Inc.  
Post Office Box 1084  
Concord, Mass. 01742, USA



GREGORY ELECTRONICS  
The FM Used  
Equipment People.



# START THE NEW YEAR WITH A COPY OF GREGORY ELECTRONICS NEW 1978 CATALOG




GREGORY ELECTRONICS CORP.

245 Rt. 46, Saddle Brook, N.J. 07662  
Phone: (201) 489-9000
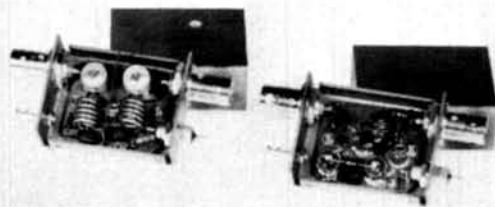
## PREAMPS from LUNAR

Originally developed by Chip Angle N6CA, the "Anglelinear" receiving preamplifiers meet the most demanding needs where low noise figure is important.



Model	Noise Figure	Gain	Bandwidth 3 dB	10 dB	List Price
28N	1.25	15	1.3	4	34.95
28W	1.25	10	2.6	7	34.95
50	1.5	12	2.5	5	34.95
144N	1.5	12	2.5	8	34.95
144W	1.5	11	5	15	34.95
222	2.0	11	6	18	34.95
432-2	1.6	15	150	400	39.95
E432-3	1.0 ± .1	11	180	325	125.00
450-2	1.7	15	150	400	39.95
490-2	1.7	15	150	400	44.95

BNC Connectors standard, except E432-3 SMA only. Others, specify RCA Phono, TNC, etc.

New "Anglelinear" line products coming soon: Preamps thru 2.5 GHz, converters & transverters systems filters 28 MHz thru 2.5 GHz.

Write for descriptive brochure on all Lunar Products.

Please add \$3.00 shipping/handling

California residents add 6%. Order today at your dealer or direct from:



**LUNAR**  
electronics

SUITE 10  
2785 KURTZ ST.  
SAN DIEGO, CA 92110  
714-299-9740  
Louis N. Anciaux WB6NMT

# Gift ideas from Vhf engineering

THE WORLD'S MOST COMPLETE LINE OF VHF-FM KITS AND EQUIPMENT

RX28C	28-35 MHz FM receiver with 2 pole 10.7 MHz crystal filter	\$ 59.95
RX28C W/T	same as above—wired & tested	104.95
RX50C Kit	30-60 MHz rcvr w/2 pole 10.7 MHz crystal filter	59.95
RX50C W/T	same as above—wired & tested	104.95
RX144C Kit	140-170 MHz rcvr w/2 pole 10.7 MHz crystal filter	69.95
RX144C W/T	same as above—wired & tested	114.95
RX220C Kit	210-240 MHz rcvr w/2 pole 10.7 MHz crystal filter	69.95
RX220C W/T	same as above—wired & tested	114.95
RX432C Kit	432 MHz rcvr w/2 pole 10.7 MHz crystal filter	79.95
RX432C W/T	same as above—wired & tested	124.95

## RECEIVERS

RXCF	accessory filter for above receiver kits gives 70 dB adjacent channel rejection	8.50
RF28 Kit	10 mtr RF front end 10.7 MHz out	12.50
RF50 Kit	6 mtr RF front end 10.7 MHz out	12.50
RF144D Kit	2 mtr RF front end 10.7 MHz out	17.50
RF220D Kit	220 MHz RF front end 10.7 MHz out	17.50
RF432 Kit	432 MHz RF front end 10.7 MHz out	27.50
IF 10.7F Kit	10.7 MHz IF module includes 2 pole crystal filter	27.50
FM455 Kit	455 KHz IF stage plus FM detector	17.50
AS2 Kit	audio and squelch board	15.00

TX50	transmitter exciter, 1 watt, 6 mtr.	39.95
TX50 W/T	same as above—wired & tested	59.95
TX144B Kit	transmitter exciter—1 watt—2 mtrs	29.95
TX144B W/T	same as above—wired & tested	49.95
TX220B Kit	transmitter exciter—1 watt—220 MHz	29.95

## TRANSMITTERS

TX220B W/T	same as above—wired & tested	49.95
TX432B Kit	transmitter exciter 432 MHz	39.95
TX432B W/T	same as above—wired & tested	59.95
TX150 Kit	300 milliwatt, 2 mtr transmitter	19.95
TX150 W/T	same as above—wired & tested	29.95

PA2501H Kit	2 mtr power amp—kit 1w in—25w out with solid state switching, case, connectors	59.95
PA2501H W/T	same as above—wired & tested	74.95
PA4010H Kit	2 mtr power amp—10w in—40w out—relay switching	59.95
PA4010H W/T	same as above—wired & tested	74.95
PA50/25 Kit	6 mtr power amp, 1w in, 25w out, less case, connectors & switching	49.95
PA50/25 W/T	same as above, wired & tested	69.95
PA144/15 Kit	2 mtr power amp—1w in—15w out—less case, connectors and switching	39.95
PA144/25 Kit	same as PA144/15 kit but 25w	49.95
PA220/15 Kit	similar to PA144/15 for 220 MHz	39.95
PA432/10 Kit	power amp—similar to PA144/15 except 10w and 432 MHz	49.95
PA140/10 W/T	10w in—140w out—2 mtr amp	179.95
PA140/30 W/T	30w in—140w out—2 mtr amp	159.95

## POWER AMPLIFIERS

Model	BAND	Power Input	Power Output	
BLC 10/70	144 MHz	10W	70W	139.95
BLC 2/70	144 MHz	2W	70W	159.95
BLC 10/150	144 MHz	10W	150W	259.95
BLC 30/150	144 MHz	30W	150W	239.95
BLD 2/60	220 MHz	2W	60W	159.95
BLD 10/60	220 MHz	10W	60W	139.95
BLD 10/120	220 MHz	10W	120W	259.95
BLE 10/40	420 MHz	10W	40W	139.95
BLE 2/40	420 MHz	2W	40W	159.95
BLE 30/80	420 MHz	30W	80W	259.95
BLE 10/80	420 MHz	10W	80W	289.95

PS15C Kit	15 amp—12 volt regulated power supply w/case, w/fold-back current limiting and overvoltage protection	79.95
PS15C W/T	same as above—wired & tested	94.95
PS25C Kit	25 amp—12 volt regulated power supply w/case, w/fold-back current limiting and ovp	129.95
PS25C W/T	same as above—wired & tested	149.95
PS25M Kit	same as PS25C with meters	149.95
PS25M W/T	same as above—wired & tested	169.95

## POWER SUPPLIES

O.V.P.	adds over voltage protection to your power supplies, 15 VDC max.	9.95
PS3A Kit	12 volt—power supply regulator card with fold-back current limiting	8.95
PS3012 W/T	new commercial duty 30 amp 12 VDC regulated power supply w/case, w/fold-back current limiting and overvoltage protection	239.95

RPT50 Kit	repeater—6 meter	465.95
RPT50	repeater—6 meter, wired & tested	695.95
RPT144 Kit	repeater—2 mtr—15w—complete (less crystals)	465.95
RPT220 Kit	repeater—220 MHz—15w—complete (less crystals)	465.95
RPT432 Kit	repeater—10 watt—432 MHz (less crystals)	515.95
RPT144 W/T	repeater—15 watt—2 mtr	695.95
RPT220 W/T	repeater—15 watt—220 MHz	695.95
RPT432 W/T	repeater—10 watt—432 MHz	749.95
DPLA50	6 mtr close spaced duplexer	575.00

## REPEATERS

DPLA144	2 mtr, 600 KHz spaced duplexer, wired and tuned to frequency	379.95
DPLA220	220 MHz duplexer, wired and tuned to frequency	379.95
DPLA432	rack mount duplexer	319.95
DSC-U	double shielded duplexer cables with PL259 connectors (pr.)	25.00
DSC-N	same as above with type N connectors (pr.)	25.00

TRX50 Kit	Complete 6 mtr FM transceiver kit, 20w out, 10 channel scan with case (less mike and crystals)	229.95
TRX144 Kit	same as above, but 2 mtr & 15w out	219.95
TRX220 Kit	same as above except for 220 MHz	219.95
TRX432 Kit	same as above except 10 watt and 432MHz	254.95
TRC-1	transceiver case only	19.95
TRC-2	transceiver case and accessories	39.95

## TRANSCIVERS

## OTHER PRODUCTS BY VHF ENGINEERING

CD1 Kit	10 channel receive xtal deck w/diode switching	\$ 6.95
CD2 Kit	10 channel xmit deck w/switch and trimmers	14.95
CD3 Kit	UHF version of CD1 deck, needed for 432 multi-channel operation	12.95
COR2 Kit	carrier operated relay	19.95
SC3 Kit	10 channel auto-scan adapter for RX with priority	19.95
Crystals	we stock most repeater and simplex pairs from 146.0-147.0 (each)	5.00
CWID Kit	159 bit, field programmable, code identifier with built-in squelch tail and ID timers	39.95
CWID	wired and tested, not programmed	54.95
CWID	wired and tested, programmed	59.95
MIC 1	2,000 ohm dynamic mike with P.T.T. and coil cord	12.95
TS1 W/T	tone squelch decoder	59.95
TS1 W/T	installed in repeater, including interface accessories	89.95
TD3 Kit	2 tone decoder	29.95
TD3 W/T	same as above—wired & tested	39.95
HL144 W/T	4 pole helical resonator, wired & tested, swept tuned to 144 MHz ban	24.95
HL220 W/T	same as above tuned to 220 MHz ban	24.95
HL432 W/T	same as above tuned to 432 MHz ban	24.95

SYN II Kit	2 mtr synthesizer, transmitt offsets programmable from 100 KHz—10 MHz, (Mars offsets with optional adapters)	169.95
SYN II W/T	same as above—wired & tested	239.95
MO-1 Kit	Mars/cap offset optional	2.50
TO-1 Kit	18 MHz optional tripler	2.50

## SYNTHESIZERS

HT 144B Kit	2 mtr, 2w, 4 channel, hand held transceiver with crystals for 146.52 simplex	129.95
NICAD	battery pack, 12 VDC, 1/2 amp.	29.95
BC12	battery charger for above	5.95
Rubber Duck	2 mtr, with male BNC connector	12.95

## WALKIE-TALKIES



**Vhf engineering**

DIVISION OF BROWNIAN ELECTRONICS CORP.

BOX H / 320 WATER ST. / BINGHAMTON, N.Y. 13901 / Phone 607-723-9574



More Details? CHECK—OFF Page 150

december 1977 **hr** 97

# “Wasyerbespriz?”

OK, so you want to save money — can't blame you for that!

After you have called the 800 numbers, got your “best price,” sent your money — what do you get? A box. Suppose it doesn't work? (Murphy's law). Ship it back (at your own expense) and wait. Or — two weeks after the warranty expires — so goes the rig... what to do? And since you got that great discount how much attention will you get? Rotsaruck fella!

Today's amateur equipment is far more sophisticated than that of even a few years ago, and it's getting more so every day. Service becomes an important issue. *At CFP we have decided to offer you an alternative: If you are willing to pay the regular list price on any Drake or Yaesu product, CFP will provide an additional 90 days of warranty protection. This warranty will be identical with the normal warranty with the exception that we will pay all charges including shipping both ways!*

There may be occasions when we won't have the item you desire. Should you place an order and we don't, we will refund your money and advise you when it will be available. We won't sit on your money! If you wish a high demand item and want to make a deposit to ensure getting what you want — fine.

Because we are amateurs and concerned about the issues, we limit our transmitter and amplifier sales to licensed amateurs (a license photocopy will do).

Amateur radio is a great service and a greater hobby — lets keep it that way!

Mail Orders accepted. N. Y. residents add sales tax. SASE will get our list of used Amateur Equipment.

**WANTED: GOOD  
CLEAN TRADES!**

WA2KTJ  
WB2LVW

**C F P COMMUNICATIONS, INC.**

211 NORTH MAIN STREET  
HORSEHEADS, N.Y. 14845  
PHONE: 607-739-0187



**Store Hours**  
Tues. to Fri. 10-6 p.m.  
Sat. 10-4 p.m.

Fri. & Sat. subject to  
Hamfest weekends  
Closed Sun. & Mon.

# Fascinating.

**our 1977 WRAP-UP issue**

A real nostalgia trip for the old timer

A super eye opener for the newcomer

Chocked full of real goodies for everybody. Those old Radio magazines of the 30's — war surplus gear of the 40's — exciting OSCAR in the 70's — QSO's of the future. HORIZONS 1977 WRAP-UP a completely unique issue — one you must have.

At your local store — NOW

Better yet, why not subscribe now and get your WRAP-UP issue absolutely FREE?

## Subscribe Today!

- ☐ Enclosed is check or money order for \$10.00 send my FREE Wrap-Up Issue and One Full Year (12 issues) of HORIZONS
- ☐ Here's \$1.00 for the Wrap-Up Issue only. No subscription please.
- ☐ Charge a 1 year (12 issue) subscription and send the FREE Wrap-Up Issue.
- ☐ VISA ☐ Mastercharge  
Acct. # \_\_\_\_\_ Exp. Date. \_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Mail to: Ham Radio HORIZONS, Greenville, NH 03048

**FREE  
ISSUE!**



## ALUMA TOWERS

60 Ft.  
Ham Crank-Up  
Model T-60-H

40 Ft.  
Crank-Up  
Ham Model T-140

HIGHEST QUALITY

MADE IN ALUMINUM

- ★ TELESCOPING  
(CRANK UP)
- ★ GUYED
- ★ TILT OVER MODELS

QUALITY MADE

*Excellent for*

**HAM  
COMMUNICATIONS**

MANY MODELS MFG.

Towers to 100 feet. Specials  
designed & made. See dealer  
or send for free catalog.

**ALUMA TOWER CO.**  
BOX 2806HR  
VERO BEACH, FLA. 32960  
PHONE (305) 567-3423




## NEW LSI TECHNOLOGY FREQUENCY COUNTER

TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION [PORTABLE BATTERY OPERATION IS NOW PRACTICAL], DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!

KIT #FC-50C ..... 60 MHZ COUNTER WITH CABINET & P.S. ....  
KIT #PSL-650 ..... 650 MHZ PRESCALER [NOT SHOWN] .....  
MODEL #FC-50WT ..... 60 MHZ COUNTER WIRED, TESTED & CAL. ....  
MODEL #FC-50/600WT ..... 600 MHZ COUNTER WIRED, TESTED & CAL. ....

**\$119<sup>95</sup> COMPLETE!**

SIZE:  
3" High  
6" Wide  
5 1/2" Deep

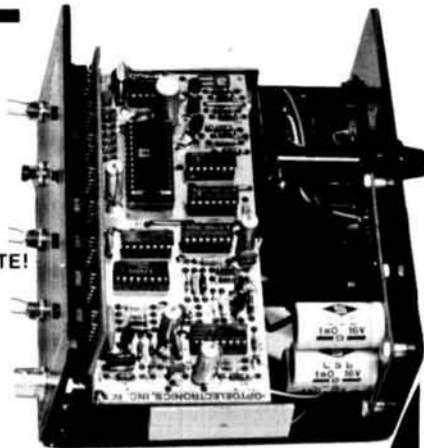

### FEATURES AND SPECIFICATIONS:

DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT  
GATE TIMES: 1 SECOND AND 1/10 SECOND  
PRESCALER WILL FIT INSIDE COUNTER CABINET  
RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.  
FREQUENCY RANGE: 10 HZ TO 60 MHZ. [65 MHZ TYPICAL].  
SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.  
INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.  
[DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]  
ACCURACY:  $\pm 1$  PPM  $\pm .0001\%$ . AFTER CALIBRATION TYPICAL.  
STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [1.001% XTAL]  
IC PACKAGE COUNT: 8 [ALL SOCKETED]  
INTERNAL POWER SUPPLY: 5 V DC REGULATED.  
INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.  
POWER CONSUMPTION: 4 WATTS

KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED.

### PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.

#### CABINET I

3"H, 6 1/4"W, 5 1/2"D Black, White or Clear Cover

#### CABINET II

2 1/2"H, 5"W, 4"D \$6.50 ea.

RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS  
3"x6"x1/8" 95¢ ea. 4/13


### SEE THE WORKS Clock Kit Clear Plexiglas Stand

- 6 Big .4" digits
- 12 or 24 hr. time
- 3 set switches
- Plug transformer
- all parts included

Plexiglas is Pre-cut & drilled  
Kit #850-4 CP

Size: 6"H, 4 1/2"W, 3 1/2"D

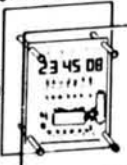Assembled \$29<sup>95</sup>  
\$23<sup>50</sup> ea. 2/45.



### 60 HZ.

XTAL TIME BASE  
Will enable  
Digital Clock Kits  
or Clock-Calendar  
Kits to operate  
from 12V DC.  
1"x2" PC Board  
Power Req. 5-15V  
(2.5 MA TYP.)  
Easy 3 wire hookup  
Accuracy:  $\pm 2$  PPM  
#TB-1 (Adjustable)  
Complete Kit \$4<sup>95</sup>  
Wir & Cal \$9.95

### SPECIAL PRICING!

PRIME - HIGH SPEED RAM

**21L02-3 400 NS**

LOW POWER - FACTORY FRESH

1-24 \$1.75 ea. 100-199 \$1.45 ea.  
25-99 1.60 ea. 200-999 1.39 ea.


1000 AND OVER \$1.29 ea.

## 6-DIGIT LED CLOCK CALENDAR KIT DATE-TIME-SNOOZE ALARM & MORE... KIT 7001

FOR THE BUILDER THAT WANTS THE BEST. FEATURING 12 OR 24 HOUR TIME —  
29-30-31 DAY CALENDAR. ALARM, SNOOZE AND AUX. TIMER CIRCUITS

Will alternate time (8 seconds) and date (2 seconds) or may be wired for time or date display only, with other functions on demand. Has built-in oscillator for battery back-up. A loud 24 hour alarm with a repeatable 10 minute snooze alarm, alarm set & timer set indicators. Includes 110 VAC/60Hz power pack with cord and top quality components through-out.

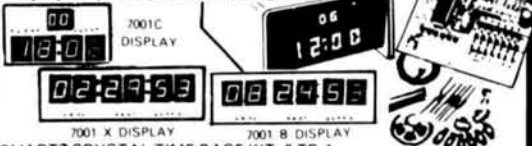KIT - 7001B WITH 6 - .5" DIGITS ..... \$39.95  
KIT - 7001C WITH 4 - .6" DIGITS &  
2 - .3" DIGITS FOR SECONDS ..... \$42.95  
KIT - 7001X WITH 6 - .6" DIGITS ..... \$45.95



KITS ARE COMPLETE (LESS CABINET)

ALL 7001 KITS FIT CABINET I AND ACCEPT QUARTZ CRYSTAL TIME BASE KIT # TB-1

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout.

Specify for 7001

B, Cor X - \$7.95

### AUTO BURGLAR ALARM KIT

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. KEYLESS ALARM HAS PROVISION FOR P.O.S. & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT 1/2 RATE OR DRIVE SIREN. KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH. REMOTE SWITCH RELIABILITY RESISTS FALSE ALARMS & PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.



KIT #ALR-1

\$9.95

#ALR-1WT

WIRED & TESTED

\$19.95

### VARIABLE REGULATED 1 AMP POWER SUPPLY KIT

- VARIABLE FROM 4 TO 14V
- SHORT CIRCUIT PROOF
- 723 IC REGULATOR
- 2N3055 PASS TRANSISTOR
- CURRENT LIMITING AT 1 Amp

KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (LESS TRANSFORMER) KIT #PS-01 \$8.95

TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 5V. \$3.50

### MOBILE LED CLOCK

12/24 HR. 4" DIGITS!

MODEL 12 VOLT AC or DC POWERED #2001

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY — TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY [Use When Key Off in Car, Etc.]
- TOP QUALITY PC BOARDS & COMPONENTS — INSTRUCTIONS.
- MOUNTING BRACKET INCLUDED

KIT #2001 COMPLETE KIT

\$27<sup>95</sup> 3 OR MORE

\$25<sup>95</sup> ea.

115 VAC Power Pack #AC-1 \$250

ASSEMBLED UNITS WIRED & TESTED ORDER #2001 WT (LESS 9V. BATTERY) \$37<sup>95</sup> ea.

3 OR MORE \$35<sup>95</sup> ea.

Wired for 12-Hr. Op. if not otherwise specified.

ORDER BY PHONE OR MAIL COD ORDERS WELCOME

ORDERS TO USA & CANADA ADD 5% FOR SHIPPING, HANDLING & INSURANCE. ALL OTHERS ADD 10% ADDITIONAL \$1.00 CHARGE FOR ORDERS UNDER \$15.00 - COD FEE \$1.00. FLA. RES. ADD 4% STATE TAX.

master charge

THE MASTERCARD CARD

BANKAMERICARD

welcome here



## OPTOELECTRONICS, INC.

BOX 219 HOLLYWOOD, FLA. 33022  
PHONE [305] 921-2056 / 921-4425

# Joy to the World...

And the angel said unto her, Fear not, Mary: for thou hast found favor with God. And, behold, thou shalt conceive in thy womb, and bring forth a son, and shalt call His name Jesus. Luke 1: 30,31 KJV

Then said Mary unto the angel, How shall this be, seeing I know not a man? And the angel answered and said unto her, The Holy Ghost shall come upon thee, and the power of the Highest shall overshadow thee; therefore also that holy thing which shall be born of thee shall be called the Son of God. Luke 1: 34,35 KJV

And she brought forth her firstborn son, and wrapped him in swaddling clothes, and laid him in a manger; because there was no room for them in the inn. Luke 2:7 KJV

For God so loved the world, that he gave his only begotten Son, that whosoever believeth in him should not perish, but have everlasting life. John 3:16 KJV

Nearly 2000 years ago, God reached out and touched the world with his love. He is still reaching out today seeking the lost.

Let his love reach into your heart this Christmas season. Become a member of God's family by turning from your way, and trusting in God's way today.

May you and your family reach out and accept the joy he has for you this Christmas.

## Joy to the World...

Lee, Andy, Denny, Don, Bill, Denny, Linda, Lydia, Billie, Kim, Lee, Rick, Jane, Deb, Barb, Les, Merrill, and Paul.

**MATRIC**

RD 1 • BOX 185A • FRANKLIN, PA 16323

DICK  
K4RYR

EXPERIENCE the Ultimate  
in Scanners

BOB  
W4YYS



**The Touch.™**

by *Regency*

\$329 LIST

our price  
**\$279<sup>00</sup>**

- Over 15,000 frequencies at your fingertips
- Scans the Channels in 1.3 Seconds
- Special Weather Alert® and Priority Scan features

**LAFAYETTE RADIO ELECTRONICS**

ASSOC.  
STORE

1811 HWY 17-92, MAITLAND, FL. 32751

305-831-2271

AMECO • ARRL BOOKS • ASTATIC • B & W • BEARCAT  
• CALLBOOK • CDE HAM III • CUSHCRAFT • DENTRON  
• HALLICRAFTERS • HY-GAIN • KLM • LARSEN  
• MALLORY • J. W. MILLER • MOSLEY • NPC POWER  
SUPPLIES • SHURE • W2AU BALUN • MORE TO COME!

Orlando's Most Complete Stock of Electronic Hardware

Transistors • Diodes • Integrated Circuits • Variable Capacitors • Connectors • Audio Cables  
• Variable Resistors • Antenna Wire • RG-8/U Coax (foam) • Rotor Cable • Steel Mast  
• Ceramic Insulators • and much more

**LAFAYETTE RADIO ELECTRONICS**

ASSOC.  
STORE

1811 N. HWY 17-92, MAITLAND, FL. 32751

(Near Orlando)

305-831-2271

**GEM-QUAD FIBRE-GLASS**


ANTENNA FOR 10, 15, and 20 METERS

Two Elements \$139.00

Extra Elements \$99.00

Price is F.O.B. Transcona

INCLUDES U.S. Customs  
Duty

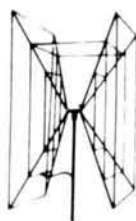

KIT COMPLETE WITH

\*SPIDER

\*ARMS

\*WIRE

\*BALUN KIT

\*BOOM WHERE  
NEEDED

WINNER OF MANITOBA  
DESIGN INSTITUTE  
AWARD OF EXCELLENCE

Buy two elements now — a third and fourth may be added later with little effort.

Enjoy up to 8 db forward gain on DX, with a 25 db back to front ratio and excellent side discrimination.

Get maximum structural strength with low weight, using our "Tridetic" arms.

**GEM QUAD PRODUCTS**

Box 53

Transcona, Manitoba

Canada R2C 2Z5

Tel: (204) 866-3338

# YOUR BEST BUY IN KITS

## WOW — FREE

FROM NOW UNTIL  
DECEMBER 31, 1977

RECEIVE ABSOLUTELY FREE — A SIX-DIGIT 12- OR 24-HOUR ELECTRONIC CLOCK KIT, COMPLETE WITH POWER SUPPLY AND CASE, WITH THE PURCHASE OF ANY ONE OF THE FOLLOWING FREQUENCY COUNTER KITS. HAL-600A, HAL-300A, HAL-50A OR THE ANALOG DIGILAB. JUST MENTION THIS AD WAS FOUND IN HAM RADIO MAGAZINE.

OR RECEIVE A GIFT CERTIFICATE WORTH \$15.00 ON YOUR NEXT PURCHASE OF \$50.00 OR MORE.

## 6 GOOD REASONS

FOR BUYING A HAL-TRONIX  
FREQUENCY COUNTER

(1) 100% COMPLETE KIT, (2) EASY ASSEMBLY, (3) COMPLETELY ENCLOSED IN METAL CABINET, (4) IC SOCKETS USED THROUGHOUT FOR EASY TTL REPLACEMENT (5) EASY ON YOUR POCKET BOOK, AND (6) NO EXPENSIVE CHIPS TO REPLACE (EXAMPLE — IF YOU LOSE A DECODER, LATCH OR DRIVER IN A HAL-TRONIX COUNTER, THE AVERAGE COST OF REPLACEMENT OF THE LOW-COST TTLS IS LESS THAN \$1.00 EXCLUDING THE PRE-SCALE CHIP. IN SOME OF THE NEWER COUNTERS NOW BEING MARKETED BY MY COMPETITION, THEY ARE USING THE EXOTIC SINGLE CHIP AND WOULD COST YOU CLOSE TO \$30.00 TO REPLACE). THIS IS SOMETHING YOU SHOULD CONSIDER.



## ANALOG-DIGILAB KIT \$139.50

DESIGNED BY HAL-TRONIX  
AND MIKE GOLDEN OF  
R.E.T.S. ELECTRONICS  
SCHOOL OF DETROIT. FOR  
RUGGED CLASSROOM USE.

FOR THE RADIO AMATEUR, THE STUDENT,  
THE EXPERIMENTER OR DESIGNER

**SPECIFICATIONS:** OUTPUT VOLTAGES: +5V, +12V, -12V;  
USABLE CURRENT: 750mA; % Regulation at 500mA: 0.2%;  
Short-circuit limited at 1.0 amp; Thermal overload protected.  
Power requirements: 117VAC, 60Hz, 40 Watts.

Function Generator: Frequency range: 1Hz to 100 Hz in 5  
bands. Amplitude adjustable from 0 to 10 VPP. DC offset  
adjustable from 0 to  $\pm 10V$ . Waveforms: Sine, square, tri-  
angular and TTL Clock. TTL Clock 0 to +5V level, 200 ns rise  
and fall time. Frequency determined by Function Generator.  
Output impedance 1.2K ohm.

Most of all, it's easy to construct and service. PC boards are  
pre-drilled, plated thru and solder flowed. Over 1000 units  
sold to schools.

### 6-DIGIT CLOCK

12/24 HOUR

COMPLETE KIT CONSISTING OF 2  
PC G10 PRE-DRILLED PC BOARDS,  
1 CLOCK CHIP, 6 FND 359 READ-  
OUTS, 13 TRANSISTORS, 3 CAPS,  
9 RESISTORS, 5 DIODES, 3 PUSH-  
BUTTON SWITCHES, MOLDED  
POWER TRANSFORMER CORD AND  
INSTRUCTIONS.

DON'T BE FOOLED BY PARTIAL  
KITS WHERE YOU HAVE TO BUY  
EVERYTHING EXTRA.

PRICED AT \$12.95

### 4-DIGIT ALARM CLOCK

12 HOUR ONLY

COMPLETE KIT CONSISTING OF 2  
PC G10 PRE-DRILLED PC BOARDS,  
1 CLOCK CHIP, 4 FND 503 READ-  
OUTS, ALL NECESSARY TRANSIS-  
TORS, CAPS AND RESISTORS  
INCLUDING 5 PUSH-BUTTON  
SWITCHES, MOLDED POWER  
TRANSFORMER CORD PLUS  
SPEAKER; COMES COMPLETE  
WITH INSTRUCTIONS.

PRICED AT \$16.95

### CLOCK CASE

Available and will fit any one of the above clocks  
Regular Price ... \$6.50 But Only \$4.50 when bought with clock

### 60-HZ TIME BASE

CRYSTAL TIME BASE KIT. WILL  
ENABLE MOST ALL DIGITAL  
CLOCKS TO OPERATE FROM 12  
VDC. LOW PROFILE UNIT, EASY  
3-WIRE HOOKUP. ACC 2PPM,  
ADJUSTABLE.  
COST ONLY \$5.95 EACH OR 2  
FOR \$10.00 — OR ONLY \$4.50  
WITH CLOCK PURCHASE.

### 10-MHz CRYSTALS

HI-QUALITY CRYSTALS, DESIGNED  
FOR FREQUENCY CONTROL AND  
ELECTRONIC TIME PIECES; AGING  
FACTOR 5PPM. MEETS OR EX-  
CEEDS MIL-C-3098 SPECS. MADE  
ESPECIALLY FOR HAL-TRONIX  
BY SENTRY.

PRICE \$5.95 OR 2 FOR \$10.00



EXCEL CIRCUITS

ETCH-IT-YOURSELF

PRINTED CIRCUIT KIT  
ONLY  
\$19.95

PLUS \$1.00 SHIPPING


KIT INCLUDES:

4 PCS PHOTO-SENSITIZED GLASS EPOXY BOARD; DEVELOPER & RESIST  
STRIPPER; DRY ETCHANT CRYSTALS; 1 - 8 x 12 x 3 PLASTIC TRAY  
AND COVER. 2 - 8 1/2 x 11 SHEETS OF .100 GRID PAPER. 2 - 8 1/2 x 11  
SHEETS OF .002 MYLAR; 1 PAIR OF PLASTIC GLOVES, MISC. ART-  
WORK SUPPLIES.

DISTRIBUTOR FOR A P PRODUCTS, INCORPORATED



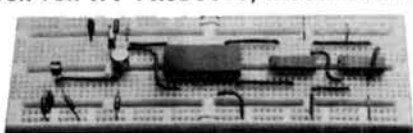SUPER STRIP  
SS-2 #923252  
PRICE \$17.00



# FREQUENCY COUNTERS



**COMPLETE KITS:** CONSISTING OF EVERY ESSENTIAL  
PART NEEDED TO MAKE YOUR COUNTER COMPLETE.

**HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY  
RANGE OF ZERO TO 600 MHz. FEATURES TWO IN-  
PUTS: ONE FOR LOW FREQUENCY AND ONE FOR  
HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION.  
TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OP-  
TIONAL 10 SEC GATE AVAILABLE. ACCURACY  $\pm$   
.001%, UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$149.00**

**HAL-300A** 7-DIGIT COUNTER WITH FREQUENCY  
RANGE OF ZERO TO 300 MHz. FEATURES TWO IN-  
PUTS: ONE FOR LOW FREQUENCY AND ONE FOR  
HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION.  
TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OP-  
TIONAL 10 SEC GATE AVAILABLE. ACCURACY  $\pm$   
.001%, UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$124.00**

**HAL-50A** 8-DIGIT COUNTER WITH FREQUENCY  
RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DEC-  
IMAL POINT, ZERO SUPPRESSION UPON DEMAND.  
FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY  
INPUT, AND ONE ON PANEL FOR USE WITH ANY  
INTERNALLY MOUNTED HAL-TRONIX PRE-SCALER  
FOR WHICH PROVISIONS HAVE ALREADY BEEN  
MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY  
 $\pm$  .001%. UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$124.00**

## HAL-TRONIX BASIC COUNTER KITS

### STILL AVAILABLE

THE FOLLOWING MATERIAL DOES NOT COME WITH  
THE BASIC KIT: THE CABINET, TRANSFORMER,  
SWITCHES, COAX FITTINGS, FILTER LENS, FUSE  
HOLDER, T-03 SOCKET, POWER CORD AND MOUNT-  
ING HARDWARE.

**HAL-600X** (Same Specifications as HAL-600A) \$124.00

**HAL-300X** (Same Specifications as HAL-300A) \$99.00

**HAL-50X** (Same Specifications as HAL-50A) \$99.00

## PRE-SCALER KITS

**HAL-0-300PRE** (Pre-drilled G10 board and all com-  
ponents) \$19.95

**HAL-0-300P/A** (Same as above but with preamp)  
\$29.95

**HAL-0-600PRE** (Pre-drilled G10 board and all com-  
ponents) \$39.95

**HAL-1GHZ** (New Item - Available in December)  
\$124.95

## PRE-BUILT COUNTERS AVAILABLE

(HAL-600A — \$229.00) (HAL-300A — \$199.00) HAL-  
50A — \$199.00). ALLOW 4- TO 6-WEEK DELIVERY  
ON PRE-BUILT UNITS.



**Hal-Tronix**

P. O. BOX 1101

SOUTHGATE, MICH. 48195

PHONE (313) 285-1782

"HAL" HAROLD C. NOWLAND  
WBZXH

### SHIPPING

### INFORMATION:

ORDERS OVER \$15.00 WILL BE SHIPPED POSTPAID  
EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES  
ARE REQUESTED. ON ORDERS LESS THAN \$15.00  
PLEASE INCLUDE ADDITIONAL \$1.00 FOR HANDLING  
AND MAILING CHARGES.

SEND SASE FOR FREE FLYER

# THE BIG STEAL

★starring★  
The Touch. by Regency



*Alan, check out these reviews*  
—13  
"TRULY AMAZING!" The Montrose Gazette  
"MAGNIFICENT!" The Salida Post Tribune  
"...HUH?" The Cotopaxi Chronic Bugler  
"ATSA MY BOY," Mrs. Capone

Frequency Coverage (MHz)  
30-50  
146-148  
146-174  
440-450  
450-512

NOW SHOWING AT:

The Touch by Regency. The first fully synthesized 16 channel scanner to put over 15,000 frequencies at the command of a fingertip.  
Now that's not just a new scanner. It's a revolution in scanning.

Reg. \$329 Now

**\$269**

Offer good to licensed hams only.  
Include call with order.



1401 Blake Street  
Denver, Co. 80202



electronics  
303-893-5525



talk  
power by **TPL**  
**Econo-line**

- Quality for an Economy Price
- Solid State Construction
- Linear Switch (FM/SSB)
- Broad Band



Model	Input	Output	Typical	Frequency	Price
702	10W-20W	50W-90W	10W in/70W out	143-149MHz	\$149.00
702B	1W-5W	60W-80W	1W in/70W out	143-149MHz	\$179.00

Now get TPL COMMUNICATIONS quality and reliability at an economy price. The solid state construction, featuring magnetically coupled transistors and a floating ground, gives you an electronically protected amplifier that should last and last.

The Linear Bias Switch allows you to operate on either FM or SSB. The 702 and 702B are exceptionally well suited for 2-meter SSB. Typical power output levels as high as 100W PEP can be achieved with the proper drive.

The broad band frequency range means that your amplifier is immediately ready to use. No tuning is required for the entire 2-meter band and adjacent MARS channels on TPL's new **Econo-line**.

See these great new additions to the TPL COMMUNICATIONS product line at your favorite radio dealer.

**TPL**

Call or write for prices and information on TPL's complete line of amateur and commercial amplifiers.

COMMUNICATIONS INC.

1324 W. 135TH ST., GARDENA, CA 90247 • (213) 538-9814

Canada: A.C. Simmonds & Sons Ltd., 285 Yorkland Blvd., Willowdale, Ontario M2J 1S8  
Export: EMEC Inc., 2350 South 30th Avenue, Hollandale, Fla. 33009



**BIND 'EM  
AND  
FIND 'EM**

Don't let your valuable issues of HAM Magazine get dog-eared or lost! Collect the whole years worth and protect them in one of our washable, durable, attractively designed buckram binders.

Order HR-BDL

**\$6.95 each  
3 for \$17.95**

*the really deluxe way to build your  
HAM RADIO Magazine library*  
**BOUND VOLUMES OF HAM RADIO**  
Each volume is a years collection of HAM RADIO Magazine bound as a handsome hardcover book. Available for the years 1973, 1974, 1975, and 1976.

1973	Order BV-73
1974	Order BV-74
1975	Order BV-75
1976	Order BV-76
1977	Order BV-77*

**\$24.95 each**

**Set of all 5**

**SAVE over 10%  
\$109.95**

\*Bound volumes for 1977 will be available around February 15, 1978.



**Ham Radio's Communications Bookstore**  
Greenville, NH 03048

## PREAMPS

### HIGH GAIN • LOW NOISE

30 dB power gain, 2.5-3.0 dB N.F. at 150 MHz, 2 stage, R.F. protected, dual-gate MOSFETS. Manual gain control and provision for AGC. 4-3/8" x 1-7/8" x 1-3/8" aluminum case with power switch and your choice of BNC or RCA receptacles. Available factory tuned to the frequency of your choice from 5 MHz to 350 MHz with approximately 3% bandwidth. Up to 10% B.W. available on special order. Requires 12 VDC @ 10mA.



Model 201 price (5 200 MHz) ..... \$29.95  
201-350 MHz ..... \$34.95

### EXTRA LOW NOISE

Excellent for weather satellite reception and recommended by Dr. Ralph E. Taggart in his Weather Satellite Handbook. Less than 2 dB noise figure and approximately 17 dB gain. Uses a low noise J-FET in a common source neutralized circuit. Available factory tuned to your choice of frequency from 135 MHz to 250 MHz. Bandwidth approximately 4 MHz. Supplied in a 2-1/4" x 1-1/8" x 1-3/8" die cast aluminum weather-proof case with a filter for powering it through the antenna. Requires 12 VDC @ 5 mA. Choice of VHF, type "N", or BNC receptacles.



Model 102 PRICE ..... \$36.95

### UHF

#### 3 TO 5 dB MAX. N.F. 20 dB MIN. POWER GAIN

Uses 2 of TI's low noise J-FETS in our special circuit board design which gives a minimum of 20 dB power gain at 450 MHz. Stability is such that you can have mismatched loads without it oscillating and you can retune (using the capped openings in the case) over a 15-20 MHz range simply by peaking the maximum signal. Available tuned to the frequency of your choice between 300-550 MHz. 4-3/8" x 1-7/8" x 1-3/8" aluminum case with power switch and your choice of BNC or RCA receptacles. Requires 12 VDC @ 10mA.



Model 202 price ..... \$34.95

## CONVERTERS

### 2 METERS

This converter has a minimum of 20 dB gain and a noise figure of 2.5-3.0 dB which assures you of a sensitivity of .1 microvolt or better. The circuit uses a dual-gate MOSFET R.F. stage and a dual-gate MOSFET mixer (thereby giving you a minimum of cross-modulation products), 6 tuned circuits, a bipolar oscillator and .005% crystal. Covers 144-146 MHz at 28-30 MHz output with one crystal included and 146-148 MHz at 28-30 MHz with an extra crystal (available for \$6.00 more). The glass epoxy circuit board is enclosed in a 16 gauge aluminum case measuring 3-1/2" x 2-1/4" x 1-1/4" with your choice of either BNC or RCA receptacles. Also included is a power and antenna switch. Requires 12 VDC @ 15 mA. The converter is also available at other input and output frequencies. Call us for prices. PRICE: Model C-144-A available from stock at \$39.95 with one crystal. Additional crystal \$6.00 extra.



### HF & VHF

#### 40 dB GAIN 2.5-3.0 N.F. 150MHz

2 RF stages with transient protected dual-gate MOSFETS give this converter the high gain and low noise you need for receiving very weak signals. The mixer stage is also a dual-gate MOSFET as it greatly reduces spurious mixing products — some by as much as 100 dB over that obtained with bipolar mixers. A



bipolar oscillator using 3rd or 5th overtone plug-in crystals is followed by a harmonic bandpass filter, and where necessary an additional amplifier is used to assure the correct amount of drive to the mixer. Available in your choice of input frequencies from 5-350 MHz and with any output you choose within this range. The usable bandwidth is approximately 3% of the input frequency with a maximum of 4 MHz. Wider bandwidths are available on special order. Although any frequency combination is possible (including converting up) best results are obtained if you choose an output frequency not more than 1/3 nor less than 1/20 of the input frequency. Enclosed in a 4-3/8" x 3" x 1-1/4" aluminum case with power and antenna transfer switch and your choice of BNC or RCA receptacles. Requires 12 VDC @ 25 mA.

Model 407A price:  
5-200 MHz ..... \$54.95  
201-350 MHz ..... \$59.95  
Prices include .005% crystal. Additional crystals \$8.95 ea.

### UHF

#### 20 dB MIN. GAIN 3 TO 5 dB MAX. N.F.

This model is similar in appearance to our Model 407A but uses 2 low noise J-FETS in our specially designed RF stage which is tuned with high-Q miniature trimmers. The mixer is a special dual-gate MOSFET made by RCA to meet our requirements. The oscillator uses 5th overtone



crystals to reduce spurious responses and make possible fewer multipliers in the oscillator chain which uses 1200 MHz bipolars for maximum efficiency. Available with your choice of input frequencies from 300-550 MHz and output frequencies from 14-220 MHz. Usable bandwidth is about 1% of the input frequency but can be easily returned to cover more. Requires 12 VDC @ 30 mA.

Model 408 price ..... \$59.95  
.005% crystal included.

## VHF RECEIVER

11 crystal controlled channels. Available in your choice of frequencies from 135-250 MHz in any one segment from 1-4 MHz wide. I.F. bandwidth (channel selectivity) available in your choice of  $\pm 7.5$  kHz or  $\pm 15$  kHz. 8-pole quartz filter and a 4-pole ceramic filter gives more than 80 dB rejection at 2X channel bandwidth. Phase locked loop detector. Frequency trimmers for each crystal. .2 to .3 microvolt for 20 dB quieting. Dual-gate MOSFETS and integrated circuits. Self contained speaker and external speaker jack. Mobile mount and tilt stand.



Aluminum case, 6" x 7" x 1-3/8"  
Model FMR 260-PL price:  
135-180 MHz ..... \$149.95  
181-250 MHz ..... \$159.95  
Price includes one .001% crystal. Additional crystals \$8.95 ea. This receiver is recommended in Dr. Taggart's Weather Satellite Handbook.

## SYNTHESIZERS

### FOR ALL TRANSCIEVERS

The STR series synthesizers are available for any transceiver operating from 20 MHz to 475 MHz that uses crystals in the 5 to 85 MHz range. It has a thumbwheel dial calibrated for your operating frequency plus a selectable transmit offset of plus or minus 600 kHz, plus or minus 1 MHz, and 2 spare offsets that you can add later. Frequency accuracy is .0005% and spurious outputs are 60 to 70 dB down. To process your order we must have the crystal formula of your transmit and receive crystals. If your transceiver uses 1 crystal for both transmitting and receiving (like the Motorola Metrum 11), you can use our receive synthesizer described to the right. Maximum tuning range per synthesizer is 10 MHz above 100 MHz and proportionally less at lower frequencies. Dial increments are in 1 kHz steps from 5 to 30 MHz and 5 kHz steps above.



Model STR synthesizer price:  
5-150 MHz ..... \$259.95  
151-475 MHz ..... \$279.95

### FOR VHF RECEIVERS

This synthesizer has 8000 channels and can tune a continuous 40 MHz segment of your choice from 110-180 MHz in 5 kHz steps. This will satisfy most of your requirements in the VHF range and can save you hundreds of dollars in crystals plus a lot of time. Stock units are programmed for receivers with the crystal formula  $F_c = F_s - 10.7$  divided by 3 but we can program it to almost any other IF at no additional cost at the time of your order. It is supplied with an interface for plugging in to your existing crystal socket. Requires 12 VDC @ 1/2 amp which is easily obtainable from a low cost power supply. The synthesizer has 4 voltage regulators therefore the power supply need not be regulated. Phase noise is not detectable as the VCO is coarse tuned by a DAC thereby easing the requirements of the phase locked loop. Not affected by vibrations encountered in mobile use. Enclosed in an 8" x 3-7/8" x 1-1/2" aluminum case and supplied with a combination tilt stand/mobile mounting bracket.



Price: Model SR 140D-05 ..... \$179.95

NOTE: We can make any synthesizer from audio to 475 MHz. Call us for prices.

**HOW TO ORDER:** All items on this page are available only from Vanguard Labs. For receivers and converters state model, input and output frequencies, and bandwidth where applicable. For the fastest service call (212) 468-2720 between 9 AM and 4 PM Monday through Friday, except holidays. Your order can be shipped COD by Air Parcel Post.

**BY MAIL:** Send your order to Vanguard Labs, 196-23 Jamaica Avenue, Hollis, NY 11423 and include remittance by postal money order, cashiers check or certified check. Personal checks are also accepted, but banks now require 3 weeks for checks to clear, therefore this will delay your order. Include sales tax if you reside in New York State.

**PURCHASE ORDERS:** We accept purchase orders from US and Canadian government agencies, universities, and AAA rated corporations. Our terms are Net 30 days.

**FOREIGN ORDERS:** Must remit payment in full in US funds plus postage and insurance fees. If complicated customs forms are required, please forward your order to an import-export agent.

**SHIPPING:** We ship all our merchandise by insured parcel post or air mail. Special delivery is also available. Prices include shipping by regular parcel post if you remit with your order. For air mail shipping add \$1.00. Postage will be added on all CODs, purchase orders, and foreign orders.

**Vanguard  
Labs**  
196-23 Jamaica Ave.  
Hollis NY 11423  
(212) 468-2720

 <b>CEK'S DPDT PUSH BUTTON SWITCH.</b> \$1.50	<b>14 PIN CHIP CLIP</b> \$3.00	<b>.1 ohm FIVE WATT RESISTOR</b> 5/\$1.00	 <b>SO-239 65C PL-259 65C</b> 10/\$6.00 MIX/MATCH	<b>CIGARETTE LIGHTER PLUG</b> 79¢	<b>1N914</b> NEW HOUSE MARKED 100 for \$2.95	<b>NYLON CABLE TIES</b> 4 INCH 100/\$1.00 6 INCH 100/\$1.75 15 INCH 100/\$4.25
<b>1N4007</b> 1000 PIV AT 1 AMP NEW 8¢ PRIME	 <b>toggle switch</b> P-C OR PANNEL MOUNT MINI SWITCH SPDT \$1.00 10/\$8.	<b>HEAT Shrink</b> ASSORTED SIZES 10 FOOT BUNDLE 95¢	 <b>MJE3055</b> 90 WATTS 60VCE 10 AMPS. NPN 2/\$1.50	<b>MOLEX PINS</b> 200 EACH \$1.95 1000 EACH \$7.95	 <b>MALLORY SONALERT electronic signal</b> Model SC628-M 6 TO 28 VOLTS \$5.50	<b>30 AWG wire wrap</b> LT. GREEN DK. GREEN RED 100 FT. \$2.50
<b>50 ohm COAX</b> RG 174 U 50 FT. \$2.75	 <b>100 PIN EDGE CONNECTOR</b> S-100 BUSS -125 CENTERS \$3.95	 <b>SOUND ACTUATED RELAY CONTROL ASSEMBLED ON 1 X 2 1/4" BOARD HAS ALL PARTS LESS RELAY USES 3 TO 12 VOLTS \$1.50 3/\$4.00</b>	<b>WIRE WRAP TOOL</b> (FOR 30 AWG WIRE) Part Number WSU 30 \$5.95 ea WRAP STRIP INSULATION UNWRAP			
 <b>DIP SWITCH 5 POSITION</b> \$1.00	 <b>HOUSE MARKED 4 WATTS NPN 27MHZ 13.5VCE</b> \$2.75 EA.	 <b>2N5590</b> 10 WATTS 175MHZ VCC13.5 \$4.50	 <b>SUPER MINI BELL 5 TO 12 VOLTS DC. BELL DIA. 1-1/2"</b> \$1.50	 <b>BRIDGES 25 AMP.</b> 200 \$1.75 400 \$2.75 600 \$3.95	 <b>SOLDER TAIL IC SOCKETS</b> 14 PIN \$1.18 16 PIN \$1.18 24 PIN \$1.35 40 PIN \$1.85	 <b>TRANSFORMER 12.8 VAC 4 AMPS CENTER TAP</b> \$5.95
 <b>THIS ASSORTMENT OF POTS ARE NEW. WE JUST HAVE NOT HAD TIME TO SORT THEM. ALL ARE PC TYPE.</b> 10/\$1.00	 <b>4 'AA' SIZE CELL 500 MILL. AT 5 V</b> \$3.95	<b>DANGER HIGH VOLTAGE diode</b> 12,000 PIV 500 MA IF 60 AMP SURG. \$3.50	 <b>CRYSTAL OSCILLATOR</b> 4 MHz OSC. DIP SQU. WAVE Vcc 5V \$3.50	 <b>ALPHA NUMERIC 5 X 7 DOT MATRIX TIL-305 same as MAN-2, DL 57</b> \$3.50	 <b>115 VOLT OUTLET WITH SWITCH TAKES A 1X2 7/16 IN. HOLE</b> \$1.75 3/\$2.00	 <b>T. TONE PAD HOUSING BLACK ONLY</b> \$2.75
 <b>THIS USEFUL PIN WILL FIT OVER ANY .025 SQUARE OR ROUND PIN. SOLDERED OR CRIMPED. MANY USES OPTION CHANGES, ADDRESSING, LOGIC BOARDS, OR BREADBOARDS. 100 for \$1.00</b>	 <b>PROTECT YOUR EQUIPMENT INSTALL A THERMAL SWITCH CLOSING AT 240°F OPENS AT 200°F</b> \$3.25	 <b>SPECTRA STRIP</b> 12 CONDUCTOR 22AWG 5 FOOT \$1.75	 <b>BOXER FANS 100CFM 4.5 INCH FAN OPENING 1.5 INCHS DEEP EXHAUST OR BLOW 115 VOLT A.C. USED BUT GUARANTEED \$6.95</b>			
<b>Martin P. Jones and Associates</b>	P.O. BOX 9023 DEPT. HR RIVIERA BEACH, FLA. 33404 305-848-8236	 <b>FLA. RES. ADD 4% SALES TAX PLEASE ADD \$1.00 FOR ORDERS UNDER \$10.00. POST &amp; HAND MC &amp; BA ACCEPTED.</b>	 <b>NEW* MUFFIN FANS SAME SPEC. AS ABOVE EXCEPT NEW IN FACTORY BOXES \$12.95</b>			

# "THE PROFESSIONALS"

## DAVIS ELECTRONICS

### 500 MHz and 1 GHz COUNTERS

The CTR-2 Series Counters are designed and built to the highest standards to fulfill the needs of commercial communications, engineering labs and serious experimentors. With an accuracy of  $\pm .00005\%$  (oven option) the CTR-2 can handle the most critical measurements and is about half the cost of other commercial counters.

If you need a reliable counter at an affordable price, the CTR-2 is the answer.

- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler
- Automatic Dp Placement
- TCXO Std.  $\pm 2$  ppm
- Input Diode Protected
- 12V-DC Operation (Optional)
- Oven Controlled Crystal (Optional)  $\pm .5$  ppm
- Selectable Gate Times

	CTR-2-500	CTR-2-1000
RANGE	10 Hz to 512 MHz	10 Hz to > 1000 MHz

500 MHz Kit CTR-2-500K	\$249.95
500 MHz Assembled CTR-2 500A	349.95
1 GHz Kit CTR-2-1000K	399.95
1 GHz Assembled CTR-2 1000A	549.95

(OPTIONS)	(OPTIONS)	
(02) Oven Crystal \$49.95	(04) 12V DC	\$10.00
(03) .43" LED 10.00	(05) 10 sec. Time Base	10.00



DAVIS ELECTRONICS 636 Sheridan Dr., Tona., N.Y. 14150 716/874-5848



## NO COMPROMISE!



### ANTENNA BALUN

- Full 2KW, 3 to 30 MHz, 1:1 or 1:4 ratios.
- Special TEFLON insulated wire windings.
- May be used with tuned matching lines or antenna tuners. Withstands accidental high VSWR, great for antenna experimentation.
- Built-in hang-up and dipole center insulator.
- Totally weatherproofed by encapsulation, silver plated SO-239 coax connector input, and brass terminal output.

Balance your antenna, end radiation from coax, improve beam patterns, and lower receiving noise pick-up.

Free literature upon request.

Available at your dealer  
or order direct:

ONLY \$11.45 ppd. (specify ratio)

## K. E. ELECTRONICS


130A North Sherman Avenue  
Corona, CA 91720  
Tel. No. (714) 734-3820

ORDER NOW  
Call Toll Free  
1 800 828-7422

# Tone Encoding - Decoding at its **BEST**

## EXCITING NEW PRODUCTS

### RAP-200

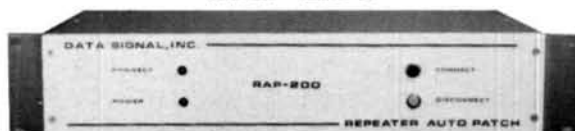

A Complete Autopatch facility that requires only a repeater and a telephone line. Features include single-digit access/disconnect, direct dialing from mobile or hand-held radios, adjustable amplifiers for transmitter and telephone audio, and tone-burst transponder for acknowledgement of patch disconnect.

RAP-200 P. C. Card  
RAP-200R Rack Mount

\$199.50  
\$249.50

### DATA TONE TO DIAL PULSE CONVERTER



The Data Tone to Dial Pulse converter Model DPC-221 provides full compatibility between Touch-Tone® encoders and rotary dial-pulse telephone exchanges. Two separate outputs for the \* and # digits provide remote control operation, and a cancel function permits the caller to automatically stop and reset the converter's dialing circuits.

DPC-221 P. C. Board  
DPC-221R Rack Mount

\$219.00  
\$299.00

### MIGHTY MOS



Complete C-MOS keyer, versatile controls allow wide character-weight variations, speeds from 5- to 50-wpm plus volume and tone control. Solid state output switching transistors are compatible with both grid-block and solid-state transmitters. Unit also available in kit and wired p. c. board only versions.

MIGHTY MOS  
P. C. Card - Wired  
P. C. Card - Kit

\$39.50  
\$24.95  
\$19.95

### TTP-1



### TTP-2



### UNIVERSAL TOUCH-TONE ENCODERS


The Data Signal TTP Series of keyboard encoders is used to generate the standard 12 or 16 DTMF digits. The encoders provide fully automatic transmitter keying and feature a delayed Transmit Ready light, an interdigit timer, and a built-in audio monitor. Features also include all solid-state, crystal-controlled, digitally-synthesized tones and an optional internal mount Automatic Number Identifier (ANI).

TTP-1 (12-digit)  
TTP-2 (16-digit)

\$59.00  
\$69.00

\*Touch-Tone is a registered trade name of AT&T.

### RAP-400

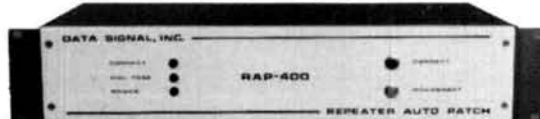

A complete Autopatch facility, similar to the RAP-200, that additionally provides for half- or full-duplex operation and features built-in compression amplifiers plus a long-distance inhibit function on digits 1 and 0.

RAP-400

\$749.00

### SME



### SUB-MINIATURE TOUCH TONE ENCODERS

MODEL SME — Smallest available Touch Tone Encoder. Thin, only .05" thick, keyboard mounts directly to front of hand-held portable, while sub-miniature tone module fits inside. This keyboard allows use of battery chargers. Price \$34.50, with your choice of keyboards.

### DTM



MODEL DTM — Completely self-contained miniature encoder for hand-held portables. Only 5/16" thick. Three wire connection. Automatic PTT keying optional. With your choice of keyboards. Price: DTM - \$49.50, DTM-PTT - \$59.50.

### DATA SIGNAL AND DIGITRAN KEYBOARDS

Style A



2 1/4" x 3"

Style B



1 5/8" x 2 1/8"

Style C



2 1/8" x 1 5/8"

Style D




2 1/8" x 2 1/8" 2" x 2 11/16" 2 1/2" x 2 11/16"

Style F



Style G

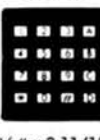

Ask About Our Deluxe Receiver Preamplifier For HF & VHF  
and

Send For Free New Catalog

**ds**


**DATA SIGNAL, INC.**

2403 COMMERCE LANE  
ALBANY, GA. 31707, 912-883-4703


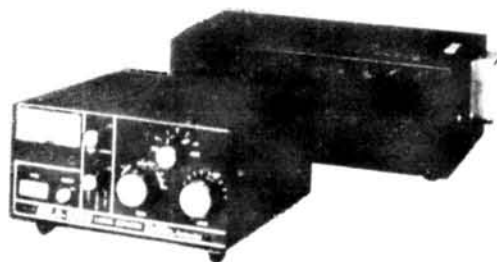
# We have DenTron's New MLA-1200

The MLA-1200 is a compact KW designed to fill the gap between your barefoot transceiver or transmitter and a full power 2 KW amplifier. A single 8875 external-anode ceramic/metal triode, (the same revolutionary tubes that power the MLA 2500) yields 1200 Watts PEP SSB and 1000 Watts DC CW with as little as 70 Watts drive. (An automatic swamping circuit prevents damage to the final if more than 100 Watts drive is applied to the MLA 1200.) There are scores of features common to both the MLA-1200 and MLA 2500, like forced-air cooling, all-steel chassis construction with tight fitting black wrinkle finish cabinetry, a plug-in PC board for metering, ALC, and mandatory warm-up timing. The MLA-1200 is the same size as our Super Tuner (just 10" W x 6 1/4" H x 10" D), and weighs only 10 pounds! Twin outboard power supplies are available for AC or DC operation, with the MLA-1200's low filament current drain characteristics allowing for standard 6 foot cabling between units. Both supplies are constructed of high quality, high current components, and are designed for a lifetime of trouble-free operation.




MLA-1200 - \$399.50

AC-1200 - \$159.50 DC-1200 - \$199.50

- 80 thru 10 meters
- 1200 Watts PEP input on SSB
- 1000 Watts DC input on CW, RTTY, or SSTV
- Forced Air Cooling System

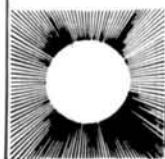- AC or DC Outboard Power Supplies (AC-1200, DC-1200)
- EIMAC 8875 external-anode ceramic/metal triode operating in grounded grid



# WESTCOM

COMMUNICATIONS DIVISION  
1320 Grand Ave. San Marcos, CA.  
(714) 744-0728 92069

## TEN-TEC ULTRAMATIC KEYS

### MODEL KR50

- SUPERLATIVE "FEEL" 5-50 GRMS PADDLE FORCE
- AUTOMATIC OR MANUAL WEIGHTING
- DIT AND DAH MEMORIES WITH SEPARATE DEFEATS
- "STRAIGHT KEY" OVERRIDE FOR QRS OR TUNE-UP
- GUARANTEED FOR LIFE BEARING PIVOTS

A sparkling new keyer with a host of exciting features. A powerful aid to cleaner, more articulate CW that is relaxing to use and a joy to copy.

The paddle assembly will delight the CW purist as well as the recent graduate from a bug or hand key. The superlative "feel" is attained by a magnetic return force, instantly adjustable to exactly the right touch for you.

Weighting, the ratio of dit and dah (bits) lengths to the spacing between them, is either automatically or manually varied. In the automatic position, it is programmed to lengthen the bits at slow speed for enhanced smoothness and decrease them as you advance the speed, for highest articulation. Or, it can be adjusted to a constant value.

The KR50 is versatile. Dit and dah memories are provided for full iambic (squeeze) keying. Either dit or dah, or both, may be turned off for operation as a conventional type keyer. Self-completing characters at all times.

A convenient "Straight key" is built-in for QRS sending or tune-up. Also an internal side-tone and 115VAC/12VDC operation is provided.

The KR50 is designed to have a permanent place in your shack for the years, perhaps decades, ahead. An investment in the enjoyment of CW.

PRICE \$110.00



### KR20-A

Paddle has unique principle with excellent feel for rhythmic CW. Characters are self-completing. Bit weighting is optimized for normal speeds. Manual key button conveniently located for hand sending. Side tone signal. Reed relay. Plug-in circuit boards. 115VAC or 6 to 14 VDC. HWD 2 1/2" X 4 1/2" X 8 1/4". Wt. 2 1/2 lbs.

PRICE \$69.50

### KR5-A

Similar to the KR20A but without monitor signal and AC power supply. A great value. For 6-14 VDC operation. Size HWD 2" X 4" X 6". Weight: 1 1/2 lbs.

PRICE \$39.50

### KR1-A

This is the paddle mechanism used in the KR50. Requires 6-14 VDC for adjustable electromagnetic paddle return force. Adjustable contact spacing. For iambic or conventional keyers. "Straight key" button. Housed in an attractive metal case with cream front panel, walnut vinyl top. Size: 2" X 4" X 6". Wt. 1 1/2 lbs.

PRICE \$35.00

### KR2-A

The paddle used in the KR20A. Single paddle for non-iambic keyers. "Straight key" button conveniently located, cream aluminum case with walnut vinyl top. Size: 2" X 4" X 6". Weight: 1 1/2 lb.

PRICE \$17.00

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862  
EXPORT: 5715 LINCOLN AVE., CHICAGO, ILL. 60646

**ASTRAL ELECTRONICS CORP.**  
321 PENN. AVE. P.O. BOX 707  
LINDEN, NEW JERSEY 07036  
201 - 486-3365

**PRIME QUALITY**  
**TUBES • SEMICONDUCTORS • IC'S • LED'S**  
IF YOU DON'T SEE IT, SEND A SASE  
AND WE WILL QUOTE.

FAIRCHILD	4051	5450	7489	135
VHF Preselector	4071	10160	7490	5/300
Chaps	4073	10230	7493	10/445
95H900C	8.90		74121	10/325
95H910C	9.40	3400Z	74132	10/660
1102H1C	15.35	3500Z	74148	1/20
1102S0C	74.30	31000Z	74150	5/450
1102S6C	12.20	5728	74151	5/475
1102Z4C	2.35	811A	74154	5/475
1102Z4C	2.35	1625	74155	1/15
1102S8C	4.50	5894	74157	5/475
1102Z0C	12.30	6146B	74163	5/300
1102S3C	29.15	6360	74164	5/475
1102Z0C	14.90	6883B	74170	2/75
1102S1C	15.90	7094	74176	5/375
Quantity:	8072	4200	74190	1/15
Discretes	8122	4950	74192	5/475
1N270	5/100	8236	74193	5/350
1N914	10/115	8950	74197	5/375
1N4001	25/115	8560	74211	10/300
1N4002	100/425	8643	74215	5/375
1N4007	20/110	8877	74230	Quantity:
100/525	7400	Quantity:	Linear IC	Price
1N4003	20/130	7400	301AH	10/290
100/570	7400	10/150	301 DHP	10/290
1N4004	20/150	7402	10/150	309A
100/590	7404	10/160	34015	2/190
1N4005	20/160	7407	10/250	34018
100/690	7408	10/170	34018	2/190
1N4006	20/180	7410	10/150	340112
100/760	7414	10/20	340115	2/190
1N4007	20/190	7425	10/250	340118
100/850	7430	10/150	340124	2/190
2N3055	2/185	7432	10/230	NE555V
2N3904	8/100	7438	10/200	565CN
2N3906	8/100	7441	10/700	566
Quantity:	7442	10/370	567	1/25
CMOS IC	7447	10/790	709105	10/250
4001	10/160	7453	10/150	723 DHP
4012	10/160	7454	10/150	741105
4017	5/350	7470	10/260	741MIN DHP
4028	5/375	7473	10/250	741DHP
4043	5/225	7474	10/280	747 DHP
4049	10/350	7476	10/300	1458 MIN DHP
4050	10/350	7485	10/990	5558

Free Metric Converter With Each Order

**FREE CATALOG WITH ORDER**  
**WE PAY POSTAGE**  
N.J. RES. ADD 5% SALES TAX MINIMUM \$10.00  
**SEND STAMP FOR FREE CATALOG**

# NEW

## Frequency Counter

### \$79<sup>95</sup> kit



UTILIZES NEW MOS-LSI CIRCUITRY

You've requested it, and now it's here! The CT-50 frequency counter kit has more features than counters selling for twice the price. Measuring frequency is now as easy as pushing a button, the CT-50 will automatically place the decimal point in all modes, giving you quick, reliable readings. Want to use the CT-50 mobile? No problem, it runs equally as well on 12 V dc as it does on 110 V ac. Want super accuracy? The CT-50 uses the popular TV color burst freq. of 3.579545 MHz for time base. Tap off a color TV with our adapter and get ultra accuracy — .001 ppm! The CT-50 offers professional quality at the unheard of price of \$79.95. Order yours today!

CT-50, 60 MHz counter kit ..... \$79.95  
CT-50 WT, 60 MHz counter, wired and tested ..... 159.95  
CT-600, 600 MHz prescaler option for CT-50, add ..... 29.95

#### SPECIFICATIONS

Sensitivity: less than 25 mv.  
Frequency range: 5 Hz to 60 MHz, typically 65 MHz  
Gatettime: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale  
Display: 8 digit red LED .4" height  
Accuracy: 10 ppm, .001 ppm with TV time base!  
Input: BNC, 1 megohm direct, 50 Ohm with prescale option  
Power: 110 V ac 5 Watts or 12 V dc @ 1 Amp  
Size: Approx. 6" x 4" x 2", high quality aluminum case  
Color burst adapter for .001 ppm accuracy available in 6 weeks.

CB-1, kit ..... \$14.95



#### CLOCK KIT 6 digit 12/24 hour

Want a clock that looks good enough for your living room? Forget the competitor's kludges and try one of ours! Features: jumbo .4" digits, Polaroid lens filter, extruded aluminum case available in 5 colors, quality PC boards and super instructions. All parts are included, no extras to buy. Fully guaranteed. One to two hour assembly time. Colors: silver, gold, black, bronze, blue (specify).  
Clock kit, DC-5 ..... \$22.95  
Alarm clock, DC-8, 12 hr only ..... 24.95  
Mobile clock, DC-7 ..... 25.95  
Clock kit with 10 min ID timer, DC-10 ..... 25.95  
Assembled and tested clocks available, add \$10.00

#### CHEAP CLOCK KIT \$8.95

DC-4 Features:  
• 6 digit .4" LED  
• 12 or 24 format  
Does not include board or transformer  
PC Board \$2.95  
Transformer \$1.49

#### 600 MHz PRESCALER



Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. Specify -10 or -100  
Wired, tested, PS-1B ..... \$59.95  
Kit, PS-1B ..... \$44.95

#### 30 watt 2 meter Power Amp

The famous RE class C power amp now available mail order! Four Watts in for 30 Watts out, 2 in for 15 out, 1 in for 8 out, incredible value, complete with all parts, instructions and details on T-R relay. Case not included.  
Complete Kit, PA-1 ..... \$22.95

#### VIDEO TERMINAL KIT \$149.95

A compact 5 x 10 inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are single 5-volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page control, parity error display and control, power-on initialization, full 64-character ASCII display, block type see thru cursor. Keyboard/computer control backspaces, forward spaces, line feeds, rev. line feeds, home, returns cursor. Also clears page, clears to end of line, selects page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 900 ma and outputs standard 75 ohm composite video.

TH3216 Kit ..... \$149.95  
TH3216, Assembled and Tested ..... 239.95  
V.D. 1, Video to RF Modulator Kit ..... 6.95

#### CAR CLOCK KIT \$27.95



12/24 Hour 12-Volt AC or DC  
• High Accuracy (1 minute/month)  
• 6 jumbo .4" LED readouts  
• Easy, no polarity hook-up  
• Display blanks with ignition  
• Case, mounting bracket included  
• Super instructions  
Complete Kit, DC-11 ..... \$27.95  
AUTO DIMMER \$2.50  
Automatically adjusts display brightness according to ambient light level. For DC-11 Car Clock.

#### CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car!

FEATURES:  
• 6 Digits, 5" High LED  
• 12/24 Hour Format  
• Calendar shows mo./day  
• Snooze button  
• True 24 Hour Alarm  
• 7001 chip does all!  
• Battery back up with built in on chip time base

Complete Kit, less case, DC-9 ..... \$34.95

## MINI-KITS

#### TONE DECODER KIT

A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.  
Complete Kit, TD-1 ..... \$4.95



#### SUPER-SNOOP AMPLIFIER

A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.  
Complete Kit, BN-9 ..... \$4.95

#### FM WIRELESS MIKE KIT

Transmit up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9 V. Type FM-2 has added super sensitive mike preamp.  
FM-1 ..... \$2.95 FM-2 ..... \$4.95

#### COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.  
Complete Kit, ML-1 ..... \$7.95

#### LED BLINKY KIT

A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.  
Complete Kit ..... \$2.95

#### POWER SUPPLY KIT

Complete triple regulated power supply provides variable .15 volts at 200 mA and +5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8 V at 1 Amp and 18 to 30 VCT.  
Complete Kit, PS-3LT ..... \$6.95



#### SIREN KIT

Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.  
Complete Kit, SM-3 ..... \$2.95

#### DECADE COUNTER PARTS

Includes: 7490A, 7475, 7447, LED readout, current limit resistors, and instructions on an easy to build low cost frequency counter.  
Kit of parts, DCU-1 ..... \$3.50

LINEAR			REGULATOR			TRANSISTORS		
5314 Clock	\$2.95	555	\$.50	78MG	\$1.49	MRF-238 30W VHF		\$11.95
74S00	.35	556	.75	309K	.89	NPN 2N3904 type	10/\$1.00	
74S112	.75	566	1.49	309H	.99	PNP 2N3906 type	10/\$1.00	
7447	.79	567	1.49	340K-12	.99	NPN Power Tab 40W	3/\$1.00	
7473	.35	1458	.50	7805	.89	PNP Power Tab 40W	3/\$1.00	
7475	.50	LED DRIVER		7812	.89	FET MPF-102 type	3/\$2.00	
7490A	.55	75491	.50	7815	.89	UJT 2N2646 type	3/\$2.00	
74143	3.50	75492	.50	7818	.89	2N3055 NPN Power	.75	

DIODES: 1KV.25A ..... 5/\$1.00 100V.1A ..... 10/\$1.00 1N914A type ..... 50/\$2.00

#### LED DISPLAYS

FND 359 ..... .75  
FND 510 ..... 1.25  
DL 707 ..... 1.25  
HP 7730 ..... 1.25

Red Polaroid Filter ..... 4.25" X 1.125" ..... .59

#### 741 OP-AMP SPECIAL

Factory prime mini dip with both Xerox and 741 part numbers  
10 for \$2.00

#### SOCKETS

14 PIN 5/\$1.00  
16 PIN 5/\$1.00  
24 PIN 2/\$1.00  
40 PIN 3/\$2.00

#### FERRITE BEADS

with info and specs  
15/\$1.00  
6 hole Balun Beads  
5/\$1.00

# ramsey electronics

P.O. Box 4072 Rochester NY 14610

(716) 271-6487

TELEPHONE ORDERS  
WELCOME



Satisfaction guaranteed or money refunded. COD, add \$1.00. Orders under \$10.00 add \$.75. NY residents add 7% tax.

When the winter winds blow you need...

# TOWER POWER by TRISTAO

**Superior Quality and Construction at a price you can afford.**

Tristao is a pioneer. Years of designing and manufacturing show in structural performance and practical pricing. Certified welded construction; sand-blasted surfaces; hot-dipped galvanized; heavy duty for capacity, strength, safety. Send for FREE Catalog.

Dealer Inquires always invited.

## Self-supporting or Guyed TOWERS

### CZ SERIES

Self-supporting 38' to 84' for most tri-band beams in 60 mph winds. Equipped with heavy duty winch.

### CTL SERIES

Guyed crank-up 18' thru 105' for tri-band beams to 8 sq. ft. Takes CDR HAM II and similar rotors. Complete installation packages available.

## TRISTAO MAST MASTER

Self-supporting  
Rotating - Crank-up

### SUPER AND STANDARD MINI-MASTS

Supports 10 sq. ft. antenna in 50 mph winds. Self-supporting. With winch and cable. Models from 40' to 67'.

### FULL-LINE OF MINI-MAST ACCESSORIES

### NEW EXCLUSIVE ROTOR BASE

For standard CDE or others including HAM II. Entire mast is rotated from ground level.

### CUSTOM TOWERS BUILT TO YOUR SPECIFICATIONS

Masts priced  
from \$198.50

All specs available on request.

## TRISTAO TOWER

Division of Palmer Industries, Inc.

415 E. 5th St. - P.O. Box 115  
Hanford, CA 93230 / Ph. (209)582-9016

Send me your complete catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

## CW Operators using Drake and Kenwood?

**Finally! Superior 8-Pole CW Selectivity for  
Drake TR-4, TR-4C, TR-4 Cw**

350 Hz at - 6db, 850 Hz at - 60db. Cuts QRM. More selective than 6-pole CW filter in new TR-4Cw which is 500 Hz at - 6db, and 2000 Hz at - 60db. CF-350/R \$100.00. Switch and mounting kit \$10.00

**At Last! Superior 8-Pole CW Selectivity for  
Kenwood TS-820**

350 Hz at - 6db, 850 Hz at - 60db, 1500 Hz at - 60db. Cuts QRM. More selective than standard YG-88C 6-pole CW filter which is 500 Hz at - 6db, and 1800 Hz at - 60db. CF-600/R \$100.00

**600 Hz 6-Pole First-IF Filter for Drake R-4C**

Improve the early stage selectivity. Eliminate those high-pitched beat notes from signals that leak around the switchable second IF filter. Minimize the chance of strong signals overloading the second mixer, causing intermodulation and desensitization. Both the existing filter and our CF-600/R can be mounted in the receiver and relay switched to retain phone capabilities. CF-600/R \$75.00. Relay switch kit \$29.00

**125 Hz 8-Pole Second-IF Filter for Drake R-4C**

Still sharpest available! 300 Hz at - 60db! Cuts QRM. Ideal for DX and contest work. Unexcelled under crowded band conditions. Does what no audio filter can do. More selective than audio filters. Puts selectivity in AGC loop. Unlike with audio filters, receiver gain not reduced by QRM outside passband. Yet works well with an audio filter to improve receiver performance. Plug directly into an accessory filter socket of the R-4C. CF-125/R \$125.00

**Attention:**  
*These crystal filters  
are for you!*

All filters contain  
specially-treated high-Q crystals.  
**Sherwood Engineering Inc.**

Dept. A  
1268 South Ogden St.  
Denver, Colo. 80210  
(303) 722-2257

Money back if not satisfied

Dealer Inquiries Welcome



**Rugged...compact (10"x17.5"x4.5")...lightweight (17.5 lbs.)**

**An extraordinary world of DX from  
your mobile station with the**

## All Solid State Metron 1000

**No tuning or adjustment whatever over  
80, 40, 20, 15 and 10 meters**

- For direct use with standard automobile battery/alternator
- Base station with optional 13.6V power supply
- Fully remote controlled
- Suitable for use with any transceiver in the 100W class
- Heatsink convector-cooled and thermostatically controlled
- 8 power transistors of latest stripline RF linear devices; rated for operation at infinite VSWR
- Meets all applicable specifications

Power input ..... 13.6V DC 1000W  
Power output ..... 13.6V DC 600W PEP typical  
Harmonics ..... -50dB all amateur bands  
Drive level ..... 60W PEP 50 ohms

For further details, send for free informative brochure.

**Dealer inquiries invited.**

## MAGNUS ELECTRONICS CORPORATION

5715 Lincoln Avenue, Chicago, Illinois 60659  
Phone (312) 334-1502 • Telex 253503 MAGNUS CGO

**OH!**

.....Have you been thinking about a wonderful Florida vacation, to places such as Disney World, Cypress Gardens, Sea World, the famous East and West coast beaches, and many of our other near by attractions???.....  
.....NOW, think about combining that vacation with one of the South's greatest Hamfest.....

# ORLANDO'S HAMCATION '78' and the FLORIDA STATE A R R L CONVENTION

AT THE SHERATON'S TWIN TOWERS HOTEL & CONVENTION CENTER, ON S-435  
NEAR THE CROSSROADS OF THE FLORIDA TURNPIKE AND I-4 INTERCHANGE.

**FEBRUARY 17\*-18-19, 1978**

DOORS OPEN.....\*6PM FRI. the 17th (Swapfest area only),  
7AM SAT. the 18th, 8AM SUN. the 19th.

●  
A R R L  
FORUMS

**ADMISSION, \$3 Advance, \$4 At the door.  
Ladies FREE, Children 14 and under FREE!!!**

●  
TECHNICAL  
FORUMS

THOSE ADMITTED FREE MUST BE IN THE COMPANY OF A REGISTERED TICKET HOLDER AT THE DOOR.

● MANY DOOR AWARDS ●

## GIGANTIC SWAPFEST AREA

25,000 SQ. FT. OF AIR CONDITIONED INDOOR COMFORT.

SWAPFEST TABLES \$5 PER TABLE PER DAY

●  
LARGE  
COMMERCIAL  
EXHIBIT AREA

## SATURDAY NIGHT BANQUET

\$8 per person —Great speaker lineup.

RESERVE BANQUET TICKETS IN ADVANCE, LIMITED QUANTITY AVAILABLE.

### FOR ADVANCE REGISTRATION, SWAPFEST AND BANQUET TICKETS

SEND CHECK PAYABLE TO : THE ORLANDO AMATEUR RADIO CLUB, INC.

HAMCATION CHAIRMAN, WB4HAK  
6 CAMELLIA DRIVE  
De BARY, FLORIDA 32713

●  
LADIES'  
ACTIVITIES

All advance ticket sales will be confirmed by return mail. Last postmark for advance sales will be Feb. 12th 1978.

FOR SHERATON TWIN TOWERS HOTEL RESERVATIONS, WRITE DIRECTLY TO:

The Sheraton Towers, 5780 Major Blvd. Orlando, Fla. 32805. Sing. \$28, Doub. \$36 per day.

Call toll free 1-800-325-3535. Mention that you are attending Hamfest Convention.

*Sorry!!! City ordinance prohibits overnight camping (Rec. vehicles, etc.) on parking lots.*

# 2 METER FM

and HF too ...  
SATELLITE  
HEADQUARTERS

See Erickson  
for all your  
Amateur Radio  
needs!

**WB9EBP, WB9JKT,  
WB9VIK serving you  
with ...**

- Ameco • ASP • Atlas
- Belden • Bird • CDE
- CES • Collins • Cushcraft
- Dentron • Drake • HAL
- Hy-Gain • Icom • KLM
- Kenwood • Larsen • MFJ
- Midland • Mosley • NPC
- Newtronics • Nye
- Regency • Shure • Swan
- Standard • TPL • Tempo
- Ten-Tec • Wilson • Yaesu



Hours: 9:30-9 Mon. & Thurs,  
9:30-5:30 Tues, Wed. & Fri.  
9-3 Sat.

**ERICKSON  
COMMUNICATIONS**  
5935 N. Milwaukee Ave.  
Chicago, IL 60646  
(312) 631-5181

**NEW!**

## Mini Counter

60 MHz  
600 MHz  
(with optional prescaler)

General Purpose Low Cost Counter Without the Sacrifice of Basic Performance  
"Check the features we have that some other low cost counters don't have."

- All Metal Cabinet
- 8 Digit 4" LED Display
- Input Cable Included
- 12V Input Jack
- Crystal Time Base
- 115V or 12V Operation
- Push Button Controls
- Gate Light
- Completely Auto Decimal Point
- Selectable Gate Times (1 sec & .1 sec)
- State of the Art LSI Circuitry
- Sensitivity < 10 MV

7208 60 MHz Kit ..... \$119.95 Assembled .... 169.95  
7208A 600 MHz Kit .. \$149.95 Assembled .... 199.95



DAVIS ELECTRONICS 636 Sheridan Dr., Tonawanda, NY 14150 716/874-5848



ORDER NOW  
Call Toll Free  
1-800-828-7422



### DIPLOLE ANTENNA CONNECTOR



**HYE-QUE (HQ-1)** dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip-cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers, or \$1.95 postpaid. Companion insulators 2/\$.99.

**BUDWIG MFG. Co.** PO Box 97H, Ramona, CA 92065

**See our HAM MART  
listings to find the  
Amateur Radio  
dealers nearest you.**

## ALL-MODE VHF amplifiers

FOR BASE STATION & REPEATER USE



MODEL	INPUT	OUTPUT	PRICE
V70	10-20W	60-70W	\$298
V71	1-5W	60-70W	\$329
V130	25-40W	110-130W	\$389
V131	1-5W	110-130W	\$419
V135	5-10W	110-130W	\$419
V180	10-15W	180-200W	\$525
Universal 19" Rack Mount			\$25

- ☆ 143-149 MHz No Tuning
- ☆ AM - FM - CW - SSB
- ☆ Low Harmonics
- ☆ Heavy Duty
- ☆ No Power Supply Needed
- ☆ Illuminated Panel Meter
- ☆ + 13.5V/3 Amp Socket

- ☆ 115 or 230V AC
- ☆ 60dB Spurious
- ☆ Fully Protected Output
- ☆ Internal T/R Switch
- ☆ U.S. Manufactured
- ☆ 19" Rack Panel Option
- ☆ Size 8-1/2 x 13 x 7" H

Only two things are needed to put this power house on the air with your handy-talkie or mobile transceiver: a two foot piece of coaxial cable and a 115 or 230 volt AC outlet. That's all. You do not need anything else. The mobile transceiver can be powered directly from the accessory socket located in the rear panel of the RFPL amplifier. It puts out + 13.5 volts at 3 amperes. This is sufficient for powering most 15 watt transceivers.



DEALER INQUIRIES INVITED



**RF POWER LABS, INC.**

11013-118th Place N.E. • Kirkland, Washington 98033 • Telephone: (206) 822-1251 • TELEX No. 32-1042

# BULLET ELECTRONICS

P. O. BOX 19442 DALLAS, TEXAS 75219

- No COD'S.
- Send check or MO.
- MasterCharge or VISA accepted.
- Texas Residents add 5% sales tax.

- Foreign orders add 10% (20% airmail)
- Catalog included with each order
- Orders over \$50. take 10% discount.

PHONE ORDERS (214/823-3240) ON MASTERCARD & VISA

*Did Somebody Mention Parts? Well, Here Are Just A Few Of The Items We Have. All Parts Are Prime & Guaranteed!*

## 160W NPN Darlington

HOUSE NO. 2N6283 TO-3 Power Transistors with Hfe of over 5,000! 80V V<sub>ceo</sub>. Output forms MJ3001.

**Limited Qty! - \$1.00**

**PICK A PAIR!**



8A Complimentary Darlington Power Transistors. MJ900 PNP, MJ1000 NPN. 90 Watts. Build high power audio amps.

**Buy a Pair for \$3.00!**

## ZENER Special!

ALL UNITS PRIME!  
Overstocked on these units:  
1N3030 1W 27 volt  
House no. 1/4W 5.4V  
House no. 1/4W 12.6V

**9 for \$1.00** (Same type)

## MC1351P FM IF, Limiter, Discriminator & AF Pre-Amp

14 PIN IC. COMPLETE FM SOUND SUB SYSTEM USES MINIMUM EXTERNAL COMPONENTS. COMPLETE SPECS AND APPLICATIONS INFORMATION.

**House # - 5/\$1.00**

## General Purpose NPN

2N3569 Fairchild V<sub>ceo</sub> = 60V  
Hfe to 300. 800MW power.  
epoxy TO-5. Limited Qty!

**6 for \$1.00**

## Wideband AMP IC, High Gain

100Khz to over 20Mhz. Good for IF's and low frequency Complete Specs!

**CA3011 50¢ each**

## MULTICOLORED 26 CONDUCTOR

Ribbon Cable No. 28 wire with a woven binder for easy separation. Super flexibility! Compare our price!

10' Roll \$2.95  
50' Roll \$9.95

## MC1469R

VOLTAGE REGULATOR IC  
Versatile 500Ma regulator is adjustable with a single external resistor from 3 to 30 volts. Provisions for current limit and remote shutdown. Complete specs and application notes are included. \$1.25 each or 10/\$10. External series pass will provide currents to 20 amps.

## Heatshrink Tubing

SPECIAL A very good assortment of 3/32", 1/8", 3/16", 1/4" and 7/16" heatshrink tubing 12 6" lengths for .75 Assorted colors

## Quad Matched Diodes

Four closely matched 1N914 type diodes for balanced bridge or modulator circuits. One set - \$1.00

## 2N5590

RF POWER TRANSISTOR

Just what you've been looking for: 10 Watts with 13.5VDC supply. Frequencies to 300 MHZ. Limited Quantity!

**\$3.95**

## PMOS Counter Chips

Single digit pre-settable up or down BCD counter with 7 segment decoded output/driver has internal latch. Requires +12, & +24VDC. Build counters, timers, etc. Complete specs. 24 Pin IC 4/\$5.00

## #30 Silver Plated

Wirewrap wire with Kynar® jacket. 4 colors available, 100 ft. of each color.

**\$4.95 (400')**

**BULLET LUCKY NUMBER!** Starting next issue a number will be listed in our ad that corresponds to a number on one of our catalogs. The number is worth \$100! Watch for the special number on your Bullet Catalog.

**WE ALSO SELL A GROWING LINE OF QUALITY KITS. WE HAVE SHIPPED 1000's!**

## PS-14 HIGH CURRENT REGULATED POWER SUPPLY KIT

A low cost, no frills, heavy duty power supply. Designed for use and abuse!

**12V @ 15A CONTINUOUS**

Less Case, meters & jacks

- Better than 200MV load & line regulation
- Foldback Current Limiting
- Short Circuit Protected
- Thermal Shutdown
- Adjustable Current Limiting
- Less than 1% ripple
- 15amps 11.5 to 14.5V
- All parts supplied including heavy duty transformer
- Quality plated fiberglass PC board

**\$39.95**

UPS SHIPPING PAID!

## POWER SUPPLY ACCESSORIES

Quality 3 1/2" Meters for PS-14 (0-25A; 0-15 VDC) Individually Packaged. Not Surplus \$12.50/set

## OVERVOLTAGE PROTECTION KIT

Provides cheap insurance for your expensive equipment. Trip voltage is adjustable from 3 to 30 volts. Overvoltage instantly fires a 25A SCR and shorts the output to protect equipment. Should be used on units that are fused. Directly compatible with the PS 12 and PS 14. All electron users supplied. Drilled and plated PC board. (Order OVP 1)

**\$6.95**

**MINI GRANDFATHER CLOCK KIT**  
Just in case you have spent the last six months in Siberia, we will tell you one more time that BULLET has the ONLY Completely Electronic Grandfather Clock Kit in the world that has all the below listed features. The biggest problem we have is to try and describe how unique and fascinating this clock really is! The Swinging LED Pendulum and Matching Tick-tock sound are available only on our clock. In addition the electronic chime notes each hour (ie. 3 times for 3 o'clock). Housed in the optional SOLID HARDWOOD CASE, the unit makes a beautiful addition to any room as well as a great gift.

- 1/2" 4 digit LED readout
- Adjustable Tone & Duration on Chime
- AM/PM indicator
- Simulated swinging pendulum uses LEDs
- All CMOS construction
- All electronics, switches and transformer inc.
- Quality plated PC boards (2) 6.5" x 4.5"

**MG-01 \$39.95**

**BEAUTIFUL SOLID HARDWOOD CASE FOR MG-01:** Case is cut, grooved and finished for clock. Includes Ruby front filter. Quick easy assembly requires only 4 screws (included) \$19.95  
**CHRISTMAS/HOLIDAY SPECIAL:** Buy an MG-01 at regular price and get the case for a low \$12.95. Your total cost \$52.90. Good till 1/31/78.

## MK-05 MINI MOBILE CLOCK

The smallest and best priced mobile clock kit on the market. Designed to be a mobile clock from the ground up. There has been no compromise on quality.

### FEATURES:

- Quartz crystal timebase
- Toroid & zener noise & overvoltage protection.
- Magnified 15", 6 digit LED readout
- Complete with presettable 24 hr. alarm
- 9-14 VDC @ 40 to 50 ma
- Readouts can be suppressed
- EASY, QUICK ASSEMBLY
- All components required included (you supply the speaker)
- Top quality drilled and plated PC boards.
- Clock board: 2.6" x 2"
- Readout board: 2.3/8" x .75"

**\$12.95**

With purchased front aluminum case - \$15.95




Small enough to mount on the instrument panel!

## MK-06 CLOCK/CALENDAR AUTO/HOME CLOCK KIT

Nothing else to buy!  
Can be panel mounted.  
Great for Vans & RV's!

We designed this to be a SUPER CLOCK with ALL the features you want. Quality double sided PC boards make assembly easy. Mobile (12VDC) or home (12VAC)

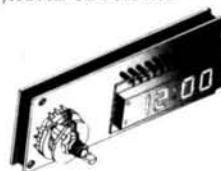- Large 1/2" LED Readout
- AM/PM Indication
- 28/30/31 day calendar displays automatically or manually
- Display can be dimmed or blanked
- Flashing Colon counts the seconds
- Integral Timebase is adjustable
- Presettable Alarm with Snooze Feature.
- Noise and voltage protection circuits
- Single front mounted rotary switch selects all functions



Additional Options  
24 hour format; Add \$2.  
12VAC XFMR for 110 operation add \$1.75

**\$21.50 LESS CASE**

# POLY PAKS® IS THE WORLD'S LARGEST ELECTRONIC SUPERMARKET DISCOUNT

DEC. 77 HAM MAGAZINE SPECIALS

## CONDENSER MIKE "TIE-PIN" TYPE

It's a little giant in sound quality. Metal encased with built-in PET circuit, omnidirectional, freq. resp. 20-12,000Hz. Less tie pin or lapel clip. 600 ohm impedance, 1.5VDC. No. 12H3178 **4.95**

7/16" x 1/8" long

# SANTA'S BARGAINS

## "GEL-SEL" POWER PAK

Rechargeable! Perfect for back-up power for computers, alarms, and more. Sealed, spill-proof, leak-proof. Better than Ni-CADS, recharges to 100% efficiency. Compact, only 4" x 1" x 2", stack 'em in series or parallel. Lead or lead/antimony gel (sorry, no choosing). Wt. 16 ozs. No. 12H4088 **\$4.95**

## AM-FM-MPX TUNER AMP

40 Matrix for 2 & 4 speaker systems or Wall/Console Contemporary design black and chrome front panel

**The Philharmonic**  
SPECIFICATIONS: AMP: Pwr. out 5W x 2 RMS, both chn into 8 ohms, 40-20000 Hz. THD 0.9%. Freq. resp. 15-20,000±2db, S/N ratio 56db, FM: Sens 2.7 uV for 20 db S/N. Requires 115VAC 60 Hz. Size: 8 1/2" x 13 1/2" x 3 1/2", Wt. 7 lbs. Cat. No. 12H3933 **\$14.95**

## 4D MATRIX

Simulates quad sound from stereo FM, tapes, and records. Gives feel of a live performance. Slide controls for VOLUME, BASS, TREBLE and BALANCE. Selector for PHONO, TAPE, AM, FM, FM-MPX. Rocker switches for POWER ON/OFF, APC, STEREO/4D MATRIX. Also features stereo headphone jack, FM stereo indicator. Cat. No. 12H4007 **\$69.95**

## 1-AMP REGULATED POWER SUPPLY

New! Easy to assemble! Uses LM340K positive voltage regulator. Reverse leads for a negative supply. Buy 2 for a 2-amp supply! With transformer, regulator, PC board & all components. Complete kit, nothing else to buy. Wt. 4 lbs. Your choice

Cat. No.	Volts	Price
12H3854	5	2 for \$15.95
12H3857	12	
12H3858	15	

## 100 KHZ MARKER CRYSTALS

Build your own marker generator at 100, 200, 300 KHz etc. Calibrated receiver. Accuracy 0.001% size 1 1/2" x 1/2". With instructions for building marker generator. \*100 KHz after trimming. Wt. 1 oz. Order by Cat. No.

12H3859	<b>\$2.95</b>
104.067 KHz	105.000 KHz
104.092 KHz	114.000 KHz

## POLY PAKS "CHIPS" AWAY IC PRICES!

Order Cat. No. 12H4048 and Type No.

Type	Stopwatch	Sale
ICM7205	6 1/2" Digit DVM	\$14.95
AV2-8500-1	Six Tr. Counter	9.95
MM5330	300 MHz Prescaler	4.95
8038C	Volt Control Osc.	4.95
KR2376	Encoder ROM BCD	6.95
98H800C	250 MHz Prescaler	6.95
MM14410	Touch Tone Encoder	9.95
MM2002P	Char. Gen. (2513 equl)	3.95
7207A/7208	Frequency Counter, pair	29.95
ICM7107	3 1/2" Digit DPM	12.50
MM5316	Alarm Clock	2.95
8080A	Microprocessor	14.95
1702A	8080A EPROM	4.95
2708	8K EPROM	22.95
2102-1	1K RAM	1.39

## LAB-N-HOBBY TEST EQUIPMENT FACTORY OVERSTOCK

### TRANSISTOR CHECKER DYNAMIC

Tests NPN, PNP, Powers and unknown semi's. Simple to use, both in-or-out of circuit. Automatically identifies polarity. Tests leakage, similar transistors. Use with VOM to test noise, dynamic leakage and more. Built-in quick test socket. Requires 1 1/2" "D" cell. With instructions. 2 1/2" x 2" x 5". Wt. 16 ozs. Cat. No. 12H5932 **\$14.95**

### Transistorized SIGNAL TRACER

It's like having a third hand. Simplifies locating circuit troubles in AF, RF, and IF circuits. Easy to use, compact and lightweight, only 2 1/2" x 2" x 5". Built-in speaker and gain control, with test leads. Requires 9V battery. 16 ozs. Cat. No. 12H3934 **\$12.95**

## STEREO TO QUAD ADAPTOR

Derives quad sound from 2 channels. Works with all mod-12H3910 els. all makes, hooks up in seconds. Gives the feel of a "live" performance. No power necessary. Inputs 2 RCA plugs, outputs 4 RCA jacks. Size: 3 1/4" x 2 1/2" x 2". Wt. 14 ozs. Cat. No. 12H3934 **\$2.95**

## 25% OFF BUY 100

## 15% OFF BUY 10

We know we have the lowest prices!

Type	Sale	Order by Cat. No. 12H1981	A Type No.
SN7400	\$0.14	SN7400	SN74141 .92
SN7401	.14	SN7401	SN74145 .89
SN7403	.14	SN7402	SN74146 .91
SN7404	.17	SN7403	SN74147 .93
SN7405	.19	SN7404	SN74148 .94
SN7406	.19	SN7405	SN74149 .96
SN7407	.24	SN7406	SN74150 .98
SN7410	.14	SN7407	SN74151 .99
SN7411	.14	SN7408	SN74152 .99
SN7412	.14	SN7409	SN74153 .99
SN7587	.14	SN7584	SN74328 .99
SN7588	.14	SN7585	SN7432

# flea market



**RATES** Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N.H. 03048.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

**YAESU EQUIPMENT OWNERS** — Present or Prospective — Join the six-year-old, 2500 member, 42-country, International Fox-Tango Club. Members receive valuable monthly Newsletter, money-saving purchasing service, technical committee consultation, free ads, FT net, more. Back issues of Newsletter available from 1972. To join, send \$5 for calendar year (includes all 1977 issues of Newsletter) or \$1 creditable towards dues, for complete information and sample Newsletter. Milton Lowens, W2A0Q/N4ML, 248 Lake Dora Drive, W. Palm Beach, FL 33411.

**QRP TRANSMATCH** with Preamp for HW7 Ten-Tec. Send stamp for details to Peter Meacham Associates, 19 Lorreta Road, Waltham, Mass. 02154.

**WANTED** — Manual for Panoramic Electronics Model SPA-4a Spectrum Analyzer — Judson Snyder, K2CBA, Petersburg, N.Y. 12138.

**CANADIANS** 1,000,000 surplus parts. Bargains galore. Free catalog. Etco-HR. Box 741, Montreal, H3C 2v2.

## Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria  
Karl Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio Belgium  
Sterehouse  
Brusselsesteenweg 416  
B-9218 Gent  
Belgium

Ham Radio Canada  
Box 114, Goderich  
Ontario, Canada N7A 3Y5

Ham Radio Europe  
Box 444  
S-194 04 Upplands Vasby  
Sweden

Ham Radio France  
Christiane Michel  
F-89117 Parly  
France

Ham Radio Germany  
Karl Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio Holland  
ML Etconics  
Postbus 98  
NL-2204 Delft  
Holland

Ham Radio Italy  
STE, Via Maniagio 15  
I-20134 Milano  
Italy

Ham Radio Switzerland  
Karl Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio UK  
P.O. Box 63, Harrow  
Middlesex HA3 6HS,  
England

Holland Radio  
143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

**PORTA PAK** the accessory that makes your mobile really portable. \$67.50 and \$88.00. Dealer inquiries invited. P.O. Box 67, Somers, Wisc. 53171.

**TRAVEL PAK QSL KIT** — Send call and 25¢; receive your call sample kit in return. Samco, Box 203, Wynantskill, N.Y. 12198.

**MERRY XMAS and HAPPY NEW YEAR** from W0CVU. Now Using: KENWOOD TS-820S, DRAKE L-4B and TELREX Xmas Tree.

**MULTIBAND INVERTED VEE** 80-10m. Shorter than 75m "V" G5RV plans \$1. WB3EZH, 229 Noble, Souderton, PA. 18964.

**QSL — BROWNIE W3CJI** — 3035B Lehigh, Allentown, Pa. 18103. Samples with cut catalog 50¢.

**VHF ENGINEERING COMPANY REPEATER** 35 watt Power Amplifier. North Shore Technology Duplexer Power Supply All in one package — Operating Xtals for 31-91. Ozone Amateur Radio Club, P.O. Box 553, Slidell, LA 70459.

**NATIONAL NC-183** General Coverage receiver complete with manual. Poor condition as is \$40. Steven Terhaar, WA0PXQ, 650 Beech, Moorhead, MN. 56560.

**FOR SALE**, Brand new boxed advance coax relays. 6, 12, 24, 100VDC. 117VAC. \$15.00 with aux. contacts. \$12.00 each without. Antique R.R. Sounders (new) \$50.00 each — have three. Add \$1.00 shipping. James Gysan W1VYB, 53 Lothrop Street, Beverly, Mass. 01915.

**SELL:** ROBOT 70A monitor, 61 viewfinder, 80A camera with 25mm 1.4 lens, 8- and 15-foot camera cables. Original cartons and instruction books. Recently factory calibrated. \$500. Gordon Buckner, W0VZK, Box 721, Marshall, MO. 65340.

**MOTOROLA HT220, HT200**, and Pageboy service and modifications performed at reasonable rates. WA4FRV (804) 320-4439, evenings.

**AUTHORIZED DEALER** for Dention, KLM, Larsen, Bearcat, etc., Big Catalog 201-962-4695 Narwid Electronics, 61 Bellot Road, Ringwood, N.J. 07456.

**RECONDITIONED TEST EQUIPMENT** for sale. Catalog \$50. Walter, 2697 Nickel, San Pablo, Ca. 94606.

**PERSONALIZED CODE TAPES** Specify: Speed (5-99 WPM), Content (Letters, or Punctuation and Numbers, or Both). 60 minutes for \$4.00. TRICOMM, P.O. Box 5036, Aloha, OR 97005.

**VERY in-ter-est-ing!** Next 4 issues \$1. "The Ham Trader", 2435 Fruitville, Sarasota, FL 33577.

**D & V RADIO PARTS** — variable & trimmer capacitors, chokes, Miniductors, stocked for immediate shipment. First class stamp for flyer — 12805 W. Sarle Rd., R#2, Freeland, Michigan 48623.

**REGENCY:** HR2A with SYN II, Synthesizer, P-107 Power Supply, all \$180.00: in mint condition. C. P. Gibson, 101 N. Henniger, Leitchfield, Kentucky 42754.

**CASH** for your clean ham gear. Beacon Communications — used equipment specialists, 879 Beacon St., Boston, Mass. 02215. 617-267-1975.

**BECKMAN/BERKELEY** Counter manuals. Most models, \$5.00 each postpaid. 51J4; \$425.00, 618T3; \$1,990.00. W9AMZ, 2069 Hopi, Mont Prospect, IL. 60056.

**HAM RADIO HORIZONS**, a super new magazine for the Beginner, the Novice and anyone interested in Amateur Radio... What it's all about, How to get started, The fun of ham radio. It's all here and just \$10.00 per year. HURRY! HURRY! Ham Radio HORIZONS, Greenville, NH 03048.


**FOR SALE:** Send long, stamped SASE for list of Radio and Optical parts. Fred Redburn, 3300 Hobbs #127, Amarillo, Texas 79106. 806-352-2443.

**TELETYPE FOR SALE:** Model 28ASR's, KSR's, typing reperts, and TD's. New and used parts available including cabinets, tables, mod kits, gears and gearshifts. Paper, ribbons, and supplies. Some 8-level Model 33 and 35 equipment available. Send SASE for complete list and prices. K9WJB, Lawrence R. Pfleger, 2141 N. 52nd St., Milwaukee, WI 53208.

**BUY-SELL-TRADE.** Write for free mailer. Give name, address and call letters. Complete stock of major brands new and reconditioned equipment. Call for best deals. We buy Collins, Drake, Swan etc. SSB & FM. Associated Radio, 8012 Conser Overland Park, Kansas 66204.

**LET'S TRADE.** I have new HORNET ANTENNAS. 6-10-15 & 20 meter beams; 10 to 80 element 2-meter antenna systems; stacking kits, antenna hardware, etc. I need good clean transmitters, receivers, transceivers, test equipment. Jack W5AJZ, Box 880, Duncan, OK 73533.

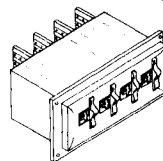**Thumbwheel Switch**, 0-9, BCD encoded, 4 sections. Size app. 1" x 3", factory new. Quan. limited.



\$5.50 ea. ppd.



**Wire-Wrap Prototype Board.** Factory new — never wired. Assorted sockets. Some 8 pin — 14 pin — 16 pin — 24 pin. Our choice: Boards with 10 to 30 sockets \$12.50 ea. Boards with 30 to 55 sockets \$18.00 ea. ppd.

**Matching wire wrap 86 pin edge connector** while supply lasts \$2.50 ea. ppd.

**4PDT Relay**, 12VDC coil, Potter Brumfield, 5 amp contacts, factory new of course, a beauty \$1.90 ea.



**Mini-Toggle Switches**, factory new and complete with all hardware. SPST 90c ea. ppd.

**Jumbo LEDs.** .2 inch diameter. Color-Red. Prime factory units. Not seconds or retests. 20c ea. ppd.

**2" Square Speaker.** 8 ohms. Mounting holes in the corners. Very nice unit and easy to mount. \$1.00 ea. ppd.



**6 foot AC Line Cords.** 2 conductor heavy duty. Color white. 40c ea. ppd.

**1/16" Copper Clad PC Board Material** 3"x3" — 2 for 25¢; 3"x6" — 30c ea.; 6"x6" — 75c ea.

**18 pin Solder Tail, IC Socket** — for that memory chip. 28c ea. ppd.

**Ceramic Disc Capacitors** all new full leads .004 @ 1000 volts; .1 @ 12 volts; .02 @ 100 volts; .001 @ 100 volts; .05 @ 100 volts; Your choice 20 for \$1.00

**2-1/4" Round Speaker.** 8 ohms — .3 watts. Factory new of course. \$1.00 ea. ppd.



**Resistor Assortment.** All new FULL leads. Color coded. Some 1/8 - 1/4 - 1/2 watt. 100/\$3.00 ppd.

**88 mHz unpotted toroids** 5 for \$3.50

**2N3391A NPN plastic transistors** 7c ea.

**1N4148 diodes** — cut and formed leads 100/\$1.10

**Wire Wrap Sockets**  
8 pin ..... .22 ea.  
14 pin ..... .28 ea.  
16 pin ..... .35 ea.  
24 pin ..... .70 ea.

**8.0000 MHz Crystal** — HC6 holder 3.50 ea.

**1000 volt PIV 2 amp diodes** .10 ea.

ALL ITEMS PPD USA  
SEND STAMP FOR LIST OF BARGAINS  
PA RESIDENTS ADD 6% SALES TAX  
FONE 412-863-7006



**Full Electronics**  
12690 ROUTE 30  
NORTH HUNTINGDON, PA. 15642

**250 MHz... ONLY \$129.95**

**STOP!** Don't order that counter kit until you see what EEB has come up with.

The **NEW B & K 1827, 30 MHz counter (assembled and tested)**, a famous pre-scaler kit, hardware and complete instructions to result in 250 MHz Counter. **ALL FOR \$129.95 postpaid!**



## Model 1827

- 30 MHz reading guaranteed, 50 MHz typical.
- Full 6-digit display with range switch allows 8-digit accuracy.
- 1Hz resolution — even at 30 MHz and beyond.
- Completely portable for use anywhere.
- Exclusive battery saver features auto-shutoff of display to reduce battery drain.
- Operates on AA size batteries, AC with optional charger/adaptor or 12VDC with optional power cord/adaptor.
- **SPECS:**  
FREQUENCY CHARACTERISTICS  
Range: 100Hz to 30 MHz (guaranteed); 50 MHz typical. Accuracy:  $\pm 1$  count. Resolution: 1 PPM of a 6 digit scale.  
INPUT CHARACTERISTICS  
Impedance: 10 K $\Omega$  minimum. Connector: RCA Phono. Sinewave Sensitivity: 100mV RMS; 200 kHz—30MHz. 200mV RMS; 100Hz—200kHz.  
INTERNAL TIME BASE CHARACTERISTICS (25° C).  
Frequency and Type: 4.0MHz crystal oscillator. Setability:  $\pm 0.25$  PPM ( $\pm 1$ Hz). Temperature Stability: Better than  $\pm 0.001\%$  (i.e.  $\pm 10$  PPM) from 0-50°C ambient.

**Model 1827 only** \$119.95  
**Prescaler Kit** 22.50  
**Misc. & Instructions** 12.50  
**\$154.95**

**YOU PAY ONLY \$129.95**

**AC Charger and NICADS** \$31.00  
**Test Antenna (BNC)** \$4.00

## NEW MS-15 MINISCOPE



A Serviceman's Small Oscilloscope with Big, Big Performance and a Low, Low Price. The Model MS-15 by Non-Linear Systems, Inc.

### FEATURES

- 15 megahertz bandwidth.
- External and internal trigger.
- Time Base — 0.1 microseconds to 0.5 Sec/div — 21 settings.
- Battery or line operation.
- Size: 2.7"H x 6.4"W x 7.5"D
- Automatic and line sync modes.
- Power consumption less than 15W.
- Vertical Gain - 0.01 to 50 volts/div 12 settings.
- Weight is only 3 pounds.

**• \$289.00**

**Guess who's got your BIRD**



- EEB DOES, and here's why...
- We pay the **AIR FREIGHT** on all prepaid or credit card orders.
  - Call our order desk collect: 703-938-3511.
  - We stock in depth: Bird 43 Thruline, All Table 1 elements, CC-1 & EC-1 cases.

**\$120.00**

**AUTHORIZED BIRD DISTRIBUTOR**

All Prepaid & Charge Orders  
Shipped **NO CHARGE** To You.  
Sales tax 4% to Virginia residents only.

**ELECTRONIC EQUIPMENT BANK, INC.**

516 Mill St., Vienna, VA 22180  
Call **COLLECT 703-938-3511**

# flea market

**SELLING:** 120 Hz sharpest CW filter for TS-820. New. \$95. Yamada, Box 272, FPO, Seattle 98761.

**FREE Catalog** Solar Cells, Nicads, Kits, Calculators, Digital Watch Modules, Ultrasonics, Strokes, LEDs, Transistors, IC's, Unique Components. Chaney's, Box 27038, Denver, Colo. 80227.

**TELETYPE EQUIPMENT** for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

**KEYER** Micro-T0 MKII PC boards, parts. K3CU(W), 5414 Old Branch, Washington, DC 20031.

**MOBILE BONDING STRAPS** under 50¢ each. Literature. Estes Engineering, 930 Marine Drive, Port Angeles, Wash. 98362.

**COLLINS CW Filter**, 300Hz bandwidth X455KF300. For use in 75S3, 75S3B and 75A4 receivers. See Sept. 1975 H.R. for article. \$60.00 postpaid. W1EBC, Gary Firtick, 40 Pilgrim Trail, Woodbury, CT. 06798.

**FERRITE BEADS:** w/specification and application sheet - 10/\$1.00. Assorted PC pots - 5/\$1.00. Miniature mica trimmers, 3-40 pf. - 5/\$1.00. Postpaid. Includes latest catalog. Stamp for catalog alone. CPO Surplus, Box 189, Braintree, MA 02184.

**THE "CADILLAC"** of QSL's! New! Samples: \$1.00 (Refundable) — MAC'S SHACK; Box #1171-D; Garland, Texas 75040.

**CASH** for any Collins unit, 618T, 490T, modules, parts, accessories. Air Ground Electronics, P.O. Box 416, Kearny, NJ 07032.

**TELETYPEWRITER PARTS**, gears, manuals, supplies, tools, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, FL. 33310. N4TT Buy parts, late machines.

**EXCLUSIVELY HAM TELETYPE** 23rd year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 35¢. \$3.50 per year. 1155 Arden Drive, Encinitas, Calif. 92024.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada M1S 3B4.

**RUBBER STAMP**, name/call/QTH \$2.50 ppd. (CA residents add tax). LWM Press, Box 22161, San Diego, CA 92122.

**COMPUTER HOBBYISTS** — Classified advertising newsletter. Ads, New Products, etc. Every 3 wks. — Since Jan 76. \$3.75/year. Free Sample. ON LINE, 24695 Santa Cruz Hwy., Los Gatos, CA 95030.

**FOR SALE:** Cleaning our garage and store room. Many choice items. SASE for large list. W9ZPP 2824 Forest Ave., Evansville, Ind. 47712.

**FOR SALE:** GE TPL rear mount 80 watt RE73 130-150 MHz, 2-freq. transceivers. No accessories. \$40 each. W9ZPP 2824 Forest Ave., Evansville, Ind. 47712.

**TRANSFORMER** Brand new with application note. 115V Primary, Dual Secondaries each 18VCT at 4 amperes. \$24.00 NY Residents add 8% Tax. Inquiries Invited. Classical Electrodynamics Labs, PO Box 190, Jackson Heights, NY 11372.

**WANTED:** HRO dial w/drive, 455 kHz SSB, CW filters. Thurtell, Rte. #1, Paw Paw, MI 49079.

**TOROID CORES!** 20 for \$6.00. Various sizes. SASE Catalog. OK Electronics, Box 291, Onalaska, WI. 54650.

**WANTED:** 40 Channel SSB/AM CB Transceiver with Antenna, ATLAS 180/210/215X. TRADE or SELL: New Television Camera with Zoom lens, SLR viewfinder, 2:1 interlace; OR HW-2021 Handytalky 2M transceiver. W6DOM, 6017 Majorca Ct., San Jose, Calif. 95120 (408) 997-0132.

**OLD TELEPHONE WANTED**, Handheld upright with or without dial. Also Old spring suspended mike & Old Key. Del Popwell, K4NBN, Box 23413, Jacksonville, Fla. 32217.

**QSL FORWARDING SERVICE** — 30 cards per dollar. Write: QSL Express, 30 Lockwood Lane, West Chester, PA. 19380.

**ELECTRONIC PARTS** — Service supplies. Talk to me! Free list — Tommy, WD4EKJ, Comm-Tech, 104 North Third Street, Richmond, Kentucky.



**BE ON TARGET**

with  
**JAN QUARTZ CRYSTALS**  
for

- CB Synthesized • CB Standard
- General Communications
- Industry • Two-Meter
- Monitor • Scanners
- Marine VHF • Amateur Bands

*Dependable USA Mfg. for*

- Frequency Control
- Frequency Stability
- High Performance

Write or phone for more details Send 10" for our latest catalog



**2400 Crystal Drive**  
**Ft. Myers, Florida 33901**  
**all Phones (813) 936-2397**

## IF WE WERE YOU



the indispensable **BIRD 43**  
**THRULINE® WATTMETER**  
**I'D BUY FROM US**

**YOUR INQUIRY OR ORDER WILL GET OUR PROMPT ATTENTION**

**AUTHORIZED DISTRIBUTOR**

**WEBSTER COMMUNICATIONS**

115 BELLARMINE  
ROCHESTER, MI 48063

CALL TOLL FREE


800-521-2333

MICHIGAN 313-375-0420



# NEW! IC KEYS

The World's Greatest  
Sending Device

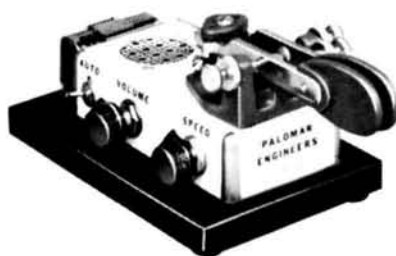

Adjustable to Any  
Desired Speed

Now available from Palomar Engineers — the new Electronic IC KEYS. Highly prized by professional operators because it is EASIER, QUICKER, and MORE ACCURATE.

It transmits with amazing ease CLEAR, CLEAN-CUT signals at any desired speed. Saves the arm. Prevents cramp, and enables anyone to send with the skill of an expert.

## SPECIAL RADIO MODEL

Equipped with large specially constructed contact points. Keys any amateur transmitter with ease. Sends Manual, Semi-Automatic, Full Automatic, Dot Memory, Squeeze, and Iambic — MORE FEATURES than any other keyer. Has built-in sidetone, speaker, speed and volume controls. BATTERY OPERATED, heavy shielded die-cast metal case. FULLY ADJUSTABLE contact spacing and paddle tension. The perfect paddle touch will AMAZE you.

Every amateur and licensed operator should know how to send with the IC KEYS. EASY TO LEARN. Sent anywhere on receipt of price. Free brochure sent on request.

Send check or money order. IC KEYS \$97.50 postpaid in U.S. and Canada. IC KEYS LESS PADDLE and non-skid base \$67.50. Add 6% sales tax in California.

Italy write i2VTT, P.O. Box 37, 22063 Cantu.

Fully guaranteed by the world's oldest manufacturer of electronic keys. ORDER YOURS NOW!

**PALOMAR  
ENGINEERS**  
BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

# flea market

**ELECTRONIC** Voltage Regulators for Automobile Alternators. Available for most cars. Free literature. Send \$14.95 (ppd) to SOLID STATE DEVELOPMENT CO. P.O. Box 108, Clarkson, Mississauga, Ontario, Canada L5J3X9

**ELIMINATE QRM and QRN** problems with our superior CW and SSB Filters. Also CW keyers, speech compressors, power supplies, teletype converters, and multi-band antennas assembled or in kits. Dealer discounts. Dynamic Electronics, Box 896, Hartselle, AL 35640. (205) 773-2758.

**EZ** does it best. Deals, that is, on Yaesu, ICOM, Drake, Swan, Cushcraft, Larsen, KLM, Dentron, VHF Engineering and Wilson. For new or used gear call, see or write W0EZ, Bob Smith Electronics, 12 So. 21st St., Fort Dodge, Iowa 50501. (515) 576-3886.

**WANTED** General Electric Mast Pro Mobile Radio, High band for 2 meters. Must be late model, clean and in good operating condition. SID PURVIS, 1306 Sioux Dr., Jacksonville, N.C. 28540. (919) 455-2080.

**LOOKING** for a used fax-equipment suitable for amateurs. H.-Ch. Als, Stegerwaldweg 7, 6800 Mannheim 31, W-Germany.

**STOP LOOKING** For a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. We are factory-authorized dealers for Kenwood, Drake, Collins, ICOM, Ten-Tec, Atlas, Hallicrafters, KLM, Wilson, Regency, Tempo, Swan, Midland, Alpha, Standard, Dentron, Hy-Gain, Mosley, Cushcraft, and CDE, plus accessories. Thousands of thrifty hams from coast to coast already know us and we invite you to join them by writing or calling us today for our low quote and trying our personal and friendly Hoosier service. HOOSIER ELECTRONICS, P. O. Box 2001, Terre Haute, Indiana 47802. (812) 238-1456.

**TECH MANUALS** for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8A/U, TS-173/UR. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

**WANTED:** Military freq. counter USM-207. Will consider non-working unit in reparable condition. R. Allen, WA3GQL, 606 Patterson Ave., Willow Grove, PA. 19090.

**WANTED:** Riders TV, Sams Photofacts #650-#1000, RADEXs, 1940's and 1950's SWL club bulletins, ARRL Handbooks, 1930's Callbooks, and anything else for radio library. Swap or buy. State price and condition. Don Erickson, 6059-N Essex Street, Riverside, California 92504. (714) 687-5910.

**PC BOARDS HAM RADIO ARTICLES** Tone encoder 8/77 \$3.50, Freq. Standard 8/77 \$3.50, Capacitor checker 4/75 \$3.50, Prescaler 12/75 \$3.00. Glass, plated, drilled, instructions. RTC Electronics, Box 2514, Lincoln, Nebr. 68502.

**OLD QSTs WANTED**, also HT-100, W1BL Al Blank, 727 Pine St., Bristol, CT. 06010.

**GALAXY V**, with AC power supply, calibrator, VOX, \$200.00. James Honey, WA9ZCK, (618) 687-1937.


**HEATH HW-16**, with MFJ audio filter and Accu-Keyer, \$125.00. James Honey, WA9ZCK, (618) 687-1937.

## Coming Events

**SOUTH BEND, INDIANA** Hamfest Swap & Shop January 8, 1978, first Sunday after New Years Day at NEW CENTURY CENTER downtown by river on U.S. 31 ONEWAY North across from St. Joseph Bank Building. Half acre in one large room at same ground level as entrances and loading dock. Tables \$2 each. Food catering service, automobile museum and Art Center in the same building. Four lane highways to door from all directions. Talk-in freq: 146.52-52, 04-64 East, 13-73, 25-85 SE, 34-94; 147.99-39, 93-33, 84-24, 69-09. Wayne Werts K9IXU, 1889 Riverside Drive 46616.

**THE ANNUAL FORT WAYNE WINTER HAMFEST** is at Shiloh Hall, North of Fort Wayne, on January 22 from 8 AM until 4 PM local time. Early parking is available and 28/88 and 52/52 will be monitored. This yearly event is sponsored by the Allen County Amateur Radio Technical Society (AC/ARTS). Admission is \$2.00 at the door. Table space is available at \$1.50 per half table (about 4 feet). For information or table reservations (held until 9:30 AM) write: Hamfest Chairman; AC/ARTS, P.O. Box 342, Fort Wayne, IN. 46801.

## WANTED FOR CASH

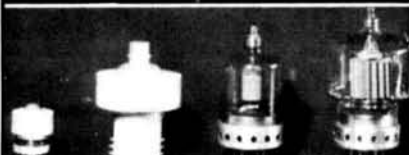

4CX150	4CX1000	4-65	4-250
4CX250	4CX1500	4-125A	4-400
4CX300A	4CX3000		4-1000
4CX350A	4CX5000		304TL
	4CX10,000		
	5CX1500		

Other tubes and Klystrons also wanted.  
See last month for other items available.

**The Ted Dames Company**

308 Hickory St. Arlington, N.J. 07032  
(201) 998-4246 Evenings (201) 998-6475

## GROTH-Type

COUNTS & DISPLAYS  
YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

**PRICES** POST PAID  
TC 2 — \$8.00  
TC 3 — \$8.75  
Spinner (\$) — \$1.00  
Add \$0.75 for Air or UPS

Model TC2: Skirt 2-1/8";  
Knob 1-5/8"  
Model TC3: Skirt 3";  
Knob 2-3/8"

**R. H. BAUMAN SALES**

P.O. Box 122, Itasca, Ill. 60143

## IMPROVES ALL SSB & CW STATIONS PR-1000 VARIABLE AUDIO FILTER



Greatly improves reception and audio selectivity of even the best ham receiver. Easy to operate and quickly connects between any ham receiver, transceiver or SWL receiver and speaker (or headphones). Provides variable selectivity bandpass of 40 Hertz to 3000 Hertz with selectivity skirts a minimum of 80db! Super sharp 70db variable notch rejects nearby CW stations as close as 100 Hertz! Incorporates the latest electronic audio filtering circuitry. Five (5) integrated circuits with self-contained 110 volt AC power supply and one watt audio amplifier. Attractive low profile eggshell white cabinet with walnut-like sides.

**PRIME ELECTRONICS, INC.** Dept. HR  
221 West Market St. Derby, KS. 67037

- ☐ Please send me more information
- ☐ Rush me \_\_\_\_\_ PR-1000 Variable Audio Filters @ \$59.95 each plus \$1.50 postage & handling. Check or M.O. enclosed.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Distributor and dealer inquiries invited.

## DIODES/ZENERS

1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N753A	6.2v	z	.25
1N758A	10v	z	.25
1N759A	12v	z	.25
1N4733	5.1v	z	.25
1N5243	13v	z	.25
1N5244B	14v	z	.25
1N5245B	15v	z	.25

## SOCKETS/BRIDGES

8-pin	pcb	.25	ww	.45
14-pin	pcb	.25	ww	.40
16-pin	pcb	.25	ww	.40
18-pin	pcb	.25	ww	.75
22-pin	pcb	.45	ww	1.25
24-pin	pcb	.35	ww	1.10
28-pin	pcb	.35	ww	1.45
40-pin	pcb	.50	ww	1.25
Molex pins	.01	To-3 Sockets		.45
2 Amp Bridge		100-prv		1.20
25 Amp Bridge		200-prv		1.95

## TRANSISTORS, LEDS, etc.

2N2222	NPN	(Plastic .10)	.15
2N2907	PNP		.15
2N3906	PNP		.10
2N3054	NPN		.35
2N3055	NPN	15A 60v	.50
T1P125	PNP	Darlington	.35
LED Green, Red, Clear			.15
D.L.747	7 seg 5/8" high com-anode		1.95
XAN72	7 seg com-anode		1.50
FND 359	Red 7 seg com-cathode		1.25

## C MOS

4000	.15
4001	.20
4002	.20
4004	3.95
4006	1.20
4007	.35
4008	.95
4009	.30
4010	.45
4011	.20
4012	.20
4013	.40
4014	1.10
4015	.95
4016	.35
4017	1.10
4018	1.10
4019	.60
4020	.85
4021	1.35
4022	.95
4023	.25
4024	.75
4025	.35
4026	1.95
4027	.50
4028	.95
4030	.35
4033	1.50
4034	2.45
4035	1.25
4040	1.35
4041	.69
4042	.95
4043	.95
4044	.95
4046	1.75
4049	.70
4050	.50
4066	.95
4069	.40
4071	.35
4081	.70
4082	.45

7400	.15
7401	.15
7402	.20
7403	.20
7404	.15
7405	.25
7406	.35
7407	.55
7408	.25
7409	.15
7410	.10
7411	.25
7412	.30
7413	.45
7414	1.10
7416	.25
7417	.40
7420	.15
7426	.30
7427	.45
7430	.15
7432	.30
7437	.35
7438	.35
7440	.25
7441	1.15
7442	.45
7443	.85
7444	.45
7445	.65
7446	.95
7447	.95
7448	.70
7450	.25
7451	.25
7453	.20
7454	.25
7460	.40
7470	.45
7472	.40

7473	.25
7474	.35
7475	.35
7476	.30
7480	.55
7481	.75
7483	.95
7485	.95
7486	.30
7489	1.35
7490	.55
7491	.95
7492	.95
7493	.40
7494	1.25
7495	.60
7496	.80
74100	1.85
74107	.35
74121	.35
74122	.55
74123	.55
74125	.45
74126	.35
74132	1.35
74141	1.00
74150	.85
74151	.75
74153	.95
74154	1.05
74156	.95
74157	.65
74161	.85
74163	.95
74164	.60
74165	1.50
74166	1.35
74175	.80

## - T T L -

74176	1.25
74180	.85
74181	2.25
74182	.95
74190	1.75
74191	1.35
74192	1.65
74193	.85
74194	1.25
74195	.95
74196	1.25
74197	1.25
74198	2.35
74221	1.00
74367	.85
75108A	.35
75110	.35
75491	.50
75492	.50
74H00	.25
74H01	.25
74H04	.25
74H05	.25
74H08	.35
74H10	.35
74H11	.25
74H15	.30
74H20	.30
74H21	.25
74H22	.40
74H30	.25
74H40	.25
74H50	.25
74H51	.25
74H52	.15
74H53J	.25
74H55	.25

74H72	.55
74H101	.75
74H103	.75
74H106	.95
74L00	.35
74L02	.35
74L03	.30
74L04	.35
74L10	.35
74L20	.35
74L30	.45
74L47	1.95
74L51	.45
74L55	.65
74L72	.45
74L73	.40
74L74	.45
74L75	.55
74L93	.55
74L123	.55
74S00	.55
74S02	.55
74S03	.30
74S04	.35
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.35
74S40	.25
74S50	.25
74S51	.45
74S64	.25
74S74	.40
74S112	.90
74S114	1.30

74S133	.45
74S140	.75
74S151	.35
74S153	.35
74S157	.80
74S158	.35
74S194	1.05
74S257 (8123)	.25
74LS00	.35
74LS01	.35
74LS02	.35
74LS04	.35
74LS05	.45
74LS08	.35
74LS09	.35
74LS10	.35
74LS11	.35
74LS20	.35
74LS21	.25
74LS22	.25
74LS32	.40
74LS37	.35
74LS40	.45
74LS42	1.10
74LS51	.50
74LS74	.65
74LS86	.65
74LS90	.95
74LS93	.95
74LS107	.85
74LS123	1.00
74LS151	.95
74LS153	1.20
74LS157	.85
74LS164	1.90
74LS367	.85
74LS368	.85

## LINEARS, REGULATORS, etc.

8266	.35
MCT2	.95
8038	3.95
LM201	.75
LM301	.25
LM308 (Mini)	.75
LM309H	.65
LM309K (340K-5)	.85
LM310	1.15
LM311D (Mini)	.75
LM318 (Mini)	.65

LM320K5 (7905)	1.65
LM320K12	1.65
LM320T5	1.65
LM320T12	1.65
LM320T15	1.65
LM339	.95
7805 (340T5)	.95
LM340T12	1.00
LM340T15	1.00
LM340T18	1.00

LM340T24	.95
LM340K12	2.15
LM340K15	1.25
LM340K18	1.25
LM340K24	.95
LM373	2.95
LM380	.95
LM709 (8,14 PIN)	.25
LM711	.45

LM723	.50
LM725	1.75
LM739	1.50
LM741 (8-14)	.25
LM747	1.10
LM1307	1.25
LM1458	.95
LM3900	.50
LM75451	.65
NE555	.50
NE556	.95
NE565	.95
NE566	1.75
NE567	1.35

## 9000 SERIES

9301	.85
9309	.35
9322	.85
95H03	.55
9601	.75
9602	.50

## MEMORY CLOCKS

74S188 (8223)	3.00
1702A	6.95
MM5314	3.00
MM5316	3.50
2102-1	1.75
2102L-1	1.95
TR 1602B/	
TMS 6011	6.95
8080AD	15.00
8T13	1.50
8T23	1.50
8T24	2.00
2107B-4	4.95

## INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Boulevard, San Diego, California 92111  
(714) 278-4394 (Calif. Res.)

All orders shipped prepaid

Open accounts invited

No minimum

COD orders accepted

Discounts available at OEM Quantities California Residents add 6% Sales Tax

All IC's Prime/Guaranteed. All orders shipped same day received.


24 Hour Toll Free Phone 1-800-854-2211

MasterCharge / BankAmericard / AE

## SPECIAL DISCOUNTS

Total Order	Deduct
\$35 - \$99	5%
\$100 - \$300	10%
\$301 - \$1000	15%
\$1000 - Up	20%

## RF TRANSFORMER

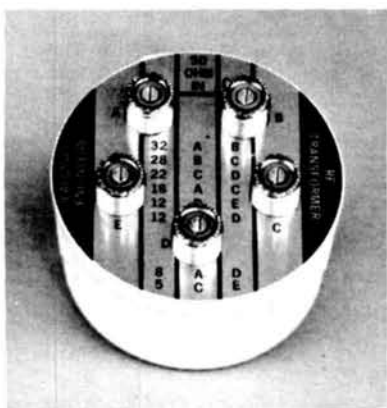

- **New! Broadband antenna matching.**
- **For all verticals and mobile whip antennas.**
- **Smaller size and higher efficiency. Only 3 1/2" diameter for full 5-Kw PEP capability.**

Here is the answer to the matching problem for vertical antennas and mobile whips. A broadband transformer that matches your 50 ohm transmitter to 32, 28, 22, 18, 12, 8, or 5 ohms. Plenty of taps to match any vertical or whip.

And with no tuning or other adjustment. The RF Transformer is completely broadband 1-30 MHz (1-10 MHz on three lowest taps). So when you change frequency within a band you need only re-tune the antenna to resonance; not fiddle with a matching network.

Also, more power goes to your antenna. The RF Transformer is more efficient than a matching network or tuner—less than 0.1 db loss.

As always, when you buy Palomar Engineers you get the best: large ferrite toroid core, teflon insulated wire, sealed epoxy-encapsulated weatherproof construction, stainless steel mounting hardware, full 2000 watt CW (5-Kw PEP) capability.

Send for free brochure.

Improve your station. Simplify your tuneup. Get better results with the new Palomar Engineers RF Transformer.

Order direct. \$42.50 postpaid U.S. and Canada. California residents add sales tax.

### PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

## flea market

**LAPORTE ARC'S WINTER HAMFEST**, Sunday, February 26, 1978 at the LaPorte Civic Auditorium, 50 miles southeast of Chicago. Plenty of room, free tables, good food. Donation \$2 at gate. Talk in on 01/61 and 52 simplex. LPARC, Box 30, LaPorte, IN 46350.

**RICHMOND, VIRGINIA WINTERFEST** — 78 January 15, 1978, Bon Air Community Center, sponsored by The Richmond Amateur Telecommunications Society. Talk in 28-88 and 52 simplex. ARRL coordinated. Technical symposium, drawing, home brewers contest — 2 divisions, over 18 and under — with framed certificate to winners with Most Original Idea, Best Mechanical and Best Electrical Construction. FCC exams will be administered, starting at 10:00 AM, to take exam, mail Form 610 at least five days prior to Fest to address below. Send self-addressed, stamped envelope if you need Form 610. Commercial Exhibits, Indoor Flea Market, \$2.00 (table included), Outdoor Frost Bite Tail Gate Flea Market, \$1.00. Admission \$2.00, children under 12 free. R.A.T.S. members excluded from contest and drawing. Bring the family and spend the weekend in beautiful, historic Richmond. Richmond Amateur Telecommunications Society, Post Office Box 1070, Richmond, Virginia 23208.

## Stolen Equipment

**DRAKE ML-2**, SN 11546, with 34/94, 94/94, 16/76, 07/67, 22/82, and 25/85 crystals installed. Stolen from Tom Fraser, WA0QQT, Colorado Springs, Colorado. Call (303) 635-8911, Ext. 3874. Anyone desiring to list stolen Amateur radio equipment please send information to Colorado Council of Amateur Radio Clubs c/o Charles E. Myers W0RNT 1120 Yosemite Drive, Colorado Springs, Co. 80910. Please include as much identification information as possible. Free distribution will be made to all Amateur radio magazines and Colo. Amateur radio clubs. Funds for postage and printing will be greatly appreciated.

**ATLAS 350 XL** with DD6-XL Digital dial Ser. #877025. **AC POWER SUPPLY** for the Atlas, Ser. #877104PS. Jay Leonard, Rt. 1, Box 32A, Pottsville, Ark. 72858.

## MAXI TUNER SOLVES ANTENNA PROBLEMS!



### THE FINEST ANTENNA TUNER AVAILABLE

- Presents 50-75 Ohm Resistive Load to Your Transmitter Using Virtually Any Antenna System
- Improved Ultimate Transmatch Circuit Matches Coax, Random Wire and Balanced Antennas
- Continuous 1.7-30 MHz Coverage
- 229-203 Rotary Inductor (28  $\mu$ H)
- Rugged Cast Aluminum Turns Counter
- Handles 3 KW PEP
- Monimatch SWR Circuit
- Heavy Duty Balun
- Velvet-Smooth 6 to 1 Vernier Tuning
- 0-100 Logging Scale on Capacitors
- Available in Kit Form or Assembled
- One Year Factory Warranty
- Available without SWR for use with your present SWR meter or wattmeter.
- Custom Vacuum Capacitor Designs and Individual Components Available

Call or Write for Pricing, Spec Sheet, and FREE Amateur Market Antenna Tuner Comparison Chart That Tells It Like It Is! Dealer Inquiries Invited.

**RF POWER COMPONENTS**

P. O. Box 11  
Ladysmith, WI 54848  
(715) 532-3971

## ALDELCO SEMI-CONDUCTOR SUPERMARKET RF DEVICES

2N3375 3W 400 MHz	5.50	2N6080 4W 175 MHz	5.40
2N3866 1W 400 MHz	1.15	2N6081 15W 175 MHz	8.45
2N5590 3W 175 MHz	4.75	2N6082 25W 175 MHz	10.95
2N5590 10W 175 MHz	7.80	2N6083 30W 175 MHz	12.30
2N5591 25W 175 MHz	10.95	2N6084 40W 175 MHz	16.30
2SC517	3.95	2SC1307	5.25
2SC1226	1.25	2N4427	1.35
2SC1306	4.30	2N5109	2.05

**NOW NEW IMPROVED DIGITAL ALARM CLOCK KIT** Hours + Minutes + Seconds displayed on six BIG 0.5 Fairchild 7 Segment Display LEDs. 12-hour format 24-hour alarm with snooze feature, plus elapsed time indicator and freeze feature. Eight pages of pictorials and instructions. NEW on-board power transformer and circuitry for optional time base with simulated wood grain cabinet \$23.95

**12/24 Hour Clock Kit** Six big 5 LEDs freeze feature with simulated wood cabinet. \$23.95


**COMBINATION DIGITAL CLOCK AND FREQUENCY COUNTER KIT** 6 digit 40 MHz counter AND 12/24 hour clock kit. Battery operated with 110V charger. 2" x 4 1/4" x 6" cabinet. Assembled unit complete for \$139.95

ONLY \$99.95

**VARIABLE POWER SUPPLY KITS** — 600 Ma, 5-15 VDC \$6.95  
12/28 VDC \$6.95 75 cents per unit shipping

**NOW!**

**Dual Digital  
12-24 hour clock kit**

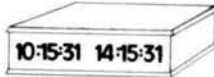

MODEL ALDS:

Six big 5 display LEDs in an attractive black plastic cabinet with a red front filter. Great for a ham or broadcast station. Set one clock to GMT the other to local time. Or have a 24 hour format on one clock and 12 hour on the other. Freeze feature lets the clock be set to the second. Each clock is controlled separately. Cabinet measures 2 1/2" x 4 1/4" x 9 1/4". Complete Kit \$44.95.

We have 7400 series ICs send stamp for catalog.

Add 5% for shipping. Add \$1 to orders under \$10. Out of USA send Certified Check or Money Order. Include postage.

## ALDELCO

2281H Babylon Tnpk., Merrick, NY 11566  
(516) 378-4555

### BUILD YOUR OWN TV CAMERA!

Ideal for home & business



GREAT FOR AMATEUR TV INDUSTRIAL SURVEILLANCE HOME ENTERTAINMENT & MONITORING PLUS HUNDREDS OF OTHER USES  
MODEL KIT 1A SERIES 0 — KIT \$185  
FACTORY ASSEMBLED \$265  
STATE CONNECT TO ANY TV SET  
OPTIONAL SOUND KIT \$28.95  
PHONE OR WRITE FOR FREE CATALOG  
DIAL 402-987-3771

1301 BROADWAY N.W. ATV Research DAKOTA CITY, NEBR 68731


**See our HAM MART  
listings to find the  
Amateur Radio  
dealers nearest you.**

**NEW ELECTRONIC PARTS**  
IC'S - TRANSISTORS - PROTOBOARDS - RESISTORS  
CAPACITORS - DIODES - SWITCHES - CONNECTORS  
VOLTAGE REGULATORS - CABINETS - HEAT SINKS  
FUSES & MUCH MORE -- STAMP BRINGS CATALOG

### SPECIALS

### KEYBOARD ENCLOSURES

TWO SIZES W D H PRICE				
14	8.3	3	\$13.50*	
14	11.3	3	\$14.50*	

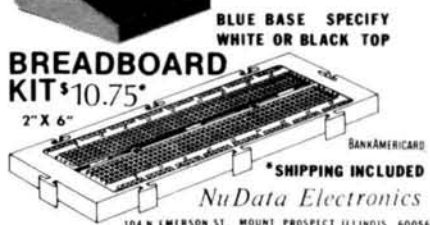



- Advance Registration \$14.00 per person; with Hotel Sahara Late Show and two drinks \$28.00 per person or with Hotel Sahara Congo Dinner Show (entree Cornish Hen), no drinks \$35.00 per person. Tax and Gratuity included.
- Entertainment in Hotel Sahara's Congo Room has not been selected at press time.
- Advance Registration must be received by **SAROC** on or before December 22, 1977.

The NATION'S ANNUAL LAS VEGAS PRESTIGE CONVENTION



HOTEL SAHARA'S CONVENTION SPACE CENTER

January 5-8, 1978

- **SAROC** Registration includes: registration tickets, admission to technical sessions, Friday cocktail party hosted by TRI-EX Tower Corp.; Saturday cocktail party hosted by Ham Radio Magazine; Hotel Sahara Buffet Brunch on Sunday, Tax and Gratuity.
- Hotel Sahara room rate for **SAROC** registered delegates \$22.00 per night plus room tax, single or double occupancy.
- Hotel Sahara room reservation request card will be sent only to **SAROC** registered delegates and exhibitors only until December 22, 1977.



Send your check or money order to **SAROC** , P. O. Box 945, Boulder City, NV 89005

# TOROID CORES



- ✓ All the popular sizes and mixes.
- ✓ Fast Service. Same day shipment via first class mail or air.
- ✓ No minimum order.

## IRON POWDER TOROIDS:

CORE SIZE	MIX 2 5-30 MHz u=10	MIX 6 10-90 MHz u=8.5	MIX 12 60-200 MHz u=4	SIZE OD (in.)	PRICE USA \$
T-200	120			2.00	3.25
T-106	135			1.06	1.50
T-80	55	45		.80	.80
T-68	57	47	21	.68	.65
T-50	51	40	18	.50	.55
T-25	34	27	12	.25	.40

## RF FERRITE TOROIDS:

CORE SIZE	MIX Q1 u=125 1-70 MHz	MIX Q2 u=40 10-150 MHz	SIZE OD (in.)	PRICE USA \$
F-240	1300	400	2.40	6.00
F-125	900	300	1.25	3.00
F-87	600	190	.87	2.05
F-50	500	190	.50	1.25
F-37	400	140	.37	1.25
F-23	190	60	.23	1.10

Chart shows uH per 100 turns.

## FERRITE BEADS:



\$2.00 DOZEN

## WIDE BAND CHOKES



95¢ EACH

TO ORDER: Specify both core size and mix for toroids. Packing and shipping 50 cents per order USA and Canada. Californians add 6% sales tax.


Fast service. Free brochure and winding chart on request.

# PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

# This is easy- anyone can solder- WITH KESTER SOLDER

**KESTER  
SOLDER**

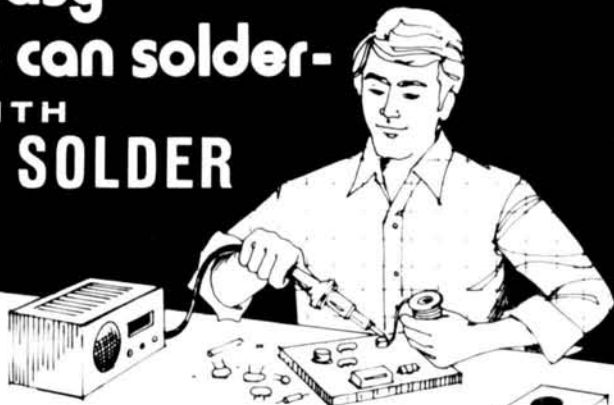

## Handymen! Hobbyists! DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.

When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



**KESTER SOLDER**

Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

## RADIO WORLD

CENTRAL NEW YORK'S FASTEST  
GROWING HAM DEALER



FT-101E

TRITON IV

Featuring - Yaesu, Atlas, Dentron, Ten-Tec, Swan, Regency, Standard, Tempo, KLM, Hy-Gain, Mosley, Larsen, Midland, Wilson. We service everything we sell! Write or call for quote. YOU WON'T BE DISAPPOINTED. We are just a few minutes off the NYS Thruway (I-90) - Exit 32.

## RADIO WORLD

ONEIDA COUNTY AIRPORT  
TERMINAL BUILDING  
ORISKANY, NY 13424  
315-337-2622

Warren  
K21XN

Joe  
WB2GJR

## ENERGY CRISIS SOLVED!

Personal energy crisis? Get precious RF on DX target with World Record Breaking antenna that won W6TYP the QRP ARC 1,000,000 miles/watt award.

### THE JOYSTICK VFA

(Variable freq. ant) gives low angle, omnidirectional, harmonic free radiation on all bands 160 thru 10.1 - MARS and receive on all BC & SW!

1000's of glowing reports in our files of the VFA in use, often in poor QTH and/or under GRP, contests, etc.

**SYSTEM 'A' \$75.00**

250W P.E.P. &/or Receiving Only

**SYSTEM 'J' \$99.00**

500W P.E.P. &/or Improved Q Factor Receive

Air Mail cost included. (Each system 3 sections easily assembled to make unit 7' 6" long Matching ATU). Not only will you save space but you will save \$\$\$ at present low exchange rate and by buying direct UK manu. Rush your order - Mastercharge or check, or ask for brochure.

**PARTRIDGE (HR)  
ELECTRONICS LTD.**

Brooklands, Kent, England  
Tel. Thanet 62535

G3CED

G3VFA

## TRANSFORMERS

American made, 115V Primaries:

6.3V, 1 Amp Shielded	\$1.80 ea.
12V, 250 mls, for P. C. Board.	\$1.66 ea.
12 volt 1/2 amp.	\$2.05
12V 1.2 Amp	\$2.84
12V, 3 Amp	\$4.48
36V CT, 1A; 14V CT, 400 Ma	\$4.20 ea.
44V CT — 1A; 6.3V, 1/4 amp tap	\$3.47 ea.
48V CT — 1A; 6.3V, 1/4 amp tap	\$3.46 ea.

NEW ITEM — PHILCO TRANSFORMER — 115V Pri., Secs 6.3V 3A, 115V 1A, 24V 2A w/6.3V TAP 2A Shlded. Wt. 7 lbs. 4" x 3 1/2" x 3 1/4". \$7.55 ppd. Qty Prices Available

8 PIN "TO5" IC Socket, gold plt. 6/\$1.08



3000 MFD  
@ 30 Volts  
Capacitors.

1" Dia. x 3" — 90¢ ea. or 3/\$2.25

UNPOTTED TOROIDS — Center tapped.

88 MHY - 5 oz. 5/\$2.95; 9 oz. - 5/\$3.49

44 MHY - 5/\$3.95



## SEMTECH BRIDGES

Heat sink w/center hole  
mtg. 10 Amp — Tested —  
200V P.I.V. \$1.75 ea. ppd.  
400V P.I.V. \$1.95 ea. ppd.  
600V P.I.V. \$2.15 ea. ppd.

25 AMP — TESTED  
200V P.I.V. \$2.25 ea. ppd.  
400V P.I.V. \$2.50 ea. ppd.  
600V P.I.V. \$2.85 ea. ppd.



CARBON TRIMMERS  
Miniature 1/4 watt units, PC  
type. Values: 200, 700, 1000,  
1.5K, 250K, 700K  
30¢ ea. or 5/\$1.35 ppd.




NEW SIZES — VERTICAL MOUNT  
PC BOARD POTENTIOMETERS  
American made (CRL) Cermet  
sizes: 25K, 100K ohms. 5/\$1.30 ppd.  
CTS Blue wheel. Values: 750, 1K,  
1.5K, 50K, 300K ohms. 5/\$1.25 ppd.

**m. weinschenker**  
electronic specialties-BOX 353, IRWIN, PA 15642

Everybody likes power and nowhere can you get more of it for \$349.95 than with our Cygnet 1200X linear amplifier.

With 100 watts of driving power you're on the air with a solid 1200 watts PEP input and most people won't be able to tell you from somebody operating full bore.

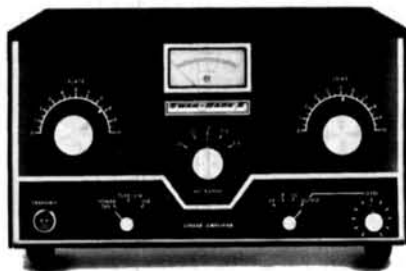Linearity on the 1200X is excellent, efficiency is outstanding, 117/230 A.C. power supply is built in, and features like provision for external ALC give you the flexibility you need to get the most out of your rig.



Mark II for power and glory, too. But if you've got your heart set on block-buster power we've also got the right linear amp for you.

It's the Mark II, the proven unit everybody thinks of when you talk about workhorse linear amplifiers.

The Mark II dominates the bands with all the power that's allowed—2000 watts PEP—and a clean, linear signal that's music to your ears.

The Mark II features a separate, matching power supply, big, quiet

blowers for both the RF deck and the power supply, all bands from 10 to 80 meters and all you need to enjoy it is 100 watts driving power.

Get a Swan 1200X or Mark II linear amplifier today and stop letting people shout you down. Use your Swan credit card. Applications at your dealer or write to us.

**Cygnet 1200X** 1200-watt linear amplifier complete with built in 110/220V power supply ..... \$349.95

**Mark II** 2000-watt linear amplifier complete with separate 117/230 VAC power supply and two 3-500Z tubes ..... \$849.95  
(Prices FOB Oceanside, CA)

Dealers throughout the world or order direct from




**SWAN**  
ELECTRONICS®

A subsidiary of Cubic Corporation

305 Airport Road, Oceanside, CA 92054
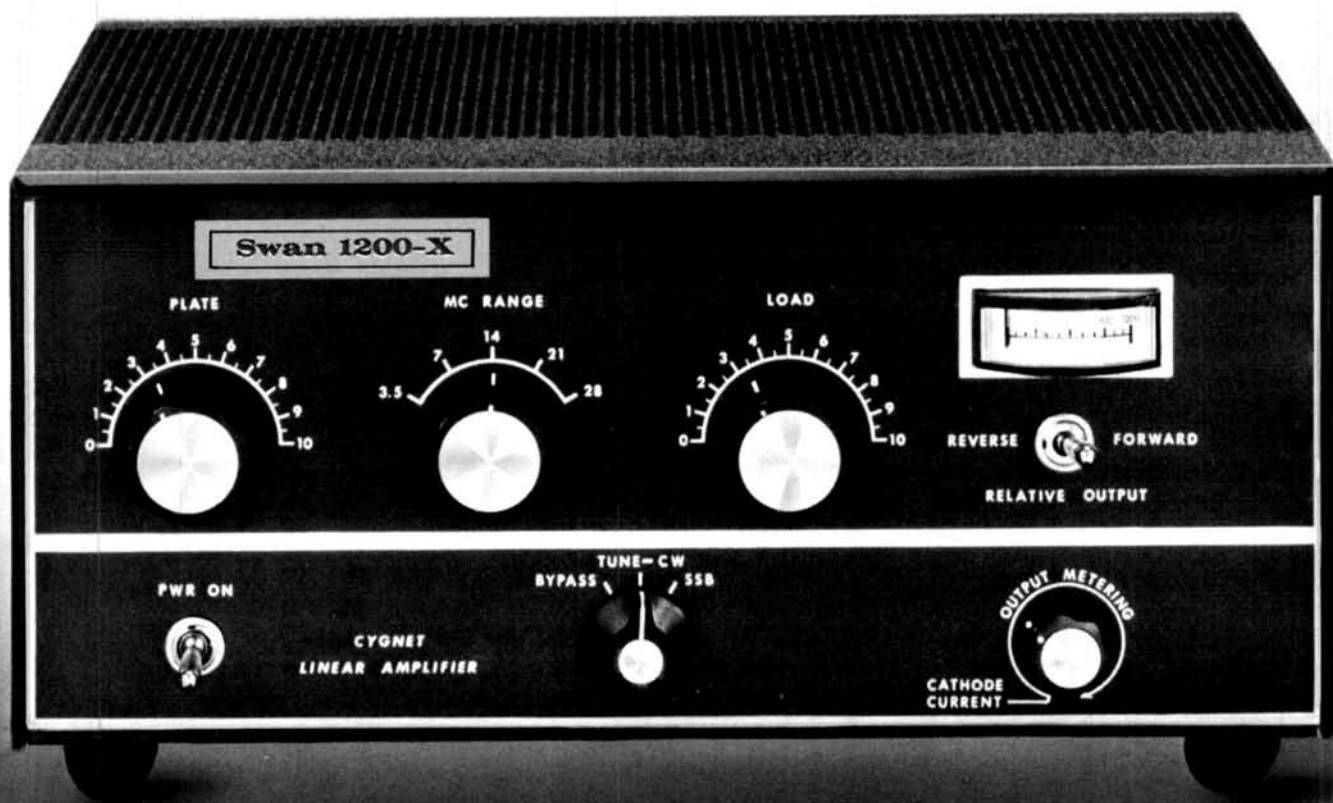
# SWAN 1200X LINEAR AMPLIFIER. TALK LOUD FOR A SONG. \$349.95




## Comprehensive Sentry's Quartz Technology Manual

One reference does all this:

- Takes the mystery out of understanding and using quartz crystals
- Specifies what you need for commercial two-way, marine, aircraft, public service, ham and monitor radio
- Gives the most complete military specifications ever published
- Shows how to convert your 23-channel CB to 40 channels
- Explains how to understand and use digital quartz clocks

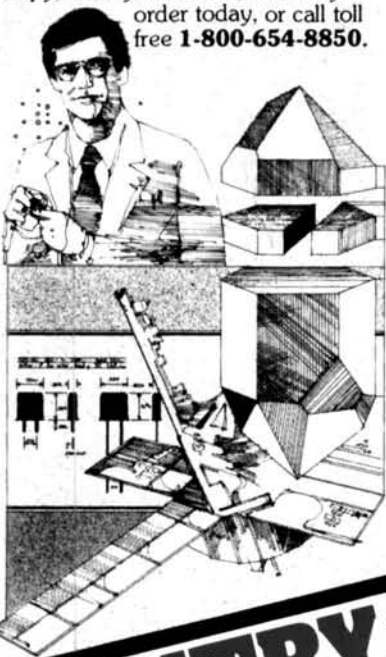Never before has so much information been compiled under one cover . . . for the low price of \$2.95. If your profession or hobby involves a working knowledge of crystals, everything you need is here . . . in an easy-to-find, easy-to-assimilate form. The first printing is just 20,000 copies. To assure a first edition copy, send your check or money order today, or call toll free **1-800-654-8850**.



# SENTRY

Quartz Technology Manual HAM2

Sentry Mfg. Co.,  
Crystal Park,

Chickasha, Oklahoma 73018


Please rush my copy of Sentry's comprehensive 150-page **Quartz Technology Manual** today. Enclosed is my check or money order for \$2.95, which includes postage and handling.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_
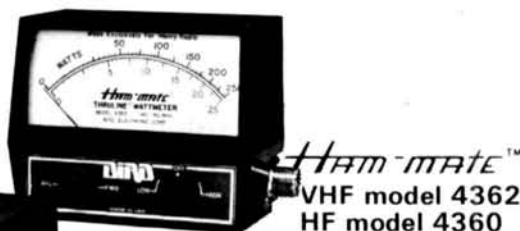
## Two New Wattmeters for the radio amateur



### specifications

	HF Model 4360	VHF Model 4362
Frequency Range	1.8-30 MHz	140-180 MHz
Forward Power Range	0-200/2000W	0-25/250W
Reflected Power Range	0-200/2000W	0-25/250W
Impedance $Z_0$	50 ohms*	
Insertion VSWR	1.1 to 1.0 max.	
Accuracy	± 8% of Full Scale	
Directivity	20 dB min.	
Dimensions	3 1/8" x 6" x 3 3/4"	
	(100 x 150 x 85 mm)	
Weight	1 lb. (0.43 kg)	
Connectors—Input & Output	Female UHF (SO-239)	
Price	\$94.00	

\*May be used with 50-52 ohm cable

The 4360, 4362 HAM-MATE Directional Wattmeters are insertion type instruments for measuring forward or reflected power in 50-ohm coaxial transmission lines. They are direct descendants of the model 43 THRULINE® Wattmeter—the professional standard of the industry—and will accurately measure RF power flow under any load condition.

HENRY RADIO  
IS THE EXCLUSIVE DISTRIBUTOR FOR

**BIRD**  
HAM-MATE™

Available at select dealers throughout the U.S.

**Henry Radio**

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701  
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200  
Butler, Missouri 64730 816/679-3127

— PCB — PCB — PCB — PCB — PCB — PCB —

ETCH-IT-YOURSELF  
Printed Circuit  
Kit

**\$19.95**  
ppd.

NOW YOU CAN design and produce your own printed circuit boards.  
IT'S EASY. Photo positive method. No darkroom required.  
LESS THAN 2 HOURS to produce a p.c. board direct from magazine article.  
KIT INCLUDES materials to make 4 p.c. boards direct from magazine article.  
Add \$1 for COD. S.A.S.E. for details.

**EXCEL CIRCUITS CO.**  
4412 Fernlee 313-549-0440  
Royal Oak, MI 48073

— PCB — PCB — PCB — PCB — PCB — PCB —

**See our HAM MART  
listings to find the  
Amateur Radio  
dealers nearest you.**

## MILITARY SURPLUS WANTED

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787.  
**SPACE ELECTRONICS CO.**  
div. of Military Electronics Corp.  
35 Ruta Court, S. Hackensack, N.J. 07606

## Bearcat® 210 Scanner



**\$289.**

The Bearcat 210 super synthesized receiver scans and searches over 16,000 different frequencies without expensive crystals. The Bearcat 210 covers 32-50, 146-174 & 416-512 Mhz., and has AC/DC operation. Save over \$60.00 now by ordering on our 24 hour toll-free credit card order line 800-521-4414. In Michigan and outside the U.S. call 313-994-4441. Add \$5.00 for shipping in the U.S. or \$9.00 for air UPS to the west coast. Charge cards or money orders only. Foreign orders invited.

**COMMUNICATIONS ELECTRONICS**  
P.O. BOX 1002 DEPT. 912  
ANN ARBOR, MICHIGAN 48106



# YOU... AND AMSAT PHASE III



An exciting new era in amateur radio is about to begin... the era of AMSAT PHASE III OSCAR satellites.

Many of you are familiar with the benefits of the AMSAT OSCAR satellites, notably OSCAR 6 and 7. These satellites, with a combined total of over 8 years in orbit, have provided communications between amateurs throughout the world. They have also provided a capability for an educational program in space sciences and many interesting experiments.

AMSAT, with members and contributing groups worldwide, and headquarters in Washington, D.C., has been responsible for our current satellite program. Many people feel that perhaps the greatest value of the amateur satellite program is the dramatic demonstration of amateur resourcefulness and technical capability to radio spectrum policy makers around the world.

The value of this aspect of amateur radio as we prepare for the 1979 World Administrative Radio Conference (WARC) is enormous.

The AMSAT PHASE III satellite program promises a continuing demonstration that amateur radio is at the forefront of modern technology. PHASE III satellites will routinely provide reliable communications over paths of up to 11,000 miles (17,600 km) for 17 hours each day. You can think of them as a resource equivalent to a new band.

The cost of these PHASE III satellites is a projected \$250,000. Commercial satellites of similar performance would cost nearly \$10,000,000.

Your help is needed to put these PHASE III OSCAR satellites in orbit.

Your valued, tax-deductible contribution can be as small as one of the 5000+ solar cells needed. A handsome certificate will acknowledge the numbered cells you sponsor for \$10 each. Larger components of the satellites may also be sponsored with contribution acknowledgements ranging to a plaque carrying your name aboard the satellites. Call or write us for the opportunities available.

Your membership in AMSAT is important to the satellite program, and will give AMSAT a stronger voice in regulatory matters concerned with satellites. At \$10 per year or \$100 for life, you will be making a most significant contribution to the satellite program and the future of amateur radio. You will also receive the quarterly AMSAT newsletter.

Clip the AMSAT PHASE III coupon below and send your support today, or call 202-488-8649 and charge your contribution to your BankAmericard (VISA) or Master Charge card.

	AMSAT PHASE III		HR
	Radio Amateur Satellite Corporation Box 27, Washington, D.C. 20044 202-488-8649		
YES, I want to support AMSAT PHASE III OSCAR satellites. Enclosed is:			
<input type="checkbox"/> \$ _____ in sponsorship of _____ solar cells (@ \$10 each)			
<input type="checkbox"/> \$10 Annual membership <input type="checkbox"/> \$100 Life membership			
<input type="checkbox"/> Send information on sponsoring larger satellite components.			
Name _____		Call _____	AMSAT Member? _____
Street _____			
City _____		State _____	Zip _____
The publisher has donated this space to AMSAT in support of AMSAT and the PHASE III program.			



*Ham Radio's guide to help you find your local*

### *Alabama*

#### **LONG'S ELECTRONICS**

2808 7TH AVENUE SOUTH  
BIRMINGHAM, AL 35202  
800-633-3410  
Call us Toll Free to place your order

### *Arizona*

#### **HAM SHACK**

4506 A NORTH 16TH STREET  
PHOENIX, AZ 85016  
602-279-HAMS  
Serving all amateurs from  
beginner to expert.

#### **MASTERS COMMUNICATIONS**

7025 N. 57th DRIVE  
GLENDALE, AZ 85301  
602-939-8356  
Rohn tower distributor, Atlas,  
Icom, Tempo, HyGain & service.

#### **POWER COMMUNICATIONS**

6012 NORTH 27th AVE.  
PHOENIX, AZ 85017  
602-242-8990  
Arizona's #1 Ham Store.

### *California*

#### **C & A ELECTRONICS**

2529 EAST CARSON ST.  
P. O. BOX 5232  
CARSON, CA 90745  
213-834-5868  
Not the biggest, but the best —  
since 1962.

#### **CARSON ELECTRONICS**

12010 EAST CARSON ST.  
HAWAIIAN GARDENS, CA 90716  
213-421-3786  
Dealing exclusively in ICOM  
communications equipment.

#### **COMMUNICATIONS CENTER**

705 AMADOR STREET  
VALLEJO, CA 94590  
707-642-7223  
Who else has a Spectrum  
Analyzer?

#### **HAM RADIO OUTLET**

999 HOWARD AVENUE  
BURLINGAME, CA 94010  
415-342-5757  
Visit our stores in Van Nuys  
and Anaheim.

#### **QUEMENT ELECTRONICS**

1000 SO. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-5900  
Serving the world's Radio Amateurs  
since 1933.

#### **TOWER ELECTRONICS CORP.**

24001 ALICIA PARKWAY  
MISSION VIEJO, CA 92675  
714-768-8900  
Authorized Yaesu Sales & Service.  
Mail orders welcome.

### *Colorado*

#### **C W ELECTRONIC SALES CO.**

1401 BLAKE ST.  
DENVER, CO 80202  
303-573-1386  
Rocky Mountain area's complete  
ham radio distributor.

#### **MILE-HI COMMUNICATIONS, INC.**

1970 SOUTH NAVAJO  
DENVER, CO 80223  
303-936-7108  
Rocky Mountain's newest  
ham store. Lee Tingle KØLT.

### *Connecticut*

#### **ARCOMM ELECTRONICS**

2865 MAIN STREET  
BRIDGEPORT, CT 06606  
Come on in, Tues. thru Sat.  
10:00 - 6:00

#### **AUDIOTRONICS INC.**

18 ISAAC STREET  
NORWALK, CT 06850  
203-838-4877  
The Northeast's fastest growing  
Ham Dept. dedicated to service.

### *Florida*

#### **AGL ELECTRONICS, INC.**

1800-B DREW ST.  
CLEARWATER, FL 33515  
813-461-HAMS  
West Coast's only full service  
Amateur Radio Store.

#### **CENTRAL EQUIPMENT CO.**

18451 W. DIXIE HIGHWAY  
NORTH MIAMI BEACH, FL 33160  
305-932-1818  
Specializing in Amateur, CB  
& Marine Equipment.

#### **RAY'S AMATEUR RADIO**

1590 US HIGHWAY 19 SO.  
CLEARWATER, FL 33516  
813-535-1416  
West coast's only dealer:  
Drake, Icom, Cushcraft, Hustler.

### *Illinois*

#### **ERICKSON COMMUNICATIONS, INC.**

5935 NORTH MILWAUKEE AVE.  
CHICAGO, IL 60646  
312-631-5181  
Hours: 9:30-9 Mon. & Thurs. 9:30-5  
Tues., Wed., Fri. 9-3 Sat.

#### **KLAUS RADIO, INC.**

8400 NORTH PIONEER PARKWAY  
PEORIA, IL 61614  
309-691-4840  
Let us quote your Amateur needs.

#### **SPECTRONICS, INC.**

1009 GARFIELD STREET  
OAK PARK, IL 60304  
312-848-6777  
Chicagoland's Amateur Radio  
leader.

### *Indiana*

#### **HOOSIER ELECTRONICS**

P. O. BOX 2001  
TERRE HAUTE, IN 47802  
812-238-1456  
Ham Headquarters of the Midwest.  
Store in Meadow Shopping Center.

#### **KRYDER ELECTRONICS**

GEORGETOWN NORTH  
SHOPPING CENTER  
2810 MAPLECREST RD.  
FORT WAYNE, IN 46815  
219-484-4846  
We service what we sell. 10-9 T,  
TH, F; 10-5 W, SAT.

### *Iowa*

#### **BOB SMITH ELECTRONICS**

12 SOUTH 21ST STREET  
FT. DODGE, IA 50501  
515-576-3886  
For an EZ deal.

### *Kansas*

#### **ASSOCIATED RADIO**

8012 CONSER P.O.B. 4327  
OVERLAND PARK, KS 66204  
913-381-5901  
Amateur Radio's Top Dealer.  
Buy — Sell — Trade.

*Dealers - You should be here too! Contact Ham Radio today for complete details.*

# Amateur Radio Dealer

## Kentucky

**COHOON AMATEUR SUPPLY**  
HIGHWAY 475  
TRENTON, KY 42286  
502-886-4535  
Yaesu, Ten-Tec, Tempo, Dentron.  
Our service is the BEST.

## Maryland

**COMM CENTER, INC.**  
9624 FT. MEADE ROAD  
LAUREL PLAZA RT. 198  
LAUREL, MD 20810  
301-792-0600  
New & Used Amateur Equipment.  
Wilson, Ten-Tec, R. L. Drake, Tempo

**PROFESSIONAL  
ELECTRONICS CO., INC.**  
1710 JOAN AVENUE  
BALTIMORE, MD 21234  
301-661-2123  
A professional place for amateurs.  
Service-sales-design.

## Massachusetts

**TUFTS RADIO ELECTRONICS**  
209 MYSTIC AVENUE  
MEDFORD, MA 02155  
617-395-8280  
New England's friendliest  
ham store.

## Michigan

**RADIO SUPPLY & ENGINEERING**  
1207 WEST 14 MILE ROAD  
CLAWSON, MI 48017  
313-435-5660  
10001 Chalmers, Detroit, MI  
48213, 313-371-9050.

## Minnesota

**DACOM**  
3926 BEAU D'RUE DRIVE  
EAGAN, MN 55122  
612-454-7420  
Full Sales & Service  
HF thru UHF

**ELECTRONIC CENTER, INC.**  
127 THIRD AVENUE NORTH  
MINNEAPOLIS, MN 55401  
612-371-5240  
ECI is still your best buy.

## Missouri

**HAM RADIO CENTER, INC.**  
8340-42 OLIVE BLVD.  
ST. LOUIS, MO 63132  
800-325-3636  
See Our Ads  
In This Issue.

**MIDCOM ELECTRONICS, INC.**  
2506 SO. BRENTWOOD BLVD.  
ST. LOUIS, MO 63144  
314-961-9990  
At Midcom you can try before you  
buy!

## Nebraska

**COMMUNICATIONS CENTER, INC.**  
2226 NORTH 48 ST.  
LINCOLN, NE 68504  
800-228-4097  
Yaesu, Drake, Tempo, Swan,  
HyGain - call Toll Free

## New Hampshire

**EVANS RADIO, INC.**  
BOX 893, RT. 3A BOW JUNCTION  
CONCORD, NH 03301  
603-224-9961  
Icom, Dentron & Yaesu dealer.  
We service what we sell.

## New Jersey

**ATKINSON & SMITH, INC.**  
17 LEWIS ST.  
EATONTOWN, NJ 07724  
201-542-2447  
Ham supplies since "55".

## New Mexico

**ELECTRONIC MODULE**  
601 N. TURNER  
HOBBS, NM 88240  
505-397-3012  
Yaesu, Kenwood, Swan, Dentron,  
Tempo, Atlas, Wilson, Cushcraft

## New York

**ADIRONDACK RADIO SUPPLY, INC.**  
185 W. MAIN STREET  
AMSTERDAM, NY 12010  
518-842-8350  
Yaesu dealer for the Northeast.

**CFP COMMUNICATIONS**  
211 NORTH MAIN STREET  
HORSEHEADS, NY 12010  
607-739-0187  
Jim Beckett, WA2KTJ, Manager  
Bryant Hozempa, WB2LVW, Sales

**GRAND CENTRAL RADIO**  
124 EAST 44 STREET  
NEW YORK, NY 10017  
212-682-3869  
Drake, Atlas, Ten-Tec, Midland,  
Hy-Gain, Mosley in stock

**HARRISON**  
"HAM HEADQUARTERS, USA"  
ROUTE 110 & SMITH STREET  
FARMINGDALE, L. I., N. Y. 11735  
516-293-7990  
Since 1925 . . . Service, Satisfaction,  
Savings. Try Us!

**RADIO WORLD**  
ONEIDA COUNTY AIRPORT  
TERMINAL BLDG.  
ORISKANY, NY 13424  
315-337-2622  
New & used ham equipment.  
See Warren K2IXN or Joe WB2GJR

## Ohio

**UNIVERSAL SERVICE**  
114 N. THIRD STREET  
COLUMBUS, OH 43215  
614-221-2335  
Give U.S. a try when ready to buy.

## Oklahoma

**RADIO STORE, INC.**  
2102 SOUTHWEST 59th ST.  
(AT 59th & S. PENNSYLVANIA)  
OKLAHOMA CITY, OK 73119  
405-682-2929  
New and used equipment —  
parts and supply.

## Oregon

**PORTLAND RADIO SUPPLY CO.**  
1234 S.W. STARK STREET  
PORTLAND, OREGON 97205  
503-228-8647  
Second location, 1133 S. Riverside  
Avenue, Medford, OR 97501.

## Pennsylvania

**ELECTRONIC EXCHANGE**  
136 N. MAIN STREET  
SOUDERTON, PA 18964  
215-723-1200  
New & Used Amateur Radio  
sales and service.

**"HAM" BUERGER, INC.**  
68 N. YORK ROAD  
WILLOW GROVE, PA 19090  
215-659-5900  
Communications specialists.  
Sales and service.

**HAMTRONICS, DIV. OF  
TREVISE ELECT.**  
4033 BROWNSVILLE ROAD  
TREVISE, PA 19047  
215-357-1400  
Same location for 25 years.

# HAMART

## South Carolina

**AMATEUR RADIO ELECTRONICS**  
100 STATE ST.  
WEST COLUMBIA, SC 29169  
803-796-7957  
Featuring Swan Equipment

## Tennessee

**GERMANTOWN AMATEUR SUPPLY**  
3203 SUMMER AVE.  
MEMPHIS, TN 38112  
800-238-6168  
No monkey business. Call  
Toll Free.

**J-TRON ELECTRONICS**  
505 MEMORIAL BLVD.  
SPRINGFIELD, TN 37172  
615-384-3501  
Ten-Tec dealer — call or  
write for best trade.

## Texas

**AGL ELECTRONICS**  
3068 FOREST LANE, SUITE 309  
DALLAS, TX 75234  
214-241-6414 (within Texas)  
Out-of-State, Call our toll-free  
number 800-527-7418.

**HARDIN ELECTRONICS**  
5635 E. ROSEDALE  
FT. WORTH, TX 76112  
817-461-9761  
Your Full Line Authorized  
Yaesu Dealer.

## Wisconsin

**AMATEUR  
ELECTRONIC SUPPLY, INC.**  
4828 WEST FOND DU LAC AVENUE  
MILWAUKEE, WI 53216  
414-442-4200  
Open Mon & Fri 9-9, Tues, Wed,  
Thurs, 9-5:30, Sat, 9-3.

## Washington

**AMATEUR RADIO SUPPLY CO.**  
6213 13TH AVENUE SOUTH  
SEATTLE, WA 98108  
206-767-3222  
First in Ham Radio in Washington  
Northwest Bird Distributor

## Wyoming

**DENCO COMMUNICATIONS CENTER**  
1728 EAST 2ND STREET  
CASPER, WY 82601  
307-234-9197  
Sales, Service to Wyoming  
and the Northern Rockies.

# NEWS Update

from **DRAKE**

The R.L. Drake Company is  
pleased to report that the

## Drake UV-3 Multi-Band FM Transceiver covers the new FM Repeater Sub-Band expansions



See the Drake UV-3 Brochure  
for complete specifications.

... which were just  
announced by the  
FCC for 2 meter  
and 220 MHz  
Amateur Bands.

**NO RETUNING  
NECESSARY**

## R. L. DRAKE COMPANY



540 Richard Street, Miamisburg, Ohio 45342 • Phone (513) 866-2421 • Telex 288-017

Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470

## ALL BAND TRAP ANTENNA!



**5 BAND OPERATION - ONLY ONE NEAT SMALL ANTENNA. FOR CONGESTED HOUSING AND APARTMENT DWELLERS!**

**FOR ALL AMATEUR HF TRANSMITTERS GUARANTEED FOR 1,000 WATTS POWER. LIGHT, NEAT WEATHERPROOF.**

Complete as shown total length 102 ft. with 90 ft. of 52 ohm RG58U coax and PL259 connector. Hi-impact molded resonant traps. (wt. 3 oz. 1" x 5" long) You just tune to desired band for excellent reports! Excellent for ALL world - wide receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Can be used as inverted V. NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION!

80-40-20-15-10 meter bands. Complete .....	\$39.95
40-20-15-10 meter bands. 54-ft. ant. ....	\$38.95
20-15-10 meter bands. 24-ft. ant. ....	\$37.95

SEND ONLY \$5.00 (cash, ck., mo.) and pay postman balance COD plus postage on arrival or send full price for pp. del. BankAmericard - - Master Charge - - Ph 308-236-5333 Free info. available only from. WESTERN ELECTRONICS Dept. AH-12 Kearney, Nebraska, 68847

## PLANET XP-7 CALLING EARTH

Takes you "to the exciting frontiers of astronomy, with a sense of great adventures to come"

Dinah Moche THE PHYSICS TEACHER

"Lively, human, thought-provoking"  
Ron Bracewell IEEE SPECTRUM

"An inspiration to any young scientist"  
Bernard Burke PHYSICS TODAY

A FASCINATING, POPULAR, PERSONAL INSIGHT INTO THE EXPLORATION OF THE COSMOS BY RADIO AND THE DISCOVERY OF THE OLDEST SIGNALS IN THE UNIVERSE (12 BILLION YEARS) COMING FROM THE GREATEST DISTANCE, LEADING TO THE SEARCH FOR SIGNALS FROM EXTRATERRESTRIAL CIVILIZATIONS

**BIG EAR** John Kraus W8JK

228 pages Illustrated

Cygnus Quasar Books, Box 85, Powell, Ohio 43065  
\$3.25 paper, \$6.25 hard, postpaid

## tone ENCODER PAD

MODEL TTP-03

- DIGITRAN® Keyboard
- Output Level Set Pot
- Crystal Controlled-Digitally Synthesized Tones
- Strapping for Hi-Low Z Output
- Internal 5 V. Regulator  
Supply Voltage Range 7 to 24 V.
- RFI Suppression
- Velcro and Case Included
- Size 2.80 - 2.00 - 0.60 Inches



**\$54.95**

POSTPAID  
IN U.S.A.

TEXAS RESIDENTS  
ADD 5% SALES TAX  
CHECK OR M.O.  
SEE UP-COMING AD FOR NEW  
AUTOMATIC UNIT: ATD-70  
2 NUMBERS, FIELD PROGRAM-  
MABLE. \$79.95

**SATISFACTION  
GUARANTEED**

# CLENG

**CLENG ELECTRONICS COMPANY**  
BOX 12171 DALLAS, TEXAS 75225



# Tropical Hamboree

ARRL Southeastern  
Division

## CONVENTION

FLAGLER  
DOG TRACK

(37th Ave. at N.W. 7th St.)

MIAMI, FLA.

Jan. 21-22,  
1978

FREE PARKING INCLUDING  
OVERNIGHT SPACE FOR  
COMPLETELY  
SELF-CONTAINED RV's

Pre-  
Registration  
**\$2.50**

FOR SPECIAL HOTEL RATES  
AND FURTHER INFORMATION  
WRITE:

P.O. BOX 350045  
RIVERSIDE STA.  
MIAMI, FLA. 33135

# WESTCOM POWER




## the new 2 meter VHF amplifier from Westcom.

- An add-on unit, no internal connections or adjustments required to associated equipment • Standard Amplifier Models operate FM. Linear Models operate all modes: SSB, FM, AM, RTTY, CW, etc. • "Microstrip" design provides high stability and optimum performance over wide bandwidth • Factory adjusted, no tuning required. • Mobile mounting bracket included • RF sensing T/R switching, adjustable dropout delay • Remote keying capability • Thermally coupled biasing • Reverse Voltage protected and fused • Conservatively rated with oversized heat sink • Red LED indicators for monitoring DC and RF • VSWR protected • Ninety day material and workmanship warranty

MODEL NO.	INPUT POWER (watts)	NOM OUTPUT (watts)	NOM CURRENT 13.8 VDC	PRICE
2M 3X30	1-4	30	4	\$72.95
2M 3X30L*	1-4	30	4	\$82.95
2M 10X40	2-12	40	5	\$77.95
2M 15X50L*	5-15	50	6	\$94.95
2M 15X80	5-15	80	11	\$129.95
2M 15X80L*	5-15	80	11	\$139.95

\*Linear; AM, CW, FM, SSB, RTTY; Size: 4 1/4 x 5 1/2 x 2 1/4  
technical specifications and data subject to change without notice

Call your local dealer, or write direct:

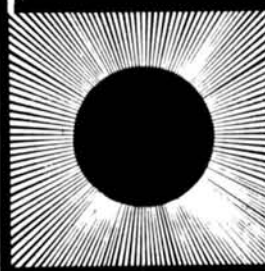

## WESTCOM

ENGINEERING

1320 Grand Avenue San Marcos,  
California 92069 (714) 744-0700

**NEW**

713/658-0268      Nites 713/497-5683

Subsidiary "Little Giant Antenna Labs"

**419-646-3495**

## UNIVERSAL TOWERS

FREE STANDING  
ALUMINUM TOWER  
10' to 100'  
Prices from  
\$128.00 (30')

**MOST  
POPULAR  
HAM TOWER  
EVER MADE!**



REQUEST

**NEW CATALOG  
OF**

**TOWERS &  
ANTENNAS**

Communication Specialists  
Midwest Ham Headquarters

For Over 38 Years  
HAMS! Write For Free Catalog  
and Wholesale Prices!

Electronic Distributors, Inc.

1960 Peck Muskegon, MI 49441  
Tel: 616-726-3196 TELEX: 22-8411

## COLLINS & MORE

Collins 75S3B, Ham rcvr	\$725.00
Collins 312B4, Excell., round.	\$250.00
Collins KWM-2 transcvr. V.G.	\$650.00
Collins 32S3, Ham Xmtr	\$695.00
Collins 30S1, like new	\$175.00
Collins 75S3, very good	\$475.00
Collins 32S3, round, late	\$1195.00
Collins 75S3C, round, late	\$1295.00
Collins R388/51J3, vy. gd.	\$425.00
Drake R4C, new, boxed, w/250-500 Hz filters.	\$535.00
National HRO500 receiver, exc.	\$795.00

We stock good, used equipment from Collins, Drake, Heath and other manufacturers. Hundreds of test items also available. Call for specific requirements, or write for free catalog.

**DAMES COMMUNICATION SYSTEMS**

201-998-4256

10 SCHUYLER AVENUE  
NORTH ARLINGTON, N. J. 07032

Merry Christmas and Happy New Year

## 16-POLE R-4C SSB!

Improve the early-stage selectivity of your Drake R-4C while adding 8 additional poles (total 16) with an internally-mounted, switchable set of first IF crystal filters. Reduce ORM, leakage, overload. Ideal for DX and contest work. Overall shape factor better than 1.4. Maximum skirt selectivity with maximum intelligibility. Two models available: CF-2.6K/8 retain modest passband tuning since they are slightly wider than second IF filter. Total bandwidth: 2300 Hz at 6dB, 3100 Hz at 60dB. CF-2.3K/8 provide greater selectivity. Total bandwidth: 2100 Hz at 6dB, 2900 Hz at 60dB. Either set of filters can be mounted in receiver and relay switched with our kits which start at \$29.00. USB and LSB CF-2.6K/8 and CF-2.3K/8 pairs are \$120.00 per set. Money back if not satisfied.

**Sherwood Engineering Inc.**

Dept. A

1268 South Ogden St.  
Denver, Colo. 80210  
(303) 722-2257



## NOW YOU CAN RECEIVE THE WEAK SIGNALS WITH THE NEW AMECO PREAMPLIFIER



Model PT-2 is a continuous tuning 6-160 meter preamp, designed for use with a transceiver. It contains new sophisticated control circuitry that permits it to be added to virtually any transceiver with NO modification. No serious ham can be without one! Other features include: \*Improves sensitivity and signal-to-noise ratio. \*Boosts signals up to 26 db. \*For AM, SSB, or CW. \*Dual gate FET amplifier gives superior cross-modulation protection. \*Simple to install. \*Improves immunity to transceiver front-end overload by use of its variable gain attenuator. \*Provides master power control for station equipment. .... \$69.95

Model PLF-2 is similar to the PT-2, except that it is used for receivers only. Does not have gain control. .... \$49.95

At leading distributors or write to:

**AMECO EQUIPMENT CO. Div. Ameco Publishing Corp.**  
275 Hillside Ave., Williston Park, N. Y. 11596

## An invitation to join The "Argonaut Club"

### Argonaut 509

Tired of push-button

QSOs? Then the excitement

of Argonauting is for you! A challenge?

Of course, The test of an operator? Perhaps. But above all it is the thrill of working the world with five watts.

The club is exclusive but if you enjoy the spirit of conquering distance with lower power, you are "in". There are no dues — just \$359.00, the price of an Argonaut. Join more than two thousand fellow members with Argo fun. Your membership awaits you at most ham dealers.



Argonaut 509 \$359.00

### SPECIFICATIONS:

Five bands, 3.5-30 MHz.  
SSB and CW modes. Fully solid state. Permeability tuning.  
Instant break-in. Instant band change. Built-in SWR bridge.  
S-Meter. WWV. Internal speaker.  
Direct frequency readout.  
Receiver offset tuning. Five watts input. Automatic sideband selection. Plug-in circuit boards.  
1/2 uV receiver sensitivity.  
12-14 VDC or AC pack power.  
Weight 6 pounds. Size HWD: 4 1/2" x 13" x 7".

### ACCESSORIES:

Model 206 — 100 kHz Crystal	
Calibrator .....	\$29.00
Model 208 — CW Filter .....	\$29.00
Model 210 — One Ampere	
Power Supply .....	\$30.00
Model 215P — Ceramic	
Microphone .....	\$29.50
Model KR5-A — Keyer .....	\$39.50

For further information, write:

**TEN-TEC**

SEVIERVILLE, TENNESSEE 37862  
EXPORT: 5715 LINCOLN AVE.  
CHICAGO, ILLINOIS, 60646

# ham radio cumulative index

## 1968-1977

### antennas and transmission lines

#### general

Antenna control, automatic azimuth/elevation for satellite communications  
WA3HLT p. 26, Jan 75  
Correction p. 58, Dec 75

Antenna dimension (HN)  
WA9JMY p. 66, Jun 70

Antennas and capture area  
K6MIO p. 42, Nov 69

Antenna and control-link calculations for repeater licensing  
W7PUG p. 58, Nov 73  
Short circuit p. 59, Dec 73

Antenna and feedline facts and fallacies  
W5JJ p. 24, May 73

Antenna design, programmable calculator simplifies (HN)  
W3DVO p. 70, May 74

Antenna gain (letter)  
W3AFM p. 62, May 76

Antenna gain, measuring  
K6JYO p. 26, Jul 69

Antenna switching, solid-state  
W2EEY p. 30, Nov 68

Antenna wire, low-cost copper (HN)  
W2EUQ p. 73, Feb 77

Anti-QRM methods  
W3FQJ p. 50, May 71

Bridge for antenna measurements, simple  
W2CTK p. 34, Sep 70

Cubical quad measurements  
W4YM p. 42, Jan 69

Dipole center insulator (HN)  
WA1ABP p. 69, May 69

Diversity receiving system  
W2EEY p. 12, Dec 71

Dummy load and rf wattmeter, low-power  
W2OLU p. 56, Apr 70

Dummy loads, experimental  
W8YFB p. 36, Sep 68

Dummy load, low-power vhf  
WB9DNI p. 40, Sep 73

Effective radiated power (HN)  
VE7CB p. 72, May 73

Feedpoint impedance characteristics of practical antennas  
W5JJ p. 50, Dec 73

Filters, low-pass, for 10 and 15  
W2EEY p. 42, Jan 72

Gain vs antenna height, calculating  
WB8IFM p. 54, Nov 73

GDO, new uses for  
K2ZSQ p. 48, Dec 68

Gin pole, simple lever for raising masts  
WA2ANU p. 72, May 77

Ground screen, alternative to radials  
WBØJGP p. 22, May 77

Grounding, safer (letter)  
WA5KTC p. 59, May 72

Ground rods (letter)  
W7FS p. 66, May 71

Ground systems, vertical antenna  
W7LR p. 30, May 74

Headings, beam antenna  
W6FFC p. 64, Apr 71

Hook, line 'n sinker (HN)  
WA4NED p. 76, Sep 68

Horizontal or vertical (HN)  
W7IV p. 62, Jun 72

Impedance measurements, nonresonant antenna  
W7CSD p. 46, Apr 74

Insulators, homemade antenna (HN)  
W7ZC p. 70, May 73

Isotropic source and practical antennas  
K6FD p. 32, May 70

Lightning protection (C&T)  
W1DTY p. 50, Jun 76

Line-of-sight distance, calculating  
WB5CBC p. 56, Nov 76

Measurement techniques for antennas and transmission lines  
W4OQ p. 36, May 74

Measuring antenna gain  
K6JYO p. 26, Jul 69

Mobile mount, rigid (HN)  
VE7ABK p. 69, Jan 73

Power in reflected waves  
Woods p. 49, Oct 71

Reflected power, some reflections on  
VE3AAZ p. 44, May 70

Reflectometers  
K1YZW p. 65, Dec 69

Rf current probe (HN)  
W6HPH p. 76, Oct 68

Rf power meter, low-level  
W5WGF p. 58, Oct 72

Sampling network, rf — the milli-trap  
W6QJW p. 34, Jan 73

Smith chart, how to use  
W1DTY p. 16, Nov 70  
Correction p. 76, Dec 71

Standing-wave ratios, importance of  
W2HB p. 26, Jul 73  
Correction (letter) p. 67, May 74

Time-domain reflectometry, practical experimenter's approach  
WAØPIA p. 22, May 71

T-R switch  
K3KMO p. 61, Apr 69

Voltage-probe antenna  
W1DTY p. 20, Oct 70

#### high-frequency antennas

All band antenna portable (HN)  
W2INS p. 68, Jun 70

All-band phased-vertical  
WA7GXO p. 32, May 72

Antenna, 3.5 MHz, for a small lot  
W6AGX p. 28, May 73

Antenna potpourri  
W3FQJ p. 54, May 72

Antenna systems for 80 and 40 meters  
K6KA p. 55, Feb 70

Army loop antenna — revisited  
W3FQJ p. 59, Sep 71  
Added notes p. 64, Jan 72

Beam antenna, improved triangular shaped  
W6DL p. 20, May 70

Beam for ten meters, economical  
W1FPF p. 54, Mar 70

Beverage antenna  
W3FQJ p. 67, Dec 71

Big beam for 10 meters  
VE1TG p. 32, Mar 68

Bobtail curtain array  
W8YFB p. 81, May 77

Bobtail curtain array, forty-meter  
VE1TG p. 58, Jul 69

Coaxial dipole antenna, analysis of  
W2DU p. 46, Aug 76

Coaxial dipole, multiband (HN)  
W4BDK p. 71, May 73

Collinear, six-element, for  
WØYBF p. 22, May 76

Compact antennas for 20 meters  
W4ROS p. 38, May 71

Converted-vee, 80 and 40 meter  
W6JKR p. 18, Dec 69

Corner-fed loop, low frequency  
ZL1BN p. 30, Apr 76  
Installation modified p. 41, Feb 77

Cubical quad antenna design parameters  
K6OPZ p. 55, Aug 70

Cubical-quad antennas, mechanical design of  
VE3II p. 44, Oct 74

Cubical-quad antennas, unusual  
W1DTY p. 6, May 70

Cubical quad, improved low-profile, three band  
W1HXU p. 25, May 76

Cubical quad, three-band  
W1HXU p. 22, Jul 75

Curtain antenna (HN)  
W4ATE p. 66, May 72

Dipole, all-band tuned  
ZS6BT p. 22, Oct 72

Dipole antennas on non-harmonic frequencies (HN)  
W2CTK p. 72, Mar 69

Dipole beam  
W3FQJ p. 56, Jun 74

Dipole pairs, low SWR  
W6FPO p. 42, Oct 72

Dipole sloping inverted-vee  
W6NIF p. 48, Feb 69

Double bi-square array  
W6FFF p. 32, May 71

Dual-band antennas, compact  
W6SAI p. 18, Mar 70

DX antenna, single-element  
W6FHM p. 52, Dec 72

Performance (letter)  
p. 65, Oct 73

Folded mini-monopole antenna  
W6SAI p. 32, May 68

Four-band wire antenna  
W3FQJ p. 53, Aug 75

Ground-plane antenna: history and development  
K2FF p. 26, Jan 77

Ground-plane, multiband (HN)  
JA1QIY p. 62, May 71

Groundplane, three-band  
LA1EI p. 6, May 72  
Correction p. 91, Dec 72  
Footnote (letter) p. 65, Oct 72

High-frequency amateur antennas  
W2WLR p. 28, Apr 69

High-frequency diversity antennas  
W2WLR p. 28, Oct 69

Horizontal-antenna gain at selected vertical radiation angles  
W7LR p. 54, Feb 76

Horizontal antennas, optimum height for  
W7LR p. 40, Jun 74

Horizontal antennas, vertical radiation patterns  
WA9RQY p. 58, May 74

Inverted-vee antenna (letter)  
WB6AQF p. 66, May 71

Inverted-vee antenna, modified  
W2KTW p. 40, Oct 71

Inverted-vee installation, improved low-band (HN)  
W9KNI p. 68, May 76

Inverted V or delta loop, how to add to tower  
K4DJC p. 32, Jul 76

Large vertical, 160 and 80 meters  
W7IV p. 8, May 75

Log-periodic antenna, 14, 21 and 28 MHz  
W4AEO p. 18, Aug 73

Log-periodic antennas, 7-MHz  
W4AEO p. 16, May 73

Log-periodic antennas, feed system for  
W4AEO p. 30, Oct 74

Log periodic antennas, graphical design method for  
W4AEO p. 14, May 75

Log-periodic antennas, vertical monopole, 3.5 and 7.0 MHz  
W4AEO p. 44, Sep 73

Log-periodic beams, improved (letter)  
W4AEO p. 74, May 75

Log-periodic beam, 15 and 20 meters  
W4AEO p. 6, May 74

Log periodic feeds (letter)  
W4AEO p. 66, May 74

Log-periodic, three-band  
W4AEO p. 28, Sep 72

Longwire antenna, new design  
K4EF p. 10, May 77

Long-wire multiband antenna  
W3FQJ p. 28, Nov 69

Loop antennas  
W4OQ p. 18, Dec 76

Loop receiving antenna  
W2IMB p. 66, May 75  
Correction p. 58, Dec 75

Loop-yagi antennas  
VK2ZTB p. 30, May 76

Low-mounted antennas  
W3FQJ p. 66, May 73

Mobile antenna, helically wound  
ZE6JP p. 40, Dec 72

Mono-loop antenna (HN)  
W8BW p. 70, Sep 69

Multiband dipoles for portable use  
W6SAI p. 12, May 70

Phased array, design your own  
K1AON p. 78, May 77

Phased array, electrically-controlled  
W5TRS p. 52, May 75

Phased vertical array, fine tuning  
W4FXE p. 46, May 77

Phased vertical array, four-element  
W8HXR p. 24, May 75

Quad antenna, multiband  
DJ4VM p. 41, Aug 69

Receiving antennas  
K6ZGQ p. 56, May 70

Satellite antenna, simple (HN)  
WA6PXY p. 59, Feb 75

Selective antenna system minimizes unwanted signals  
W5TRS p. 28, May 76

Shunt-feed systems for grounded vertical radiators, how to design  
W4OQ p. 34, May 75

Simple antennas for 40 and 80 W5RUB	p. 16, Dec 72
Simple 1-, 2- and 3-band antennas W9EGQ	p. 54, Jul 68
Sloping dipoles W5RUB	p. 19, Dec 72
Performance (letter)	p. 76, May 73
Small-loop antennas W4YOT	p. 36, May 72
Stub bandswitched antennas W2EEY	p. 50, Jul 69
Suitcase antenna, high-frequency VK5BI	p. 61, May 73
Tailoring your antenna, how to KH6HDM	p. 34, May 73
Telephone-wire antenna (HN) K9TBD	p. 70, May 76
Three-band ground plane W6HPH	p. 32, Oct 68
Triangle antennas W3FQJ	p. 56, Aug 71
Triangle antennas W6KIW	p. 58, May 72
Triangle antennas (letter) K4ZZV	p. 72, Nov 71
Triangle beams W3FQJ	p. 70, Dec 71
Tuning aid for the sightless (HN) W6VX	p. 83, Sep 76
Unidirectional antenna for the low-frequency bands GW3NJV	p. 61, Jan 70
Vertical antenna radiation patterns W7LR	p. 50, Apr 74
Vertical antenna, low-band W4IYB	p. 70, Jul 72
Vertical antenna, three-band W9BQE	p. 44, May 74
Vertical antennas, improving performance of K6FD	p. 54, Dec 74
Vertical antennas, performance characteristics W7LR	p. 34, Mar 74
Vertical beam antenna, 80 meter VE1TG	p. 26, May 70
Vertical dipole, gamma-loop-fed W6SAI	p. 19, May 72
Vertical for 80 meters, top-loaded W2MB	p. 20, Sep 71
Vertical radiators W4OQ	p. 16, Apr 73
Vertical, top-loaded 80 meter VE1TG	p. 48, Jun 69
Vertical-tower antenna system W4OQ	p. 56, May 73
Whips and loops as apartment antennas W2EEY	p. 80, Mar 68
Windom antenna, four-band W4VUO	p. 62, Jan 74
Correction (letter)	p. 74, Sep 74
Zepp antenna, extended W6QVI	p. 48, Dec 73
ZL special antenna, understanding the WA6TKT	p. 38, May 76
3.5-MHz phased horizontal array K4JC	p. 56, May 77
7-MHz short vertical antenna W8TYX	p. 60, Jun 77
160-meter loop, receiving K6HTM	p. 46, May 74
160-meter vertical, shortened (HN) W6VX	p. 72, May 76
160 meters with 40-meter vertical W2IMB	p. 34, Oct 72

## vhf antennas

Antennas for satellite communications, simple K4GSX	p. 24, May 74
Circularly-polarized ground-plane antenna for satellite communications K4GSX	p. 28, Dec 74
Collinear antenna for two meters, nine-element W6RJO	p. 12, May 72
Collinear antenna (letter) W6SAI	p. 70, Oct 71
Collinear array for two meters, 4-element W6KGF	p. 6, May 71
Collinear antenna, four element 440-MHz WA6HTP	p. 38, May 73
Collinear, six meter K4ERO	p. 59, Nov 69
Converting low-band mobile antenna to 144-MHz (HN) K7ARR	p. 90, May 77
Corner reflector antenna, 432 MHz WA2FSQ	p. 24, Nov 71
Cubical quad, economy six-meter W6DOR	p. 50, Apr 69
Feed horn, cylindrical, for parabolic reflectors WA9HUV	p. 16, May 76
Ground plane, 2-meter, 0.7 wavelength W3WZA	p. 40, Mar 69
Ground plane, portable vhf (HN) K9DHD	p. 71, May 73
J-pole antenna for 6-meters K4SDY	p. 48, Aug 68

Log-periodic, yagi beam K6RIL, W6SAI	p. 8, Jul 69
Correction	p. 68, Feb 70
Magnet-mount antenna, portable (HN) WB2YU	p. 67, May 76
Matching techniques for vhf/uhf antennas W1JAA	p. 50, Jul 76
Microwave antenna, Low-cost K6HIJ	p. 52, Nov 69
Mobile antenna, magnet-mount W1HCL	p. 54, Sep 75
Mobile antenna, six-meter (HN) W4PSJ	p. 77, Oct 70
Mobile antennas, vhf, comparison of W4MNW	p. 52, May 77
Moonbounce antenna, practical 144-MHz K6HCP	p. 52, May 70
Oscar antenna, mobile (HN) W6OAL	p. 67, May 76
Parabolic reflector antennas VK3ATN	p. 12, May 74
Parabolic reflector element spacing WA9HUV	p. 28, May 75
Parabolic reflector gain W2TQK	p. 50, Jul 75
Parabolic reflectors, finding the focal length (HN) WA4WDL	p. 57, Mar 74
Parabolic reflector, 16-foot homebrew WB6IOM	p. 8, Aug 69
Quad-yagi arrays, 432- and 1296-MHz W3AED	p. 20, May 73
Short circuit	p. 58, Dec 73
Simple antennas, 144-MHz WA3NFW	p. 30, May 73
Switch, antenna for 2 meters, solid-state K2ZSQ	p. 48, May 69
Two-meter antenna, simple (HN) W6BLZ	p. 78, Aug 68
Two-meter fm antenna (HN) WB6KYE	p. 64, May 71
Two-meter mobile antennas W6BLZ	p. 76, May 68
Vertical antennas, truth about $\frac{1}{4}$ -wavelength KØDOK	p. 48, May 74
Added note (letter)	p. 54, Jan 75
Vhf antenna switching without relays (HN) K2ZSQ	p. 76, Sep 68
Whip, 5/8-wave, 144 MHz (HN) VE3DDD	p. 70, Apr 73
Yagi antennas, how to design W1JR	p. 22, Aug 77
Yagi, 1296-MHz W2CQH	p. 24, May 72
7-MHz attic antenna (HN) W2ISL	p. 68, May 76
10-GHz dielectric antenna (HN) WA4WDL	p. 80, May 75
144-MHz vertical, $\frac{1}{4}$ -wavelength K6KLO	p. 40, Jul 74
144-MHz antenna, $\frac{1}{4}$ -wavelength built from CB mobile whip (HN) WB4WSU	p. 67, Jun 74
144-MHz colinear uses PVC pipe mast (HN) K8LLZ	p. 66, May 76
144-MHz mobile antenna (HN) W2EUQ	p. 80, Mar 77
144-MHz vertical mobile antennas, $\frac{1}{4}$ and $\frac{1}{2}$ wavelength, test data on W2LTJ, W2CQH	p. 46, May 76
144-MHz, $\frac{1}{4}$ -wavelength vertical W1RHN	p. 50, Mar 76
144-MHz, $\frac{1}{4}$ -wavelength, vertical antenna for mobile K4LPQ	p. 42, May 76
432-MHz high-gain Yagi K6HCP	p. 46, Jan 76
Comments, WØPW	p. 63, May 76
432-MHz OSCAR antenna (HN) W1JAA	p. 58, Jul 75
1296-MHz Yagi array W3AED	p. 40, May 75

## matching and tuning

Antenna coupler for three-band beams ZS6BT	p. 42, May 72
Antenna coupler, six-meter K1RAK	p. 44, Jul 71
Antenna impedance transformer for receivers (HN) W6NIF	p. 70, Jan 70
Antenna instrumentation, simple, (repair bench) K4IPV	p. 71, Jul 77
Antenna matcher, one-man W4SD	p. 24, Jun 71
Antenna tuner adjustment (HN) W4MTH	p. 53, Dec 75
Antenna tuner, automatic WAØAQC	p. 36, Nov 72
Antenna tuner, medium-power toroidal WB2ZSH	p. 58, Jan 74
Antenna tuner for optimum power transfer W2WLR	p. 28, May 70
Antenna tuners W3FQJ	p. 58, Dec 72
Antenna tuning units W3FQJ	p. 58, Jan 73

Balun, adjustable for yagi antennas W6SAI	p. 14, May 71
Balun, Simplified (HN) WAØKKC	p. 73, Oct 69
Baluns, wideband bridge W6SAI, WA6BAN	p. 28, Dec 68
Broadband Antenna Baluns W6SAI	p. 6, Jun 68
Couplers, random-length antenna W2EEY	p. 32, Jan 70
Dummy loads W4MB	p. 40, Mar 76
Feeding and matching techniques for vhf/uhf antennas W1JAA	p. 54, May 76
Gamma-match capacitor, remotely controlled K2BT	p. 74, May 75
Gamma-matching networks, how to design W7ITB	p. 46, May 73
Impedance bridge, low-cost RX W8YFB	p. 6, May 73
Impedance-matching baluns, open-wire W6MUR	p. 46, Nov 73
Impedance-matching systems, designing W7CSD	p. 58, Jul 73
Loads, affect of mismatched transmitter W5JJ	p. 60, Sep 69
Matching, antenna, two-band with stubs W6MUR	p. 18, Oct 73
Matching system, two-capacitor W6MUR	p. 58, Sep 73
Measuring complex impedance with swr bridge WB4KSS	p. 46, May 75
Mobile transmitter, loading W4YB	p. 46, May 72
Noise bridge, antenna WB2EGZ	p. 18, Dec 70
Noise bridge, antenna (HN) K8EEG	p. 71, May 74
Noise bridge for impedance measurements YA1GJM	p. 62, Jan 73
Added notes	p. 66, May 74; p. 60, Mar 75
Phase meter, rf VE2AYU, Korth	p. 28, Apr 73
Quadrifilar toroid (HN) W9LL	p. 52, Dec 75
Stub-switched, stub-matched antennas W2EEY	p. 34, Jan 69
Swr alarm circuits W2EEY	p. 73, Apr 70
Swr bridge WB2ZSH	p. 55, Oct 71
Swr bridge and power meter, integrated W6DOB	p. 40, May 70
Swr bridge readings (HN) W6FPO	p. 63, Aug 73
Swr indicator, aural, for the visually handicapped K6HTM	p. 52, May 76
Swr meter W6VSV	p. 6, Oct 70
Swr meter, improving (HN) W5NPD	p. 68, May 76
Transmatch, five-to-one W7IV	p. 54, May 74
Transmission lines, grid dipping (HN) W2OLU	p. 72, Feb 71
Transmission lines, uhf WA2VTR	p. 36, May 71
Uhf coax connectors (HN) WØLCP	p. 70, Sep 72

## towers and rotators

Antenna and rotator preventive maintenance WA1ABP	p. 66, Jan 69
Antenna and tower restrictions W7IV	p. 24, Jan 76
Antenna mast, build your own tilt-over W6KRT	p. 42, Feb 70
Correction	p. 76, Sep 70
Az-el antenna mount for satellite communications W2LX	p. 34, Mar 75
Cornell-Dubilier rotators (HN) K6KA	p. 82, May 75
Ham-M modifications (HN) W2TQK	p. 72, May 76
Ham-M rotator automatic position control WB6GNM	p. 42, May 77
Keeping your beam, tips for W6BLZ	p. 50, Aug 68
Pipe antenna masts, design data for W3MR	p. 52, Sep 74
Added design notes (letter)	p. 75, May 75
Rotator, AR-22, fixing a sticky WA1ABP	p. 34, Jun 71
Rotator for medium-sized beams K2BT	p. 48, May 76
Rotator, T-45, Improvement (HN) WAØVAM	p. 64, Sep 71
Stress analysis of antenna systems W2FZJ	p. 23, Oct 71
Telescoping tv masts (HN) WAØKKC	p. 57, Feb 73
Tilt-over tower base, low-cost WA1ABP	p. 86, Apr 68
Tilt-over tower uses extension ladder W5TRS	p. 71, May 75

Tower guying (HN)	p. 98, Nov 77
Tower, homemade tilt-over	
WA3EWH	p. 28, May 71
Tower, wind-protected crank-up (HN)	p. 74, Oct 69
Towers and rotators	
K6KA	p. 34, May 76
Wind loading on towers and antenna structures, how to calculate	
K4KJ	p. 16, Aug 74
Added note	p. 56, Jul 75

## transmission lines

Antenna-transmission line analog, part 1	p. 52, Apr 77
W6UYH	
Antenna-transmission line analog, part 2	p. 29, May 77
W6UYH	
Balun, coaxial	
WAØRDX	p. 26, May 77
Coax cable dehumidifier	
K4RJ	p. 26, Sep 73
Coax connectors, repairing broken (HN)	p. 66, Jun 70
WØHKF	
Coaxial cable (C&T)	
W1DTY	p. 50, Jun 76
Coaxial cable, checking (letter)	
W2OLU	p. 68, May 71
Coaxial cable connectors (HN)	
WA1ABP	p. 71, Mar 69
Coaxial-cable fittings, type-F	
K2MDO	p. 44, May 71
Coaxial cable supports (HN)	
W2GA	p. 56, Jun 68
Coaxial cable, what you know about	
W9ISB	p. 30, Sep 68
Coaxial connectors can generate rfi	
W1DTY	p. 48, Jun 76
Coaxial feedthrough panel (HN)	
W3URE	p. 70, Apr 69
Coaxial-line loss, measuring with reflectometer	
W2VCI	p. 50, May 72
Coax, Low-cost (HN)	
K6BIJ	p. 74, Oct 69
Coaxial transmission lines, underground	
WØFCH	p. 38, May 70
Impedance transformer, non-synchronous (HN)	
W5TRS	p. 66, Sep 75
Comments, W3DVO	p. 63, May 76
Open-wire feedthrough insulator (HN)	
W4RNL	p. 79, May 75
Remote switching multiband antennas	
G3LTZ	p. 68, May 77
Single feedline for multiple antennas	
K2ISP	p. 58, May 71
Solenoid rotary switches	
W2EEY	p. 36, Apr 68
Transmission line calculations, using your pocket calculator for	
W5TRS	p. 40, Nov 76
Tuner, receiver (HN)	
WA7KRE	p. 72, Mar 69
Tuner, wall-to-wall antenna (HN)	
W2OUX	p. 56, Dec 70
Uhf microstrip swr bridge	
W4CGC	p. 22, Dec 72
VSWR indicator, computing	
WB9CYY	p. 58, Jan 77
short circuit	p. 94, May 77

## audio

Audio agc principles and practice	
WA5SNZ	p. 28, Jun 71
Audio amplifier and squelch circuit	
W6AJF	p. 36, Aug 68
Audio CW filter	
W7DI	p. 54, Nov 71
Audio filter, tunable, for weak-signal communications	
K6HCP	p. 28, Nov 75
Audio filters, aligning (HN)	
W4ATE	p. 72, Aug 72
Audio filters, inexpensive	
W8YFB	p. 24, Aug 72
Audio filter mod (HN)	
K6HIL	p. 60, Jan 72
Audio mixer (HN)	
W6KNE	p. 66, Nov 76
Audio module, a complete	
K4DHC	p. 18, Jun 73
Audio-oscillator module, Cordover	
WB2GQY	p. 44, Mar 71
Correction	p. 80, Dec 71
Audio-power integrated circuits	
W3FQJ	p. 64, Jan 76
Audio transducer (HN)	
WA1OPN	p. 59, Jul 75
Binaural CW reception, synthesizer for	
W6NRW	p. 46, Nov 75
Comment	p. 77, Feb 77
Compressor, dual channel	
W2EEY	p. 40, Jul 68

Distortion and splatter	
K5LLI	p. 44, Dec 70
Dynamic microphones (C&T)	
W1DTY	p. 46, Jun 76
Filter for CW, tunable audio	
WA1JSM	p. 34, Aug 70
Filter-frequency translator for cw reception, integrated audio	
W2EEY	p. 24, Jun 70
Filter, lowpass audio, simple	
OD5CG	p. 54, Jan 74
Filter, simple audio	
W4NVK	p. 44, Oct 70
Filter, tunable peak-notch audio	
W2EEY	p. 22, Mar 70
Filter, variable bandpass audio	
W3AEX	p. 36, Apr 70
Gain control IC for audio signal processing	
Jung	p. 47, Jul 77
Hang agc circuit for ssb and CW	
W1ERJ	p. 50, Sep 72
Headphone cords (HN)	
W2OLU	p. 62, Nov 75
Headphones, lightweight	
K6KA	p. 34, Sep 68
Impedance match, microphone (HN)	
W5JJ	p. 67, Sep 73
Increased flexibility for the MFJ Enterprises CW filters	
K3NEZ	p. 58, Dec 76
Intercom, simple (HN)	
W4AYV	p. 66, Jul 72
Microphone preamplifier with agc	
Bryant	p. 28, Nov 71
Microphone, using Shure 401A with the Drake TR-4 (HN)	
G3XOM	p. 68, Sep 73
Microphones, muting (HN)	
W6IL	p. 63, Nov 75
Notch filter, tunable RC	
WA5SNZ	p. 16, Sep 75
Comment	p. 78, Apr 77
Oscillator, audio, IC	
W6GXN	p. 50, Feb 73
Oscillator-monitor, solid-state audio	
WA1JSM	p. 48, Sep 70
Phone patch	
W8GRG	p. 20, Jul 71
Pre-emphasis for ssb transmitters	
OH2CD	p. 38, Feb 72
RC active filters using op amps	
W4IYB	p. 54, Oct 76
Receivers, better audio for	
K7GCO	p. 74, Apr 77
Rf clipper for the Collins S-line	
K6JYO	p. 18, Aug 71
Rf speech processor, ssb	
W2MB	p. 18, Sep 73
Speaker-driver module, IC	
WA2GCF	p. 24, Sep 72
Speech amplifiers, curing distortion	
Allen	p. 42, Aug 70
Speech clipper, IC	
K6HTM	p. 18, Feb 73
Added notes (letter)	p. 64, Oct 73
Speech clippers, rf	
G6XN	p. 26, Nov; p. 12, Dec 72
Added notes	p. 58, Aug 73; p. 72, Sep 74
Speech clipping in single-sideband equipment	
K1YZW	p. 22, Feb 71
Speech clipping (letter)	
W3EJD	p. 72, Jul 72
Speech compressor (HN)	
Novotny	p. 70, Feb 76
Speech processing	
W1DTY	p. 60, Jun 68
Speech processing, principles of	
ZL1BN	p. 28, Feb 75
Added notes	p. 75, May 75; p. 64, Nov 75
Speech processing technique, split audio band	
W1DTY	p. 30, Jun 76
Speech processor, audio-frequency	
K3PDW	p. 48, Aug 77
Short circuit	p. 68, Dec 77
Speech processor for ssb, simple	
K6PHT	p. 22, Apr 70
Speech processor, IC	
VK9GN	p. 31, Dec 71
Speech processor, logarithmic	
WA3FIY	p. 38, Jan 70
Squelch, audio-actuated	
K4MOG	p. 52, Apr 72
Synthesizer-filter, binaural	
W6NRW	p. 52, Nov 76
Tape head cleaners (letter)	
K4MSG	p. 62, May 72
Tape head cleaning (letter)	
Buchanan	p. 67, Oct 72
Voice-operated gate for carbon microphones	
W6GXN	p. 35, Dec 77

## commercial equipment

Alliance rotator improvement (HN)	
K6JVE	p. 68, May 72
Alliance T-45 rotator Improvement (HN)	
WAØVAM	p. 64, Sep 71

CDR AR-22 rotator, fixing a sticky	
WA1ABP	p. 34, Jun 71
Clegg 27B, S-meter for (HN)	
WA2YUD	p. 61, Nov 74
Collins KWM-2/KWM-2A modifications (HN)	
W6SAI	p. 80, Aug 76
Collins KWM2 transceivers, improved reliability (HN)	
W6SAI	p. 81, Jun 77
Collins R390 rf transformers, repairing (HN)	
WA2SUT	p. 81, Aug 76
Collins receivers, 300-Hz crystal filter for	
W1DTY	p. 58, Sep 75
Collins S-line, improved frequency readout for the	
W1GFC	p. 53, Jun 76
Collins S-line power supply mod (HN)	
W6IL	p. 61, Jul 74
Collins S-line receivers, improved selectivity	
W6FR	p. 36, Jun 76
Collins S-line, reducing warm-up drift	
W6VFR	p. 46, Jun 75
Collins S-line, rf clipper for	
K6JYO	p. 18, Aug 71
Correction	p. 80, Dec 71
Collins S-line spinner knob (HN)	
W6VFR	p. 69, Apr 72
Collins S-line, syllabic vox system for	
WØIP	p. 29, Oct 77
Collins S-line transceiver mod (HN)	
W6VFR	p. 71, Nov 72
Collins 32S-series ALC meter improvement (HN)	
W6FR	p. 100, Nov 77
Collins 32S-3 audio (HN)	
K6KA	p. 64, Oct 71
Collins 32S-1 CW modification (HN)	
W1DTY	p. 82, Dec 69
Correction	p. 76, Sep 70
Collins 51J PTO restoration	
W6SAI	p. 36, Dec 69
Collins 70E12 PTO repair (HN)	
W6BIH	p. 72, Feb 77
Collins 70K-2 PTO, correcting mechanical backlash (HN)	
K9WEH	p. 58, Feb 75
Collins 75A4 avc mod (letter)	
W9KNI	p. 63, Sep 75
Collins 75A4 hints (HN)	
W6VFR	p. 68, Apr 72
Collins 75A4, increased selectivity for (HN)	
W1DTY	p. 62, Nov 75
Collins 75A-4 modifications (HN)	
W4SD	p. 67, Jan 71
Collins 75A4 noise limiter	
W1DTY	p. 43, Apr 76
Collins 75A4 PTO, making it perform like new	
W3AFM	p. 24, Dec 74
Collins 75A-4 receiver, improving overload response in	
W6ZO	p. 42, Apr 70
Short circuit	p. 76, Sep 70
Collins 75S frequency synthesizer	
W6NBI	p. 8, Dec 75
Short circuit	p. 85, Oct 76
Collins 75S-series crystal adapter (HN)	
K1KXA	p. 72, Feb 77
Collins R-388(51J), inter-band calibration stability (HN)	
W5OZF	p. 95, Sep 77
Collins R390A, improving the product detector	
W7DI	p. 12, Jul 74
Collins R390A modifications	
WA2SUT	p. 58, Nov 75
Collins R392, improved ssb reception with (HN)	
VE3LF	p. 88, Jul 77
Comdel speech processor, increasing the versatility of (HN)	
W6SAI	p. 67, Mar 71
Cornell-Dubilier rotators (HN)	
K6KA	p. 82, May 75
Drake gear, simple tune-up (HN)	
W7DIM	p. 79, Jan 77
Drake R-4 receiver frequency synthesizer for	
W6NBI	p. 6, Aug 72
Modification (letter)	p. 74, Sep 74
Drake R-4C, electronic bandpass tuning in	
Horner	p. 58, Oct 73
Drake TR-4, using the Shure 401A microphone with (HN)	
G3XOM	p. 68, Sep 73
Drake W-4 directional wattmeter	
W1DTY	p. 86, Mar 68
Elmac chirp and drift (HN)	
W5OZF	p. 68, Jun 70
EX crystal and oscillator	
WB2EGZ	p. 60, Apr 68
Galaxy feedback (HN)	
WA5TFK	p. 71, Jan 70
Genave transceivers, S-meter for (HN)	
K9OXX	p. 80, Mar 77
Hallicrafters HT-37, increased sideband suppression	
W3CM	p. 48, Nov 69
Ham-M modification (HN)	
W2TQK	p. 72, May 76
Ham-M rotator automatic position control	
WB6GNM	p. 42, May 77

Hammarlund HQ215, adding 160-meter coverage  
W2GHH p. 32, Jan 72

Heath CA1, ten-minute timer from (HN)  
K8MHZ p. 74, Jul 68

Heath HG-10B vfo, independent keying of (HN)  
K4BRR p. 67, Sep 70

Heath HM-2102 wattmeter, better balancing (HN)  
VE6RF p. 56, Jan 75

Heath HM 2102 vhf wattmeter, high power calibration for (HN)  
W9TKR p. 70, Feb 76

Heath HM-2102 wattmeter mods (letter)  
K3VNR p. 64, Sep 75

Heath HO-10 as RTTY monitor scope (HN)  
K9HVV p. 70, Sep 74

Heath HW-7 mods, keying and receiver blanking (HN)  
WA5KPG p. 60, Dec 74

Heath HW-12 on MARS (HN)  
K8AUH p. 63, Sep 71

Heath HW-16 keying (HN)  
W7DI p. 57, Dec 73

Heath HW-16, low-impedance headphones for (HN)  
WN8WJR p. 88, Jul 77

Heath HW16, vfo operations for  
WB6MZN p. 54, Mar 73  
Short circuit p. 58, Dec 73

Heath HW-17A, perking up (HN)  
p. 70, Aug 70

Heath HW-17 modifications (HN)  
WA5PWX p. 66, Mar 71

Heath HW-100, HW-101, grid-current monitor for  
K4MFR p. 46, Feb 73

Heath HW-100 incremental tuning (HN)  
K1GUU p. 67, Jun 69

Heath HW-100, the new  
W1NLB p. 64, Sep 68

Heath HW-100 tuning knob, loose (HN)  
VE3EPY p. 68, Jun 71

Heath HW-101, using with a separate receiver (HN)  
WA1MKP p. 63, Oct 73

Heath HW-202, adding private-line  
WA8AWJ p. 53, Jun 74

Heath HW-202, another look at the fm channel scanner for  
K7PYS p. 68, Mar 76

Heath HW-202 lamp replacement (HN)  
W5UNF p. 83, Sep 76

Heath IM-11 vtm, convert to IC voltmeter  
K6VCI p. 42, Dec 74

Heath intrusion alarm (HN)  
Rossman p. 81, Jun 77

Heath SB-100, using an outboard receiver with (HN)  
K4GMR p. 68, Feb 70

Heath SB-102 headphone operation (HN)  
K1KXA p. 87, Oct 77

Heath SB102 modifications (HN)  
W2CNQ p. 58, Jun 75

Heath SB-102 modifications (HN)  
W2CNQ p. 79, Mar 77

Heath SB-102, rf speech processor for  
W6IVI p. 38, Jun 75

Heath SB-102, receiver incremental tuning for (HN)  
K1KXA p. 81, Aug 76

Heath SB-102, WWV on (HN)  
K1KXA p. 78, Jan 77

Heath SB-200 amplifier, modifying for the 8873 zero-bias triode  
W6UOV p. 32, Jan 71

Heath SB-200 amplifier, six-meter conversion  
K1RAK p. 38, Nov 71

Heath SB200 CW modification  
K6YB p. 99, Nov 77

Heath SB-300, RTTY with  
W2ARZ p. 76, Jul 68

Heath SB-303, 10-MHz coverage for (HN)  
W1JE p. 61, Feb 74

Heath SB-400 and SB-401, improving alc response in (HN)  
WA9FDQ p. 71, Jan 70

Heath SB-610 as RTTY monitor scope (HN)  
K9HVV p. 70, Sep 74

Heath SB-650 using with other receivers  
K2BYM p. 40, Jun 73

Heath SB receivers, RTTY reception with (HN)  
K9HVV p. 64, Oct 71

Heath SB-series crystal control and narrow shift RTTY with (HN)  
WA4VYL p. 54, Jun 73

Heathkit SB-series equipment, heterodyne crystal switching (HN)  
K1KXA p. 78, Mar 77

Heath ten-minute timer  
K6KA p. 75, Dec 71

Heathkit Sixer, spot switch (HN)  
WA6FNR p. 84, Dec 69

Heathkit, noise limiter for (HN)  
W7CKH p. 67, Mar 71

Heathkit HW202, fm channel scanner for  
W7BZ p. 41, Feb 75

ICOM-22A wiring change (HN)  
K1KXA p. 73, Feb 77

Icom IC-230, adding splinter channels (HN)  
WA10JX p. 82, Sep 76

ICs, drilling template for (HN)  
WA4WDL, WB4LJM p. 78, Mar 77

James Research oscillator/monitor  
W1D7Y p. 91, Mar 68

James Research permflex key  
W1D7Y p. 73, Dec 68

Kenwood TS-520 CW filter modification (HN)  
W7ZZ p. 21, Nov 75

Kenwood TS-520, TVI cure for (HN)  
W3FUN p. 78, Jan 77

Knight-kit inverter/charger review  
W1D7Y p. 64, Apr 69

Knight-kit two-meter transceiver  
W1D7Y p. 62, Jun 70

Mini-mitter II  
W6SLQ p. 72, Dec 71

Mini-mitter II modifications (HN)  
K1ETU p. 64, Apr 76

Motorola channel elements  
WB4NEX p. 32, Dec 72

Motorola Dispatcher, converting to 12 volts  
WB6HXU p. 26, Jul 72

Short circuit  
p. 64, Mar 74

Motorola fm receiver mods (HN)  
VE4RE p. 60, Aug 71

Motorola P-33 series, improving  
WB2AEB p. 34, Feb 71

Motorola receivers, op-amp relay for  
W6GDO p. 16, Jul 73

Motorola voice commander, improving  
W0DKU p. 70, Oct 70

Motrac Receivers (letter)  
K5ZBA p. 69, Jul 71

Quement circular slide rule  
W2DXH p. 62, Apr 68

Regency HR transceivers, signal-peaking indicator and generator for (HN)  
W8HVG p. 68, Jun 76

Regency HR-2, narrowbanding  
WA8TMP p. 44, Dec 73

Regency HR-212, channel scanner for  
WA0SJK p. 28, Mar 75

R-392 receiver mods (HN)  
KH6FOX p. 65, Apr 76

SBE linear implifier tips (HN)  
WA6DCW p. 71, Mar 69

SB301/401, improved sidetone operation  
W1WLZ p. 73, Oct 69

Signal One review  
W1NLB p. 56, May 69

Spurious causes (HN)  
K6KA p. 66, Jan 74

Standard 826M, more power from (HN)  
WB6KVF p. 68, Apr 75

Swan television interference: an effective remedy  
W2OUX p. 46, Apr 71

Swan 120, converting to two meters  
K6RIL p. 8, May 68

Swan 250 Carrier suppression (HN)  
WB8LGA p. 79, Oct 76

Swan 350 CW monitor (HN)  
K1KXA p. 63, Jun 72

Correction (letter)  
p. 77, May 73

Swan 350, receiver incremental tuning (HN)  
K1KXA p. 64, Jul 71

Swan 350 and 400, RTTY operation (HN)  
WB2MIC p. 67, Aug 69

Swan 250, update your (HN)  
K8ZHZ p. 84, Dec 69

Telefax transceiver conversion  
K0QMR p. 16, Apr 74

Ten-Tec Argonaut, accessory package for  
W7BBX p. 26, Apr 74

Ten-Tec KR-20 keyer, stabilization of (HN)  
W3CRG p. 69, Jul 76

Ten-Tec RX10 communicators receiver  
W1NLB p. 63, Jun 71

T150A frequency stability (HN)  
WB2MCP p. 70, Apr 69

Yaesu sideband switching (HN)  
W2MUU p. 56, Dec 73

Yaesu spurious signals (HN)  
K6KA p. 69, Dec 71

Units affected (letter)  
p. 67, Oct 73

Yaesu FT101 clarifier (letter)  
K1NUN p. 55, Nov 75

## construction techniques

AC line cords (letter)  
W6EG p. 80, Dec 71

A dab of paint, a drop of wax (HN)  
VE3BUE p. 78, Aug 68

Aluminum's new face  
W4BRS p. 60, May 68

Aluminum tubing, clamping (HN)  
WA9HUV p. 78, May 75

Antenna insulators, homemade (HN)  
W7ZC p. 70, May 73

APC trimmer, adding shaft to (HN)  
W1ETT p. 68, Jul 69

Blower-to-chassis adapter (HN)  
K6JYO p. 73, Feb 71

BNC connectors, mounting (HN)  
W9KXJ p. 70, Jan 70

Capacitors, custom, how to make  
WB0ESV p. 36, Feb 77

Capacitors, oil-filled (HN)  
W2OLU p. 66, Dec 72

Center insulator, dipole  
WA1ABP p. 69, May 69

Circuit boards with terminal inserts (HN)  
W3KBM p. 61, Nov 75

Coaxial cable connectors (HN)  
WA1ABP p. 71, Mar 69

Coax connectors, repairing broken (HN)  
W0HKF p. 66, Jun 70

Coax relay coils, another use (HN)  
K0VQY p. 72, Aug 69

Coils, self-supporting  
Anderson p. 42, Jul 77

Cold galvanizing compound (HN)  
W5UNF p. 70, Sep 72

Color coding parts (HN)  
WA7BPO p. 58, Feb 72

Component marking (HN)  
W1JE p. 66, Nov 71

Deburring holes (HN)  
W2DXH p. 75, Jul 68

Drill guide (HN)  
W5BVF p. 68, Oct 71

Drilling aluminum (HN)  
W6IL p. 67, Sep 75

Enclosures, homebrew custom  
W4YUU p. 50, Jul 74

Etch tank (HN)  
W3HUC p. 79, Jan 77

Exploding diodes (HN)  
VE3FEZ p. 57, Dec 73

Ferrite beads  
W5JJ p. 48, Oct 70

Files, cleaning (HN)  
Walton p. 66, Jun 74

Ferrite beads, how to use  
K1ORV p. 34, Mar 73

Filter chokes, unmarked  
W0KMF p. 60, Nov 68

Grommet shock mount (HN)  
VE3BUE p. 77, Oct 68

Grounding (HN)  
W9KXJ p. 67, Jun 69

Heat sinks, homemade (HN)  
WA0WOZ p. 69, Sep 70

Homebrew art  
W0PEM p. 56, Jun 69

Hot etching (HN)  
K8EKG p. 66, Jan 73

Hot wire stripper (HN)  
W8DWT p. 67, Nov 71

IC holders (HN)  
W3HUC p. 80, Aug 76

IC lead former (HN)  
W5ICV p. 67, Jan 74

Indicator circuit, LED  
WB6AFT p. 60, Apr 77

Inductance, toroidal coil (HN)  
W3WLX p. 26, Sep 75

Inductors, graphical aid for winding  
W7POG p. 41, Apr 77

Industrial cartridge fuses, using (HN)  
VE3BUE p. 76, Sep 68

Magnetic fields and the 7360 (HN)  
W7DI p. 66, Sep 73

Metric conversions for screw and wire sizes  
W1D7Y p. 67, Sep 75

Miniature sockets (HN)  
Lawyer p. 84, Dec 69

Minibox, cutting down to size (HN)  
W2OUX p. 57, Mar 74

Mobile installation, putting together  
W0FCH p. 36, Aug 69

Mobile mount bracket (HN)  
W4NJF p. 70, Feb 70

Modular converter, 144-MHz  
W6UOV p. 64, Oct 70

Neutralizing tip (HN)  
ZE6JP p. 69, Dec 72

Noisy fans (HN)  
W8IUF p. 70, Nov 72

Correction (letter)  
p. 67, Oct 73

Nuvistor heat sinks (HN)  
WA0KKC p. 57, Dec 73

Parasitic suppressor (HN)  
WA9JMY p. 80, Apr 70

Printed-circuit boards, cleaning (HN)  
W5BVF p. 66, Mar 71

Printed-circuit boards, how to clean  
K2PMA p. 56, Sep 76

Printed-circuit boards, how to make  
K4EEU p. 58, Apr 73

Printed-circuit boards, low-cost  
W6CMQ p. 44, Aug 71

Printed-circuit boards, low-cost  
W8YFB p. 16, Jan 75

Printed-circuit boards, practical photofabrication of  
Hutchinson p. 6, Sep 71

Printed-circuit labels (HN)  
WA4WDK p. 76, Oct 70

Printed-circuit standards (HN)  
W6JVE p. 58, Apr 74

Printed-circuit tool (HN)	
W2GZ	p. 74, May 73
Printed circuits without printing	
W4ZG	p. 62, Nov 70
Professional look, for that	
VE3GFN	p. 74, Mar 68
Punching aluminum panels (HN)	
W7D1M	p. 57, Jun 68
Rack and panel construction	
W7OE	p. 48, Jun 68
Rack construction, a new approach	
K1EUJ	p. 36, Mar 70
Rectifier terminal strip (HN)	
W5PKK	p. 80, Apr 70
Restoring panel lettering (HN)	
W8CL	p. 69, Jan 73
Screwdriver, adjustment (HN)	
WAØKGS	p. 66, Jan 71
Silver plating (letters)	
WAØAGD	p. 94, Nov 77
Silver plating for the amateur	
W4KAE	p. 62, Dec 68
Silver plating made easy	
WA9HUV	p. 42, Feb 77
Small parts tray (HN)	
W2GA	p. 58, Jun 68
Solder dispenser, simple (HN)	
W2KID	p. 76, Sep 68
Soldering aluminum (HN)	
ZE6JP	p. 67, May 72
Soldering fluxes (HN)	
K3HNP	p. 57, Jun 68
Soldering tip (HN)	
Lawyer	p. 68, Feb 70
Soldering tip cleaner (HN)	
W3HUC	p. 79, Oct 76
Soldering tips	
WA4MTH	p. 15, May 75
Thumbwheel switch modification (HN)	
VE3DGX	p. 56, Mar 74
Tilt your rig (HN)	
WA4NED	p. 58, Jun 68
Toroids, plug-in (HN)	
K8EEG	p. 60, Jan 72
Transfer letters (HN)	
WA2TGL	p. 78, Oct 76
Transformers, repairing	
W6NIF	p. 66, Mar 69
Trimmers (HN)	
W5LHG	p. 76, Nov 69
Uhf coax connectors (HN)	
WØLCP	p. 70, Sep 72
Uhf hardware (HN)	
W6CMQ	p. 76, Oct 70
Underwriter's knot (HN)	
W1DTY	p. 69, May 69
Vectorbord tool (HN)	
WA1KWJ	p. 70, Apr 72
Volume controls, noisy, temporary fix (HN)	
W9JUV	p. 62, Aug 74
Watercooling the 2C39	
K6MYC	p. 30, Jun 69
Wiring and grounding	
W1EZT	p. 44, Jun 69
Workbench, electronic	
W1EZT	p. 50, Oct 70

## features and fiction

Alarm, burglar-proof (HN)	
Eisenbrandt	p. 56, Dec 75
Binding 1970 issues of <b>ham radio</b> (HN)	
W1DHZ	p. 72, Feb 71
Brass pounding on wheels	
K6QD	p. 58, Mar 75
Dynistor, the	
W6GXN	p. 49, Apr 68
Catalina wireless, 1902	
W6BLZ	p. 32, Apr 70
Early wireless stations	
W6BLZ	p. 64, Oct 68
Electronic bugging	
K2ZSQ	p. 70, Jun 68
Fire protection in the ham shack	
Darr	p. 54, Jan 71
First wireless in Alaska	
W6BLZ	p. 48, Apr 73
Ham Radio sweepstakes winners, 1972	
W1NLB	p. 58, Jul 72
Ham Radio sweepstakes winners, 1973	
W1NLB	p. 68, Jul 73
Ham Radio sweepstakes winners, 1975	
W1NLB	p. 54, Jul 75
How to be DX	
W4NXD	p. 58, Aug 68
Nostalgia with a vengeance	
W6HDM	p. 28, Apr 72
Photographic illustrations	
WA4GNW	p. 72, Dec 69
QSL return, statistics on	
WB6IUH	p. 50, Dec 68
Reminisces of old-time radio	
K4NW	p. 40, Apr 71
Secret society, the	
W4NXD	p. 82, May 68
Ten commandments for technicians	
	p. 58, Oct 76

Use your old magazines	
Foster	p. 52, Jan 70
What is it?	
WA1ABP	p. 84, May 68
Wireless Point Loma	
W6BLZ	p. 54, Apr 69
1929-1941, the Golden years of amateur radio	
W6SAI	p. 34, Apr 76
1979 world administrative radio conference	
W6APW	p. 48, Feb 76

## fm and repeaters

Amateur vhf fm operation	
W6AYZ	p. 36, Jun 68
Antenna and control-link calculations for repeater licensing	
W7PUG	p. 58, Nov 73
Short circuit	p. 59, Dec 73
Antennas, simple, for two-meter fm	
WA3NFW	p. 30, May 73
Antenna, two-meter fm (HN)	
WB6KYE	p. 64, May 71
Antenna, 1/2-wavelength, two-meter	
K6KLO	p. 40, Jul 74
Antenna, 1/2 wavelength two-meter, build from CB mobile whips (HN)	
WB4WSU	p. 67, Jun 74
Audio-amplifier and squelch unit	
W6AJF	p. 36, Aug 68
Automatically controlled access to open repeaters	
W8GRG	p. 22, Mar 74
Autopatch system for vhf fm repeaters	
W8GRG	p. 32, Jul 74
Base station, two-meter fm	
W9JTQ	p. 22, Aug 73
Carrier-operated relay	
KØPHF, WAØUZO	p. 58, Nov 72
Carrier-operated relay and call monitor	
VE4RE	p. 22, Jun 71
Cavity filter, 144-MHz	
W1SNN	p. 22, Dec 73
Channel scanner	
W2FFP	p. 29, Aug 71
Channels, three from two (HN)	
VE7ABK	p. 68, Jun 71
Charger, fet-controlled for nicad batteries	
WAØJYK	p. 46, Aug 75
Collinear antenna for two meters, nine-element	
W6RJO	p. 12, May 72
Collinear array for two meters, 4-element	
WB6KGF	p. 6, May 71
Continuous tuning for fm converters (HN)	
W1DHZ	p. 54, Dec 70
Control head, customizing	
VE7ABK	p. 28, Apr 71
Converting low-band mobile antenna to 144 MHz (HN)	
K7ARR	p. 90, May 77
Decoder, control function	
WA9FTH	p. 66, Mar 77
Detectors, fm, survey of	
W6GXN	p. 22, Jun 76
Deviation measurement (letter)	
K5ZBA	p. 68, May 71
Deviation measurements	
W3FQJ	p. 52, Feb 72
Deviation meter (HN)	
VE7ABK	p. 58, Dec 70
Digital touch-tone encoder for vhf fm	
W7FBB	p. 28, Apr 75
Discriminator, quartz crystal	
WAØJYK	p. 67, Oct 75
Distortion in fm systems	
W5JJ	p. 26, Aug 69
Encoder, combined digital and burst	
K8AUH	p. 48, Aug 69
European vhf-fm repeaters	
SM4GL	p. 80, Sep 76
Filter, 455-kHz for fm	
WAØJYK	p. 22, Mar 72
Fm demodulator, TTL	
W3FQJ	p. 66, Nov 72
Fm receiver frequency control (letter)	
W3AFN	p. 65, Apr 71
Fm techniques and practices for vhf amateurs	
W6SAI	p. 8, Sep 69
Short circuit	p. 79, Jun 70
Fm transmitter, solid-state two-meter	
W6AJF	p. 14, Jul 71
Fm transmitter, Sonobaby, 2 meter	
WAØUZO	p. 8, Oct 71
Short Circuit	p. 96, Dec 71
Crystal deck for Sonobaby	p. 26, Oct 72
Frequency meter, two-meter fm	
W4JAZ	p. 40, Jan 71
Short circuit	p. 72, Apr 71
Frequency synthesizer, inexpensive all-channel, for two-meter fm	
WØOA	p. 50, Aug 73
Correction (letter)	p. 65, Jun 74
Frequency-synthesizer, one-crystal for two-meter fm	
WØMV	p. 30, Sep 73
Frequency synthesizer, for two-meter fm	
WB4FPK	p. 34, Jul 73

Frequency synthesizer sidebands, filter reduces (HN)	
K1PCT	p. 80, Jun 77
Heath HD-1928 Micoder for low-impedance operation (HN)	
Johnson	p. 95, Dec 77
IC-230 modification (HN)	
W8PEY	p. 80, Mar 77
Identifier, programmable repeater	
W6AYZ	p. 18, Apr 69
Short circuit	p. 76, Jul 69
I-f system, multimode	
WA2IKL	p. 39, Sep 71
Indicator, sensitive rf	
WB9DNI	p. 38, Apr 73
Interface problems, fm equipment (HN)	
W9DPY	p. 58, Jun 75
Interference, scanning receiver (HN)	
K2YAH	p. 70, Sep 72
Logic oscillator for multi-channel crystal control	
W1SNN	p. 46, Jun 73
Magnet mount antenna, portable (HN)	
WB2YYU	p. 67, May 76
Mobile antenna, magnet-mount	
W1HCI	p. 54, Sep 75
Mobile antennas, vhf, comparison of	
W4MNV	p. 52, May 77
Mobile operation with the Touch-Tone pad	
WØLPQ	p. 58, Aug 72
Correction	p. 90, Dec 72
Modification (letter)	p. 72, Apr 73
Mobile rig, protecting from theft (C&T)	
W1DTY	p. 42, Apr 76
Modulation standards for vhf fm	
W6TEE	p. 16, Jun 70
Monitor receivers, two-meter fm	
WB5EMI	p. 34, Apr 74
Motorola channel elements	
WB4NEX	p. 32, Dec 72
Motorola fm receiver mods (HN)	
VE4RE	p. 60, Aug 71
Motorola P-33 series, improving the	
WB2AEB	p. 34, Feb 71
Motorola voice commander, improving	
WØDKU	p. 70, Oct 70
Motrac Receivers (letter)	
K5ZBA	p. 69, Jul 71
Multimode transceivers, fm-ing on uhf (HN)	
W6SAI	p. 98, Nov 77
Narrow-band fm system, using ICs in	
W6AJF	p. 30, Oct 68
Phase-locked loop, tunable, 28 and 50 MHz	
W1KNI	p. 40, Jan 73
Phase modulation principles and techniques	
VE2BEN	p. 28, Jul 75
Correction	p. 59, Dec 75
Power amplifier, rf 220-MHz fm	
K7JUE	p. 6, Sep 73
Power amplifier, rf, 144 MHz	
Hatchett	p. 6, Dec 73
Power amplifier, rf, 144-MHz fm	
W4CGC	p. 6, Apr 73
Power amplifier, two-meter fm, 10-watt	
W1DTY	p. 67, Jan 74
Power supply, regulated ac for mobile fm equipment	
WA8TMP	p. 28, Jun 73
Preamplifier, two-meter	
WA2GCF	p. 25, Mar 72
Preamplifier, two meter	
W8BBB	p. 36, Jun 74
Private call system for vhf fm	
W66TTY	p. 62, Sep 77
Private-line, adding to Heath HW-202	
WA8AWJ	p. 53, Jun 74
Push-to-talk for Styleline telephones	
W1DRP	p. 18, Dec 71
Receiver alignment techniques, vhf fm	
K4IPV	p. 14, Aug 75
Receiver for six and two meters, multichannel fm	
W1SNN	p. 54, Feb 74
Receiver for two meter, fm	
W9SEK	p. 22, Sep 70
Short circuit	p. 72, Apr 71
Receiver isolation, fm repeater (HN)	
W1DTY	p. 54, Dec 70
Receiver, modular fm communications	
K8AUH	p. 32, Jun 69
Correction	p. 71, Jan 70
Receiver, modular, for two-meter fm	
WA2GBF	p. 42, Feb 72
Added notes	p. 73, Jul 72
Receiver performance, comparison of	
VE7ABK	p. 68, Aug 72
Receiver performance of vacuum-tube vhf-fm equipment, how to improve	
W6GGV	p. 52, Oct 76
Receiver, tunable vhf fm	
K8AUH	p. 34, Nov 71
Receiver, vhf fm	
WA2GCF	p. 6, Nov 72
Receiver, vhf fm	
WA2GCF	p. 8, Nov 75
Receiver, vhf fm (letter)	
K8IHQ	p. 76, May 73

**Relay, operational-amplifier, for Motorola receivers** W6GDO p. 16, Jul 73

**Remote base, an alternative to repeaters** WA6LBV, WA6FVC p. 32, Apr 77

**Repeater control with simple timers** W2FPP p. 46, Sep 72  
Correction p. 91, Dec 72

**Repeater decoder, multi-function** WA6TBC p. 24, Jan 73

**Repeater installation** W2FPP p. 24, Jun 73

**Repeater kerchunk eliminator** WB6GTM p. 70, Oct 77

**Repeater linking, carrier-operated relay for** KØPHF p. 57, Jul 76

**Repeater problems** VE7ABK p. 38, Mar 71

**Repeater, receiving system degradation** K5ZBA p. 36, May 69

**Repeater transmitter, improving** W6GDO p. 24, Oct 69

**Repeater shack temperature, remote checking** ZL2AMJ p. 84, Sep 77

**Repeaters, single-frequency fm** W2FPP p. 40, Nov 73

**Reset timer, automatic** W5ZHV p. 54, Oct 74

**Satellite receivers for repeaters** WA4YAK p. 64, Oct 75

**Scanner, two-channel, for repeater monitoring** W8GRG p. 48, Oct 76

**Scanner, vhf receiver** K2LZG p. 22, Feb 73

**Scanning receiver, improved for vhf fm** WA2GCF p. 26, Nov 74

**Scanning receiver modifications, vhf fm** WA5WOU p. 60, Feb 74

**Scanning receivers for two-meter fm** K4IPV p. 28, Aug 74

**Sequential encoder, mobile fm** W3JJU p. 34, Sep 71

**Sequential switching for Touch-Tone repeater control** W8GRG p. 22, Jun 71

**Single-frequency conversion, vhf/uhf** W3FQJ p. 62, Apr 75

**Single-sideband fm, introduction to** W3EJD p. 10, Jan 77

**S-meter, audible, for repeaters** ZL2AMJ p. 49, Mar 77

**S-meter for Clegg 27B (HN)** WA2YUD p. 61, Nov 74

**Squelch-audio amplifier for fm receivers** WB4WSU p. 68, Sep 74

**Squelch circuit, another (HN)** WB4WSU p. 78, Oct 76

**Squelch circuits for transistor radios** WB4WSU p. 36, Dec 75

**Synthesized channel scanning** WAØUZO p. 68, Mar 77

**Synthesized two-meter fm transceiver** W1CMR, K1IJZ p. 10, Jan 76  
Letter, W5GQV p. 78, Sep 76

**Telephone controller, automatic for your repeater** KØPHF, WAØUZO p. 44, Nov 74

**Telephone controller for remote repeater operation** KØPHF, WAØUZO p. 50, Jan 76  
Precautions (letters) p. 79, Apr 77

**Test set for Motorola radios** KØBKD p. 12, Nov 73  
Short circuit p. 58, Dec 73  
Added note (letter) p. 64, Jun 74

**Time-out warning indicator for fm repeater users** K3NEZ p. 62, Jun 76

**Timer, simple (HN)** W3CIX p. 58, Mar 73

**Tone-burst generator (HN)** K4COF p. 58, Mar 73

**Tone-burst generator for repeater accessing** WA5KPG p. 68, Sep 77

**Tone-burst keyer for fm repeaters** W8GRG p. 36, Jan 72

**Tone encoder and secondary frequency oscillator (HN)** K8AUH p. 66, Jun 69

**Tone encoder, universal for vhf fm** W6FUB p. 17, Jul 75  
Correction p. 58, Dec 75

**Tone generator, IC** Ahrens p. 70, Feb 77

**Touch-tone circuit, mobile** K7QWR p. 50, Mar 73

**Touch-tone decoder, multi-function** KØPHF, WAØUZO p. 14, Oct 73

**Touch-tone decoder, three-digit** W6AYZ p. 37, Dec 74  
Circuit board for p. 62, Sep 75

**Touch-Tone encoder** W3HB p. 41, Aug 77

**Touch-tone, hand-held** K7YAM p. 44, Sep 75

**Touch-tone handset, converting slim-line** K2YAH p. 23, Jun 75

**Transceiver for two-meter fm, compact** W6AOI p. 36, Jan 74

**Transmitter for two meters, phase-modulated** W6AJF p. 18, Feb 70

**Transmitter, two-meter fm** W9SEK p. 6, Apr 72

**Tunable receiver modification for vhf fm** WB6VKY p. 40, Oct 74

**Two-meter synthesizer, direct output** WB2CPA p. 10, Aug 77

**Short circuit** p. 68, Dec 77

**Up/down repeater-mode circuit for two-meter synthesizers, 600 kHz** WB4PHO p. 40, Jan 77

**Short circuit** p. 94, May 77

**Vertical antennas, truth about ¼-wavelength** KØDDK p. 48, May 74

**Added note (letter)** p. 54, Jan 75

**Weather monitor receiver, retune to two-meter fm (HN)** W3WTO p. 56, Jan 75

**Whip, 5/8-wave, 144 MHz (HN)** VE3DDD p. 70, Apr 73

**144-MHz digital synthesizers, readout display** WB4TZE p. 47, Jul 76

**144-MHz fm exciter, high performance** WA2GCF p. 10, Aug 76

**144-MHz mobile antenna (HN)** W2EUQ p. 80, Mar 77

**144-MHz vertical mobile antennas, ¼ and ½ wavelength, test data on** W2LTI, W2CQH p. 46, May 76

**144-MHz, ¾-wavelength vertical antenna** W1RHN p. 50, Mar 76

**144-MHz, ¾-wavelength, vertical antenna for mobile** K4LPQ p. 42, May 76

**220 MHz frequency synthesizer** W6GXN p. 8, Dec 74

**450-MHz preamplifier and converter** WA2GCF p. 40, Jul 75

## integrated circuits

**Amateur uses of the MC1530 IC** W2EY p. 42, May 68

**Amplifiers, broadband IC** W6GXN p. 36, Jun 73

**Applications, potpourri of IC** W1DTY, Thorpe p. 8, May 69

**Audio-power ICs** W3FQJ p. 64, Jan 76

**Balanced modulator, an integrated-circuit** K7QWR p. 6, Sep 70

**Cmos logic circuits** W3FQJ p. 50, Jun 75

**Counter gating sources** K6KA p. 48, Nov 70

**Counter reset generator (HN)** W3KBM p. 68, Jan 73

**C³L logic circuit** W1DTY p. 4, Mar 75

**Digital counters (letter)** W1GGN p. 76, May 73

**Digital ICs, part I** W3FQJ p. 41, Mar 72

**Digital ICs, part II** W3FQJ p. 58, Apr 72  
Correction p. 66, Nov 72

**Digital mixers** WB8IFM p. 42, Dec 73

**Digital multivibrators** W3FQJ p. 42, Jun 72

**Digital oscillators and dividers** W3FQJ p. 62, Aug 72

**Digital readout station accessory, part I** K6KA p. 6, Feb 72

**Digital station accessory, part II** K6KA p. 50, Mar 72

**Digital station accessory, part III** K6KA p. 36, Apr 72

**Divide-by-n counters, high-speed** W1OOP p. 36, Mar 76

**Electronic counter dials, IC** K6KA p. 44, Sep 70

**Electronic keyer, cosmos IC** WB2DFA p. 6, Jun 74  
Short circuit p. 62, Dec 74

**Emitter-coupled logic** W3FQJ p. 62, Sep 72

**Flip-flops** W3FQJ p. 60, Jul 72

**Flop-flip, using (HN)** W3KBM p. 60, Feb 72

**Function generator, IC** W1DTY p. 40, Aug 71

**Function generator, IC** K4DHC p. 22, Jun 74

**Gain control IC for audio signal processing** Jung p. 47, Jul 77

**IC power (HN)** W3KBM p. 68, Apr 72

**IC-regulated power supply for ICs** W6GXN p. 28, Mar 68

**IC tester, TTL** WA4LCO p. 66, Aug 76

**Integrated circuits, part I** W3FQJ p. 40, Jun 71

**Integrated circuits, part II** W3FQJ p. 58, Jul 71

**Integrated circuits, part III** W3FQJ p. 50, Aug 71

**I²L logic circuits** W1DTY p. 4, Nov 75

**Logic families, IC** W6GXN p. 26, Jan 74

**Logic monitor (HN)** WA5SAF p. 70, Apr 72  
Correction p. 91, Dec 72

**Logic test probe** VE6RF p. 53, Dec 73

**Logic test probe (HN)** Rossman p. 56, Feb 73

**Short circuit** p. 58, Dec 73

**Low-cost linear ICs** WA7KRE p. 20, Oct 69

**Missent ID** K6KA p. 25, Apr 76

**Modular modules** W9SEK p. 63, Aug 70

**Motorola MC1530 IC, amateur uses for** W2EY p. 42, May 68

**Multi-function integrated circuits** W3FQJ p. 46, Oct 72

**National LM373, using in ssb transceiver** W5BAA p. 32, Nov 73

**Op amp (741) circuit design** WA5SNZ p. 26, Apr 76

**Operational amplifiers** WB2EGZ p. 6, Nov 69

**Phase-locked loops, IC** W3FQJ p. 54, Sep 71

**Phase-locked loops, IC, experiments with** W3FQJ p. 58, Oct 71

**Plessey SL600-series ICs, how to use** G8FNT p. 26, Feb 73

**Removing ICs (HN)** W6NIF p. 71, Aug 70

**Seven-segment readouts, multiplexed** W5NPD p. 37, Jul 75

**Ssb detector, IC (HN)** K4ODS p. 67, Dec 72  
Correction (letter) p. 72, Apr 73

**Ssb equipment, using TTL ICs in** G4ADJ p. 18, Nov 75

**Surplus ICs (HN)** W4AYV p. 68, Jul 70

**Sync generator, IC, for ATV** WØKGI p. 34, Jul 75

**Transceiver, 9-MHz ssb, IC** G3ZVC p. 34, Aug 74  
Circuit change (letter) p. 62, Sep 75

**TTL sub-series ICs, how to select** WA1SNG p. 26, Dec 77

**U/ART, how it works** Titus p. 58, Feb 76

**Using ICs in a nbfm system** W6AJF p. 30, Oct 68

**Using ICs with single-polarity power supplies** W2EY p. 35, Sep 69

**Using integrated circuits (HN)** W9KXJ p. 69, May 69

**Voltage regulators** W6GXN p. 31, Mar 77

**Voltage regulators, IC** W7FLC p. 22, Oct 70

**Voltage-regulator ICs, adjustable** WB9KEY p. 36, Aug 75

**Voltage-regulator ICs, three-terminal** WB5EMI p. 26, Dec 73  
Added note (letter) p. 73, Sep 74

**Vtvm, convert to an IC voltmeter** K6VCI p. 42, Dec 74

## keying and control

**Accu-Mill, keyboard interface for the Accu-Keyer** WN9OVY p. 26, Sep 76

**ASCII-to-Morse code translator** Morley, Scharon p. 41, Dec 76

**Automatic beeper for station control** WA6URN p. 38, Sep 76

**Break-in circuit, CW** W8SYK p. 40, Jan 72

**Break-in control system, IC (HN)** W9ZTK p. 68, Sep 70

**Bug, solid-state** K2FV p. 50, Jun 73

**Carrier-operated relay** KØPHF, WAØUZO p. 58, Nov 72

**Cmos keying circuits (HN)** WB2DFA p. 57, Jan 75

**Contest keyer (HN)** K2UBC p. 79, Apr 70

**Contest keyer, programmable** W7BBX p. 10, Apr 76

**CW reception, enhancing through a simulated-stereo technique** WA1MKP p. 61, Oct 74

**CW regenerator for interference-free communications** Leward, WB2EAX p. 54, Apr 74

CW sidetone (C&T)	
W1D7Y	p. 51, Jun 76
Differential keying circuit	
W4IYB	p. 60, Aug 76
Electronic hand keyer	
K5TCK	p. 36, Jun 71
Electronic keyer, cosmos IC	
WB2DFA	p. 6, Jun 74
Short circuit	p. 62, Dec 74
Electronic keyer, IC	
VE7BFK	p. 32, Nov 69
Electronic keyer notes (HN)	
ZL1BN	p. 74, Dec 71
Electronic keyer package, compact	
W4ATE	p. 50, Nov 73
Electronic keyer with random-access memory	
WB9FHC	p. 6, Oct 73
Corrections (letter)	p. 58, Dec 74
	p. 57, Jun 75
Improvements (letter)	p. 76, Feb 77
Increased flexibility (HN)	p. 62, Mar 75
Electronic keyer, 8043 IC	
W6GXN	p. 8, Apr 75
Electronic keyers, simple IC	
WA5TRS	p. 38, Mar 73
Grid-block keying, simple (HN)	
WA4DHU	p. 78, Apr 70
Improving transmitter keying	
K6KA	p. 44, Jun 76
Key and vox clicks (HN)	
K6KA	p. 74, Aug 72
Keyboard electronic keyer, the code mill	
W6CAB	p. 38, Nov 74
Keying, paddle, Siamese	
WA5KPG	p. 45, Jan 75
Keyer modification (HN)	
W9KNI	p. 80, Aug 76
Comments	p. 94, Nov 77
Keyer mods, micro-TO	
DJ9RP	p. 68, Jul 76
Keyer paddle, portable	
WA5KPG	p. 52, Feb 77
Keying the Heath HG-10B vfo (HN)	
K4BRR	p. 67, Sep 70
Latch circuit, dc	
W0LPQ	p. 42, Aug 75
Correction	p. 58, Dec 75
Memo-key	
WA7SCB	p. 58, Jun 72
Memory accessory, programmable for electronic keyers	
WA9LUD	p. 24, Aug 75
Mini-paddle	
K6RIL	p. 46, Feb 69
Morse generator, keyboard	
W7CUU	p. 36, Apr 75
Morse sounder, radio controlled (HN)	
K6QEQ	p. 66, Oct 71
Oscillators, electronic keyer	
WA6JNJ	p. 44, Jun 70
Paddle, electronic keyer (HN)	
KL7EVD	p. 68, Sep 72
Paddle, homebrew keyer	
W3NK	p. 43, May 69
Push-to-talk for Styleline telephones	
W1DRP	p. 18, Dec 71
RAM keyer update	
K3NEZ	p. 60, Jan 76
Relay activator (HN)	
K6KA	p. 62, Sep 71
Relays, surplus (HN)	
W2OLU	p. 70, Jul 70
Relay, transistor replaces (HN)	
W3NK	p. 72, Jan 70
Relays, undervoltage (HN)	
W2OLU	p. 64, Mar 71
Remote keying your transmitter (HN)	
WA3HOU	p. 74, Oct 69
Reset timer, automatic	
W5ZHV	p. 54, Oct 74
Sequential switching (HN)	
W5OSF	p. 63, Oct 72
Solenoid rotary switches	
W2EEY	p. 36, Apr 68
Station control center	
W7OE	p. 26, Apr 68
Step-start circuit, high-voltage (HN)	
W6VFR	p. 64, Sep 71
Suppression networks, arc (HN)	
WA5EKA	p. 70, Jul 73
Time base, calibrated electronic keyer	
W1PLJ	p. 39, Aug 75
Timer, ten-minute (HN)	
DJ9RP	p. 66, Nov 76
Transistor switching for electronic keyers (HN)	
W3QBO	p. 66, Jun 74
Transmit/receive switch PIN diode	
W9KHC	p. 10, May 76
Transmitter switching, solid-state	
W2EEY	p. 44, Jun 68
Typewriter-type electronic keys, further automation for	
W6PRO	p. 26, Mar 70
Vox and mox systems for ssb	
Belt	p. 24, Oct 68
Vox, IC	
W2EEY	p. 50, Mar 69

Vox keying (HN)	
VE7IG	p. 83, Dec 69
Vox, versatile	
W9KIT	p. 50, Jul 71
Short circuit	p. 96, Dec 71

## measurements and test equipment

Absorption measurements, using your signal generator for	
W2OUX	p. 79, Oct 76
Ac current monitor (letter)	
WB5MAP	p. 61, Mar 75
Ac power-line monitor	
W2OLU	p. 46, Aug 71
AFSK generator, crystal-controlled	
K7BVT	p. 13, Jul 72
AFSK generator, phase-locked loop	
K7ZOF	p. 27, Mar 73
Amateur frequency measurements	
K6KA	p. 53, Oct 68
A-m modulation monitor, vhf (HN)	
K7UNL	p. 67, Jul 71
Antenna gain, measuring	
K6JYO	p. 26, Jul 69
Antenna matcher	
W4SD	p. 24, Jun 71
Antenna and transmission line measurement techniques	
W4OQ	p. 36, May 74
Base step generator	
WB4YDZ	p. 44, Jul 76
Beta master, the	
K8ERV	p. 18, Aug 68
Bridge for antenna measurements, simple	
W2CTK	p. 34, Sep 70
Bridge, noise, for impedance measurements	
YA1GJM	p. 62, Jan 73
Added notes	p. 66, May 74; p. 60, Mar 75
Bridge, rf noise	
WB2EGZ	p. 18, Dec 70
Calibrating ac scales on the vtvm, icvm and fet voltmeter	
W7KQ	p. 48, Sep 76
Calibrators and counters	
K6KA	p. 41, Nov 68
Calibrator, plug-in IC	
K6KA	p. 22, Mar 69
Capacitance meter, digital	
K4DHC	p. 20, Feb 74
Capacitance meter, direct-reading	
ZL2AUE	p. 46, Apr 70
Capacitance meter, direct-reading	
W6MUR	p. 48, Aug 72
Short circuit	p. 64, Mar 74
Capacitance meter, direct-reading	
WA5SNZ	p. 32, Apr 75
Added note	p. 31, Oct 75
Capacitance meter, direct reading, for electrolytics	
W9DJZ	p. 14, Oct 71
Coaxial cable, checking (letter)	
W2OLU	p. 68, May 71
Coaxial-line loss, measuring with a reflectometer	
W2VCI	p. 50, May 72
Continuity bleeper for circuit tracing	
G3SBA	p. 67, Jul 77
Converter, mosfet, for receiver instrumentation	
WA9ZMT	p. 62, Jan 71
Counter, compact frequency	
K4EEU	p. 16, Jul 70
Short circuit	p. 72, Dec 70
Counter, digital frequency	
K4EEU	p. 8, Dec 68
Counter gating sources	
K6KA	p. 48, Nov 70
Counter readouts, switching (HN)	
K6KA	p. 66, Jun 71
Counter reset generator (HN)	
W3KBM	p. 68, Jan 73
Counters: a solution to the readout problem	
WA0GOZ	p. 66, Jan 70
CRT intensifier for RTTY	
K4VFA	p. 18, Jul 71
Crystal checker	
W6GXN	p. 46, Feb 72
Crystal test oscillator and signal generator	
K4EEU	p. 46, Mar 73
Crystal-controlled frequency markers (HN)	
WA4WDK	p. 64, Sep 71
Cubical quad measurements	
W4YM	p. 42, Jan 69
Curve master, the	
K8ERV	p. 40, Mar 68
Decade standards, economical (HN)	
W4ATE	p. 66, Jun 71
Digital counters (letter)	
W1GGN	p. 76, May 73
Digital readout station accessory, part I	
K6KA	p. 6, Feb 72

Digital station accessory, part II	
K6KA	p. 50, Mar 72
Digital station accessory, part III	
K6KA	p. 36, Apr 72
Diode tester	
W6DOB	p. 46, Jan 77
Dipper without plug-in coils	
W6BLZ	p. 64, May 68
Dummy load and rf wattmeter, low-power	
W2OLU	p. 56, Apr 70
Dummy load low-power vhf	
WB9DNI	p. 40, Sep 73
Dummy loads	
W4MB	p. 40, Mar 76
Dummy loads, experimental	
W8YFB	p. 36, Sep 68
Dynamic transistor tester (HN)	
VE7ABK	p. 65, Oct 71
Electrolytic capacitors, measurement of (HN)	
W2NA	p. 70, Feb 71
Fm deviation measurement (letter)	
K5ZBA	p. 68, May 71
Fm deviation measurements	
W3FQJ	p. 52, Feb 72
Fm frequency meter, two-meter	
W4JAZ	p. 40, Jan 71
Short circuit	p. 72, Apr 71
Frequencies, counted (HN)	
K6KA	p. 62, Aug 74
Frequency calibrator, general coverage	
W5UQS	p. 28, Dec 71
Frequency calibrator, how to design	
W3AEX	p. 54, Jul 71
Frequency counter, CMOS	
W2OKO	p. 22, Feb 77
Short circuit	p. 94, May 77
Frequency counter, how to improve the accuracy of	
W1RF	p. 26, Oct 77
Frequency counter, 50 MHz, 6 digit	
WB2DFA	p. 18, Jan 76
Comment	p. 79, Apr 77
Frequency-marker standard using cmos	
W4IYB	p. 44, Aug 77
Frequency measurement of received signals	
W4AAD	p. 38, Oct 73
Frequency measurement, vhf, with hf receiver and scaler (HN)	
W3LB	p. 90, May 77
Frequency meter, crystal controlled (HN)	
W5JSN	p. 71, Sep 69
Frequency scaler, divide-by-ten	
K4EEU	p. 26, Aug 70
Short circuit	p. 72, Apr 71
Frequency scaler, divide-by-ten	
W6PBC	p. 41, Sep 72
Correction	p. 90, Dec 72
Added comments (letter)	p. 64, Nov 73
Pre-scaler, improvements for	
W6PBC	p. 30, Oct 73
Frequency scaler, uhf (11C90)	
WB9KEY	p. 50, Dec 75
Frequency scaler, 500-MHz	
W6URH	p. 32, Jun 75
Frequency scalars, 1200-MHz	
WB9KEY	p. 38, Feb 75
Frequency-shift meter, RTTY	
VK3ZNV	p. 33, Jun 70
Frequency standard (HN)	
WA7JIK	p. 69, Sep 72
Frequency standard, universal	
K4EEU	p. 40, Feb 74
Short circuit	p. 72, May 74
Frequency synthesizer, high-frequency	
K2BLA	p. 16, Oct 72
Function generator, IC	
W1D7Y	p. 40, Aug 71
Function generator, IC	
K4DHC	p. 22, Jun 74
Function/units indicator using LED displays	
K0FOP	p. 58, Mar 77
Gate-dip meter	
W3WLX	p. 42, Jun 77
Gdo, new use for	
K2ZSQ	p. 48, Dec 68
Grid current measurement in grounded-grid amplifiers	
W6SAI	p. 64, Aug 68
Grid-dip oscillator, solid-state conversion of	
W6AJZ	p. 20, Jun 70
Harmonic generator (HN)	
W5GDQ	p. 76, Oct 70
I-f alignment generator 455-kHz	
WA5SNZ	p. 50, Feb 74
I-f sweep generator	
K4DHC	p. 10, Sep 73
Impedance bridge (HN)	
W6KZK	p. 67, Feb 70
Impedance bridge, low-cost RX	
W8YFB	p. 6, May 73
Impedance bridge, simple	
WA9QJP	p. 40, Apr 68
Impedance, measuring with swr bridge	
WB4KSS	p. 46, May 75
Impulse generator, pulse-snap diode	
Siegal, Turner	p. 29, Oct 72
Instrumentation and the ham	
VE3GFN	p. 28, Jul 68

Intermodulation-distortion measurements on ssb transmitters  
W6VFR p. 34, Sep 74

L, C, R bridge, universal  
W6AOI p. 54, Apr 76

Linearity meter for ssb amplifiers  
W4MB p. 40, Jun 76

Line-voltage monitor (HN)  
WA8VFK p. 66, Jan 74

Current monitor mod (letter)  
Logic monitor (HN) p. 61, Mar 75

WA5SAF p. 70, Apr 72

Correction p. 91, Dec 72

Logic test probe  
VE6RF p. 53, Dec 73

Logic test probe (HN)  
Rossman p. 56, Feb 73

Short circuit p. 58, Dec 73

Make-shift test equipment (HN)  
W7FS p. 77, Sep 68

Meter amplifier, electronic  
WA9HUV p. 38, Dec 76

Meter interface, high-impedance  
Laughlin p. 20, Jan 74

Meters, testing unknown (HN)  
W10NC p. 66, Jan 71

Microwave marker generator, 3cm band (HN)  
WA4WDL p. 69, Jun 76

Milliammeters, how to use  
W4PSJ p. 48, Sep 75

Mini-spotter frequency checker  
W7OE p. 48, May 68

Monitorscope, miniature  
WA3FIY p. 34, Mar 69

Monitorscope, RTTY  
W3CIX p. 36, Aug 72

Multi-box (HN)  
W3KBM p. 68, Jul 69

Multitester (HN)  
W1DTY p. 63, May 71

Noise bridge, antenna (HN)  
K8EEG p. 71, May 74

Noise-figure measurements for vhf  
WB6NMT p. 36, Jun 72

Noise figure, vhf, estimating  
WA9HUV p. 42, Jun 75

Noise generator, 1296-MHz  
W3BSV p. 46, Aug 73

Noise generators, using (HN)  
K2ZSQ p. 79, Aug 68

Oscillator, audio  
W6GKN p. 50, Feb 73

Oscillator, frequency measuring  
W6IEL p. 16, Apr 72

Added notes p. 90, Dec 72

Oscillator, two-tone, for ssb testing  
W6GKN p. 11, Apr 72

Oscilloscope calibrator (HN)  
K4EEU p. 69, Jul 69

Oscilloscope, putting it to work  
Allen p. 64, Sep 69

Oscilloscope, troubleshooting amateur gear with  
Allen p. 52, Aug 69

Oscilloscope voltage calibrator  
W6PBC p. 54, Aug 72

Panoramic reception, simple  
W2EEY p. 14, Oct 68

Peak envelope power, how to measure  
W5JJ p. 32, Nov 74

Phase meter, rf  
VE2AYU, Korth p. 28, Apr 73

Power meter, rf  
K8EEG p. 26, Oct 73

Power meter, rf, how to use (repair bench)  
W6NBI p. 44, Apr 77

Precision capacitor  
W4BRS p. 61, Mar 68

Pre-scaler, vhf (HN)  
W6MGI p. 57, Feb 73

Prescaler, vhf, for digital frequency counters  
K4GOK p. 32, Feb 76

Probe, sensitive rf (HN)  
W5JJ p. 61, Dec 74

Q measurement  
G3SBA p. 49, Jan 77

Radio Shack meters, internal resistance  
Katzenberger p. 94, Nov 77

Receiver alignment  
Allen p. 64, Jun 68

Reflectometers  
K1YZW p. 65, Dec 69

Regenerative detectors and a wideband amplifier  
W8YFB p. 61, Mar 70

Repairs, thinking your way through  
Allen p. 58, Feb 71

Resistance standard, simple (HN)  
W2OLU p. 65, Mar 71

Resistance values, measuring below 1 ohm  
W4OHT p. 66, Sep 77

Resistor decades, versatile  
W4ATE p. 66, Jul 71

Rf current probe (HN)  
W6HPH p. 76, Oct 68

Rf detector, sensitive  
WB9DNI p. 38, Apr 73

Rf generator clip  
W1DTY p. 58, Mar 68

Rf power meter, low-level  
W5WGF p. 58, Oct 72

Rf signal generator, solid-state  
VE5FP p. 42, Jul 70

Rf wattmeter, accurate low power  
WA4ZRP p. 38, Dec 77

RTTY monitor scope, solid-state  
WB2MPZ p. 33, Oct 71

RTTY signal generator  
W72TC p. 23, Mar 71

Short circuit p. 96, Dec 71

RTTY test generator (HN)  
W3EAG p. 67, Jan 73

RTTY test generator (HN)  
W3EAG p. 59, Mar 73

RX impedance bridge  
W2CTK p. 34, Sep 70

RX impedance bridge, low-cost  
W8YFB p. 6, May 73

RX noise bridge, improvements to  
W6BXI, W6NKK p. 10, Feb 77

Comments p. 100, Sep 77

Safer suicide cord (HN)  
K6JYO p. 64, Mar 71

Sampling network, rf — the milli-tap  
W6QJW p. 34, Jan 73

Signal generator, tone modulated for two and six meters  
WA8OIK p. 54, Nov 69

Signal generator, wide range  
W6GKN p. 18, Dec 73

Signal injection in ham receivers  
Allen p. 72, May 68

Signal tracing in ham receivers  
Allen p. 52, Apr 68

Slotted line, how to use (repair bench)  
W6NBI p. 58, May 77

Slow-scan tv test generator  
K4EEU p. 6, Jul 73

S-meter readings (HN)  
W1DTY p. 56, Jun 68

Spectrum analyzer, dc-100 MHz  
W6URH p. 16, Jun 77

Short circuit p. 69, Dec 77

Spectrum analyzer for ssb  
W3JW p. 24, Jul 77

Spectrum analyzer, four channel  
W9IA p. 6, Oct 72

Spectrum analyzers, understanding  
WA5SNZ p. 50, Jun 74

Ssb, signals, monitoring  
W6VFR p. 35, Mar 72

Sweep generator, how to use  
Allen p. 60, Apr 70

Sweep response curves for low-frequency i-f's  
Allen p. 56, Mar 71

Switch-off flasher (HN)  
Thomas p. 64, Jul 71

Swr bridge  
WB2ZSH p. 55, Oct 71

Swr bridge and power meter, integrated  
W6DOB p. 40, May 70

Swr bridge (HN)  
WA5TFK p. 66, May 72

Swr bridge readings (HN)  
W6FFO p. 63, Aug 73

Swr indicator, aural, for the visually handicapped  
K6HTM p. 52, May 76

Swr indicator, how to use (repair bench)  
W6NBI p. 66, Jan 77

Swr meter  
W6VSV p. 6, Oct 70

Swr meter, improving (HN)  
W5NPD p. 68, May 76

Swr meters, direct reading and expanded scale  
WA4WDK p. 28, May 72

Correction p. 90, Dec 72

Test probe accessory (HN)  
W2IMB p. 89, Jul 77

Time-base oscillators, improved calibration  
WA7LUJ, WA7KMR p. 70, Mar 77

Time-domain reflectometry, experimenter's approach to  
WAØPIA p. 22, May 71

Toroid permeability meter  
W6RJO p. 46, Jun 77

Transconductance tester for fets  
W6NBI p. 44, Sep 71

Transformer shorts  
W6BLZ p. 36, Jul 68

Transistor and diode tester  
ZL2AMJ p. 65, Nov 70

Transistor curve tracer  
WA9LCX p. 52, Jul 73

Short circuit p. 63, Apr 74

Transistor tester  
WA6NIL p. 48, Jul 68

Transistor tester for leakage and gain  
W4BRS p. 68, May 68

Transistor tester, shirt pocket  
WØMAY p. 40, Jul 76

Transmitter tuning unit for the blind  
W9NTP p. 60, Jun 71

Trapezoidal monitor scope  
VE3CUS p. 22, Dec 69

Troubleshooting around fets  
Allen p. 42, Oct 68

Troubleshooting by resistance measurement  
Allen p. 62, Nov 68

Troubleshooting transistor ham gear  
Allen p. 64, Jul 68

Turn-off timer for portable equipment  
W5OXD p. 42, Sep 76

Uhf tuner tester for tv sets (HN)  
Schuler p. 73, Sep 69

Vacuum tubes, testing high-power (HN)  
W2OLU p. 64, Mar 72

Vhf pre-scaler, improvements for  
W6PBC p. 30, Oct 73

Voltmeter, improved transistor, part I  
Maddever p. 74, Apr 68

Voltmeter, transistor, part II  
Maddever p. 60, Jul 68

Vom/vtvm, added uses for (HN)  
W7DI p. 67, Jan 73

VSWR indicator, computing  
WB9CYY p. 58, Jan 77

Short circuit p. 94, May 77

Vtvm modification  
W6HPH p. 51, Feb 69

Vtvm, convert to an IC voltmeter  
K6VCI p. 42, Dec 74

Wavemeter, indicating  
W6NIF p. 26, Dec 70

Short circuit p. 72, Apr 71

Weak-signal source, stable, variable-output  
K6JYO p. 36, Sep 71

Weak-signal source, 144 and 432 MHz  
K6JC p. 58, Mar 70

Weak-signal source, 432 and 1296 MHz  
K6RIL p. 20, Sep 68

WWV receiver, simple regenerative  
WA5SNZ p. 42, Apr 73

WWV-WWVH, amateur applications for  
W3FQJ p. 53, Jan 72

WWVB signal processor  
W9BTI p. 28, Mar 76

Zener tester, low-voltage (HN)  
K3DPJ p. 72, Nov 69

## microprocessors, calculators computers and

Accumulator I/O versus memory I/O  
WB4HYJ, Rony, Titus p. 64, Jun 76

Data converters  
WA1MOP p. 79, Oct 77

Decision, how does a microcomputer make a  
WB4HYJ, Titus, Rony p. 74, Aug 76

Device-select pulses, generating input/output  
WB4HYJ, Titus, Rony p. 44, Apr 76

How microprocessors fit into scheme of computers and controllers  
WB4HYJ, Rony, Titus p. 36, Jan 76

Input/output device, what is a?  
WB4HYJ, Rony, Titus p. 50, Feb 76

Interfacing a digital multimeter with an 8080-based microcomputer  
WB4HYJ, Rony, Titus p. 66, Sep 76

Internal registers, 8080  
Rony, Titus, WB4HYJ p. 63, Feb 77

Interrupts, microcomputer  
WB4HYJ, Rony, Titus p. 66, Dec 76

Introduction to microprocessors  
WB4HYJ, Rony, Titus p. 32, Dec 75

Comments, WB4FAR p. 63, May 76

Logical instructions  
Titus, WB4HYJ, Rony p. 83, Jul 77

MOV and MVI 8080 instructions  
Titus, WB4HYJ, Rony p. 74, Mar 77

Register pair instruction  
Rony, Titus, WB4HYJ p. 76, Jun 77

Software UAR/T, interfacing a  
WB4HYJ, Rony, Titus p. 60, Nov 76

Substitution of software for hardware  
WB4HYJ, Rony, Titus p. 62, Jul 76

UAR/T, how it works  
Titus p. 58, Feb 76

Vectored interrupts  
WB4HYJ, Rony, Titus p. 74, Jan 77

8080 logical instructions  
WB4HYJ, Rony, Titus p. 89, Sep 77

8080 microcomputer output instructions  
WB4HYJ, Rony, Titus p. 54, Mar 76

## miscellaneous technical

Admittance, impedance and circuit analysis  
Anderson p. 76, Aug 77

Alarm, wet basement (HN)  
W2EMF p. 68, Apr 72

Amateur anemometer  
W6GKN p. 52, Jun 68

Short circuit p. 34, Aug 68

Antenna masts, design for pipe  
W3MR p. 52, Sep 74

Added design notes (letter)  
p. 75, May 75

Antennas and capture area  
K6MIO p. 42, Nov 69

<b>Bandpass filter design</b> K4KJ	p. 36, Dec 73	<b>Frequency synthesizers, how to design</b> DJ2LR	p. 10, Jul 76	<b>Neutralizing small-signal amplifiers</b> WA4WDK	p. 40, Sep 70
<b>Bandpass filters for 50 and 144 MHz, etched</b> W5KHT	p. 6, Feb 71	<b>Short circuit</b>	p. 85, Oct 76	<b>Noise figure, meaning of</b> K6MIO	p. 26, Mar 69
<b>Bandpass filters, single-pole</b> W6HPH	p. 51, Sep 69	<b>Gamma-matching networks, how to design</b> W7ITB	p. 46, May 73	<b>Operational amplifiers</b> WB2EGZ	p. 6, Nov 69
<b>Bandpass filters, top-coupled</b> Anderson	p. 34, Jun 77	<b>Glass semiconductors</b> W1E2T	p. 54, Jul 69	<b>Phase detector, harmonic</b> W5TRS	p. 40, Aug 74
<b>Bandsreading techniques for resonant circuits</b> Anderson	p. 46, Feb 77	<b>Graphical network solutions</b> W1NCK, W2CTK	p. 26, Dec 69	<b>Phase-locked loops, IC</b> W3FQJ	p. 54, Sep 71
<b>Short circuits</b>	p. 69, Dec 77	<b>Gridded tubes, vhf-uhf effects</b> W6UOV	p. 8, Jan 69	<b>Phase-locked loops, IC, experiments with</b> W3FQJ	p. 58, Oct 71
<b>Basic electronic units</b> W2DXH	p. 18, Oct 68	<b>Grounding and wiring</b> W1E2T	p. 44, Jun 69	<b>Phase-shift networks, design criteria for</b> G3NRW	p. 34, Jun 70
<b>Batteries, selecting for portable equipment</b> WB7AIK	p. 40, Aug 73	<b>Ground plow</b> W1E2T	p. 64, May 70	<b>Pi and pi-L networks</b> W6SAI	p. 36, Nov 68
<b>Bipolar-fet amplifiers</b> W6HDM	p. 16, Feb 76	<b>Harmonic generator, crystal-controlled</b> W1KNI	p. 66, Nov 77	<b>Pi network design</b> W6FFC	p. 6, Sep 72
<b>Comments, Worcester</b>	p. 76, Sep 76	<b>Harmonic output, how to predict</b> Utne	p. 34, Nov 74	<b>Pi network design and analysis</b> W2HB	p. 30, Sep 77
<b>Broadband amplifier, bipolar</b> WB4KSS	p. 58, Apr 75	<b>Heatsink problems, how to solve</b> W4SSNZ	p. 46, Jan 74	<b>Short circuit</b>	p. 68, Dec 77
<b>Broadband amplifier uses mospower fet</b> Oxner	p. 32, Dec 76	<b>Hybrids and couplers, hf</b> W2CTK	p. 57, Jul 70	<b>Pi network inductors (letter)</b> W7IV	p. 78, Dec 72
<b>Broadband amplifier, wide-range</b> W6GXN	p. 40, Apr 74	<b>Short circuit</b>	p. 72, Dec 70	<b>Pi networks, series-tuned</b> W2EGH	p. 42, Oct 71
<b>Bypassing, rf, at uhf</b> WB6BHI	p. 50, Jan 72	<b>Hydroelectric station, amateur</b> K6WX	p. 50, Sep 77	<b>Power amplifiers, high-efficiency rf</b> WB8LQK	p. 8, Oct 74
<b>Calculator-aided circuit analysis</b> Anderson	p. 38, Oct 77	<b>Impedance-matching systems, designing</b> W7CSD	p. 58, Jul 73	<b>Power dividers and hybrids</b> W1DAX	p. 30, Aug 72
<b>Calculator, hand-held electronic, its function and use</b> W4MB	p. 18, Aug 76	<b>Inductors, how to use ferrite and powdered-iron for</b> W6GXN	p. 15, Apr 71	<b>Power supplies, survey of solid-state</b> W6GXN	p. 25, Feb 70
<b>Calculator, hand-held electronic, solving problems with it</b> W4MB	p. 34, Sep 76	<b>Correction</b>	p. 63, May 72	<b>Power, voltage and impedance nomograph</b> W2TQK	p. 32, Apr 71
<b>Capacitors, oil-filled (HN)</b> W2OLU	p. 66, Dec 72	<b>Infrared communications (letter)</b> K2OAW	p. 65, Jan 72	<b>Printed-circuit boards, photofabrication of</b> Hutchinson	p. 6, Sep 71
<b>Clock, 24-hour digital</b> K4ALS	p. 51, Apr 70	<b>Injection lasers (letter)</b> Mims	p. 64, Apr 71	<b>Programmable calculator simplifies antenna design (HN)</b> W3DVO	p. 70, May 74
<b>Short circuit</b>	p. 76, Sep 70	<b>Injection lasers, high power</b> Mims	p. 28, Sep 71	<b>Programmable calculators, using</b> W3DVO	p. 40, Mar 75
<b>Coil-winding data, vhf and uhf</b> K3SVC	p. 6, Apr 71	<b>Integrated circuits, part I</b> W3FQJ	p. 40, Jun 71	<b>Proportional temperature control for crystal ovens</b> VE5FP	p. 44, Jan 70
<b>Communications receivers, designing for strong-signal performance</b> Moore	p. 6, Feb 73	<b>Integrated circuits, part II</b> W3FQJ	p. 58, Jul 71	<b>Pulse-duration modulation</b> W3FQJ	p. 65, Nov 72
<b>Computer-aided circuit analysis</b> K1ORV	p. 30, Aug 70	<b>Integrated circuits, part III</b> W3FQJ	p. 50, Aug 71	<b>Q factor, understanding</b> W5JJ	p. 16, Dec 74
<b>Contact bounce eliminators (letters)</b> W7IV	p. 94, Nov 77	<b>Interference, hi-fi (HN)</b> K6KA	p. 63, Mar 75	<b>QRP operation</b> W7OE	p. 36, Dec 68
<b>Converting vacuum tube equipment to solid-state</b> W2EEY	p. 30, Aug 68	<b>Interference, rf</b> W1DTY	p. 12, Dec 70	<b>Radiation hazard, rf</b> W1DTY	p. 4, Sep 75
<b>Converting wavelength to inches (HN)</b> W4SXC	p. 56, Jun 68	<b>Interference, rf (letter)</b> G3LLL	p. 65, Nov 75	<b>Correction</b>	p. 59, Dec 75
<b>Current flow?, which way does</b> W2DXH	p. 34, Jul 68	<b>Interference, rf</b> W43NFW	p. 30, Mar 73	<b>Radio communications links</b> W1E2T	p. 44, Oct 69
<b>Digital clock, low-cost</b> W46DYW	p. 26, Feb 76	<b>Interference, rf, coaxial connectors can generate</b> W1DTY	p. 48, Jun 76	<b>Radio observatory, vhf</b> Ham	p. 44, Jul 74
<b>Digital mixer, introduction</b> WB8IFM	p. 42, Dec 73	<b>Interference, rf, its cause and cure</b> G3LLL	p. 26, Jun 75	<b>Radio-frequency interference</b> W43NFW	p. 30, Mar 73
<b>Digital readout system, simplified</b> W6OIS	p. 42, Mar 74	<b>Intermittent voice operation of power tubes</b> W6SAI	p. 24, Jan 71	<b>Radiotelegraph translator and transcriber</b> W7CUU, K7KFA	p. 8, Nov 71
<b>Double-balanced mixers</b> W1DTY	p. 48, Mar 68	<b>Isotropic source and practical antennas</b> K6FD	p. 32, May 70	<b>Eliminating the matrix</b> KH6AP	p. 60, May 72
<b>Double-balanced modulator, broadband</b> W46NCT	p. 8, Mar 70	<b>Laser communications</b> W4KAE	p. 28, Nov 70	<b>Ramp generators</b> W6GXN	p. 56, Dec 68
<b>Earth currents (HN)</b> W7OUI	p. 80, Apr 70	<b>LC circuit calculations</b> W2OUX	p. 68, Feb 77	<b>Rating tubes for linear amplifier service</b> W6UOV, W6SAI	p. 50, Mar 71
<b>Effective radiated power (HN)</b> VE7CB	p. 72, May 73	<b>LED experiments</b> W4KAE	p. 6, Jun 70	<b>Reactance problems, nomograph for</b> W6NIF	p. 51, Sep 70
<b>Electrical units: their derivation and history</b> WB6EYV	p. 30, Aug 76	<b>Lighthouse tubes for uhf</b> W6UOV	p. 27, Jun 69	<b>Resistor performance at high frequencies</b> K1ORV	p. 36, Oct 71
<b>Ferrite beads</b> W5JJ	p. 48, Oct 70	<b>Local-oscillator waveform effects on spurious mixer responses</b> Robinson, Smith	p. 44, Jun 74	<b>Resistors, frequency sensitive (HN)</b> W8YFB	p. 54, Dec 70
<b>Ferrite beads, how to use</b> K1ORV	p. 34, Mar 73	<b>Lowpass filters for solid-state linear amplifiers</b> W47JYK	p. 38, Mar 74	<b>Resistors, frequency sensitive (letter)</b> W5UHV	p. 68, Jul 71
<b>Fet biasing</b> W3FQJ	p. 61, Nov 72	<b>Short circuit</b>	p. 62, Dec 74	<b>RF amplifier, wideband</b> WB4KSS	p. 58, Apr 75
<b>Filter preamplifiers for 50 and 144 MHz, etched</b> W5KHT	p. 6, Feb 71	<b>L-networks, how to design</b> W7LR	p. 26, Feb 74	<b>Rf autotransformers, wideband</b> K4KJ	p. 10, Nov 76
<b>Filters, active for direct-conversion receivers</b> W7ZOI	p. 12, Apr 74	<b>Short circuit</b>	p. 62, Dec 74	<b>Rf power-detecting devices</b> K6JYO	p. 28, Jun 70
<b>Fire extinguishers (letter)</b> W5PGG	p. 68, Jul 71	<b>Lunar-path nomograph</b> W46NCT	p. 28, Oct 70	<b>Rf power transistors, how to use</b> W47KRE	p. 8, Jan 70
<b>Fire protection</b> Darr	p. 54, Jan 71	<b>Marine installations, amateur, on small boats</b> W3MR	p. 44, Aug 74	<b>Rf interference, suppression in telephones</b> K6LDZ	p. 79, Mar 77
<b>Fire protection (letter)</b> K7QCM	p. 62, Aug 71	<b>Matching techniques, broadband, for transistor rf amplifiers</b> W47WHZ	p. 30, Jan 77	<b>Safety circuit, pushbutton switch (HN)</b> K3RFF, W41FHB	p. 73, Feb 77
<b>Fm techniques</b> W6SAI	p. 8, Sep 69	<b>Microprocessors, introduction to</b> WB4HYJ, Rony, Titus	p. 32, Dec 75	<b>Safety in the ham shack</b> Darr, James	p. 44, Mar 69
<b>Short circuit</b>	p. 79, Jun 70	<b>Microwave rf generators, solid-state</b> W1HR	p. 10, Apr 77	<b>Satellite communications, first step to</b> K1MTA	p. 52, Nov 72
<b>Frequency counter as a synthesizer</b> DJ2LR	p. 44, Sep 77	<b>Microwaves, getting started in</b> Roubal	p. 53, Jun 72	<b>Added notes (letter)</b>	p. 73, Apr 73
<b>Freon danger (letter)</b> W45RTB	p. 63, May 72	<b>Microwaves, Introduction</b> W1CBY	p. 20, Jan 72	<b>Satellite signal polarization</b> KH6IJ	p. 6, Dec 72
<b>Frequency multipliers</b> W6GXN	p. 6, Aug 71	<b>Mini-mobile</b> K9UQN	p. 58, Aug 71	<b>Signal detection and communication in the presence of white noise</b> WB6IOM	p. 16, Feb 69
<b>Frequency multipliers, transistor</b> W6AJF	p. 49, Jun 70	<b>Mismatched transmitter loads, affect of</b> W5JJ	p. 60, Sep 69	<b>Silver/silicone grease (HN)</b> W6DDB	p. 63, May 71
<b>Frequency synchronization for scatter-mode propagation</b> K2OVS	p. 26, Sep 71	<b>Mnemonics</b> W6NIF	p. 69, Dec 69	<b>Simple formula for microstrip impedance (HN)</b> W1HR	p. 72, Dec 77
<b>Frequency synthesis</b> W45SKM	p. 42, Dec 69	<b>More electronic units</b> W1E2T	p. 56, Nov 68	<b>Single-tuned interstage networks, designing</b> K6ZGQ	p. 59, Oct 68
<b>Frequency synthesizer, high-frequency</b> K2BLA	p. 16, Oct 72	<b>Multi-function integrated circuits</b> W3FQJ	p. 46, Oct 72	<b>Smith chart, how to use</b> W1DTY	p. 16, Nov 70
<b>Frequency synthesizer sidebands, filter reduces (HN)</b> K1PCT	p. 80, Jun 77	<b>Network, the ladder</b> W2CHO	p. 48, Dec 76	<b>Correction</b>	p. 76, Dec 71
		<b>Networks, transmitter matching</b> W6FFC	p. 6, Jan 73	<b>Solar activity, aspects of</b> K3CHP	p. 21, Jun 68
				<b>Solar energy</b> W3FQJ	p. 54, Jul 74

Speech clippers, rf, performance of	p. 26, Nov 72
Square roots, finding (HN)	
K9DHD	p. 67, Sep 73
Increased accuracy (letter)	p. 55, Mar 74
Staircase generator (C&T)	
W1DITY	p. 52, Jun 76
Standing-wave ratios, importance of	
W2HB	p. 26, Jul 73
Correction (letter)	p. 67, May 74
Stress analysis of antenna systems	
W2FZJ	p. 23, Oct 71
Synthesizer design (letters)	
WB2CPA	p. 94, Nov 77
Temperature sensor, remote (HN)	
WA1NJG	p. 72, Feb 77
Tetrodes, external-anode	
W6SAI	p. 23, Jun 69
Thermoelectric power supplies	
K1AJE	p. 48, Sep 68
Thermometer, electronic	
VK3ZNV	p. 30, Apr 70
Three-phase motors (HN)	
W6HPH	p. 79, Aug 68
Thyristors, introduction to	
WA7KRE	p. 54, Oct 70
Toroidal coil inductance (HN)	
W3WLX	p. 26, Sep 75
Toroid coils, 88-mH (HN)	
WA1NJG	p. 70, Jun 76
Toroids, calculating inductance of	
WB9FHC	p. 50, Feb 72
Toroids, plug-in (HN)	
K8EEG	p. 60, Jan 72
Transistor amplifiers, tabulated characteristics of	
W5JJ	p. 30, Mar 71
Trig functions on a pocket calculator (HN)	
W9ZTK	p. 60, Nov 75
Tube shields (HN)	
W9KNI	p. 69, Jul 76
Tuning, Current-controlled	
K2ZSQ	p. 38, Jan 69
TV sweep tubes in linear service, full-blast operation of	
W6SAI, W6OUV	p. 9, Apr 68
Vacuum-tube amplifiers, tabulated characteristics of	
W5JJ	p. 30, Mar 71
Warning lights, increasing reliability of	
W3NKK	p. 40, Feb 70
White noise diodes, selecting (HN)	
W6DOB	p. 65, Apr 76
Wind direction indicator, digital	
W6GXN	p. 14, Sep 68
Wind generators	
W3FQJ	p. 24, Jul 76
Wind loading on towers and antenna structures, how to calculate	
K4KJ	p. 16, Aug 74
Added note	p. 56, Jul 75
Y parameters, using in rf amplifier design	
WAØTCU	p. 46, Jul 72
24-hour clock, digital	
WB6AFT	p. 44, Mar 77

## novice reading

Ac power line monitor	
W2OLU	p. 46, Aug 71
Amplifiers, tube and transistor, tabulated characteristics of	
W5JJ	p. 30, Mar 71
Antenna, bobtail curtain for 40 meters	
VE1TG	p. 58, Jul 69
Antenna, bow tie for 80 meters	
W9VMQ	p. 56, May 75
Antenna, converted vee for 80 and 40	
W6JKR	p. 18, Dec 69
Antenna couplers, simple	
W2EEY	p. 32, Jan 70
Antenna ground system installation	
W1E2T	p. 64, May 70
Antenna, long wire, multiband	
W3FQJ	p. 28, Nov 69
Antenna, multiband phased vertical	
WA7GXO	p. 33, May 72
Antenna systems for 40 and 80 meters	
K6KA	p. 55, Feb 70
Antenna, top-loaded 80-meter vertical	
VE1TG	p. 48, Jun 69
Antenna tuning units	
W3FQJ	p. 58, Dec 72, p. 58, Jan 73
Antenna, unidirectional for 40 meters	
GW3NJY	p. 61, Jan 70
Antenna, 80-meter vertical	
VE1TG	p. 26, May 70
Antenna, 80 meters, for small lot	
W6AGX	p. 28, May 73
Antennas, dipole	
KH6HDM	p. 60, Nov 75
Antennas, for apartment dwellers	
W2EEY	p. 80, Mar 68
Antennas, low elevation	
W3FQJ	p. 66, May 73
Antennas, QRM reducing receiving types	
W3FQJ	p. 54, May 71

Antennas, simple dual-band	
W6SAI	p. 18, Mar 70
Antennas, simple for 80 and 40 meters	
W5RUB	p. 16, Dec 72
Antennas, simple multiband	
W9EGQ	p. 54, Jul 68
Audio agc principles and practice	
W4SSNZ	p. 28, Jun 71
Audio filter, tunable	
WA1JSM	p. 34, Aug 70
Audio filters, inexpensive	
W8YFB	p. 24, Aug 72
Audio module, solid-state receiver	
K4DHC	p. 18, Jun 73
Batteries, selecting for portable equipment	
WBØAIK	p. 40, Aug 73
Battery power	
W3FQJ	p. 56, Aug 74, p. 57, Oct 74
Coaxial cable, what you should know about it	
W9ISB	p. 30, Sep 68
Current flow	
W1E2T	p. 34, Jul 68
COSMOS integrated circuits	
W3FQJ	p. 50, Jun 75
CW audio filter, simple	
W7DI	p. 54, Nov 71
CW audio filter, simplest	
W4VNNK	p. 44, Oct 70
CW monitor, simple	
WA9OHR	p. 65, Jan 71
CW reception, improved through simulated stereo	
WA1MKP	p. 53, Oct 74
CW transceiver, low-power for 40 meters	
W7BBX	p. 16, Jul 74
Detectors, CW and ssb	
Belt	p. 3, Nov 68
Detectors, regenerative	
W8YFB	p. 61, Mar 70
Diode detectors	
W6GXN	p. 28, Jan 76
Dipoles, multiband for portable use	
W6SAI	p. 12, May 70
Dummy load and rf wattmeter	
W2OLU	p. 56, Apr 70
Electronic units, basic	
W1E2T	p. 18, Oct 68, p. 56, Nov 68
Feedpoint impedance characteristics of practical antennas	
W5JJ	p. 50, Dec 73
Filter, tunable for audio selectivity	
W2EEY	p. 22, Mar 70
Filters, single sideband	
Belt	p. 40, Aug 68
Fire protection in the ham shack	
Darr	p. 54, Jan 71
Frequency spotter, crystal controlled	
W5JJ	p. 36, Nov 70
ICs, basics of	
W3FQJ	p. 40, Jun 71, p. 58, Jul 71
ICs, digital, basics	
W3FQJ	p. 41, Mar 72, p. 58, Apr 72
ICs, digital flip-flops	
W3FQJ	p. 60, Jul 72
ICs, digital multivibrators	
W3FQJ	p. 42, Jun 72
ICs, digital, oscillators and dividers	
W3FQJ	p. 62, Aug 72
Interference, hi-fi	
G3LLL	p. 26, Jun 75
Interference, radio frequency	
WA3NFW	p. 30, Mar 73
Man-made interference, how to find	
W1DITY	p. 12, Dec 70
Meters, how to use	
W4PSJ	p. 48, Sep 75
Morse code, speed standards for	
VE2ZK	p. 58, Apr 73
Mosfet circuits	
W3FQJ	p. 50, Feb 75
Power amplifiers, linear, basics of	
Belt	p. 16, Apr 68
Preamplifier, 21 MHz	
WA5SNZ	p. 20, Apr 72
Printed-circuit boards, how to make your own	
K4EEU	p. 58, Apr 73
Printed-circuit boards, low cost	
W8YFB	p. 16, Jan 75
Q factor, understanding	
W5JJ	p. 16, Dec 74
Radio communications links, basics of	
W1E2T	p. 44, Oct 69
Receiver frequency calibrator	
W5UQS	p. 28, Dec 71
Receiver, novice, for 40 and 80	
Thorpe	p. 66, Aug 68
Receiver, regenerative for WWV	
WA5SNZ	p. 42, Apr 73
Receivers, direct-conversion	
W3FQJ	p. 59, Nov 71
Rectifiers, improved half-wave	
Bailey	p. 34, Oct 73
Safety in the ham shack	
Darr	p. 44, Mar 69
Semiconductors, charge flow in	
WB6BIH	p. 50, Apr 71
Semiconductor diodes, evaluating	
W5JJ	p. 52, Dec 71
Single sideband, beginners guide to	
Belt	p. 66, Mar 68

S-meters, circuits for	
K6SDX	p. 20, Mar 75
Speaker intelligibility, improving	
WA5RAQ	p. 53, Aug 70
Ssb signals, how they are generated	
Belt	p. 24, May 68
Swr bridge	
WB2ZSH	p. 55, Oct 71
Towers and rotators	
K6KA	p. 34, May 76
Transistor power dissipation, how to determine	
WN9CGW	p. 56, Jun 71
Transistor tester, simple	
WA6NIL	p. 48, Jul 68
Transmitter keying, improving	
K6KA	p. 44, Jun 76
Transmitter, low-power, 80-meter	
W3FQJ	p. 50, Aug 75
Transmitter, multiband low power with vfo	
K8EEG	p. 39, Jul 72
Transmitter power levels	
WA5SNZ	p. 62, Apr 71
Transmitter, transistor for 40 meter	
W6BLZ	p. 44, Jul 68
Transmitters, low-power 7-MHz	
W7OE	p. 3, Dec 68
Troubleshooting, basic	
James	p. 54, Jan 76
Troubleshooting by voltage measurements	
James	p. 64, Feb 76
Troubleshooting, resistance measurements	
James	p. 58, Apr 76
Troubleshooting, thinking your way through	
Allen	p. 58, Feb 71
Tuneup, off-the-air	
W4MB	p. 40, Mar 76
Underground coaxial transmission line, how to install	
WØFCH	p. 38, May 70
Vertical antennas, improving efficiency	
K6FD	p. 54, Dec 74
Vfo for 40 and 80 meters	
W3QBO	p. 36, Aug 70
Vfo, stable solid-state	
K4BGF	p. 8, Dec 71
Wiring and grounding	
W1E2T	p. 44, Jun 69
Workbench, electronics	
W1E2T	p. 50, Oct 70

## operating

Beam antenna headings	
W6FFC	p. 64, Apr 71
Code practice stations (letter)	
WB4LXJ	p. 75, Dec 72
Code practice — the rf way	
WA4NED	p. 65, Aug 68
Code practice (HN)	
W2OUX	p. 74, May 73
Computers and ham radio	
W5TOM	p. 60, Mar 69
CW monitor	
W2EEY	p. 46, Aug 69
CW monitor and code-practice oscillator	
K6RIL	p. 46, Apr 68
CW monitor, simple	
WA9OHR	p. 65, Jan 71
CW transceiver operation with transmit-receive offset	
W1DAX	p. 56, Sep 70
DXCC check list, simple	
W2CNQ	p. 55, Jun 73
Fluorescent light, portable (HN)	
K8BYO	p. 62, Oct 73
Great-circle charts (HN)	
K6KA	p. 62, Oct 73
How to be DX	
W4NXD	p. 58, Aug 68
Identification timer (HN)	
K9UQN	p. 60, Nov 74
Magazines, use your old	
Foster	p. 52, Jan 70
Morse code, speed standards for	
VE2ZK	p. 68, Apr 73
Added note (letter)	p. 68, Jan 74
Protective material, plastic (HN)	
W6BKX	p. 58, Dec 70
QSL return, statistics on	
WB6IUH	p. 60, Dec 68
Replays, instant (HN)	
W6DNS	p. 67, Feb 70
Sideband location (HN)	
K6KA	p. 62, Aug 73
Spurious signals (HN)	
K6KA	p. 61, Nov 74
Tuning with ssb gear	
WØKO	p. 40, Oct 70
Zulu time (HN)	
K6KA	p. 58, Mar 73

## oscillators

AFSK oscillator, solid-state	
WA4FGY	p. 28, Oct 68

Audio oscillator, NE566 IC  
W1EZT p. 36, Jan 75

Blocking oscillators  
W6GXN p. 45, Apr 69

Clock oscillator, TTL (HN)  
W9ZTK p. 56, Dec 73

Crystal oscillator, frequency adjustment of  
W9ZTK p. 42, Aug 72

Crystal oscillator, high stability  
W6TNS p. 36, Oct 74

Crystal oscillator, miniature  
W6DOR p. 68, Dec 68

Crystal oscillators  
W6GXN p. 33, Jul 69

Crystal oscillator, simple (HN)  
W2OUX p. 98, Nov 77

Crystal oscillators, stable  
DJ2LR p. 34, Jun 75  
Correction p. 67, Sep 75

Crystal oscillators, survey of  
VK2ZTB p. 10, Mar 76

Crystal oven, simple (HN)  
Mathieson p. 66, Apr 76

Crystal switching (HN)  
K6LZM p. 70, Mar 69

Crystal test oscillator and signal generator  
K4EEU p. 46, Mar 73

Crystals, overtone (HN)  
G8ABR p. 72, Aug 72

Drift-correction circuit for free running oscillators  
PAQKSB p. 45, Dec 77

Goral oscillator notes (HN)  
K5QIN p. 66, Apr 76

Hex inverter vxo circuit  
W2LTJ p. 50, Apr 75

Local oscillator, phase locked  
VE5FP p. 6, Mar 71

Monitoring oscillator  
W2JIO p. 36, Dec 72

Multiple band master-frequency oscillator  
K6SDX p. 50, Nov 75

Multivibrator, crystal-controlled  
WN2MQY p. 65, Jul 71

Oscillator, audio, IC  
W6GXN p. 50, Feb 73

Oscillator, electronic keyer  
WA6JNJ p. 44, Jun 70

Oscillator, Franklin (HN)  
W5JJ p. 61, Jan 72

Oscillator, frequency measuring  
W6IEL p. 16, Apr 72  
Added notes p. 90, Dec 72

Oscillator, gated (HN)  
WB9KEY p. 59, Jul 75

Oscillator-monitor, audio  
WA1JSM p. 48, Sep 70

Oscillator, phase-locked  
VE5FP p. 6, Mar 71

Oscillator, two-tone, for ssb testing  
W6GXN p. 11, Apr 72

Oscillators (HN)  
W1DTY p. 68, Nov 69

Oscillators, cure for cranky (HN)  
W8YFB p. 55, Dec 70

Oscillators, repairing  
Allen p. 69, Mar 70

Oscillators, resistance-capacitance  
W6GXN p. 18, Jul 72

Oscillators, ssb  
Belt p. 26, Jun 68

Overtone oscillator (HN)  
W5UQS p. 77, Oct 68

Quadrature-phased local oscillator (letter)  
K6ZX p. 62, Sep 75

Quartz crystals (letter)  
WB2EGZ p. 74, Dec 72

Stable vfo (C&T)  
W1DTY p. 51, Jun 76

TTL crystal oscillators (HN)  
WQJVA p. 60, Aug 75

Vco, crystal-controlled  
WB6IOM p. 58, Oct 69

Versatile audio oscillator (HN)  
W7BBX p. 72, Jan 76

Vfo buffer amplifier (HN)  
W3QBO p. 66, Jul 71

Vfo design, stable  
W1CER p. 10, Jun 76

Vfo, digital readout  
WB8IFM p. 14, Jan 73

Vfo for solid-state transmitters  
W3QBO p. 36, Aug 70

Vfo, high stability  
W8YFB p. 14, Mar 69

Vfo, high-stability, vhf  
OH2CD p. 27, Jan 72

Vfo, multiband fet  
K8EEG p. 39, Jul 72

Vfo, stable  
K4BGF p. 8, Dec 71

Vfo, stable transistor  
W1DTY p. 14, Jun 68  
Short circuit p. 34, Aug 68

Vfo transistors (HN)  
W1OOP p. 74, Nov 69

Vxo design, practical  
K6BIJ p. 22, Aug 70

455-kHz bfo, transistorized  
W6BLZ, K5GXR p. 12, Jul 68

## power supplies

Ac current monitor (letter)  
WB5MAP p. 61, Mar 75

Ac power supply, regulated, for mobile fm equipment  
WA8TMP p. 28, Jun 73

All-mode-protected power supply  
K2PMA p. 74, Oct 77

Arc suppression networks (HN)  
WA5EKA p. 70, Jul 73

Batteries, selecting for portable equipment  
WAQAIK p. 40, Aug 73

Battery drain, auxiliary, guard for (HN)  
W1DTY p. 74, Oct 74

Battery power  
W3FQJ p. 56, Aug 74

Charger, fet-controlled, for nicad batteries  
WAQJYK p. 46, Aug 75

Converter, 12 to 6 volt (C&T)  
W1DTY p. 42, Apr 76

Current limiting (HN)  
WQLPQ p. 70, Dec 72

Current limiting (letter)  
K5MKO p. 66, Oct 73

Dc-dc converter, low-power  
W5MLY p. 54, Mar 75

Dc power supply, regulated (C&T)  
W1DTY p. 51, Jun 76

Diodes for power supplies, choosing  
W6BLZ p. 38, Jul 68

Diode surge protection (HN)  
WA7LUJ p. 65, Mar 72  
Added note p. 77, Aug 72

Dry-cell life  
W1DTY p. 41, Apr 76

Dual-voltage power supply (HN)  
W1OOP p. 71, Apr 69  
Short circuit p. 80, Aug 69

Dual-voltage power supply (HN)  
W5JJ p. 68, Nov 71

Filament transformers, miniature  
Bailey p. 66, Sep 74

High-power trouble shooting  
Allen p. 52, Aug 68

IC power (HN)  
W3KBM p. 68, Apr 72

IC regulated power supply  
W2FBW p. 50, Nov 70

IC regulated power supply  
W9SEK p. 51, Dec 70

IC regulated power supply for ICs  
W6GXN p. 28, Mar 68  
Short circuit p. 80, May 68

Klystrons, reflex power for (HN)  
W6BPK p. 71, Jul 73

Line transient protection (HN)  
W1DTY p. 75, Jul 68

Line-voltage monitor (HN)  
WA8VFK p. 66, Jan 74  
Current monitor mod (letter) p. 61, Mar 75

Load protection, scr (HN)  
W5OZF p. 62, Oct 72

Low-value voltage source (HN)  
WA5EKA p. 66, Nov 71

Low-voltage supply with short-circuit protection  
WB2EGZ p. 22, Apr 68

Low-voltage supply (HN)  
WB2EGZ p. 57, Jun 68

Low voltage, variable bench power supply (weekender)  
W6NBI p. 58, Mar 76

Meter safety (HN)  
W6VFR p. 68, Jul 72

Mobile power supplies, troubleshooting  
Allen p. 56, Jun 70

Mobile power supply (HN)  
WN8DJV p. 79, Apr 70

Mobile supply, low-cost (HN)  
W4GEG p. 69, Jul 70

Motorola Dispatcher, converting to 12 volts  
WB6HXU p. 26, Jul 72

Nicad battery care (HN)  
W1DHz p. 71, Feb 76

Operational power supply  
WA2IKL p. 8, Apr 70

Overvoltage protection (HN)  
W1AAZ p. 64, Apr 76

Pilot-lamp life (HN)  
W2OLU p. 71, Jul 73

Polarity inverter, medium current  
Laughlin p. 26, Nov 73

Power supplies for single sideband  
Belt p. 38, Feb 69

Power-supply hum (HN)  
W8YFB p. 64, May 71

Power supply, improved (HN)  
W4ATE p. 72, Feb 72

Power supply, precision  
W7SK p. 26, Jul 71

Power supply protection for your solid-state circuits  
W5JJ p. 36, Jan 70

Power supply troubleshooting (repair bench)  
K4IPV p. 78, Sep 77

Precision voltage supply for phase-locked terminal unit (HN)  
WA6TLA p. 60, Jul 74

Protection for solid-state power supplies (HN)  
W3NK p. 66, Sep 70

Rectifier, half-wave, improved  
Bailey p. 34, Oct 73

Regulated power supplies, how to design  
K5VKQ p. 58, Sep 77

Regulated power supply, 500-watt  
WA6PEC p. 30, Dec 77

Regulated solid-state high-voltage power supply  
W6GXN p. 40, Jan 75  
Short circuit p. 69, Apr 75

Regulated 5-volt supply (HN)  
W6UNF p. 67, Jan 73

SCR-regulated power supplies  
W4GOC p. 52, Jul 70

Selenium rectifiers, replacing  
W1DTY p. 41, Apr 76

Servicing power supplies  
W6GXN p. 44, Nov 76

Solar energy  
W3FQJ p. 54, Jul 74

Solar power  
W3FQJ p. 52, Nov 74

Solar power source, 36-volt  
W3FQJ p. 54, Jan 77

Step-start circuit, high-voltage (HN)  
W6VFR p. 64, Sep 71

Storage-battery QRP power  
W3FQJ p. 64, Oct 74

Super regulator, the MPC1000  
W3HUC p. 52, Sep 76

Survey of solid-state power supplies  
W6GXN p. 25, Feb 70  
Short circuit p. 76, Sep 70

Thermoelectric power supplies  
K1AJE p. 48, Sep 68

Transformers, high-voltage, repairing  
W6NIF p. 66, Mar 69

Transformer shorts  
W6BLZ p. 36, Jul 68

Transformers, miniature (HN)  
W4ATE p. 67, Jul 72

Transient eliminator (C&T)  
W1DTY p. 52, Jun 76

Transients, reducing  
W5JJ p. 50, Jan 73

Variable power supply for transistor work  
WA4MTH p. 68, Mar 76

Vibrator replacement, solid-state (HN)  
K8RAY p. 70, Aug 72

Voltage regulators, IC  
W7FLC p. 22, Oct 70

Voltage regulator ICs, adjustable  
WB9KEY p. 36, Aug 75

Voltage-regulator ICs, three-terminal  
WBSEMI p. 26, Dec 73  
Added note (letter) p. 73, Sep 74

Voltage regulators, boosting bargain (HN)  
WA7VVC p. 90, May 77

Voltage regulators, IC  
W6GXN p. 31, Mar 77

Voltage safety valve  
W2UVF p. 78, Oct 76

Wind generators  
W3FQJ p. 50, Jan 75

Zener diodes (HN)  
K3DPJ p. 79, Aug 68

## propagation

Artificial radio aurora, scattering characteristics of  
WB6KAP p. 18, Nov 74

Echoes, long delay  
WB6KAP p. 61, May 69

Ionospheric E-layer  
WB6KAP p. 58, Aug 69

Ionospheric science, short history of  
WB6KAP p. 58, Jun 69

Long-distance high frequency communications  
WB6KAP p. 80, Jul 68

Maximum usable frequency, predicting  
WB6KAP p. 70, Sep 68

Quiet sun, the  
WB6KAP p. 76, Dec 68

Scatter-mode propagation, frequency synchronization for  
K2OVS p. 26, Sep 71

Solar cycle 20, vhf'er's view of  
WA5IYX p. 46, Dec 74

Sunspot numbers  
WB6KAP p. 63, Jul 69

Sunspot numbers, smoothed  
WB6KAP p. 72, Nov 68

Sunspots and solar activity  
WB6KAP p. 60, Jan 69

Tropospheric-duct vhf communications  
WB6KAP p. 68, Oct 69

6-meter sporadic-E openings, predicting  
 WA9RAQ p. 38, Oct 72  
 Added note (letter) p. 69, Jan 74

## receivers and converters

### general

Antenna impedance transformer for receivers (HN)  
 W6NIF p. 70, Jan 70  
 Antenna tuner, miniature receiver (HN)  
 WA7KRE p. 72, Mar 69  
 Anti-QRM methods  
 W3FQJ p. 50, May 71  
 Attenuation pads, receiving (letter)  
 KØHNQ p. 69, Jan 74  
 Audio agc amplifier  
 WA5SNZ p. 32, Dec 73  
 Audio agc principles and practice  
 WA5SNZ p. 28, Jun 71  
 Audio amplifier and squelch circuit  
 W6AJF p. 36, Aug 68  
 Audio filter for CW, tunable  
 WA1JSM p. 34, Aug 70  
 Audio filter-frequency translator for CW reception  
 W2EY p. 24, Jun 70  
 Audio filter mod (HN)  
 K6HIU p. 60, Jan 72  
 Audio filter, simple  
 W4NVK p. 44, Oct 70  
 Audio filters, CW (letter)  
 6Y5SR p. 56, Jun 75  
 Audio filters for ssb and CW reception  
 K6SDX p. 18, Nov 76  
 Audio-filters, inexpensive  
 W8YFB p. 24, Aug 72  
 Audio filter, tunable peak-notch  
 W2EY p. 22, Mar 70  
 Audio filter, variable bandpass  
 W3AEX p. 36, Apr 70  
 Audio, improved for receivers  
 K7GCO p. 74, Apr 77  
 Audio module, complete  
 K4DHC p. 18, Jun 73  
 Bandspreading techniques for resonant circuits  
 Anderson p. 46, Feb 77  
 Short circuits p. 69, Dec 77  
 Batteries, how to select for portable equipment  
 WAØAIK p. 40, Aug 73  
 Bfo multiplexer for a multimode detector  
 WA3YGJ p. 52, Oct 75  
 Calibrator crystals (HN)  
 K6KA p. 66, Nov 71  
 Calibrator, plug-in frequency  
 K6KA p. 22, Mar 69  
 Calibrator, simple frequency-divider using mos ICs  
 W6GXN p. 30, Aug 69  
 Communications receivers, design ideas for  
 Moore p. 12, Jun 74  
 Communications receivers, designing for strong-signal performance  
 Moore p. 6, Feb 73  
 Converting a vacuum-tube receiver to solid-state  
 W1OOP p. 26, Feb 69  
 Counter dials, electronic  
 K6KA p. 44, Sep 70  
 Crystal-filter design, practical  
 PY2PEC p. 34, Nov 76  
 CW filter, adding (HN)  
 W2OUX p. 66, Sep 73  
 CW monitor, simple  
 WA9OHR p. 65, Jan 71  
 CW processor for communications receivers  
 W6NRW p. 17, Oct 71  
 CW reception, enhancing through a simulated-stereo technique  
 WA1MKP p. 61, Oct 74  
 CW reception, noise reduction for  
 W2ELV p. 52, Sep 73  
 CW regenerator for interference-free communications  
 Leward, Libenschek p. 54, Apr 74  
 CW selectivity with crystal bandpassing  
 W2EY p. 52, Jun 69  
 CW transceiver operation with transmit-receive offset  
 W1DAX p. 56, Sep 70  
 Detector, reciprocating  
 W1SNN p. 32, Mar 72  
 Added notes p. 54, Mar 74; p. 76, May 75  
 Detector, single-signal phasing type  
 WB9CYY p. 71, Oct 76  
 Short circuit p. 68, Dec 77  
 Detector, superregenerative, optimizing  
 Ring p. 32, Jul 72  
 Detectors, fm, survey of  
 W6GXN p. 22, Jun 76  
 Detectors, ssb  
 Belt p. 22, Nov 68

Digital frequency display  
 WB2NYK p. 26, Sep 76  
 Diode detectors  
 W6GXN p. 28, Jan 76  
 Comments p. 77, Feb 77  
 Diversity receiving system  
 W2EY p. 12, Dec 71  
 Double-balanced mixer, active, high-dynamic range  
 DJ2LR p. 90, Nov 77  
 Filter alignment  
 W7UC p. 61, Aug 75  
 Filter, vari-Q  
 W1SNN p. 62, Sep 73  
 Frequency calibrator, how to design  
 W3AEX p. 54, Jul 71  
 Frequency calibrator, receiver  
 W5UQS p. 28, Dec 71  
 Frequency-marker standard using cmos  
 W4IYB p. 44, Aug 77  
 Frequency measurement of received signals  
 W4AAD p. 38, Oct 73  
 Frequency spotter, general coverage  
 W5JJ p. 36, Nov 70  
 Frequency standard (HN)  
 WA7JIK p. 69, Sep 72  
 Frequency standard, universal  
 K4EEU p. 40, Feb 74  
 Short circuit p. 72, May 74  
 Hang agc circuit for ssb and CW  
 W1ERJ p. 50, Sep 72  
 Headphone cords (HN)  
 W2OLU p. 62, Nov 75  
 I-f amplifier design  
 DJ2LR p. 10, Mar 77  
 Short circuit p. 94, May 77  
 I-f cathode jack  
 W6HPP p. 28, Sep 68  
 I-f detector receiver module  
 K6SDX p. 34, Aug 76  
 I-f system, multimode  
 WA2IKL p. 39, Sep 71  
 Image suppression (HN)  
 W6NIF p. 68, Dec 72  
 Intelligibility of communications receivers, improving  
 WA5RAQ p. 53, Aug 70  
 Interference, electric fence  
 K6KA p. 68, Jul 72  
 Interference, hi-fi (HN)  
 K6KA p. 63, Mar 75  
 Interference, rf  
 W1DTY p. 12, Dec 70  
 Interference, rf  
 WA3NFW p. 30, Mar 73  
 Interference, rf, its cause and cure  
 G3LLL p. 26, Jun 75  
 Intermodulation distortion, reducing in high-frequency receivers  
 WB4ZNV p. 26, Mar 77  
 Short circuit p. 69, Dec 77  
 Local oscillator, phase-locked  
 VE5FP p. 6, Mar 71  
 Local-oscillator waveform effects on spurious mixer responses  
 Robinson, Smith p. 44, Jun 74  
 Mixer, crystal  
 W2LTJ p. 38, Nov 75  
 Monitor receiver modification (HN)  
 W2CNQ p. 72, Feb 76  
 Noise blanker  
 K4DHC p. 38, Feb 73  
 Noise blanker design  
 K7CVT p. 26, Nov 77  
 Noise blanker, hot-carrier diode  
 W4KAE p. 16, Oct 69  
 Short circuit p. 76, Sep 70  
 Noise blanker, IC  
 W2EY p. 52, May 69  
 Short circuit p. 79, Jun 70  
 Noise effects in receiving systems  
 DJ2LR p. 34, Nov 77  
 Noise figure, the real meaning of  
 K6MIO p. 26, Mar 69  
 Panoramic reception, simple  
 W2EY p. 14, Oct 68  
 Phase-shift networks, design criteria  
 G3NRW p. 34, Jun 70  
 Preamplifier, wideband  
 W1AAZ p. 60, Oct 76  
 Product detector, hot-carrier diode  
 VE3GFN p. 12, Oct 69  
 Radio-direction finder  
 W6JTT p. 38, Mar 70  
 Radio-frequency interference  
 WA3NFW p. 30, Mar 73  
 Radiotelegraph translator and transcriber  
 W7CUU, K7KFA p. 8, Nov 71  
 Eliminating the matrix  
 KH6AP p. 60, May 72  
 Receiver impedance matching (HN)  
 WØZFN p. 79, Aug 68  
 Receiver spurious response  
 Anderson p. 82, Nov 77  
 Receivers — some problems and cures  
 WBØJGP, K8RRH p. 10, Dec 77

Receiving RTTY, automatic frequency control for  
 W5NPO p. 50, Sep 71  
 Reciprocating detector as fm discriminator  
 W1SNN p. 18, Mar 73  
 Reciprocating-detector converter  
 W1SNN p. 58, Sep 74  
 Resurrecting old receivers  
 K4IPV p. 52, Dec 76  
 Rf amplifiers for communications receivers  
 Moore p. 42, Sep 74  
 Rf amplifiers, isolating parallel currents in  
 G3IPV p. 40, Feb 77  
 Rf amplifier, wideband  
 WB4KSS p. 58, Apr 75  
 S-meter readings (HN)  
 W1DTY p. 56, Jun 68  
 Selectivity and gain control, improved  
 VE3GFN p. 71, Nov 77  
 Selectivity, receiver (letter)  
 K4ZZV p. 68, Jan 74  
 Sensitivity, noise figure and dynamic range  
 W1DTY p. 8, Oct 75  
 Signals, how many does a receiver see?  
 DJ2LR p. 58, Jun 77  
 Comments p. 101, Sep 77  
 S meters, solid-state  
 K6SDX p. 20, Mar 75  
 Spectrum analyzer, four channel  
 W9IA p. 6, Oct 72  
 Squelch, audio-actuated  
 K4MOG p. 52, Apr 72  
 Ssb signals, monitoring  
 W6VFR p. 36, Mar 72  
 Superregenerative detector, optimizing  
 Ring p. 32, Jul 72  
 Superregenerative receiver, improved  
 JA1BHG p. 48, Dec 70  
 Threshold-gate/limiter for CW reception  
 W2ELV p. 46, Jan 72  
 Added notes (letter)  
 W2ELV p. 59, May 72  
 Troubleshooting the dead receiver  
 K4IPV p. 56, Jun 76  
 Vlf converter (HN)  
 W3CPU p. 69, Jul 76  
 Weak signal reception in CW receivers  
 ZS6BT p. 44, Nov 71  
 WWV receiver, five-frequency  
 W6GXN p. 36, Jul 76

### high-frequency receivers

Bandpass filters for receiver preselectors  
 W7ZOI p. 18, Feb 75  
 Bandpass tuning, electronic, in the Drake R-4C  
 Horner p. 58, Oct 73  
 BC-603 tank receiver, updating the  
 WA6IAK p. 52, May 68  
 BC-1206 for 7 MHz, converted  
 W4FIN p. 30, Oct 70  
 Short circuit p. 72, Apr 71  
 Collins 75A4 hints (HN)  
 W6VFR p. 68, Apr 72  
 Collins 75A-4 modifications (HN)  
 W4SD p. 67, Jan 71  
 Communications receiver, five band  
 K6SDX p. 6, Jun 72  
 Communications receiver for 80 meters, IC  
 VE3ELP p. 6, Jul 71  
 Communications receiver, micropower  
 WB9FHC p. 30, Jun 73  
 Short circuit p. 58, Dec 73  
 Communications receivers, miniature design ideas for  
 K4DHC p. 18, Apr 76  
 Communications receiver, miniaturized  
 K4DHC p. 24, Sep 74  
 Communications receiver, optimum design for  
 DJ2LR p. 10, Oct 76  
 Communications receiver, solid-state  
 I5TDJ p. 32, Oct 75  
 Correction p. 59, Dec 75  
 Companion receiver, all-mode  
 W1SNN p. 18, Mar 73  
 Converter, hf, solid-state  
 VE3GFN p. 32, Feb 72  
 Converter, tuned very low-frequency  
 OH2KT p. 49, Nov 74  
 Converter, very low frequency receiving  
 W2IMB p. 24, Nov 76  
 Crystal-controlled phase-locked converter  
 W3VF p. 58, Dec 77  
 Direct-conversion receivers  
 W3FQJ p. 59, Nov 71  
 Direct-conversion receivers  
 PAØSE p. 44, Nov 77  
 Direct-conversion receivers, improved selectivity  
 K6BIJ p. 32, Apr 72  
 Direct-conversion receivers, simple active filters for  
 W7ZOI p. 12, Apr 74  
 Double-conversion hf receiver with mechanical frequency readout  
 Perolo p. 26, Oct 76

ESSA weather receiver  
W6GXN p. 36, May 68

Fet converter, bandswitching, for  
40, 20, 15 and 10 (VE3GFN) p. 6, Jul 68  
postscript p. 68, May 69

Fet converter for 10 to 40 meters, second-  
generation  
VE3GFN p. 28, Jan 70  
Short circuit p. 79, Jun 70

Frequency synthesizer for the Drake R-4  
W6NBI p. 6, Aug 72  
Modification (letter) p. 74, Sep 74

General coverage communications receiver  
W6URH p. 10, Nov 77

Gonset converter, solid-state modification of  
Schuler p. 58, Sep 69

Hammarlund HQ215, adding 160-meter  
coverage  
W2GHH p. 32, Jan 72

Heath SB-650 frequency display, using  
with other receivers  
K2BYM p. 40, Jun 73

High dynamic range receiver input stages  
DJ2LR p. 26, Oct 75

High-frequency DX receiver  
WB2ZVU p. 10, Dec 76

Incremental tuning to your  
transceiver, adding  
VE3GFN p. 66, Feb 71

Monitoring oscillator  
W2JIO p. 36, Dec 72

Multiband high-frequency converter  
K6SDX p. 32, Oct 76

Outboard receiver with a transceiver  
W1DTY p. 12, Sep 68

Outboard receiver with the SB-100,  
using an (HN)  
K4GMR p. 68, Feb 70

Overload response in the Collins 75A-4  
receiver, improving  
W6ZO p. 42, Apr 70  
Short circuit p. 76, Sep 70

Phasing-type ssb receiver  
WA0JYK p. 6, Aug 73  
Short circuit p. 58, Dec 73  
Added note (letter) p. 63, Jun 74

Preamplifier, emitter-tuned, 21 MHz  
WA5SNZ p. 20, Apr 72

Preamplifier, low-noise high-gain transistor  
W2EEY p. 66, Feb 69

Preselector, general-coverage (HN)  
W5OZF p. 75, Oct 70

Qser, solid-state  
W5TKP p. 20, Aug 69

Receiver incremental tuning for the  
Swan 350 (HN)  
K1KXA p. 64, Jul 71

Receiver, reciprocating detector  
W1SNN p. 44, Nov 72  
Correction (letter) p. 77, Dec 72

Receiver, versatile solid-state  
W1PLJ p. 10, Jul 70

Receiving RTTY with Heath SB receivers (HN)  
K9HVV p. 64, Oct 71

Rf amplifiers, selective  
K6BIJ p. 58, Feb 72

Regenerative detectors and a wideband  
amplifier for experimenters  
W8YFB p. 61, Mar 70

RTTY monitor receiver  
K4EEU p. 27, Dec 72

RTTY receiver-demodulator for net  
operation  
VE7BRK p. 42, Feb 73

RTTY with SB-300  
W2ARZ p. 76, Jul 68

Swan 350 CW monitor (HN)  
K1KXA p. 63, Jun 72

Transceiver selectivity improved (HN)  
VE3BWD p. 74, Oct 70

Tuner overload, eliminating (HN)  
VE3GFN p. 66, Jan 73  
Attenuators for (letter) p. 69, Jan 74

Two-band novice superhet  
Thorpe p. 66, Aug 68

Weather receiver, low-frequency  
W6GXN p. 36, Oct 68

WWV receiver  
Hudor, Jr. p. 28, Feb 77

WWV receiver, fixed-tuned  
W6GXN p. 24, Nov 69

WWV receiver, regenerative  
WA5SNZ p. 42, Apr 73

WWV receiver, simple (HN)  
WA3JBN p. 68, Jul 70  
Short circuit p. 72, Dec 70

WWV receiver, simple (HN)  
WA3JBN p. 55, Dec 70

WWV-WWVH, amateur applications for  
W3FQJ p. 53, Jan 72

455-kHz bfo, transistorized  
W6BLZ, K5GXR p. 12, Jul 68

20-meter receiver with digital readout, part 1  
K6SDX p. 48, Oct 77

20-meter receiver with digital readout, part 2  
K6SDX p. 56, Nov 77

160-meter receiver, simple  
W6FPO p. 44, Nov 70

1.9 MHz receiver  
W3TNO p. 6, Dec 69

7-MHz direct-conversion receiver  
W0YBF p. 16, Jan 77

7-MHz ssb receiver and transmitter, simple  
VE3GSD p. 6, Mar 74  
Short circuit p. 62, Dec 74

28-MHz superregen receiver  
K2ZSQ p. 70, Nov 68

## vhf receivers and converters

Converters for six and two meters, mosfet  
WB2EGZ p. 41, Feb 71  
Short circuit p. 96, Dec 71

Cooled preamplifier for vhf-uhf  
WA0RDX p. 36, Jul 72

Fet converters for 50, 144, 220 and  
432 MHz  
W6AJF p. 20, Mar 68

Filter-preamplifiers for 50 and 144 MHz  
etched  
W5KNT p. 6, Feb 71

Fm channel scanner  
W2FPP p. 29, Aug 71

Fm communications receiver, modular  
K8AUH p. 32, Jun 69  
Correction p. 71, Jan 70

Fm receiver frequency control (letter)  
W3AFN p. 65, Apr 71

Fm receiver performance, comparison of  
VE7ABK p. 68, Aug 72

Fm receiver, multichannel for six and two  
W1SNN p. 54, Feb 74

Fm receiver, tunable vhf  
K8AUH p. 34, Nov 71

Fm receiver, uhf  
WA2GCF p. 6, Nov 72

Fm repeaters, receiving system  
degradation in  
K5ZBA p. 36, May 69

HW-17A, perking up (HN)  
WB2EGZ p. 70, Aug 70

Improving vhf/uhf receivers  
W1JAA p. 44, Mar 76

Interdigital preamplifier and comb-line  
bandpass filter for vhf and uhf  
W5KHT p. 6, Aug 70

Interference, scanning receiver (HN)  
K2YAH p. 70, Sep 72

Monitor receivers, two-meter fm  
WB5EMI p. 34, Apr 74

Overload problems with vhf converters,  
solving  
W1OOP p. 53, Jan 73

Receiver alignment techniques, vhf fm  
K4IPV p. 14, Aug 75

Receiver, modular two-meter fm  
WA2GFB p. 42, Feb 72

Receiver, vhf fm  
WA2GCF p. 8, Nov 75

Receiving converter, vhf four-band  
W3TQM p. 64, Oct 76

Scanning receiver for vhf fm, improved  
WA2GCF p. 26, Nov 74

Scanning receiver modifications,  
vhf fm (HN)  
WA5WOU p. 60, Feb 74

Scanning receivers for two-meter fm  
K4IPV p. 28, Aug 74

Six-meter converter, improved  
K1BQT p. 50, Aug 70

Six-meter mosfet converter  
WB2EGZ p. 22, Jun 68  
Short circuit p. 34, Aug 68

Squeelch-audio amplifier for fm receivers  
WB4WSU p. 68, Sep 74

Ssb mini-tuner  
K1BQT p. 16, Oct 70

Terminator, 50-ohm for vhf converters  
WA6UAM p. 26, Feb 77

Two-meter converter, 1.5 dB NF  
WA6SXC p. 14, Jul 68

Two-meter mosfet converter  
WB2EGZ p. 22, Aug 68  
Neutralizing p. 77, Oct 68

Two-meter preamp, MM5000  
W4KAE p. 49, Oct 68

Vhf converter performance,  
optimizing (HN)  
K2FSQ p. 18, Jul 68

Vhf fm receiver (letter)  
K8IHQ p. 76, May 73

Vhf receiver scanner  
K2LZG p. 22, Feb 73

Vhf superregenerative receiver, low-voltage  
WA5SNZ p. 22, Jul 73  
Short circuit p. 64, Mar 74

28-30 MHz preamplifier for satellite  
reception  
W1JAA p. 48, Oct 75

50-MHz preamplifier, improved  
WA2GCF p. 46, Jan 73

144-MHz converter (HN)  
K0VQY p. 71, Aug 70

144-MHz converter (letter)  
W0LER p. 71, Oct 71

144 MHz converter, hot-carrier diode  
K8CJU p. 6, Oct 69

144-MHz converter, modular  
W6UOV p. 64, Oct 70

144 MHz converters, choosing fets for (HN)  
K6JYO p. 70, Aug 69

144-MHz preamp, low-noise  
W1DTY p. 40, Apr 76

144-MHz preamp, super (HN)  
K6HCP p. 72, Oct 69

144-MHz preamplifier, Improved  
WA2GCF p. 25, Mar 72  
Added notes p. 73, Jul 72

220-MHz mosfet converter  
WB2EGZ p. 28, Jan 69  
Short circuit p. 76, Jul 69

432-MHz converter, low-noise  
K6JC p. 34, Oct 70

432-MHz fet converter, low noise  
WA6SXC p. 18, May 68

432 MHz preamp (HN)  
W1DTY p. 66, Aug 69

432 MHz preamplifier and converter  
WA2GCF p. 40, Jul 75

1296-MHz converter, solid-state  
VK4ZT p. 6, Nov 70

1296 MHz, double-balanced mixers for  
WA6UAM p. 8, Jul 75

1296-MHz preamplifier  
WA6UAM p. 42, Oct 75

1296-MHz preamplifier, low-noise  
WA2VTR p. 50, Jun 71  
Added note (letter) p. 65, Jan 72

2340-MHz converter, solid-state  
K2JNG, WA2LTM, WA2VTR p. 16, Mar 72

2304-MHz preamplifier, solid-state  
WA2VTR p. 20, Aug 72

## receivers and converters, test and troubleshooting

Receiver alignment  
Allen p. 64, Jun 68

Rf and i-f amplifiers, troubleshooting  
Allen p. 60, Sep 70

Signal injection in ham receivers  
Allen p. 72, May 68

Signal tracing in ham receivers  
Allen p. 52, Apr 68

Weak-signal source, variable-output  
K6JYO p. 36, Sep 71

Weak-signal source, 144 and 432 MHz  
K6JC p. 58, Mar 70

Weak-signal source, 432 and 1296 MHz  
K6RIL p. 20, Sep 68

## RTTY

AFSK, digital  
WA4VOS p. 22, Mar 77  
Short circuit p. 94, May 77

AFSK generator (HN)  
F8KI p. 69, Jul 76

AFSK generator and demodulator  
WB9ATW p. 26, Sep 77

AFSK generator, crystal-controlled  
K7BVT p. 13, Jul 72

AFSK generator, crystal-controlled  
W6LLO p. 14, Dec 73

Sluggish oscillator (letter)  
AFSK oscillators, solid-state  
WA4FGY p. 28, Oct 68

Audio-frequency keyer, simple  
W2LTJ p. 56, Aug 75

Audio-frequency shift keyer  
KH6FMT p. 45, Sep 76

Audio-frequency shift keyer, simple (C&T)  
W1DTY p. 43, Apr 76

Audio-shift keyer, continuous-phase  
VE3CTP p. 10, Oct 73  
Short circuit p. 64, Mar 74

Automatic frequency control for receiving RTTY  
W5NPO p. 50, Sep 71  
Added note (letter) p. 66, Jan 72

Autostart, digital RTTY  
K4EEU p. 6, Jun 73

Autostart monitor receiver  
K4EED p. 37, Dec 72

CRT intensifier for RTTY  
K4VFA p. 18, Jul 71

Carriage return, adding to the automatic  
line-feed generator (HN)  
K4EEU p. 71, Sep 74

Coherent frequency-shift keying, need for  
K3WJQ p. 30, Jun 74  
Added notes (letter) p. 58, Nov 74

Crystal test oscillator and signal generator  
K4EEU p. 46, Mar 73

CW memory for RTTY identification  
W6LLO p. 6, Jan 74

DT-500 demodulator  
K9HVV, K4OAH, WB4KUR p. 24, Mar 76  
Short circuit p. 85, Oct 76

DT-600 demodulator  
K9HVV, K4OAH, WB4KUR p. 8, Feb 76  
Letter, K5GZR p. 78, Sep 76  
Short circuit p. 85, Oct 76

Electronic speed conversion for RTTY teleprinters  
WA6JYJ p. 36, Dec 71  
Printed circuit for  
Frequency-shift meter, RTTY  
VK3ZNV p. 53, Jun 70

Line-end indicator, IC  
W2OKO p. 22, Nov 75

Line feed, automatic for RTTY  
K4EEU p. 20, Jan 73

Mainline ST-5 autostart and antispace  
K2YAH p. 46, Dec 72

Mainline ST-5 RTTY demodulator  
W6FFC p. 14, Sep 70  
Short circuit p. 72, Dec 70

Mainline ST-6 RTTY demodulator  
W6FFC p. 6, Jan 71  
Short circuit p. 72, Apr 71

Mainline ST-6 RTTY demodulator, more  
uses for (letter)  
W6FFC p. 69, Jul 71

Mainline ST-6 RTTY demodulator, troubleshooting  
W6FFC p. 50, Feb 71

Message generator, random access memory  
RTTY  
K4EEU p. 8, Jan 75

Message generator, RTTY  
W6OXP, W8KCQ p. 30, Feb 74

Monitor scope, phase-shift  
W3CIX p. 36, Aug 72

Monitor scope, RTTY, Heath  
HO-10 and SB-610 as (HN)  
K9HVV p. 70, Sep 74

Monitor scope, RTTY, solid-state  
WB2MPZ p. 33, Oct 71

Performance and signal-to-noise ratio  
of low-frequency shift RTTY  
K6SR p. 62, Dec 76

Phase-locked loop AFSK generator  
K7ZOF p. 27, Mar 73

Phase-locked loop RTTY terminal unit  
W4FQM p. 8, Jan 72  
Correction p. 60, May 72  
Power supply for  
Optimization of the phase-  
locked terminal unit p. 22, Sep 75  
Update, W4AYV p. 16, Aug 76

Precise tuning with ssb gear  
W0KD p. 40, Oct 70

Printed circuit for RTTY speed converter  
W7POG p. 54, Oct 72

RAM RTTY message generator, increasing  
capacity of (HN)  
F2ES p. 86, Oct 77

Receiver-demodulator for RTTY net  
operation  
VE7BRK p. 42, Feb 73

Ribbon re-inkers  
W6FFC p. 30, Jun 72

RTTY converter, miniature IC  
K9MRL p. 40, May 69  
Short circuit p. 80, Aug 69

RTTY distortion: causes and cures  
WB6IMP p. 36, Sep 72

RTTY for the blind (letter)  
VE7BRK p. 76, Aug 72

RTTY, introduction to  
K6JFP p. 38, Jun 69

RTTY line-length indicator (HN)  
W2UVF p. 62, Nov 73

RTTY reception with Heath SB receivers (HN)  
K9HVV p. 64, Oct 71

RTTY with the SB-300  
W2ARZ p. 76, Jul 68

Serial converter for 8-level teleprinters  
VE3CTP p. 67, Aug 77  
Short circuit p. 68, Dec 77

Signal Generator, RTTY  
W7ZTC p. 23, Mar 71  
Short circuit p. 96, Dec 71

Simple circuit replaces jack patch  
panel  
K4STE p. 25, Apr 76

Speed control, electronic, for RTTY  
W3VF p. 50, Aug 74

ST-5 keys polar relay (HN)  
W0LPD p. 72, May 74

Swan 350 and 400 equipment on RTTY (HN)  
WB2MIC p. 67, Aug 69

Synchrophase afsk oscillator  
W6FOO p. 30, Dec 70

Synchrophase RTTY reception  
W6FOO p. 38, Nov 70

Tape editor  
W3EAG p. 32, Jun 77

Teleprinters, new look in  
W6JTT p. 38, Jul 70

Terminal unit, phase-locked loop  
W4FQM p. 8, Jan 72  
Correction p. 60, May 72

Terminal unit, phase-locked loop  
W4AYV p. 36, Feb 75

Terminal unit, variable-shift RTTY  
W3VF p. 16, Nov 73

Test generator, RTTY (HN)  
W3EAG p. 67, Jan 73

Test generator, RTTY (HN)  
W3EAG p. 59, Mar 73

Test-message generator, RTTY  
K9GSC, K9PKQ p. 30, Nov 76

Time/date printout  
W0LZT p. 18, Jun 76  
Short circuit p. 68, Dec 77

Voltage supply, precision for  
phase-locked terminal unit (HN)  
WA6TLA p. 60, Jul 74

## satellites

Amateur radio in space, bibliography  
W6OLO p. 60, Aug 68  
Addenda p. 77, Oct 68

Antenna control, automatic azimuth/elevation  
for satellite communications  
WA3HLT p. 26, Jan 75  
Correction p. 58, Dec 75

Antenna, simple satellite (HN)  
WA6PXY p. 59, Feb 75

Antennas, simple, for satellite  
communications  
K4GSX p. 24, May 74

Az-el antenna mount for satellite  
communications  
W2LX p. 34, Mar 75

Circularly-polarized ground-plane  
antenna for satellite communications  
K4GSX p. 28, Dec 74

Communications, first step to satellite  
K1MTA p. 52, Nov 72  
Added notes (letter) p. 73, Apr 73

Future of the amateur satellite service  
K2UBC p. 32, Aug 77

Medical data relay via Oscar  
K7RGE p. 67, Apr 77

Oscar antenna (C&T)  
W1DTY p. 50, Jun 76

Oscar antenna, mobile (HN)  
W6OAL p. 67, May 76

Oscar tracking program, HP-65  
calculator (letters)  
WA3THD p. 71, Jan 76

Oscar 7, communications techniques for  
G3CZC p. 6, Apr 74

Picture transmission, recording satellite  
W6CCN p. 6, Nov 68

Signal polarization, satellite  
KH6IJ p. 6, Dec 72

Tracking the OSCAR satellites  
Harmon, WA6UAP p. 18, Sep 77

28-30 MHz preamplifier for satellite  
reception  
W1JAA p. 48, Oct 75

432-MHz OSCAR antenna (HN)  
W1JAA p. 58, Jul 75

## semiconductors

Antenna switch for meters, solid-state  
K2ZSQ p. 48, May 69

Avalanche transistor circuits  
W4NVK p. 22, Dec 70

Beta master, the  
K8ERV p. 18, Aug 68

Charge flow in semiconductors  
WB6BIH p. 50, Apr 71

Converting a vacuum-tube receiver to  
solid-state  
W1OOP p. 26, Feb 69  
Short circuit p. 76, Jul 69

Converting vacuum tube equipment to  
solid-state  
W2EEY p. 30, Aug 68

Curve master, the  
K8ERV p. 40, Mar 68

Diodes, evaluating  
W5JJ p. 52, Dec 71

Dynamic transistor tester (HN)  
VE7ABK p. 65, Oct 71

European semiconductor numbering system (C&T)  
W1DTY p. 42, Apr 76

Fet bias problems simplified  
WA5SNZ p. 50, Mar 74

Fet biasing  
W3FQJ p. 61, Nov 72

Fetrons, solid-state replacements for tubes  
W1DTY p. 4, Aug 72  
Added notes p. 66, Oct 73; p. 62, Jun 74

Frequency multipliers  
W6GXN p. 6, Aug 71

Frequency multipliers, transistor  
W6AJF p. 49, Jun 70

Glass semiconductors  
W1EZT p. 54, Jul 69

Grid-dip oscillator, solid-state conversion of  
W6AJZ p. 20, Jun 70

Heatsink problems, how to solve transistor  
WA5SNZ p. 46, Jan 74

Impulse generator, snap diode  
Siegal, Turner p. 29, Oct 72

Injection lasers, high power  
Mims p. 28, Sep 71

Injection lasers (letter)  
Mims p. 64, Apr 71

Linear power amplifier, high power solid-state  
Chambers p. 6, Aug 74

Linear transistor amplifier  
W3FQJ p. 59, Sep 71

Long-tail transistor biasing  
W2DXH p. 64, Apr 68

Matching techniques, broadband, for  
transistor rf amplifiers  
WA7WHZ p. 30, Jan 77

Microwave amplifier design, solid state  
WA6UAM p. 40, Oct 76

Mobile converter, solid-state modification of  
Schuler p. 58, Sep 69

Mosfet circuits  
W3FQJ p. 50, Feb 75

Mosfet transistors (HN)  
WB2EGZ p. 72, Aug 69

Motorola fets (letter)  
W1CER p. 64, Apr 71

Motorola MPS transistors (HN)  
W2DXH p. 42, Apr 68

Neutralizing small-signal amplifiers  
WA4WDK p. 40, Sep 70

Noise, zener-diode (HN)  
VE7ABK p. 59, Jun 75

Parasitic oscillations in high-power  
transistor rf amplifiers  
W0KGI p. 54, Sep 70

Pentode replacement (HN)  
W1DTY p. 70, Feb 70

Power dissipation ratings of transistors  
WN9CGW p. 56, Jun 71

Power fets  
W3FQJ p. 34, Apr 71

Power transistors, paralleling (HN)  
WA5EKA p. 62, Jan 72

Relay, transistor replaces (HN)  
W3NK p. 72, Jan 70

Replace the unijunction transistor  
K9VXL p. 58, Apr 68

Rf power detecting devices  
K6JYO p. 28, Jun 70

Rf power transistors, how to use  
WA7KRE p. 8, Jan 70

Snap diode impulse generator  
Siegal, Turner p. 29, Oct 72

Surplus transistors, identifying  
W2FPP p. 38, Dec 70

Thyristors, introduction to  
WA7KRE p. 54, Oct 70

Transconductance tester for field-effect  
transistors  
W6NBI p. 44, Sep 71

Transistor amplifiers, tabulated  
characteristics of  
W5JJ p. 30, Mar 71

Transistor and diode tester  
ZL2AMJ p. 65, Nov 70

Transistor breakdown voltages  
WA5EKA p. 44, Feb 75

Transistors for vhf transmitters (HN)  
W1OOP p. 74, Sep 69

Transistor storage (HN)  
K8ERV p. 58, Jun 68

Transistor tester  
WA6NIL p. 48, Jul 68

Transistor tester for leakage and gain  
W4BRS p. 68, May 68

Transistor testing  
Allen p. 62, Jul 70

Transistor-tube talk (HN)  
WA4NED p. 25, Jun 68

Trapatt diodes (letter)  
WA7NLA p. 72, Apr 72

Troubleshooting around fets  
Allen p. 42, Oct 68

Troubleshooting transistor ham gear  
Allen p. 64, Jul 68

Vfo transistors (HN)  
W1OOP p. 74, Nov 69

Y parameters in rf design, using  
WA0TCU p. 46, Jul 72

Zener diodes (HN)  
K3DPJ p. 79, Aug 68

Zener tester, Low voltage (HN)  
K3DPJ p. 72, Nov 69

## single sideband

Balanced modulator, integrated-circuit  
K7QWR p. 6, Sep 70

Balanced modulators, dual fet  
W3FQJ p. 63, Oct 71

Communications receiver, phasing-type  
WA0JYK p. 6, Aug 73

Converting a-m power amplifiers to  
ssb service  
WA4GNW p. 55, Sep 68

Converting the Swan 120 to two meters  
K6RIL p. 8, May 68

Detectors, ssb  
Belt p. 22, Nov 68

Detector, ssb, IC (HN) K4ODS	p. 67, Dec 72	Speech process, logarithmic WA3FIY	p. 38, Jan 70	Sync generator for black-and-white 525-line TV K4EEU	p. 79, Jul 77
Correction	p. 72, Apr 73	Speech processor, ssb VK9GN	p. 31, Dec 71	Sync generator, IC, for ATV W0KGI	p. 34, Jul 75
Double-balanced mixers W1DTY	p. 48, Mar 68	Speech splatter on single sideband W4MB	p. 28, Sep 75	Synch generator, sstv (letter) W1IA	p. 73, Apr 73
Double-balanced modulator, broadband WA6NCT	p. 8, Mar 70	Ssb exciter, 5-band K1UKX	p. 10, Mar 68	Television DX WA9RAQ	p. 30, Aug 73
Electronic bias switching for linear amplifiers W6VFR	p. 50, Mar 75	Ssb generator, phasing-type W7CMJ	p. 22, Apr 73	Test generator, sstv K4EEU	p. 6, Jul 73
Filters, single-sideband Belt	p. 40, Aug 68	Added comments (letter) W9KIT	p. 65, Nov 73	Vestigial sideband microtransmitter for amateur television WA6UAM	p. 20, Feb 76
Filters, ssb (HN) K6KA	p. 63, Nov 73	Ssb generator, 9-MHz W9KIT	p. 6, Dec 70	Short circuit	p. 94, May 77
Frequency dividers for ssb W7BZ	p. 24, Dec 71	Ssb transceiver, IC, for 80 meters VE3GSD	p. 48, Apr 76	50 years of television W1DTY, K4TWJ	p. 36, Feb 76
Frequency translation in ssb transmitters Belt	p. 22, Sep 68	Switching and linear amplification W3FQJ	p. 61, Oct 71	Letter, WA6JFP	p. 77, Sep 76
Generating ssb signals with suppressed carriers Belt	p. 24, May 68	Syllabic vox system for Drake equipment W6RM	p. 24, Aug 76		
Guide to single sideband, a beginner's Belt	p. 66, Mar 68	Transceiver, miniature 7-MHz W7BBX	p. 16, Jul 74		
Hang agc circuit for ssb and CW W1ERJ	p. 50, Sep 72	Transceiver, single-band ssb W1DTY	p. 8, Jun 69		
Intermittent voice operation of power tubes W6SAI	p. 24, Jan 71	Transceiver, ssb, IC G3ZVC	p. 34, Aug 74		
Intermodulation-distortion measurements on ssb transmitters W6VFR	p. 34, Sep 74	Circuit change (letter) W5BAA	p. 62, Sep 75		
Linear amplifier, five-band conduction- cooled W9KIT	p. 6, Jul 72	Transceiver, ssb, using LM373 IC VE6ABX	p. 32, Nov 73		
Linear amplifier, five-band kilowatt W4OQ	p. 14, Jan 74	Transmitter alignment Allen	p. 6, Mar 73		
Improved operation (letter) W7IV	p. 59, Dec 74	Transmitter and receiver for 40 meters, ssb VE3GSD	p. 62, Oct 69		
Linear amplifier, homebrew five-band W4PSJ	p. 30, Mar 70	Short circuit WA0JYK	p. 6, Mar 74		
Linear amplifier performance, improving W6WR	p. 68, Oct 71	Transmitter, phasing-type ssb K2ISP	p. 62, Dec 74		
Linear amplifier, 100-watt W7DI	p. 28, Dec 75	Transverter, 6-meter K8DOC, K8TVP	p. 8, Jun 75		
Linear, five-band hf W6HHN	p. 6, Mar 72	Trapezoidal monitor scope VE3CUS	p. 8, Apr 69		
Linear for 80-10 meters, high-power Short circuit	p. 56, Apr 71	TTL ICs, using in ssb equipment G4ADJ	p. 44, Dec 68		
Linearity meter for ssb amplifiers W4MB	p. 96, Dec 71	Tuning up ssb transmitters Allen	p. 22, Dec 69		
Linear power amplifiers Belt	p. 40, Jun 76	TV sweep tubes in linear service, full-blast operation of W6SAI, W6UOV	p. 18, Nov 75		
Linears, three bands with two (HN) W4NJF	p. 16, Apr 68	Two-tone oscillator for ssb testing W6GXN	p. 62, Nov 69		
Minituner, ssb K1BQT	p. 70, Nov 69	Vacuum tubes, using odd-ball types in linear amplifier service W5JJ	p. 9, Apr 68		
Modifying the Heath SB-200 amplifier for the new 8873 zero-bias triode W6UOV	p. 16, Oct 70	Vhf, uhf transverter, input source for (HN) F8MK	p. 11, Apr 72		
Oscillators, ssb Belt	p. 32, Jan 71	Vox and mox systems for ssb Belt	p. 58, Sep 72		
Peak envelope power, how to measure W5JJ	p. 24, Oct 68	Vox, versatile W9KIT	p. 69, Sep 70		
Phase-shift networks, design criteria for G3NRW	p. 50, Jul 71	Short circuit W6SAI	p. 24, Oct 68		
Phase-shift ssb generators Belt	p. 32, Nov 74	3-500Z in amateur service, the W6SAI	p. 50, Jul 71		
Power supplies for ssb Belt	p. 34, Jun 70	144-MHz linear, 2kW W6UOV, W6ZO, K6DC	p. 96, Dec 71		
Precise tuning with ssb gear W0KD	p. 26, Apr 70	144-MHz low-drive kilowatt linear W6HHN	p. 56, Mar 68		
Pre-emphasis for ssb transmitters OH2CD	p. 26, Jul 70	144-MHz transverter, the TR-144 K1RAK	p. 26, Apr 70		
Rating tubes for linear amplifier service W6UOV, W6SAI	p. 24, Feb 72	432-MHz rf power amplifier K6JC	p. 26, Jul 70		
Rf clipper for the Collins S-line K6JYO	p. 40, Apr 70	432-MHz ssb converter K6JC	p. 24, Feb 72		
Letter	p. 38, Feb 72	Short circuit W6HHN	p. 40, Apr 70		
Rf speech processor, ssb W2MB	p. 50, Mar 71	432-MHz ssb, practical approach to WA2FSQ	p. 48, Jan 70		
Sideband location (HN) K6KA	p. 18, Aug 71	1296-MHz ssb transceiver WA6UAM	p. 79, Jun 70		
Solid-state circuits for ssb Belt	p. 68, Dec 71		p. 6, Jun 71		
Solid-state transmitting converter for 144-MHz ssb W6NBI	p. 18, Sep 73		p. 8, Sep 74		
Short circuit	p. 18, Jan 69				
Speech clipper, IC K6HTM	p. 6, Feb 74				
Added notes (letter) G6XN	p. 62, Dec 74				
Speech clipper, rf, construction G6XN	p. 18, Feb 73				
Speech clippers, rf, performance of G6XN	p. 64, Oct 73				
Added notes p. 58, Aug 73; p. 72, Sep 74	p. 12, Dec 72				
Speech clipping K6KA	p. 26, Nov 72				
Speech clipping in single-sideband equipment K1YZW	p. 26, Nov 72				
Speech processing W1DTY	p. 72, Sep 74				
Speech processing, principles of ZL1BN	p. 24, Apr 69				
Added notes p. 75, May 75; p. 64, Nov 75	p. 22, Feb 71				
Speech processor for ssb K6PHT	p. 60, Jun 68				
	p. 28, Feb 75				
	p. 64, Nov 75				
	p. 22, Apr 70				

## transmitters and power amplifiers general

Amplitude modulation, a different approach WA5SNZ	p. 50, Feb 70
Batteries, how to select for portable equipment WA0AIK	p. 40, Aug 73
Blower maintenance (HN) W6NIF	p. 71, Feb 71
Blower-to-chassis adapter (HN) K6JYO	p. 73, Feb 71
Converting a-m power amplifiers to ssb service WA4GNW	p. 55, Sep 68
Efficiency of linear power amplifiers, how to compare W5JJ	p. 64, Jul 73
Electronic bias switching for linear amplifiers W6VFR	p. 50, Mar 75
Fail-safe timer, transmitter (HN) K9HVW	p. 72, Oct 74
Filter converter, an up/down W5DA	p. 20, Dec 77
Filters, ssb (HN) K6KA	p. 63, Nov 73
Frequency multipliers W6GXN	p. 6, Aug 71
Frequency translation in ssb Transmitters Belt	p. 22, Sep 68
Grid-current measurement in grounded-grid amplifiers W6SAI	p. 64, Aug 68
Intermittent voice operation of power tubes W6SAI	p. 24, Jan 71
Key and vox clicks (HN) K6KA	p. 74, Aug 72
Linear power amplifiers Belt	p. 16, Apr 68
Lowpass filters for solid-state linear amplifiers WA0JYK	p. 38, Mar 74
Short circuit	p. 62, Dec 74
Matching techniques, broadband, for transistor rf amplifiers WA7WHZ	p. 30, Jan 77
Multiple tubes in parallel grounding grid (HN) W7CSD	p. 60, Aug 71
National NCX-500 modification for 15 meters (HN) WA1KYO	p. 87, Oct 77
Networks, transmitter matching W6FFC	p. 6, Jan 73
Neutralizing tip (HN) ZE6JP	p. 69, Dec 72
Parasitic oscillations in high-power transistor rf amplifiers W0KGI	p. 54, Sep 70
Parasitic suppressor (HN) WA9JMY	p. 80, Apr 70
Pi and Pi-L networks W6SAI	p. 36, Nov 68
Pi network design aid W6NIF	p. 62, May 74
Correction (letter)	p. 58, Dec 74
Pi-network design, high-frequency power amplifier W6FFC	p. 6, Sep 72
Pi-network inductors (letter) W7IV	p. 78, Dec 72
Pi networks, series tuned W2EGH	p. 42, Oct 71
Power attenuator, all-band 10-dB K1CCL	p. 68, Apr 70
Power fets W3FQJ	p. 34, Apr 71
Power tube open filament pins (HN) W9KNI	p. 69, Apr 75
Pre-emphasis for ssb transmitters OH2CD	p. 38, Feb 72
Relay activator (HN) K6KA	p. 62, Sep 71
Rf power amplifiers, high-efficiency WB8LQK	p. 8, Oct 74

Rf power transistors, how to use WA7KRE	p. 8, Jan 70
Screen clamp, solid-state WQLRW	p. 44, Sep 68
Sstv reporting system WB6ZYE	p. 78, Sep 76
Step-start circuit, high-voltage (HN) W6VFR	p. 64, Sep 71
Swr alarm circuits W2EYY	p. 73, Apr 70
Temperature alarms for high-power amplifiers W2EYY	p. 48, Jul 70
Transmitter power levels, some observations regarding WA5SNZ	p. 62, Apr 71
Transmitter, remote keying (HN) WA3H DU	p. 74, Oct 69
Transmitter switching, solid-state W2EYY	p. 44, Jun 68
Transmitter-tuning unit for the blind W9NTP	p. 60, Jun 71
TV sweep tubes in linear service, full-blast operation of W6SAI, W6UOV	p. 9, Apr 68
Vacuum tubes, using odd-ball types in linear amplifiers W5JJ	p. 58, Sep 72
Vfo, digital readout WB8IFM	p. 14, Jan 73

## high-frequency transmitters

ART-13, Modifying for noiseless CW (HN) K5GKN	p. 68, Aug 69
CW transceiver for 40 and 80 meters W3NNL, K3OIO	p. 14, Jul 69
CW transceiver for 40 and 80 meters, improved W3NNL	p. 18, Jul 77
CW transceiver, low-power 20-meter W7ZOI	p. 8, Nov 74
CW transmitter, half-watt KQVQY	p. 69, Nov 69
Driver and final for 40 and 80 meters, solid-state W3QBO	p. 20, Feb 72
Electronic bias switch for negatively-biased power amplifiers WA5KPG	p. 27, Nov 76
Field-effect transistor transmitters K2BLA	p. 30, Feb 71
Filters, low-pass for 10 and 15 meters W2EYY	p. 42, Jan 72
Five-band transmitter, hf, solid-state I5TDJ	p. 24, Apr 77
Frequency synthesizer, high frequency K2BLA	p. 16, Oct 72
Grounded-grid 2 kW PEP amplifier, high frequency W6SAI	p. 6, Feb 69
Heath HW-101 transceiver, using with a separate receiver (HN) WA1MKP	p. 63, Oct 73
Linear amplifier, five-band W7IV	p. 30, Mar 70
Linear amplifier, five-band conduction-cooled W9KIT	p. 6, Jul 72
Linear amplifier performance, improving W4PSJ	p. 68, Oct 71
Linear amplifier, 100-watt W6WR	p. 28, Dec 75
Linear, five-band hf W7DI	p. 6, Mar 72
Linear, five-band kilowatt W4OQ	p. 14, Jan 74
Improved operation (letter) W4OQ	p. 59, Dec 74
Linear for 80-10 meters, high-power W6HHN	p. 56, Apr 71
Short circuit W6HHN	p. 96, Dec 71
Linear power amplifier, high-power solid-state Chambers	p. 6, Aug 74
Linears, three bands with two (HN) W4NJF	p. 70, Nov 69
Low-frequency transmitter, solid-state W4KAE	p. 16, Nov 68
Lowpass filter, high-frequency W2OLU	p. 24, Mar 75
Short circuit W2OLU	p. 59, Jun 75
Modifying the Heath SB-200 amplifier for the new 8873 zero-bias triode W6UOV	p. 32, Jan 71
Phase-locked loop, 28 MHz W1KNI	p. 40, Jan 73
QRP fet transmitter, 80-meter W3FQJ	p. 50, Aug 75
Ssb exciter, 5-band K1UKX	p. 10, Mar 68
Ssb transceiver, miniature 7-MHz W7BBX	p. 16, Jul 74
Ssb transceiver using LM373 IC W5BAA	p. 32, Nov 73
Ssb transceiver, 9-MHz, IC G3ZVC	p. 34, Aug 74
Circuit change (letter) G3ZVC	p. 62, Sep 75
Ssb transmitter and receiver, 40 meters	

VE3GSD Short circuit	p. 6, Mar 74
Ssb transmitter, phasing type WAQJYK	p. 62, Dec 74
Tank circuit, inductively-tuned high-frequency W6SAI	p. 8, Jun 75
Transceiver, single-band ssb W1DTY	p. 6, Jul 70
Transceiver, 3.5-MHz ssb VE6ABX	p. 8, Jun 69
Transmitter, five-band, CW and ssb WN3WTG	p. 6, Mar 73
Transmitter, low-power W6NIF	p. 34, Jan 77
Transmitters, QRP W7OE	p. 26, Dec 70
Transmitter, universal flea-power K2ZSQ	p. 36, Dec 68
Transverter, high-level hf K4ERO	p. 58, Apr 69
Wideband linear amplifier, 4 watt VE5FP	p. 68, Jul 68
3-400Z, 3-500Z filament circuits, notes on K9WEH	p. 42, Jan 76
3-500Z in amateur service, the W6SAI	p. 66, Apr 76
7-MHz QRP CW transmitter WA4MTH	p. 56, Mar 68
14-MHz vfo transmitter, solid-state W3QBO	p. 26, Dec 76
28-MHz transmitter, solid-state K2ZSQ	p. 6, Nov 73
40-meters, transistor rig for W6BLZ, K5GXR	p. 10, Jul 68
160-meters, 500-watt power amplifier W2BP	p. 44, Jul 68
	p. 8, Aug 75

## vhf and uhf transmitters

Converting the Swan 120 to two meters K6RIL	p. 8, May 68
Fm repeater transmitter, improving W6GDO	p. 24, Oct 69
Linear for 2 meters W4KAE	p. 47, Jan 69
Linear for 1296 MHz, high-power WB6IOM	p. 8, Aug 68
Phase-locked loop, 50 MHz W1KNI	p. 40, Jan 73
Transistors for vhf transmitters (HN) W1OOP	p. 74, Sep 69
Transmitter, flea power K2ZSQ	p. 58, Apr 69
Transmitting mixers for 6 and 2 meters K2ISP	p. 8, Apr 69
Transverter for 6 meters WA9IGU	p. 44, Jul 69
Tunnel diode phone rig, 6-meter (HN) K2ZSQ	p. 74, Jul 68
Vhf linear, 2kW, design data for W6UOV	p. 6, Mar 69
50-MHz kilowatt, inductively tuned K1DPP	p. 8, Sep 75
50-MHz linear amplifier K1RAK	p. 38, Nov 71
50-MHz linear amplifier, 2-kW W6UOV	p. 16, Feb 71
50-MHz linear, inductively tuned W6SAI	p. 6, Jul 70
50-MHz transmitter, solid-state WB2EGZ	p. 6, Oct 68
50-MHz transverter K1RAK	p. 12, Mar 71
50/144-MHz multimode transmitter K2ISP	p. 28, Sep 70
144-MHz fm transmitter W9SEK	p. 6, Apr 72
144-MHz fm transmitter, solid-state W6AJF	p. 14, Jul 71
144-MHz fm transmitter, Sonobaby WAQZUO	p. 8, Oct 71
Short circuit WAQZUO	p. 96, Dec 71
Crystal deck for WAQZUO	p. 26, Oct 72
144-MHz low-drive kilowatt linear W6HHN	p. 26, Jul 70
144-MHz low-power solid-state transmitter KQVQY	p. 52, Mar 70
144-MHz phase-modulated transmitter W6AJF	p. 18, Feb 70
144-MHz power amplifier, high performance W6UOV	p. 22, Aug 71
144-MHz power amplifier, 10-watt solid-state W1DTY	p. 67, Jan 74
144-MHz rf power amplifiers, solid state W4CGC	p. 6, Apr 73
144-MHz transmitting converter, solid-state ssb W6NBI	p. 6, Feb 74
Short circuit W6NBI	p. 62, Dec 74
144-MHz transceiver, a-m K1AOB	p. 55, Dec 71
144-MHz two-kilowatt linear W6UOV, W6ZO, K6DC	p. 26, Apr 70
144- and 432- stripline amplifier/triplier K2RIW	p. 6, Feb 70
220-MHz exciter WB6DJV	p. 50, Nov 71

220-MHz power amplifier W6UOV	p. 44, Dec 71
220-MHz, rf power amplifier for WB6DJV	p. 44, Jan 71
220-MHz rf power amplifier, vhf fm K7JUE	p. 6, Sep 73
432-MHz amplifier, 2-kW W6DAI, W6NLZ	p. 6, Sep 68
432-MHz exciter, solid-state W1OOP	p. 38, Oct 69
432-MHz rf power amplifier K6JC	p. 40, Apr 70
432-MHz solid-state linear amplifier WB6QXF	p. 30, Aug 75
432-MHz ssb converter K6JC	p. 48, Jan 70
Short circuit K6JC	p. 79, Jun 70
432-MHz 100-watt solid-state power amplifier WA7CNP	p. 36, Sep 75
1296-MHz frequency tripler K4SUM, W4API	p. 40, Sep 69
1296-MHz power amplifier W2COH, W2CCY, W2OJ, W1MU	p. 43, Mar 70
2304-MHz power amplifier WA9HUV	p. 8, Feb 75

## transmitters and power amplifiers, test and troubleshooting

Aligning vhf transmitters Allen	p. 58, Sep 68
Ssb transmitter alignment Allen	p. 62, Oct 69
Transverter, 6-meter K8DOC, K8TVP	p. 44, Dec 68
Tuning up ssb transmitters Allen	p. 62, Nov 69

## troubleshooting

Analyzing wrong dc voltages Allen	p. 54, Feb 69
Audio distortion, curing in speech amplifiers Allen	p. 42, Aug 70
Basic troubleshooting James	p. 54, Jan 76
Dc-dc converters, curing trouble in Allen	p. 56, Jun 70
Fets, troubleshooting around Allen	p. 42, Oct 68
High-voltage troubleshooting Allen	p. 52, Aug 68
Logic circuits, troubleshooting W8GRG	p. 56, Feb 77
Mobile power supplies, troubleshooting Allen	p. 56, Jun 70
Ohmmeter troubleshooting Allen	p. 52, Jan 69
Oscillators, repairing Allen	p. 69, Mar 70
Oscillator troubleshooting (repair bench) K4IPV	p. 54, Mar 77
Oscilloscope, putting to work Allen	p. 64, Sep 69
Oscilloscope, troubleshooting amateur gear with Allen	p. 52, Aug 69
Power supply, troubleshooting K4IPV	p. 78, Sep 77
Receiver alignment Allen	p. 64, Jun 68
Receiver alignment techniques, vhf fm K4IPV	p. 14, Aug 75
Receivers, troubleshooting the dead K4IPV	p. 56, Jun 76
Resistance measurement, troubleshooting by Allen	p. 62, Nov 68
Resistance measurement, troubleshooting by James	p. 58, Apr 76
Rf and i-f amplifiers, troubleshooting Allen	p. 60, Sep 70
Signal injection testing in receivers Allen	p. 72, May 68
Signal tracing in amateur receivers Allen	p. 52, Apr 68
Speech amplifiers, curing distortion Allen	p. 42, Aug 70
Ssb transmitter alignment Allen	p. 62, Oct 69
Sweep generator, how to use Allen	p. 60, Apr 70
Transistor amateur gear, troubleshooting Allen	p. 64, Jul 68
Transistor circuits, troubleshooting K4IPV	p. 60, Sep 76
Transistor testing Allen	p. 62, Jul 70
Tuning up ssb transmitters Allen	p. 62, Nov 69
Vhf transmitters, aligning Allen	p. 58, Sep 68

Voltage troubleshooting  
James p. 64, Feb 76

## vhf and microwave general

Amateur vhf fm operation  
W6AYZ p. 36, Jun 68

Artificial radio aurora, vhf  
scattering characteristics  
WB6KAP p. 18, Nov 74

A-m modulation monitor (HN)  
K7UNL p. 67, Jul 71

APX-6 transponder, notes on  
W6OSA p. 32, Apr 68

Band change from six to two meters, quick  
KØYQY p. 64, Feb 70

Bandpass filters, single-pole  
W6HPH p. 51, Sep 69

Bandpass filters, 25 to 2500 MHz  
K6RIL p. 46, Sep 69

Bypassing, rf, at vhf  
WB6BHI p. 50, Jan 72

Cavity filter, 144-MHz  
W1SNN p. 22, Dec 73

Short circuit

Coaxial filter, vhf  
W6SAI p. 36, Aug 71

Coaxial-line resonators (HN)  
WA7KRE p. 82, Apr 70

Coil-winding data, practical vhf and uhf  
K3SVC p. 6, Apr 71

Crystal mount, untuned  
W1DTY p. 68, Jun 68

Effective radiated power (HN)  
VE7CB p. 72, May 73

Frequency multipliers  
W6GXN p. 6, Aug 71

Frequency multipliers, transistor  
W6AJF p. 49, Jun 70

Frequency scaler, 500-MHz  
W6URH p. 32, Jun 75

Frequency scalars, 1200-MHz  
WB9KEY p. 38, Feb 75

Frequency synchronization for  
scatter-mode propagation  
K2OVS p. 26, Sep 71

Frequency synthesizer, 220 MHz  
W6GXN p. 8, Dec 74

Gridded tubes, vhf/uhf effects in  
W6UOV p. 8, Jan 69

Harmonic generator (HN)  
W5GDQ p. 76, Oct 70

Impedance bridge (HN)  
W6KZK p. 67, Feb 70

Improving vhf/uhf receivers  
W1JAA p. 44, Mar 76

Indicator, sensitive rf  
WB9DNI p. 38, Apr 73

Klystron cooler, waveguide (HN)  
WA4WDL p. 74, Oct 74

Lunar-path nomograph  
WA6NCT p. 28, Oct 70

Microwave communications, amateur  
standards for  
K6HIJ p. 54, Sep 69

Microwave frequency doubler  
WA4WDL p. 69, Mar 76

Microwave hybrids and couplers for  
amateur use  
W2CTK p. 57, Jul 70

Short circuit

Microwave marker generator, 3cm  
band (HN)  
WA4WDL p. 69, Jun 76

Microwave rf generators, solid-state  
W1HR p. 10, Apr 77

Microwaves, getting started in  
Roubal p. 53, Jun 72

Microwaves, introduction to  
W1CBBY p. 20, Jan 72

Microwave solid-state amplifier design  
WA6UAM p. 40, Oct 76

Comment, VK3TK, WA6UAM  
Moonbounce to Australia  
W1DTY p. 85, Apr 68

Noise figure, meaning of  
K6MIO p. 26, Mar 69

Noise figure measurements, vhf  
WB6NMT p. 36, Jun 72

Noise generators, using (HN)  
K2ZSQ p. 79, Aug 68

Phase-locked loop, tunable 50 MHz  
W1KNI p. 40, Jan 73

Polaplexer design  
K6MBL p. 40, Mar 77

Power dividers and hybrids  
W1DAX p. 30, Aug 72

Proportional temperature control for crystal  
ovens  
VE5FP p. 44, Jan 70

Radio observatory, vhf  
Ham p. 44, Jul 74

Reflex klystrons, pogo stick for (HN)  
W6BPK p. 71, Jul 73

Rf power-detecting devices  
K6JYO p. 28, Jun 70

Satellite communications  
K1TMA p. 52, Nov 72

Added notes (letter)  
Satellite signal polarization  
KH6IJ p. 73, Apr 73

Solar cycle 20, vhf'er's view of  
WA5IYX p. 6, Dec 72

Spectrum analyzer, microwave  
WA6UAM p. 46, Dec 74

Tank circuits, design of vhf  
K7UNL p. 54, Aug 77

Uhf dummy load, 150-watt  
WB6QXF p. 56, Nov 70

Uhf hardware (HN)  
W6CMQ p. 30, Sep 76

Vfo, high-stability vhf  
OH2CD p. 76, Oct 70

Vhf beacons  
K6EDX p. 27, Jan 72

Vhf beacons  
W3FQJ p. 52, Oct 69

Vhf circuits, eliminating parallel  
currents (HN)  
G3IPV p. 66, Dec 71

50-MHz bandpass filter  
W4EKO p. 91, May 77

50-MHz frequency synthesizer  
W1KNI p. 70, Aug 76

144-MHz fm frequency meter  
W4JAZ p. 26, Mar 74

Short circuit

144-MHz frequency synthesizer  
WB4FPK p. 40, Jan 71

144-MHz frequency-synthesizer, one-  
crystal  
WØKMY p. 72, Apr 71

220-MHz frequency synthesizer  
W6GXN p. 34, Jul 73

432-MHz ssb, practical approach to  
WA2FSQ p. 30, Sep 73

1296-MHz microstripline bandpass filters  
WA6UAM p. 8, Dec 74

2304-MHz stripline bandpass filter  
WA4WDL, WB4LJM p. 6, Jun 71

40-GHz record  
K7PMY p. 46, Dec 75

p. 50, Apr 77

p. 70, Dec 68

## vhf and microwave antennas

Circularly-polarized ground-plane  
antenna for satellite communications  
K4GSX p. 28, Dec 74

Feed horn, cylindrical, for parabolic reflectors  
WA9HUV p. 16, May 76

Feeding and matching techniques for  
vhf/uhf antennas  
W1JAA p. 54, May 76

Ground plane, portable vhf (HN)  
K9DHD p. 71, May 73

Log-periodic yagi beam antenna  
K6RIL, W6SAI p. 8, Jul 69

Correction p. 68, Feb 70

Matching techniques for vhf/uhf antennas  
W1JAA p. 50, Jul 76

Microstrip swr bridge, vhf and uhf  
W4CGC p. 22, Dec 72

Microwave antenna, low-cost  
K6HIJ p. 52, Nov 69

Parabolic reflector antennas  
VK3ATN p. 12, May 74

Parabolic reflector element spacing  
WA9HUV p. 28, May 75

Parabolic reflector gain  
W2TQK p. 50, Jul 75

Parabolic reflector, 16-foot homebrew  
WB6IOM p. 8, Aug 69

Parabolic reflectors, finding  
focal length of (HN)  
WA4WDL p. 57, Mar 74

Swr meter  
W6VSV p. 6, Oct 70

Transmission lines, uhf  
WA2VTR p. 36, May 71

Two-meter antenna, simple (HN)  
W6BLZ p. 78, Aug 68

Two-meter mobile antennas  
W6BLZ p. 76, May 68

Vhf antenna switching without relays (HN)  
K2ZSQ p. 77, Sep 68

10 GHz, broadband antenna  
WA4WDL, WB4LJM p. 40, May 77

10 GHz dielectric antenna (HN)  
WA4WDL p. 80, May 75

50-MHz antenna coupler  
K1RAK p. 44, Jul 71

50-MHz collinear beam  
K4ERO p. 59, Nov 69

50-MHz cubical quad, economy  
W6DOR p. 50, Apr 69

50-MHz J-pole antenna  
K4SDY p. 48, Aug 68

50-MHz mobile antenna (HN)  
W4PSJ p. 77, Oct 70

144-MHz antenna, 5/8 wave vertical  
K6KLO p. 40, Jul 74

144-MHz antenna, 5/8-wave vertical,  
build from CB mobile whips  
WB4WSU p. 67, Jun 74

144-MHz antennas, simple  
WA3NFW p. 30, May 73

144-MHz antenna switch, solid-state  
K2ZSQ p. 48, May 69

144-MHz collinear antenna  
W6RJO p. 12, May 72

144-MHz collinear uses PVC pipe mast (HN)  
K8LLZ p. 66, May 76

144-MHz four-element collinear array  
WB6KGF p. 6, May 71

144-MHz ground plane antenna, 0.7  
wavelength  
W3WZA p. 40, Mar 69

144-MHz moonbounce antenna  
K6HCP p. 52, May 70

144-MHz whip, 5/8-wave (HN)  
VE3DDD p. 70, Apr 73

432-MHz corner reflector antenna  
WA2FSQ p. 24, Nov 71

432-MHz high-gain Yagi  
K6HCP p. 46, Jan 76

Comments, WØPW

432-MHz OSCAR antenna (HN)  
W1JAA p. 58, Jul 75

432- and 1296-MHz quad-yagi arrays  
W3AED p. 20, May 73

Short circuit

440-MHz collinear antenna, four-element  
WA6HTP p. 38, May 73

1296-MHz Yagi  
W2CQH p. 24, May 72

1296-MHz Yagi array  
W3AED p. 40, May 75

## vhf and microwave receivers and converters

Audio filter, tunable, for weak-signal  
communications  
K6HCP p. 28, Nov 75

Calculating preamplifier gain from  
noise-figure measurements  
N6TX p. 30, Nov 77

Cooled preamplifier for vhf-uhf reception  
WAØRDX p. 36, Jul 72

Double-balanced mixers, circuit packaging for  
WA6UAM p. 41, Sep 77

Fet converters for 50, 144, 220 and  
432 MHz  
W6AJF p. 20, Mar 68

Interdigital preamplifier and comb-line  
bandpass filter for vhf and uhf  
W6KHT p. 6, Aug 70

Microwave amplifier design, solid state  
WA6UAM p. 40, Oct 76

Noise figure, sensitivity and dynamic range  
W1DTY p. 8, Oct 75

Noise figure, vhf, estimating  
WA9HUV p. 42, Jun 75

Overload problems with vhf converters,  
solving  
W1OOP p. 53, Jan 73

Receiver scanner, vhf  
K2LZG p. 22, Feb 73

Receiver, superregenerative, for vhf  
WA5SNZ p. 22, Jul 73

Signal detection and communication  
in the presence of white noise  
WB6IOM p. 16, Feb 69

Signal generator for two and six meters  
WA8OIK p. 54, Nov 69

Single-frequency conversion, vhf/uhf  
W3FQJ p. 62, Apr 75

Vhf converter performance,  
optimizing (HN)  
K2ZSQ p. 18, Jul 68

Weak-signal source, stable, variable output  
K6JYO p. 36, Sep 71

Weak-signal source, 144 and 432 MHz  
K6JC p. 58, Mar 70

Weak-signal source, 432 and 1296 MHz  
K6RIL p. 20, Sep 68

10 GHz hybrid-tee mixer  
G3NRT p. 34, Oct 77

28-30 MHz low-noise preamp  
W1JAA p. 48, Oct 75

50-MHz deluxe mosfet converter  
WB2EGZ p. 41, Feb 71

50-MHz etched-inductance bandpass filters  
and filter-preamplifiers  
W5KHT p. 6, Feb 71

50-MHz mosfet converter  
WB2EGZ p. 22, Jun 68

Short circuit

50-MHz preamplifier, improved  
WA2GCF p. 46, Jan 73

144-MHz converter (HN)  
KØVQY p. 71, Aug 70

144-MHz converter, high dynamic range  
DJ2LR p. 55, Jul 77

144-MHz converter, 1.5 dB noise figure  
WA6SXC p. 14, Jul 68

144-MHz converters, choosing fets (HN)  
K6JYO p. 70, Aug 69

144-MHz deluxe mosfet converter WB2EGZ Short circuit Letter, WOLER	p. 41, Feb 71 p. 96, Dec 71 p. 71, Oct 71
144-MHz etched-inductance bandpass filters and filter-preamplifiers W5KHT	p. 6, Feb 71
144-MHz fm receiver W9SEK	p. 22, Sep 70
144-MHz fm receiver WA2GBF Added notes	p. 42, Feb 72 p. 73, Jul 72
144-MHz fm receiver WA2GCF	p. 6, Nov 72
144-MHz preamplifier, improved WA2GCF	p. 25, Mar 72
144-MHz preamplifier, low noise W8BBB	p. 36, Jun 74
144-MHz preamp, low-noise W1DTY	p. 40, Apr 76
144-MHz preamp, super (HN) K6HCP	p. 72, Oct 69
144-MHz preamp, MM5000 W4KAE	p. 49, Oct 68
144-MHz transverter using power fets WB6BPI	p. 10, Sep 76
220-MHz mosfet converter WB2EGZ Short circuit	p. 28, Jan 69 p. 76, Jul 69
432-MHz converter, low-noise K6JC	p. 34, Oct 70
432-MHz fet converter, low-noise WA6SXC	p. 18, May 68
432-MHz fet preamp (HN) W1DTY	p. 66, Aug 69
432-MHz preamplifier and converter WA2GCF	p. 40, Jul 75
432-MHz preamplifier, ultra low-noise W1JAA	p. 8, Mar 75
1296-MHz converter, solid state VK4ZT	p. 6, Nov 70
1296-MHz, double-balanced mixers for WA6UAM	p. 8, Jul 75
1296-MHz noise generator W3BSV	p. 46, Aug 73
1296-MHz preamplifier WA6UAM	p. 42, Oct 75
1296-MHz preamplifier, low-noise transistor WA2VTR Added note (letter)	p. 50, Jun 71 p. 65, Jan 72
1296-MHz preamplifiers, microstripline WA6UAM Comments, W2DU	p. 12, Apr 75 p. 68, Jan 76
1296-MHz ssb transceiver WA6UAM	p. 8, Sep 74
1296-MHz rat-race balanced mixer WA6UAM	p. 33, Jul 77
2304-MHz balanced mixer WA2ZZF	p. 58, Oct 75
2304-MHz converter, solid-state K2JNG, WA2LTM, WA2VTR	p. 16, Mar 72
2304-MHz preamplifier, solid-state WA2VTR	p. 20, Aug 72
2304-MHz preamplifiers, narrow-band solid-state WA9HUV	p. 6, Jul 74

## vhf and microwave transmitters

Aligning vhf transmitters Allen	p. 58, Sep 68
Converting the Swan 120 to two meters K6RIL	p. 8, May 68
External anode tetrodes W6SAI	p. 23, Jun 69
Inductively-tuned tank circuit W6SAI	p. 6, Jul 70
Lighthouse tubes for uhf W6UOV	p. 27, Jun 69
Pi networks, series-tuned W2EGH	p. 42, Oct 71
Ssb input source for vhf, uhf transverters (HN) F8MK	p. 69, Sep 70
Transistors for vhf transmitters (HN) W1OOP	p. 74, Sep 69
Vhf linear, 2 kW, design data for W6UOV	p. 7, Mar 69
Water-cooled 2C39 (HN) WA9RPB	p. 94, Sep 77
2C39, water cooling K6MYC	p. 30, Jun 69
50-MHz customized transverter K1RAK	p. 12, Mar 71
50-MHz heterodyne transmitting mixer K2ISP Correction	p. 8, Apr 69 p. 76, Sep 70
50-MHz kilowatt, inductively-tuned K1DPP	p. 8, Sep 75

50-MHz 2 kW linear amplifier W6UOV	p. 16, Feb 71
50-MHz linear amplifier K1RAK	p. 38, Nov 71
50-MHz multimode transmitter K2ISP	p. 28, Sep 70
50-MHz transmitter, solid-state WB2EGZ	p. 6, Oct 68
50-MHz transverter K8DOC, K8TVP	p. 44, Dec 68
50-MHz transverter WA9IGU	p. 44, Jul 69
50-MHz tunnel-diode phone rig K2ZSQ	p. 74, Jul 68
144-MHz fm transceiver, compact W6AOI	p. 36, Jan 74
144-MHz fm transmitter W6AJF	p. 14, Jul 71
144-MHz fm transmitter W9SEK	p. 6, Apr 72
144-MHz fm transmitter, Sonobaby WA0UZO Crystal deck for Sonobaby	p. 8, Oct 72 p. 26, Oct 72
144-MHz heterodyne transmitting mixers K2ISP Correction	p. 8, Apr 69 p. 76, Sep 70
144-MHz linear W4KAE	p. 47, Jan 69
144-MHz linear, 2kW, design data for W6UOV	p. 7, Mar 69
144-MHz low-drive kilowatt linear W6HHN	p. 26, Jul 70
144-MHz multimode transmitter K2ISP	p. 28, Sep 70
144-MHz phase-modulated transmitter W6AJF	p. 18, Feb 70
144-MHz power amplifier, high performance W6UOV	p. 22, Aug 71
144-MHz power amplifiers, fm W4CGC	p. 6, Apr 73
144-MHz power amplifier, 10-watt solid-state (HN) W1DTY	p. 67, Jan 74
144-MHz power amplifier, 80-watt, solid-state Hatchett	p. 6, Dec 73
144-MHz stripline kilowatt W2GN	p. 10, Oct 77
144-MHz transceiver, a-m K1AOB	p. 55, Dec 71
144-MHz transmitting converter, solid-state ssb W6NBI Short circuit	p. 6, Feb 74 p. 62, Dec 74
144-MHz transverter K1RAK	p. 24, Feb 72
144-MHz two-kilowatt linear W6UOV, W6ZO, K6DC	p. 26, Apr 70
144- and 432-MHz stripline amplifier/tripler K2RIW	p. 6, Feb 70
220-MHz exciter WB6DJV	p. 50, Nov 71
220-MHz power amplifier W6UOV	p. 44, Dec 71
220-MHz rf power amplifier WB6DJV	p. 44, Jan 71
220-MHz rf power amplifier, fm K7JUE	p. 6, Sep 73
432-MHz amplifier, 2-kW W6SAI, W6NLZ	p. 6, Sep 68
432-MHz exciter, solid-state W1OOP	p. 38, Oct 69
432-MHz power amplifier using stripline techniques W3HMU	p. 10, Jun 77
432-MHz rf power amplifier K6JC	p. 40, Apr 70
432-MHz solid-state linear amplifier WB6QXF	p. 30, Aug 75
432-MHz ssb converter K6JC Short circuit	p. 48, Jan 70 p. 79, Jun 70
432-MHz ssb, practical approach WA2FSQ	p. 6, Jun 71
432-MHz stripline tripler K2RIW	p. 6, Feb 70
432-MHz 100-watt solid-state power amplifier WA7CNP	p. 36, Sep 75
1152- to 2304-MHz power doubler WA9HUV	p. 40, Dec 75
1270-MHz video-modulated power amplifier W9ZIH	p. 67, Jun 77
1296-MHz frequency tripler K4SUM, W4API	p. 40, Sep 69
1296-MHz linear, high-power WB6IOM Short circuit	p. 8, Aug 68 p. 54, Nov 68
1296-MHz power amplifier W2COH, W2CCY, W2OJ, W1IMU	p. 43, Mar 70
1296-MHz ssb transceiver WA6UAM	p. 8, Sep 74
1296-MHz transverter K6ZMW	p. 10, Jul 77
2304-MHz power amplifier WA9HUV	p. 8, Feb 75

## WARBLE ALARM CAR-VAN CLOCK WITH HEADLIGHT ALARM



**COMPLETE KIT \$35.95  
ASSEMBLED \$45.95**

- ELAPSED TIMER
- SECONDS DISPLAY SWITCH
- 9 MINUTE SNOOZE ALARM
- SIMPLE 4 WIRE HOOK UP
- JUMBO 1/2" LED DISPLAY
- 1 TO 59 MINUTE COUNTDOWN TIME - 4 HRS SIMULTANEOUSLY WITH CLOCK!
- RUGGED ABS CASE
- QUARTZ CRYSTAL ACCURACY

## DIGITAL AUTO INSTRUMENTS SEVEN MODELS!

- #1 TACHOMETER
- #2 WATER TEMP
- #3 FUEL LEVEL
- #4 SPEEDOMETER\*
- #5 OIL PRESSURE
- #6 OIL TEMP
- #7 BATTERY MONITOR



- KIT INCLUDES:
  - CASE & ALL HARDWARE
  - PRESSURE & TEMP. SENSORS
  - ASSEMBLED MAIN PC BOARD
- FEATURES:
  - 4" ORANGE LED'S
  - 4 1/2" x 1 1/2" ABS CASE

\*ADD \$10 FOR REQUIRED SPEED SENDER. \$15 FOR SPEED SENDER ALONE  
**KIT: \$49.95. . . . . ASSEMBLED: \$59.95**

## ELECTRONIC 'PENDULUM' CLOCK



- SWING PENDULUM
- 7" HOURS AND MINUTES DISPLAY
- TIME SET PUSH BUTTONS
- ALARM FEATURE

**KIT-UNFINISHED CASE . . . . . \$59.95  
ASSEMBLED-STAINED CASE . . . . . \$69.95**

## QUARTZ DIGITAL AUTO CLOCK OR ELAPSED TIMER!

ELAPSED TIMER: HRS, MINS & SECS  
SIMPLE PUSHBUTTON RESET &  
HOLD TOGGLE SWITCH  
KIT INCLUDES EVERYTHING,  
NOTHING ELSE TO BUY! 4" LED'S!  
INTERNAL BATTERY BACKUP!  
NON-POLAR INPUT!



12 OR 24 HR MODE  
DIMENSIONS: 4" x 4" x 2"  
**KIT: \$27.95. . . . . ASSEMBLED: \$37.95**

## NOW WITH ELAPSED TIME!



## 3 1/2" DIGITAL CLOCK

- 4 DIGIT KIT \$49.95 • 4 DIGIT ASSEMBLED \$59.95
- 6 DIGIT KIT \$69.95 • 6 DIGIT ASSEMBLED \$79.95

117 VAC 12 OR 24 HR MODE . . . . . KIT COMES COMPLETE!  
6 DIGIT VERSION: 27" x 5" x 1 1/2" 4 DIGIT VERSION: 12" x 5" x 1 1/2"

## TV-WALL CLOCK

- 25" VIEWING DISTANCE
- 6" HOURS & MINUTES
- 3" SECONDS
- COMPLETE WITH WOOD CASE



**KIT: \$34.95. . . . . ASSEMBLED: \$39.95**

## ECONOMY CAR CLOCK

- 1/2" LED MODULE!
- COMPLETE WITH CASE, BRACKET & TIME SET PUSHBUTTONS
- ALARM OPTION



**KIT: \$19.95. . . . . ASSEMBLED: \$26.95**

## PENDULUM

GIVE YOUR DIGITAL CLOCK A PENDULUM SWING  
9 TO 12V DC 60 HZ INPUT  
SIMPLE HOOK UP TO ANY CLOCK



**\$14.95**

**CASE WITH BRACKET \$3.75**



**MARK FOSKETS'**  
SOLID STATE TIME

P.O. BOX 2159  
DUBLIN, CALIF. 94566  
ORDERS (415) 828-1923



**24 HR  
PHONE**



CALIFORNIA RESIDENTS - ADD 6% SALES TAX



**There's  
nothing  
like it !**

**RADIO AMATEUR  
callbook**

*Respected worldwide as  
the only complete authority  
for radio amateur  
QSL and QTH information.*

The **U. S. Callbook** has over 300,000 W & K listings. It lists calls, license classes, names and addresses plus the many valuable back-up charts and references you come to expect from the **Callbook**.

Specialize in DX? Then you're looking for the **Foreign Callbook** with almost 300,000 calls, names and addresses of amateurs outside of the USA.

**U.S. Callbook \$14.95**

**Foreign Callbook \$13.95**

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.50 for shipping. Illinois residents add 5% Sales Tax.

**RADIO AMATEUR  
callbook INC.**  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# PRESTO!

## Your counter becomes a digital display!

Like magic, Hufco's Digi-Dial Adaptor turns any frequency counter into an absolutely accurate digital display! Inexpensively! With continual display of both transmit and receive frequencies — as fast as you turn your transceiver dial!

With the Digi-Dial Adaptor your counter easily adapts to Yaesu (with a modified version for the Yaesu 100 and 500 series), Tempo One, Drake (specify if "C" model), Galaxy, Hallicrafter, Heath, Kenwood and other transceiver. Tell us which other brand you have. We'll tell you if the adaptor fits.

Operation requires only a connecting cable to the transceiver VFO plug. Translates VFO output to 2 through 2.5 MHz. No internal connection or modifications necessary! Complete instructions included.

No frequency counter? Get both the Digi-Dial Adaptor and a frequency counter from Hufco. We have basic counter kits starting as low as \$29.95!

**Quick! Order yours today!**

**Please rush me:**

- ☐ Digi-Dial Adaptor  
\$29.95 kit/\$39.95 assembled
- ☐ Digi-Dial Adaptor (Yaesu 100 or 500)  
\$39.95 kit/\$49.95 assembled
- ☐ Complete date on Hufco  
frequency counters

**29<sup>95</sup>** kit form  
\$39.95 assembled



Enclosed is Check-Money Order-VISA/MC OK!

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Car No. \_\_\_\_\_

Exp. Date \_\_\_\_\_

**Hufco** Box 357, Dept. A  
Provo, Utah 84601  
801/375-8566

## Get the most from your antenna!



With the Omega-t Antenna Noise Bridge you can test for resonant frequency and impedance... adjust and retest... until your antenna performs at its optimum. Use the Noise Bridge to trim RF lines for best performance, too.

This patented design uses your sensitive receiver as a bridge detector, outperforming more expensive test equipments.

Reduce power loss due to mismatch — now! Get more details or order today.

**Model TE7-01... 1-100 MHz range: \$34.95**  
**Model TE7-02... 1-300 MHz range: \$44.95**

**ESI ELECTROSPACE  
SYSTEMS, INC.**

P.O. BOX 1395  
RICHARDSON, TEXAS 75080  
TELEPHONE (214) 231-9303

Sold at Amateur Radio Dealers  
or Direct from Electrospace Systems, Inc.

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION	
For the month of _____, 19____	
1. NAME OF PUBLICATION	U.S. CALLBOOK
2. NUMBER OF ISSUES PUBLISHED DURING THE MONTH	1
3. DATE OF NEXT ISSUE	19____
4. NAME AND ADDRESS OF PUBLISHER	callbook INC., 925 Sherwood Drive, Lake Bluff, Ill. 60044
5. NAME AND ADDRESS OF OWNER	callbook INC., 925 Sherwood Drive, Lake Bluff, Ill. 60044
6. NAME AND ADDRESS OF MANAGING EDITOR	callbook INC., 925 Sherwood Drive, Lake Bluff, Ill. 60044
7. NAME AND ADDRESS OF BUSINESS MANAGER	callbook INC., 925 Sherwood Drive, Lake Bluff, Ill. 60044
8. NAME AND ADDRESS OF CIRCULATION MANAGER	callbook INC., 925 Sherwood Drive, Lake Bluff, Ill. 60044
9. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
10. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
11. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
12. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
13. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
14. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
15. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
16. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
17. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
18. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
19. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000
20. ESTIMATED TOTAL NUMBER OF COPIES OF THIS PUBLICATION FOR THE MONTH	50,000

## TS-1 MICROMINIATURE ENCODER-DECODER

- ☐ Available in all EIA standard tones 67.0Hz-203.5Hz
- ☐ Microminiature in size, 1.25x2.0x.65" high
- ☐ Hi-pass tone rejection filter on board
- ☐ Powered by 6-16vdc, unregulated, at 3-9ma.
- ☐ Decode sensitivity better than 10mvRMS, bandwidth,  $\pm 2$ Hz max., limited
- ☐ Low distortion adjustable sinewave output
- ☐ Frequency accuracy,  $\pm 25$ Hz, frequency stability  $\pm 1$ Hz
- ☐ Encodes continuously and simultaneously during decode, independent of mike hang-up
- ☐ Totally immune to RF

Wired and tested, complete with K-1 element


**\$59.95**

K-1 field replaceable, plug-in, frequency determining elements

**\$3.00 each**
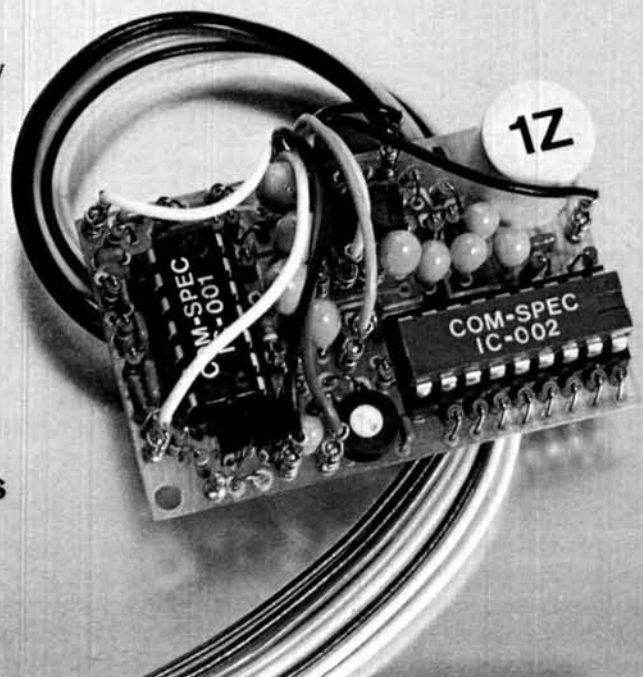
### COMMUNICATIONS SPECIALISTS

P.O. BOX 153  
BREA, CALIFORNIA 92621  
(714) 998-3021



## The Leader in the Northwest!

ATLAS ICOM KENWOOD YAESU



KENWOOD Transceiver  
TS-820S 160 thru 10M **\$1048.**



ICOM Transceiver 2M FM  
SSB IC 211 **\$749.**



YAESU HF SSB  
FT-101E, 160 thru 10M **\$729.**

Other locations:

(Walk-in customers only)

Bellevue - 12001 N. E. 12th

Everett - 6920 Evergreen Way



KENWOOD Transceiver  
TS-520S 160 thru 10M **\$649.** (less DG-5)



ICOM  
2M FM IC 22S  
**\$299.**



KENWOOD 2M FM  
TR-7400A **\$399.**



ICOM Transceiver 2M FM  
IC 245 **\$499.**



YAESU FT-221R  
2 meter FM-SSB **\$595.**

**ABC**  
COMMUNICATIONS  
17550 15th AVE. N.E.  
SEATTLE, WASH. 98155  
206-364-8300



TO PLACE ORDER  
CALL TOLL FREE  
IN STATE OF WASH.  
1-800-562-7625

# Advertisers check-off

...for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio ☒ 234

## INDEX

ABC	571	Janel	068
AGL	558	Jones	626
ALDA	625	K-Enterprises	071
ATV *		KE Elect.	072
Aldelco	347	Kampp	613
Aluma	589	Kantronics	605
Am. Whole		Kenwood *	
Elect.	003	Kester Solder *	
Ameco	331	Klaus	430
Amsat	220	Lafayette	598
Apollo	011	Little Giant	011
Artistic Label	326	Long's	468
Astral	639	Lunar	577
Atlas	198	Lyle	373
Atronics	382	MFJ	082
Bauman	017	Madison *	
Budwig	233	Magnus	578
Bullet	328	Masters	555
CFP	022	Matric	084
CW Elect.	533	Microwave Filter	637
Clegg	027	NuData	455
Clegg	465	Optoelectronics	352
Comm. Elect.	489	Orlando Hamcation *	
Comm. Spec.	330	Palomar	093
Crystal Banking	573	Partridge	439
Cushcraft	035	Pipo	481
Cygnus-Quasar	549	Poly Paks	096
DGM	458	Prime	627
DX Eng.	222	QSA 599	638
Dames Comm.	551	RF Power	
Dames	324	Comp.	542
Data Signal	270	RF Power Labs	602
Dave *		Callbook	100
Davis Elect.	332	Radio World *	
Dentron	259	Ramsey	442
Disc-Cap	449	Regency	102
Drake	039	SST	375
E. T. O. *		SAROC *	
Elect. Distr.	044	Sentry	600
Elect. Equip.		Sherwood	435
Bank	288	Solid State Time	636
Electospace	407	Space	107
Erickson	047	Spectronics	191
Excel	535	Spectrum Int.	108
GLB	552	Swan	111
Gem Quad	295	TPL	240
Gray *	055	Ten-Tec *	
Gregory *		Tri-Ex	116
Gulf Elect.	635	Tristao	118
Hal	057	Tropical Hamboree *	
Hal-Tronix	254	VHF Engineering	121
Ham Center	491	Vanguard *	
Ham Radio Pub.	150	Varian	043
Hamtronics	246	Vines	614
Heath	060	Webster Comm.	423
Henry	062	Weinschenker	122
Henny	403	Westcom	510
Icom	065	Western Elect. *	
Int. Circuits	518	Whitehouse	378
Int. Crystal	066	Wilson	123
James	333	Yaesu	127
Jan	067		

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

**December 1977**

Please use before January 31, 1978

Tear off and mail to

HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048

NAME .....

CALL .....

STREET .....

CITY .....


STATE ..... ZIP .....
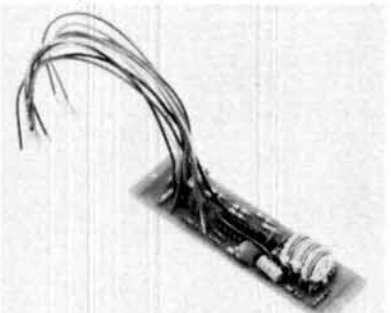
# AGL WANTS YOU TO BEGIN WITH THE BEST

As you develop your skills, increase your participation in Ham Radio activities, and add hardware for ever-increasing flexibility of operations, you'll come to know ICOM. Just ask any old Ham. ICOM is the quality name in VHF/UHF Amateur Radio equipment because it is simply the best. ICOM is the line you'll want to move up to for unequaled quality and features.



AGL has developed a new piece of hardware for your IC-211 and IC-245, the "AGL SCANNER II." It will allow you to use your transceiver to scan all 4 MHz in 5-kHz steps as the digital display in the radio tells you what frequency you are listening to. The "AGL SCANNER II" can be mounted inside or outside of your unit and has adjustable scan rate.



Don't delay in moving up. BEGIN WITH THE BEST: ICOM and AGL. "AGL SCANNER II"..... \$29.95

Both the IC-211 and IC-245 are available with SCANNER installed. Call or write for our quote.



**CALL US TODAY  
TOLL FREE AT  
1-800-527-7418**

**CALL 214-241-6414 (in Texas)**

LARRY WA5WWH    ART K9TRG    GORDON N5AU  
MIKE WA5UOB    MIKE WB5ACM  
TOM K5TM    BOB W5XC

*We service and repair all major lines of  
Amateur Radio equipment.*

**AGL Electronics**  
3068 FOREST LANE, SUITE 309  
DALLAS, TEXAS 75234

# Advertisers iNdex


ABC Communications	149
AGL Electronics	150
ALDA Communications	1
ATV Research	118
Aldelco	118
Aluma Tower Co.	96
Amateur Wholesale Electronics	86, 87
Ameco Equipment Co.	129
Amsat	123
Apollo Products	128
Artistic Label	128
Astral Electronics	106
Atlas Radio	19
Atronics	88
R. H. Bauman Sales Co.	116
Budwig Mfg. Co.	110
Bullet	111
CFP Communications	98
CW Electronics Sales Co.	102
Clegg	90
Clegg Electronics	126
Communications Electronics	126
Communications Specialists	91, 149
Crystal Banking Service	94
Cushcraft	8, 9
Cygnus-Quasar	126
DGM Engineering	82
DX Engineering	94
Dames Communications Systems	129
Dames, Ted	116
Data Signal, Inc.	105
Dave	128
Davis Electronics	104, 110
Dentron Radio Company	7, 65, 92
Disc-Cap	47
Drake Co., R. L.	29, 126
Ethorn Technologies	44
Electronic Distributors	129
Electronic Equipment Bank	114
Electospace	148
Erickson Communications	110
Excel Circuits	122
GLB	92
Gem Quad	100
Gray Electronics	90
Gregory Electronics	96
Gulf Electronics	113
Hal Communications Corp.	66, 67
Hal-Tronix	101
Ham Radio Center	37, 94
Ham Radio Publications	83, 98, 102
Hamtronics, Inc.	151
Heath Company	33
Henry Radio Stores	Cover II, 122
Hufco	148
Icom	5
Integrated Circuits Unlimited	117
International Crystal	71
James Electronics	115
Jan Crystals	114
Jones, Marlin P. & Assoc.	104
K-Enterprises	82
KE Electronics	104
Kampp Electronics, Inc.	88
Kantronics	85
Kester Solder	74, 81
Klaus Radio, Inc.	120
Lafayette Radio Electronics	100
Little Giant Antenna Labs	128
Long's Electronics	152
Lunar Electronics	55, 96
Lyle Products	88
MFJ Enterprises	2
Madison Electronic Supply	128
Magnus Electronics Corp.	108
Masters Communications	92
Matric	100
NuData Electronics	118
Optoelectronics	109
Orlando Hamcation	109
Palomar Engineers	116, 118, 120
Partridge (HR) Electronics	120
Pipo Communications	92
Poly Paks	112
Prime Electronics	116
QSA 599 Amateur Radio Center	82
RF Power Components	118
RF Power Labs	110
Radio Amateur Callbook	94, 148
Radio World	120
Ramsey Electronics	107
Regency Electronics	69
SST Electronics	89
SAROC	119
Sentry Manufacturing	122
Sherwood Engineering	108, 129
Solid State Time	147
Space Electronics	122
Spectronics	48
Spectrum International	96
Swan Electronics	56, 57, 121
TPL Communications	102
Ten-Tec	106, 129
Tri-Ex Tower Corp.	70
Tristao Tower Co.	108
Tropical Hamboree	127
VHF Engineering, Div. of Brownian	97
Vanguard Labs	103
Varian, Eimac Division	Cover IV
Vines, James K.	90
Webster Communications	114
Weinschenker	120
Westcom	34, 93, 106, 127
Western Electronics	126
G. R. Whitehouse & Co.	90
Wilson Electronics	95
Yaesu Electronics Corp.	Cover III

# ANNOUNCING--A New Generation of VHF/UHF FM RECEIVER KITS

More Sensitive, More Selective, Easier to Build, Smaller Than Ever Before!
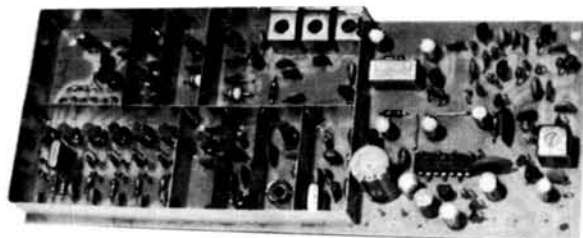
## CHECK THESE FEATURES--

- \* Lower system cost than ever before
- \* Better selectivity, 70-80 dB adjacent channel, over 100 dB with crystal filter option
- \* Six channels at no extra cost
- \* 60 dB image rejection
- \* Latest design -- new easy-to-wind high Q coils, compartmentized shielding
- \* Easy to build, test circuits on board allow tune up with only sig gen & vtm



VHF MODEL R70 \$69.95

- Available for 2M, 6M, 10M, 220 MHz, or com'l bands
- Sensitivity 0.4uV for 20 dB
- Optional Crystal Filter Kit \$10
- Channel Crystals \$5.95 ea

UHF MODEL R90 \$89.95

- For any 2 MHz segment of the 380-520 MHz range
- Sensitivity 0.8uV
- Optional crystal filter kit \$10
- Channel crystals \$5.95 ea



## These new CONVERTER KITS

let you receive OSCAR signals and other exciting VHF & UHF activity on your present HF receiver.



either one  
**ONLY \$34.95**  
including crystal



MODEL	RF RANGE (MHZ)	IF RANGE
C50	50-52	28-30
C144	144-146	28-30
C145	145-147	28-30
C146	146-148	28-30
C220	p/o 220-230	28-30
Special	Other rf & i-f ranges are available on special request	

MODEL	RF RANGE (MHZ)	IF RANGE
C432-2	432-434	28-30
C432-5	435-437	28-30
C432-9	439.25 (ATV)	61.25
Special	Other rf & i-f ranges are available on special request	

An extruded aluminum case is available for vhf and uhf converters at \$12.95, including connectors and hardware.

## TEST PROBE KITS



**only \$9.95 ea**

Contain scope type probe, ground clip, cable, & all components except plug for test equipment.

- TE-3 RF Detector Probe for vtm; good from 100 kHz to over 500 MHz
- TE-4 Direct Probe for ac/ohms, etc.
- TE-5 DC Probe w/res for 11 meg input vtm
- TE-6 Blocking Capacitor Probe for counter, signal generator, etc.
- TE-7 Wideband Detector Probe for scopes
- TE-8 High Z/Low Capacitance scope probe

## \*FREE 1978 CATALOG

is yours for the asking. NEW 40 page catalog gives details on these and other kits, including scanner adapters, receiver multicouplers, NPC power supplies, M-tech PA's, CES tone pads & mics, Hy-Gain HT's & hf rigs, & antennas. GET YOURS TODAY!

**FREE SHIPPING ON LARGE STOCK OF ANTENNAS!!!** We now offer free delivery of Cushcraft, Larsen, & Hy-Gain antennas in the 48 states. Popular models such as Ringo Rangers, VHF & tri-band beams, magnet mount whips, hf verticals, rubber duckies, lightning arrestors, Reyco traps, W2AU & Hy-Gain baluns. Call or write NOW! We'll be glad to send free catalogs.

IN CANADA:

Send order to COMTEC; 5605 Westlue Ave.; Montreal, Que H4W 2N3 or call 514-482-2640. Add 28% to prices shown above to cover customs duty, exchange rate, and federal tax.

## These low noise PREAMPS let you hear the weak ones!

Great for OSCAR, SSB, FM, ATV. Over 8000 in use throughout the world.



P8 KIT \$10.95  
P16 Wired \$21.95  
Miniature model for tight spaces -- only 1/2 x 2-3/8 inches

MODEL	RANGE
P8-LO	20-83 MHz
P8-HI	83-190 MHz
P8-220	220-230 MHz
P16 Wired	Give exact band

P9 KIT \$12.95  
P14 Wired \$24.95

Deluxe model for applications where space permits.



- 1-1/2 x 3 inches
- Covers any 4 MHz band in range
- Ideal for OSCAR
- Diode protection
- Connectors
- 20 dB gain

MODEL	RANGE
P9-LO	26-88 MHz
P9-HI	88-172 MHz
P9-220	172-230 MHz
P14 Wired	Give specific band



P15 KIT \$18.95  
P35 Wired \$34.95

- Covers any 6 MHz band in band in range of 380-520 MHz
- 20 dB gain


## FM/CW TRANSMITTER KITS


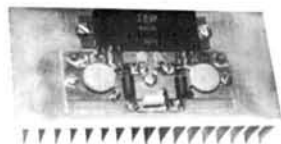
### 200 MW EXCITER MODULE KITS

T40 Eleven Channel Exciter Kit for 2M or 6M band..... \$39.95

T20 Tripler/Driver Module Kit, 150 mW 2M input, 200 mW 450 MHz output \$19.95



### RF POWER AMPLIFIER MODULES

- NO TUNING
- VSWR PROTECTED
- COMPLETELY STABLE
- 150MW DRIVE

T80-150, 140-175 MHz, 20-25W output, wired and tested, simply connect your cables.. \$79.95  
T80-450, 430-470 MHz, 13-15W..... \$79.95

### It's Easy To Order!

- CALL OR WRITE NOW FOR FREE CATALOG OR TO PLACE ORDER!
- PHONE 716-663-9254. (Answering service for evenings and weekends for your convenience. Personal service 9-5 eastern.)
- Use credit card, COD, check, m.o.
- Add \$2.00 shipping & handling.

**hamtronics, inc.**

182-A Belmont Rd; Rochester, NY 14612  
Dealer Inquiries Invited

# Buy the 599D's & get a Free gift

Call: 1-800-633-3410 for your FREE gift and 599D station from Long's



**1023.00**  
FOR THE 599D  
STATION & YOUR  
CHOICE OF ONE FREE GIFT SHOWN BELOW

## KENWOOD S-599D speaker

The S-599D speaker is designed specifically for the 599D series station. • Frequency range: 100 to 5000 Hz • Speaker diameter: 4 3/4" • Dimensions: 5 1/2" W x 5 1/2" H x 7 1/4" D • Weight: 3.3 lbs.

## KENWOOD R-599D receiver

R-599D: • Entirely solid-state • Covers 10-80 meters • Highly stable VFO • Oscillator for 5 fixed channels • Built-in crystal filters • Noise blanker • Squelch circuit • Modes: USB, LSB, CW, AM, FM • Power consumption: 15 watts.

## KENWOOD T-599D transmitter

T-599D: • Solid-state, except driver and final stage • 10-80 meters • Modes: USB, LSB, CW, AM • Effective 8-pole crystal filter • Antenna impedance: 50 to 75 ohms • Carrier suppression: 40 dB • Power consumption: 350 watts.

**CUSHCRAFT ATB-34**  
10, 15, 20 meter antenna.  
List Price: 239.00



FREE GIFT NUMBER 1.

**BIRD Model 43**  
THRULINE wattmeter  
List Price: 120.00



FREE GIFT NUMBER 2.

**KENWOOD TR-7200A**  
2m FM transceiver List Price: 189.00



FREE GIFT NUMBER 3.

**HYGAIN 3806**  
handy-talky.  
List Price: 189.95



FREE GIFT NUMBER 4.

**DENTRON 160-10AT**  
super tuner  
List Price: 129.50



FREE GIFT NUMBER 5.

**REGENCY HRT-2**  
handy-talky.  
List Price: 179.00



FREE GIFT NUMBER 6.

Remember, you can call TOLL-FREE: 1-800-633-3410 in U.S.A. or call 1-800-292-8668 in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday.




# Long's Electronics



MAIL ORDERS: P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS: 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

# YAESU PROUDLY ANNOUNCES THE SENSATIONAL
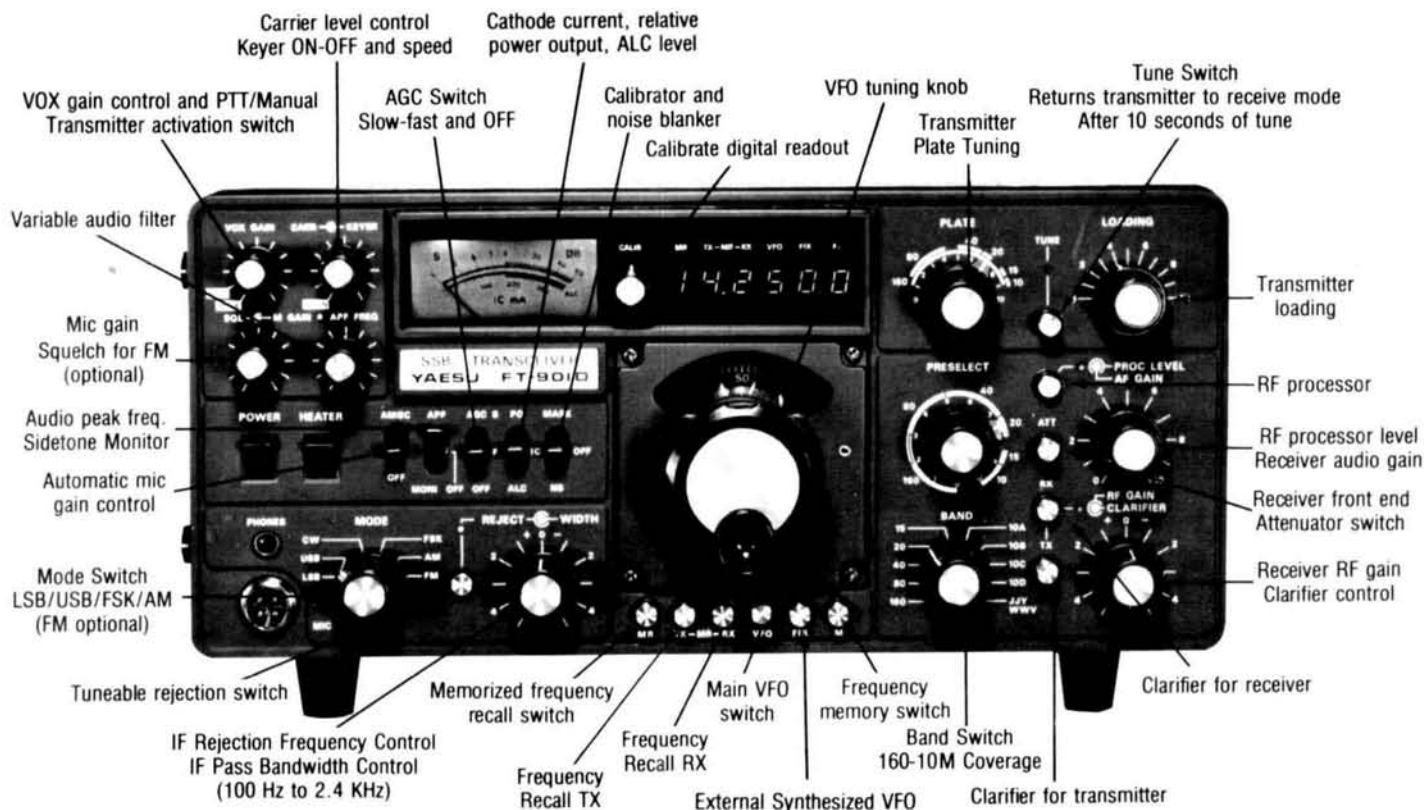
## SMART NEW <sup>^</sup> FT-901D - YEARS AHEAD WITH YAESU!



■ Two rugged 6146B's in the final, with negative feedback ■ A variable IF bandwidth that allows 100 Hz to 2.4 KHz selectivity at the turn of a knob ■ IF rejection tuning to notch out interfering signals ■ Optional synthesized VFO, or enlarged frequency memory bank ■ Selectable AGC ■ Built in speech processor ■ Built in Curtis Keyer ■ Full range 160-10M coverage ■ Provision for new WARC frequencies ■ Meets Part 97.73 of FCC requirements. . . . at your dealers soon!

Design And Specifications Subject To Change Without Notice Or Obligation



# YAESU

## ***The smart radio***

**YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 (213) 633-4007**  
**YAESU ELECTRONICS CORP., Eastern Service Ctr., 613 Redna Ter., Cincinnati, OH 45215**

Look over DenTron's low profile, stylized MLA-2500 amplifier. Two EIMAC high-mu 8875 power triodes are the heart of the modularized design. The combination of DenTron's cathode-driven circuitry and EIMAC's 8875s provides simplicity, economy and high power all in one compact package.

Unexcelled for rugged amateur service, the 8875 is a natural choice for DenTron, just as it and other EIMAC power tubes are the choice of most principal manufacturers of amateur, commercial and military communication equipment.

Whether you build or buy your equipment—go EIMAC. The EIMAC name is your assurance of power, dependability and quality. Send today for your free copy of the EIMAC Quick Reference Catalog which provides information on all popular EIMAC products. Write Varian, EIMAC Division, 301

Industrial Way, San Carlos, California 94070. Telephone (415) 592-1221. Or contact any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.



# EIMAC 8875s Power DenTron's MLA-2500 Linear Amplifier.



Send for your copy of the  
world's largest catalog of  
quality kit-form electronic  
products.

# FREE!

FILL IN THIS  
CARD AND  
MAIL TODAY

Take your pick  
of nearly 400 fun-to-build and  
practical money-saving kits — all  
backed by Heath — world leader  
in better electronic kits since 1947.

**FREE!** mail card now ▶

Yes! Please rush me my  
personal copy of the **NEW**  
Heathkit Catalog.

I am not on your mailing list.

Name

Address

City

State

Zip

Dept. 122-36  
Ham Radio

PC-124

**HEATH COMPANY**  
BENTON HARBOR MI 49022

**PUT STAMP  
HERE**  
The Post Office  
will not deliver  
mail without postage

Get your very own copy of the latest

**HEATHKIT**

MAIL-ORDER KIT CATALOG

**FREE!**

Kits for almost everything in electronics; auto and marine accessories, TV, stereo hi-fi, home products and much more. All are easy to build with crystal-clear, step-by-step Heathkit assembly manuals.

**SEND FOR IT TODAY!**

